

Name Danil Daskalov

First

Last

Student ID # XXXXXXXXXX

University of California

Los Angeles

Computer Science Department

CSM51A Midterm Exam #2

Fall Quarter 2011

Nov 9th 2011

This is a closed book exam. Absolutely nothing is permitted except pen, pencil, and eraser to write your solutions. Any academic dishonesty will be prosecuted to the full extent permissible by university regulations.

The exam has 5 problems.

Time allowed 100 minutes.

Problem (possible points)	Points <i>regrade</i>
1 (20)	20
2 (20)	17 → 20
3 (20)	20
4 (20)	6 → 14
5 (20)	15
Total (100)	78 → 89

Name: _____
 ID #: _____

Problem 1 (20 points)

Using only GH flip-flops (state transition shown below) and multiplexers, implement the system given by the high-level table.

PS, Q(t)	GH			
	00	01	10	11
0	1	1	0	-
1	-	1	0	0
NS, Q(t+1)				

PS, Q(t)	X = 0	X = 1
A	F, 0	E, 0
B	G, 0	B, 1
C	B, 0	H, 0
D	F, 0	H, 0
E	G, 0	C, 0
F	G, 0	F, 1
G	E, 0	A, 1
H	G, 0	A, 0
NS Q(t+1), Z		

$$P_1 = \{A, C, D, E, H\} \{B, F, G\}$$


$\begin{matrix} 2 & 2 & 2 & 2 & 2 & 2 & 2 & 1 \\ 1 & 1 & 1 & 1 & 1 & 2 & 2 & 1 \end{matrix}$

$$P_2 = \{A, C, D, E, H\} \{B, F\} \{G\}$$

$\begin{matrix} 1 & 1 & 1 & 1 & 1 & 2 & 2 \\ 1 & 1 & 1 & 1 & 1 & 2 & 2 \end{matrix}$

$$P_3 = P_4 = \{A, C, D\} \{E, H\} \{B, F\} \{G\} \quad \checkmark$$

PS	NS	GH
0	2	10
0	1	0-
1	0	1-
1	1	01

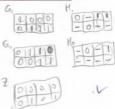

PS	X=0	X=1
00	A, 0	E, 0
01	B, 0	B, 1
11	G, 0	A, 0
10	E, 0	A, 1

PS	X=0	X=1
00	01, 0	11, 0
01	10, 0	01, 1
11	10, 0	00, 0
10	11, 0	00, 1

$$G_1 = xq_0 + xq_1 + x'q_1q_0'$$

$$H_1 = q_1$$

$$G_0 = xq_1 + x'q_0$$

$$H_0 = q_1$$

$$Z = xq_1q_0 + xq_1q_0'$$


Name: _____
 ID #: _____

Problem 1) Extra Page

$$G_1 \left| \begin{array}{l} G_{1,x} = q_1^1 q_1^1 \\ G_{1,x} = q_0^1 q_1^1 \end{array} \right.$$

$$G_2 \left| \begin{array}{l} G_{2,x} = q_0 \\ G_{2,x} = q_1 \end{array} \right.$$

$$Z \left| \begin{array}{l} Z_{q_1} = X q_0 \\ Z_{q_1} = X q_1 \end{array} \right.$$

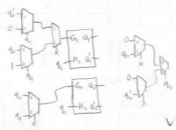

20

Name: _____

ID #: _____

Problem 2 (20 points)

Design a system that accepts as input a single input stream and outputs 1 if $x(t-4, t)$ is 100-0. You have at your disposal 1 SR flip-flop, 1 JK flip-flop, 1 T flip-flop, 1 VW flip-flop (state transition table below), and as many NAND gates and NOR gates as you need.

PS	NS			
	VW = 00	VW = 01	VW = 11	VW = 10
0	0	1	0	1
1	1	0	1	0

D	0	1
0	0	1
1	0	1

SR

PS	00	01	11	10
0	0	0	0	1
1	1	1	1	1

JK

PS	00	01	11	10
0	0	0	0	1
1	1	0	0	1

T

0	1
0	1
1	0

$$D = xq' + xq$$

$$(x'q) + (xq')$$

$$(x' + q) \cdot (x + q')$$

$$(x + q) \cdot (x' + q')$$

PS	NS	VW
0	0	00 or 11
0	1	01 or 10
1	0	01 or 10
1	1	00 or 11

V

0	0
0	1
1	1

W


0	1
0	1
1	0

$$V = X \quad W = Q$$



$$x = y = z$$

$$(xyz)'$$

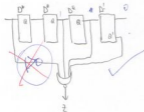

(17) → 20

Name: _____

ID #: _____

Problem 2) Extra Page

a) (10 points) Design a system that accepts as input an input stream with possible input set {a, b, c} and outputs 1 if abc^2 is a subsequence of the input.

b) (10 points) Design a system that accepts as input an input stream with possible input set {a, b, c} and outputs 1 if abc^2 is a subsequence and there have been an odd number of 'a's. (Note: you may assume any variables you designed in part a)

	FS	FS	FS	FS
00	0	0	0	0
01	0	0	0	0
10	0	0	0	0
11	0	0	0	0

	FS	FS	FS	FS
00	0	0	0	0
01	0	0	0	0
10	0	0	0	0
11	0	0	0	0

$D_1 = a, x, y = a, c, y$ $D_2 = (a, c, a)$ $Z = (a, c)$



11

Name: _____

ID #: _____

Problem 3 (20 points)

a) (10 points) Design a system that accepts as input an input stream with possible input set {a, b, c} and outputs 1 if $x(t-3, t)$ is **abc**.

b) (10 points) Design a system that accepts as input an input stream with possible input set {a, b, c} and outputs 1 if $x(t-3, t)$ is **abbc** and there have been an odd number of b's. Hint: you may re-use any modules you designed in part a).

a)


PS	$x=a$	$x=b$	$x=c$
00 S_0	$S_{0,0}$	$S_{1,0}$	$S_{1,0}$
01 S_a	$S_{0,0}$	$S_{0,0}$	$S_{1,0}$
10 S_b	$S_{1,0}$	$S_{0,0}$	$S_{1,0}$
11 S_{ab}	$S_{0,0}$	$S_{1,0}$	$S_{1,1}$

PS	$x=y$	$x=z$	$x=w$	$x=v$
00	01,0	00,0	00,0	---
01	01,0	10,0	00,0	---
10	01,0	11,0	00,0	---
11	01,0	00,0	00,1	---

$$D_1 = q_0 x' y + q_0 x y'$$

$$D_0 = q_1' q_0' + q_1' x y'$$

$$Z = q_1 x y$$

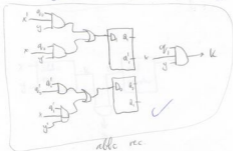

10

Name: _____

ID #: _____


Problem 3) Extra Page

b)

PS	na	x = b	x = c	PS	xy	10	11
0	S _{e,0}	S _{u,1}	S _{e,0}	0	0,0	1,1	0,0
1	S _{o,1}	S _{e,0}	S _{o,1}	1	1,1	0,0	1,1

$T = y$ $z = qy' + q'y$

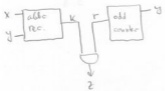b) (14 points) Design a system that adds two 2-bit numbers using the minimal number of 2-input logic gates. add counter (starts over)



Name: _____

ID #: _____

14

Problem 4 (20 points)

a) (6 points) Implement the following function using the minimal number of 2-select input (4-data input) MUXes and no other combinational logic.

	cd= 00	cd= 01	cd= 11	cd= 10
ab = 00	0	0	1	0
ab = 01	0	0	1	1
ab = 11	0	0	1	1
ab = 10	0	0	1	0

b) (14 points) Design a system that adds two 32-bit numbers using the minimal number of 4-select input (16-data input) MUXes and no other combinational logic.

a)

$$z = bc + cd$$

$$bc \begin{cases} z_{bc} = 0 \\ z_{bc} = d \\ z_{bc} = 0 \\ z_{bc} = 1 \end{cases}$$



b

Name: _____
 ID #: _____

Problem 4) Extra Page

8)

a	b	c_{in}	Z	c_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


	c_{in}	
0	0	1
1	0	1

	c_{in}	c_{out}
0	0	0
0	1	0
1	0	1
1	1	1

$$Z = a'b'c_{in} + a'bc_{in} + a'bc_{out} + ab'c_{in}$$

$$c_{out} = ac_{in} + ab + bc_{in}$$

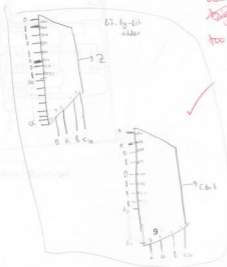adder chain? -4
~~big MUX~~
 too many MUXes = -2



no that

Name: _____

ID #: _____

Problem 5 (20 points)

Design a system that outputs 1 once it recognizes the following 4 patterns in order (otherwise, it outputs 0):

- A) 1111
- B) 1110
- C) 1101
- D) 1100

For example, the input sequence:

0111100111011010101100

will output 1 because it recognizes pattern A, then B, then C, then finally D. To clarify:


0111100111011010101100

A: 1111

B: 1110

C: 1101

D: 1100

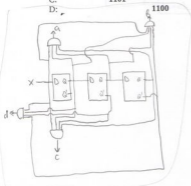

Pattern Recognizer


PS	x=0	x=1
0	0,0	1,1
1	1,1	1,1



Name: _____

ID #: _____

Extra Page

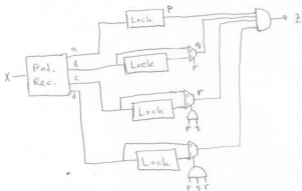

15