

Name YooJung Choi
First Last
Student ID # 004 155 700

University of California
Los Angeles
Computer Science Department

CSM51A/EEM16 Midterm Exam #1
Winter Quarter 2014
January 30th 2014

This is a closed book exam. Absolutely nothing is permitted except pen, pencil and eraser to write your solutions. Any academic dishonesty will be prosecuted to the full extent permissible by university regulations.

Time allowed 100 minutes.

Problem (possible points)	Points
1 (20)	20
2 (20)	20
3 (20)	20
4 (20)	20
5 (20)	20
Total (100)	100

20

Problem 1 (20 points)

Find x and y :

(a) $3B62A871_{32} = x_4$

(b) $46_7 + 99_{13} = y_{11}$

a) $3B62A871_{32}$

$= 00011010110011000010,01010,01000,00111,00001_2$

$= 01223030021102003201_4$

$\therefore x = 01223030021102003201$

b) $46_7 + 99_{13}$

$= (4 \times 7 + 6) + (9 \times 13 + 9)$

$= 34 + 126$

$= 160$

$= 1 \times 121 + 3 \times 11 + 6$


$= 136_{11}$

$\therefore y = 136$

Problem 2 (20 points)

Given the network below, calculate the critical path delay. Consider $L \rightarrow H$ delay when calculating the critical path.

Gate	Fan-in	t_{pLH}	t_{pHL}
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$
AND	3	$0.20 + 0.038L$	$0.18 + 0.018L$
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$
OR	3	$0.12 + 0.038L$	$0.34 + 0.022L$

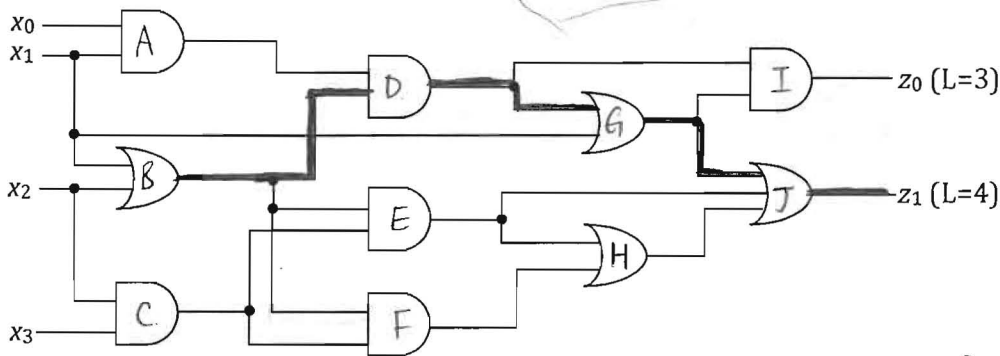

Handwritten calculations for gate delays:
 $0.037 \times 3 = 0.111$
 $0.037 \times 4 = 0.148$
 $0.037 \times 2 = 0.074$
 $0.15 + 0.037 = 0.187$

- A: $0.15 + 0.037(1) = 0.187$
- B: $0.12 + 0.037(3) = 0.231$
- C: $0.15 + 0.037(2) = 0.224$
- D: $0.15 + 0.037(2) = 0.224$, $B+D : 0.231 + 0.224 = 0.455$
- E: $0.15 + 0.037(2) = 0.224$, $B+E : 0.231 + 0.224 = 0.455$
- F: $0.15 + 0.037(1) = 0.187$, $B+F : 0.231 + 0.187 = 0.418$
- G: $0.12 + 0.037(2) = 0.194$, $B+D+G : 0.455 + 0.194 = 0.649$
- H: $0.12 + 0.037(1) = 0.157$, $B+E+H : 0.455 + 0.157 = 0.612$
- I: $0.15 + 0.037(3) = 0.261$, $B+D+G+I : 0.649 + 0.261 = 0.910$
- J: $0.12 + 0.038(4) = 0.272$, $B+D+G+J : 0.649 + 0.272 = 0.921$

\therefore Critical path delay : 0.921 ✓

20

Problem 3 (20 points)

Draw a K-map that contains 10 minterms, 6 prime implicants, and 2 essential prime implicants.

		w				
		1	1	0	1	
		1	1	0	1	y
z		0	1	1	1	
		0	1	0	0	
						x

Prime Implicants: $z'w'$, $z'x'$, $x'w$,
 zyw , zyx , yxw'

Essential Prime Implicants: $z'w'$, $x'w$

Problem 4 (20 points)

One 2-bit number, A, and two 1-bit numbers, B and C, are given. Design a system that outputs the product of the largest two inputs. Use only the star (*) gate defined below to implement your circuit. You may also use constants 0 and 1.

x	y	x*y
0	0	1
0	1	1
1	0	0
1	1	1

$$x * y = x' + y$$


$$x * 0 = x'$$

$$(x * 0) * y = x + y$$

$$x * (y * 0) = x' + y'$$

$$(x * (y * 0)) * 0 = (x' + y')' = xy$$

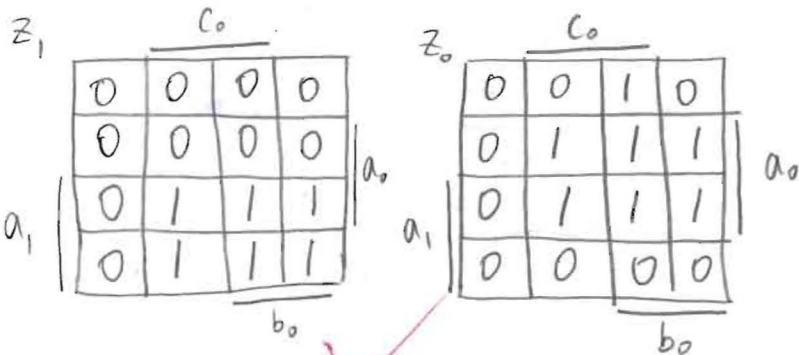Inputs: a_1, a_0, b_0, c_0 Output: z_1, z_0



$$\therefore z_1 = a_1 c_0 + a_1 b_0$$

$$= (a_1) (b_0 + c_0)$$

$$z_0 = a_0 c_0 + a_0 b_0 + a_1' b_0 c_0$$

$$= (b_0 + c_0) (a_1' + a_0) (a_0 + b_0) (a_0 + c_0)$$

$$\rightarrow z_1 = a_1 (c_0 + b_0) = a_1 ((c_0 * 0) * b_0) = (a_1 * (((c_0 * 0) * b_0) * 0)) * 0$$

$$z_0 = a_0 (c_0 + b_0) + b_0 c_0 a_1'$$





$$= (a_0 * (((c_0 * 0) * b_0) * 0)) * 0 + (b_0' + c_0' + a_1)'$$

$$= (a_0 * (((c_0 * 0) * b_0) * 0)) * 0 + (b_0 * (c_0 * a_1))'$$

$$= (a_0 * (((c_0 * 0) * b_0) * 0)) * ((b_0 * (c_0 * a_1)) * 0)$$

back →


Problem 4) Extra Page

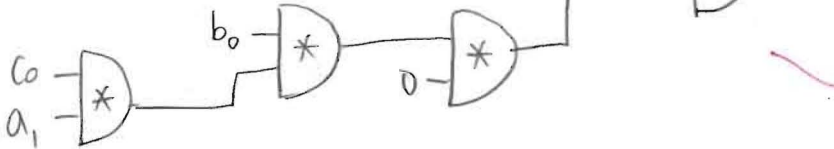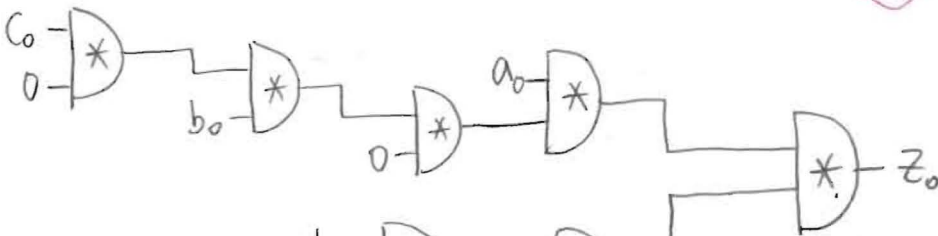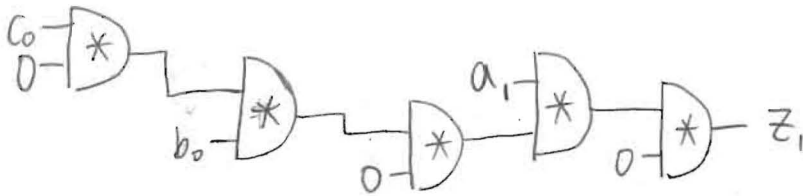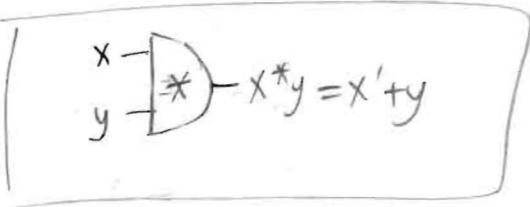

Problem 5 (20 points)

Four 1-bit numbers (A, B, C, and D) are given. Design a system that outputs the difference between the sum of the two largest numbers and the sum of the two smallest numbers. For example, say A and B are the largest and C and D are the smallest, the output should be $Z = (A+B) - (C+D)$.

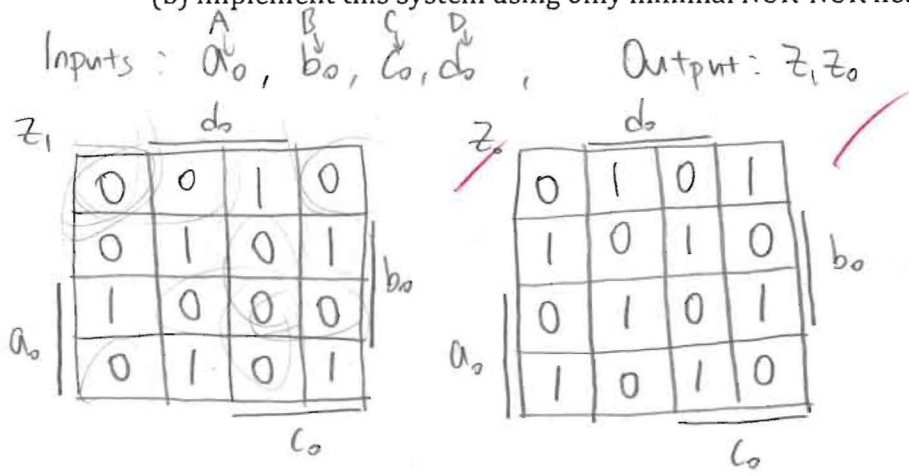- (a) Implement this system using only minimal NAND-NAND networks.
- (b) Implement this system using only minimal NOR-NOR networks.



$$z_1 = a_0 b_0 c_0' d_0' + a_0 b_0' c_0' d_0 + a_0' b_0 c_0' d_0 + a_0' b_0' c_0 d_0 + a_0' b_0 c_0 d_0' + a_0 b_0' c_0 d_0'$$

$$= (a_0 + b_0 + c_0)(a_0 + b_0 + d_0)(a_0 + c_0 + d_0)(b_0 + c_0 + d_0)(a_0' + b_0' + d_0')$$

$$(a_0' + c_0' + d_0')(a_0' + b_0' + c_0')(b_0' + c_0' + d_0')$$

$$z_0 = a_0' b_0 c_0' d_0' + a_0 b_0' c_0' d_0' + a_0' b_0' c_0' d_0 + a_0 b_0 c_0' d_0 + a_0' b_0 c_0 d_0 + a_0 b_0' c_0 d_0 + a_0' b_0' c_0 d_0'$$



$$+ a_0 b_0 c_0 d_0'$$

$$= (a_0 + b_0 + c_0 + d_0)(a_0 + b_0 + c_0' + d_0')(a_0 + b_0' + c_0 + d_0')(a_0 + b_0' + c_0' + d_0)$$

$$(a_0' + b_0' + c_0 + d_0)(a_0' + b_0' + c_0' + d_0')(a_0' + b_0 + c_0 + d_0')(a_0' + b_0 + c_0' + d_0)$$

Problem 5) Extra Page

a)

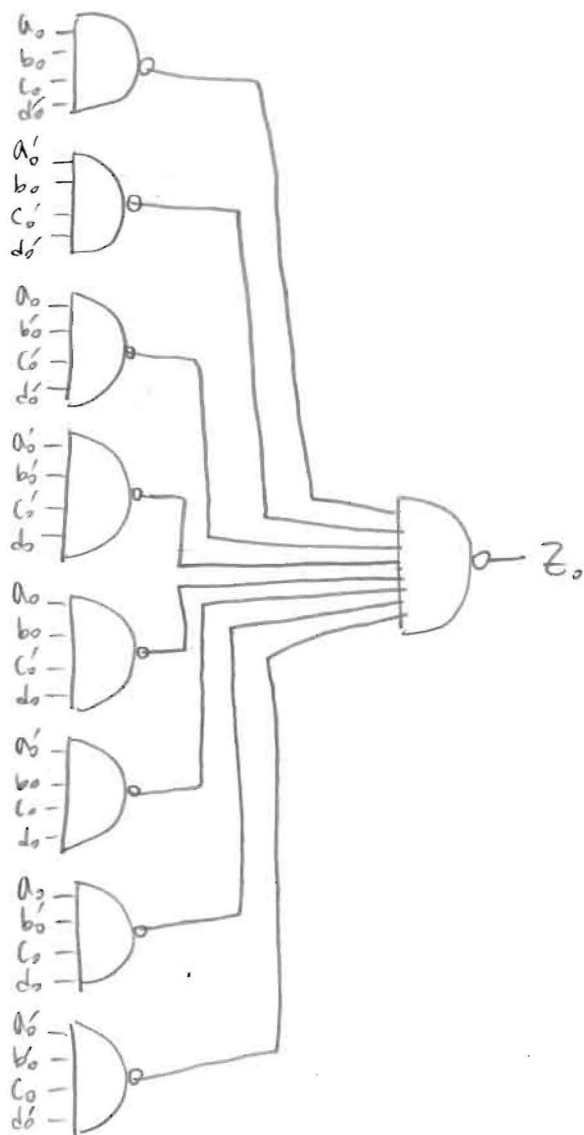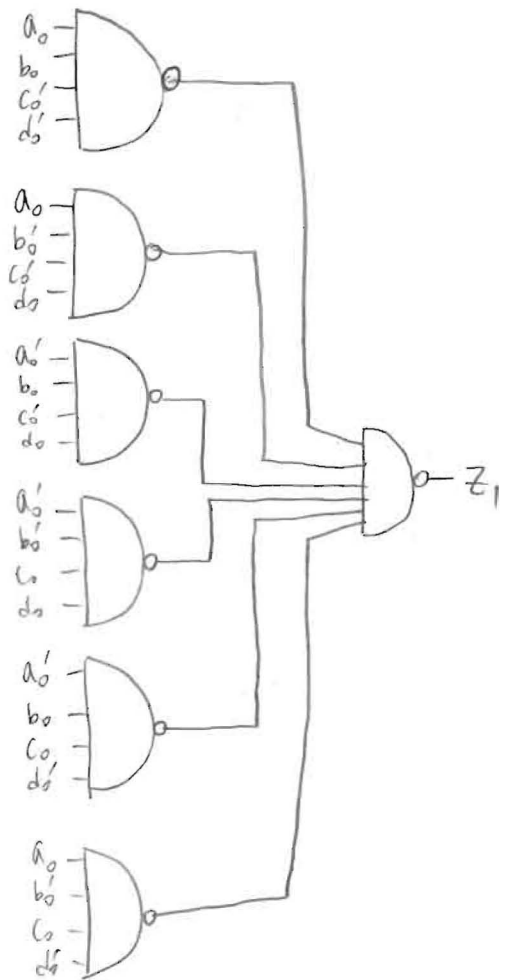

b)

