

20

### Problem 1 (20 points)

Use only the "E" gate defined below to implement Boolean function:

$$F = w'xy' + wxz + w'x'z + wx'y'z'$$


You may also use constants 0 and 1 as inputs.

a	b	c	E(a,b,c)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


1-input not gate:



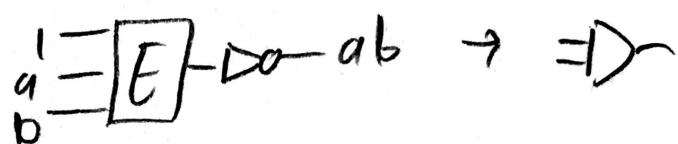
2-input and gate using not gate:  $\rightarrow$  Unusual Set




2-input or gate:

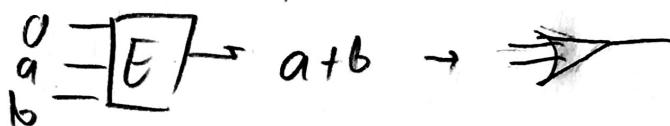


3/4 input and gate using 2-input and

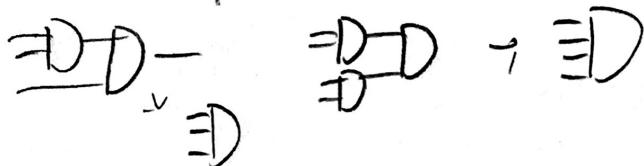

4 input OR gate using 2-input OR gate:

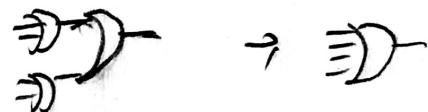

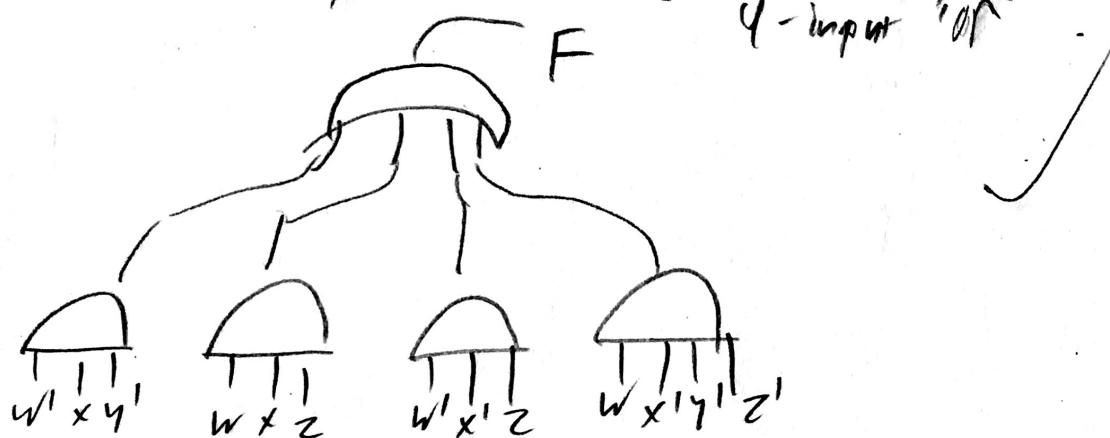Building  $F$  using 3 & 4 input "And" and 4 - input "OR"




$$\begin{array}{r}
 .194 \\
 .455 \\
 \hline
 .649 \\
 .272 \\
 \hline
 .921
 \end{array}$$

### Problem 2 (20 points)

Given the network below, calculate the critical path delay. Consider L  $\rightarrow$  H delay when calculating the critical path.

Gate	Fan-in	$t_{PLH}$	$t_{PHL}$
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$
AND	3	$0.20 + 0.038L$	$0.18 + 0.018L$
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$
OR	3	$0.12 + 0.038L$	$0.34 + 0.022L$

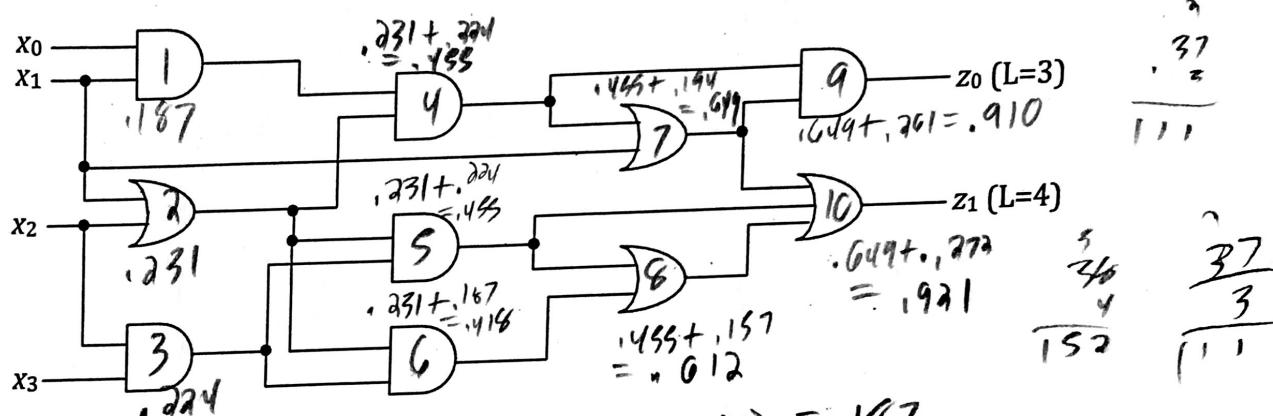

1.  $.18 + .037(1) = .187$
2.  $.12 + .037(3) = .231$
3.  $.19 + .037(2) = .224$
4.  $.19 + .037(2) = .224$
5.  $.19 + .037(2) = .224$

6.  $.19 + .037(1) = .187$
7.  $.12 + .037(2) = .194$
8.  $.12 + .037(1) = .157$
9.  $.19 + .037(3) = .261$
10.  $.12 + .038(4) = .272$



$Z_0$  critical path length: .910 (a 479)

$Z_1$  critical path length: .921 (a 4710)



16
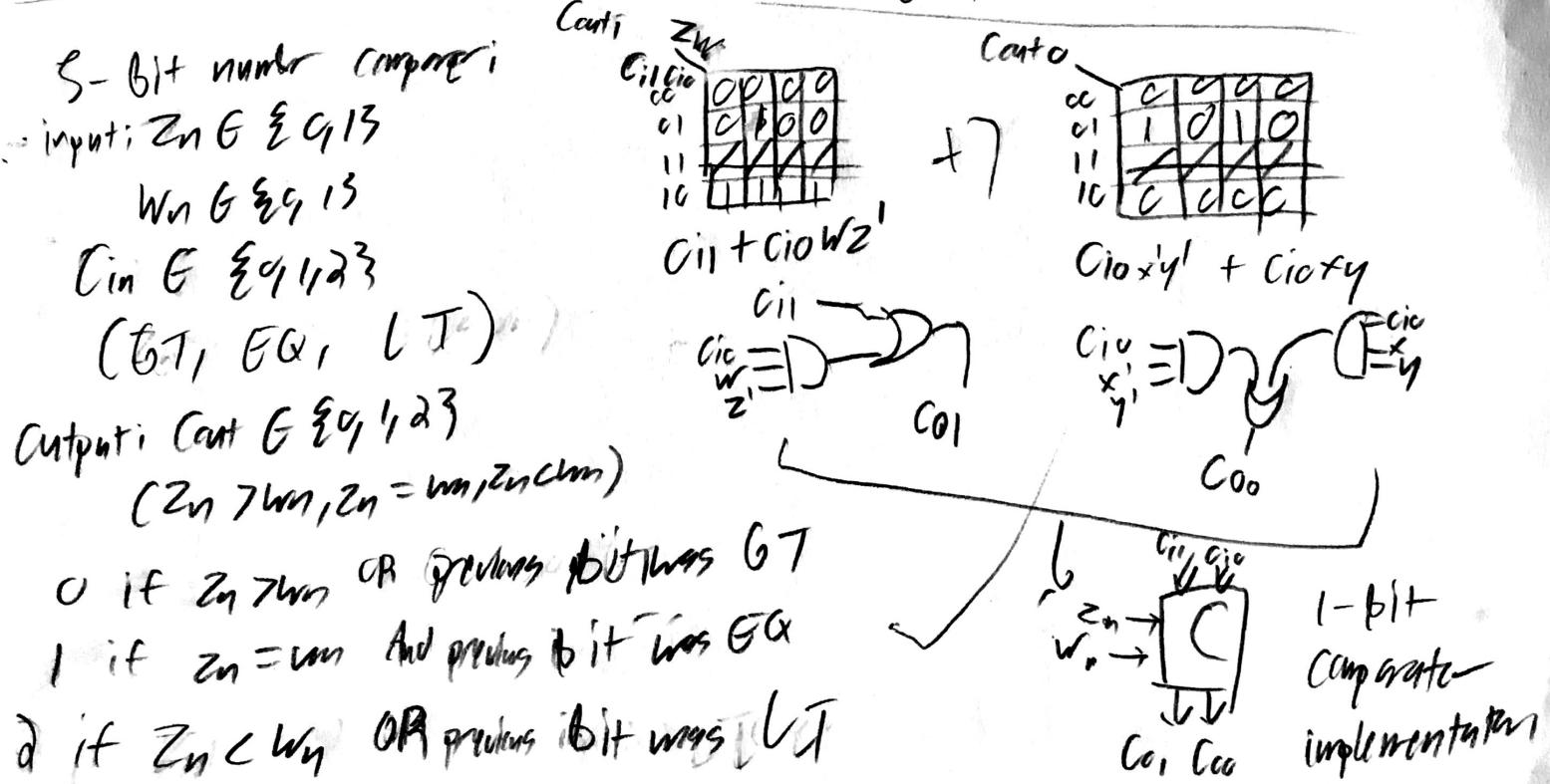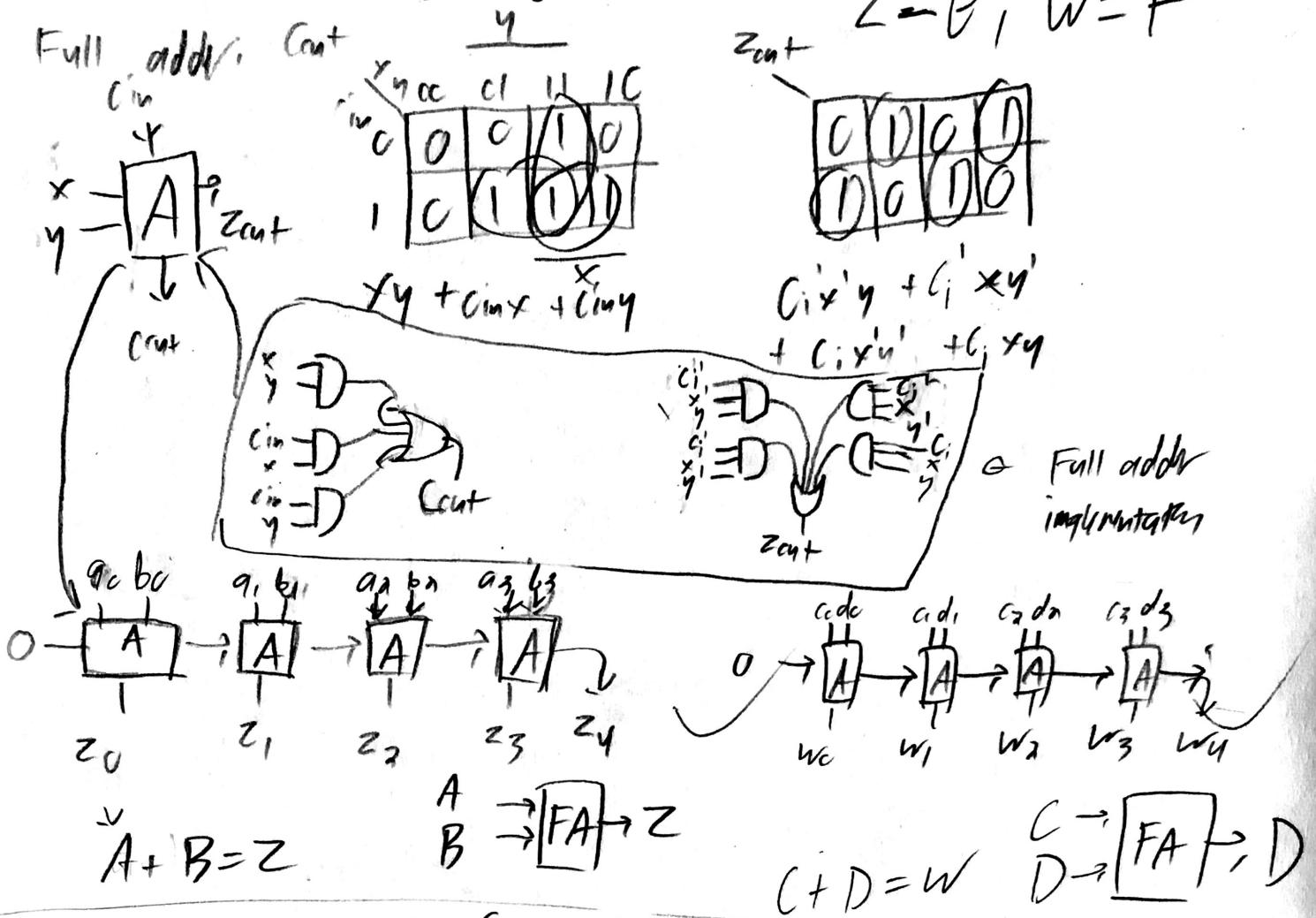
### Problem 3 (20 points)

Four 4-bit numbers A, B, C, and D are given as inputs. E = A + B, F = C + D. Design a system that outputs the larger number between E and F. If E = F, output either E or F. You can use any type of gates to implement your design.




## Problem 3) Extra Page

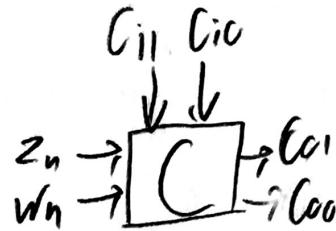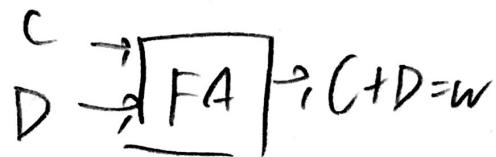


$$\begin{aligned} C_{out} = 0 & \text{ if } Z_n > W_n \\ & \text{if } Z_n = W_n \\ & 1 \text{ if } Z_n < W_n \end{aligned}$$

$C_{01}$	$C_{00}$	$Z_n$
0	0	$Z_n$
0	1	$Z_n$
1	0	$W_n$
1	1	$W_n$

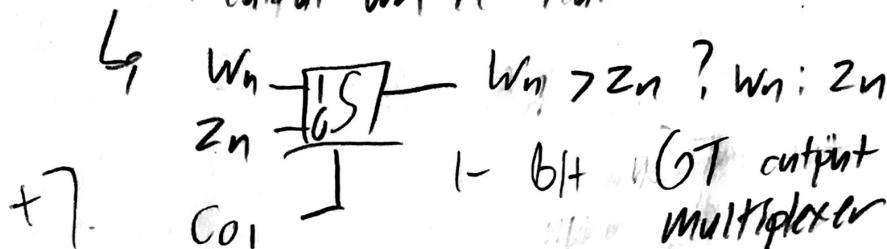

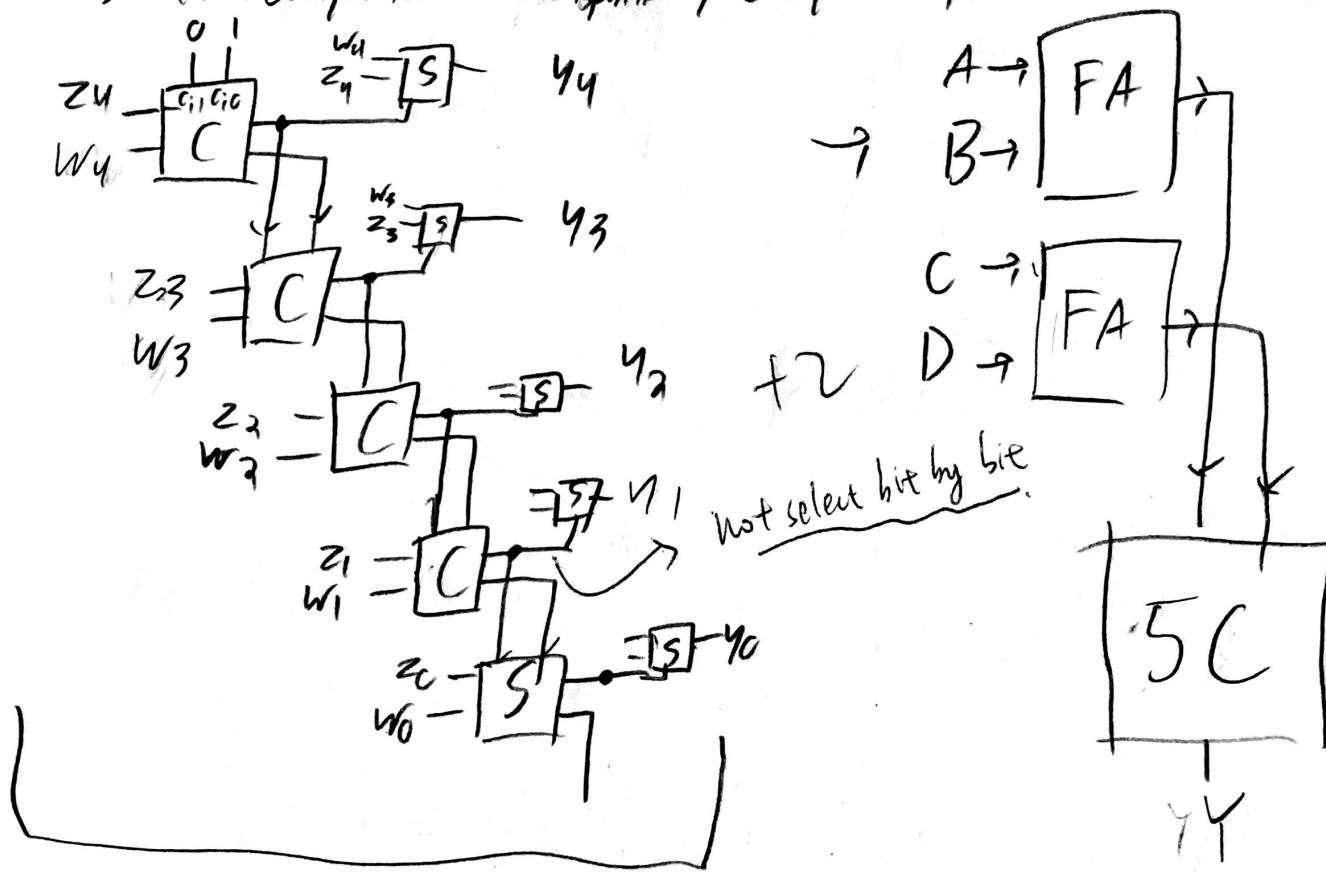5-bit Comparator and outputs  $\rightarrow$  Outputs  $Y = \text{Max}(Z, W)$




$$SC \quad \begin{matrix} Y \\ Z \\ W \end{matrix} = 5C \rightarrow Y \quad Y = \text{Max}(Z, W) = \text{Max}(A+B, C+D)$$

### Problem 4 (20 points)

20

For a K-map, M denotes the number of prime implicants of the K-map, and N denotes the number of essential prime implicants of the K-map. Draw a  $4 \times 4$  K-map that has the largest value of  $P = M - N$  among all the  $4 \times 4$  K-maps.

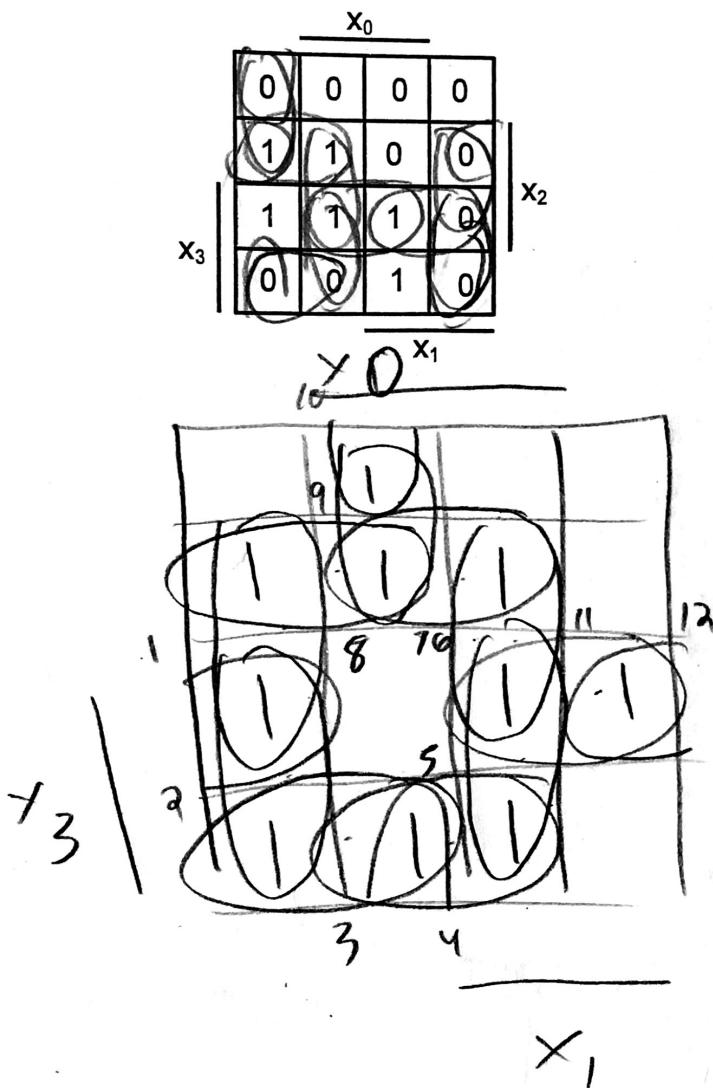For example, in the following  $4 \times 4$  K-map,  $M=3$ ,  $N=2$ ,  $P=M-N=1$ .



$$+ x_3 x_1' x_0' + x_3 x_1 x_0$$

$$+ x_2 x_1' x_0' + x_2 x_1 x_0$$

$$+ x_1 x_3 x_2 + x_3' x_0 x_1'$$

$$+ x_0' x_3 x_2 + x_2' x_0 x_1'$$

$\rightarrow$  Max # of Prime Implicants  
 $\rightarrow$  least # of Eqs

$M = 12$  prime implicants  
 $N = 0$  essential prime implicants

$$P = M - N = 12$$

$$\left. \begin{array}{l} + x_1' x_3 x_2' + x_1' x_3 x_2 \\ + x_0 x_3 x_2' + x_0 x_3 x_2 \end{array} \right\}$$

### Problem 5 (20 points)

Use only multiplexers to design a system with input  $x \in (0,1,2, \dots, 8)$ , outputs  $y$  and  $z$  that implements the following equation

$$(x)_{10} = (yz)_3$$



In the system,  $x$  is encoded as  $x_3x_2x_1x_0$  in binary.  $y$  is encoded as  $y_1y_0$  in binary, and  $z$  is encoded as  $z_1z_0$  in binary.

Note that the outputs  $y$  and  $z$  represent the two digits of a base-3 number.

For example, if  $x=7$  ( $x_3x_2x_1x_0=0111$ ), then the system will solve:  $(7)_{10} = (21)_3$ . Thus  $y = 2$  ( $y_1y_0=10$ ) and  $z = 1$  ( $z_1z_0=01$ ).


20

$y_3 + x_3$	$x_1 x_0$	$y_1 y_0$	$z_1 z_0$
0 0 0 0	0 0 0 0	0 0 0 0	00
0 0 0 1	0 0 0 1	0 0 0 1	01
0 0 1 1	0 0 1 1	0 0 1 1	02
0 1 0 0	0 1 0 0	0 1 0 0	11
0 1 0 1	0 1 0 1	0 1 0 1	12
0 1 1 1	0 1 1 1	0 1 1 1	21
1 0 0 0	1 0 0 0	1 0 0 0	22
1 0 0 1	1 0 0 1	1 0 0 1	23
1 0 1 0	1 0 1 0	1 0 1 0	30
1 0 1 1	1 0 1 1	1 0 1 1	31
1 1 0 0	1 1 0 0	1 1 0 0	32
1 1 0 1	1 1 0 1	1 1 0 1	33
1 1 1 0	1 1 1 0	1 1 1 0	40
1 1 1 1	1 1 1 1	1 1 1 1	41

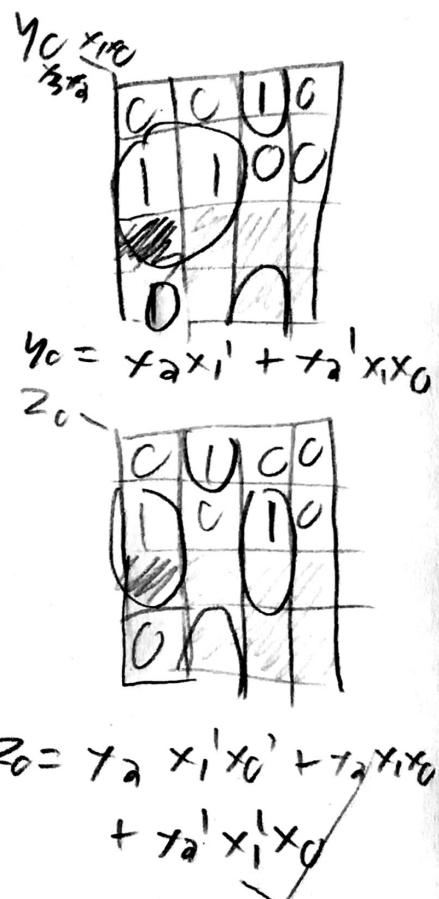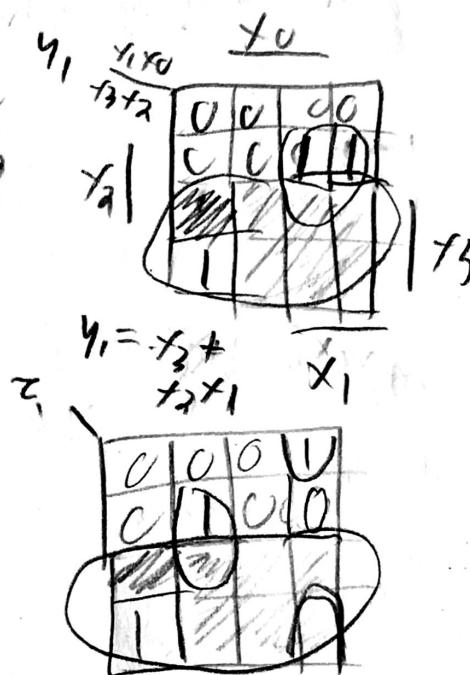




$$z_1 = y_3 + x_2 x_0 x_1' + x_2' x_0' x_1$$
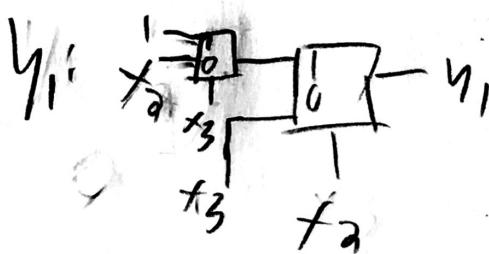
$$z_0 = x_2 x_1' x_0' + x_2 x_1 x_0' + x_2' x_1' x_0$$



$$z_1: F_{x_2} = x_0 x_1' + x_3$$

$$F_{x_2'} = x_3 + x_0' x_1$$

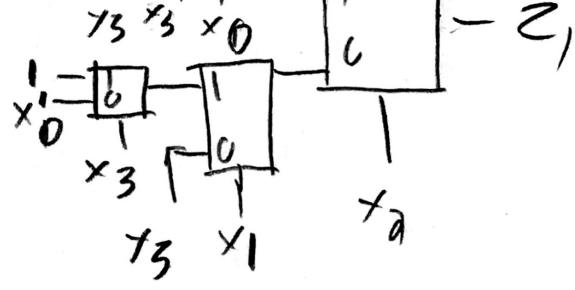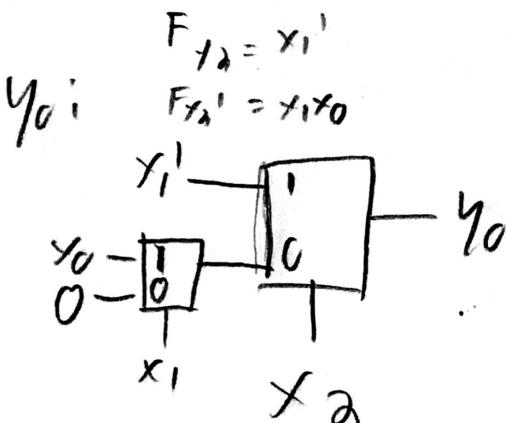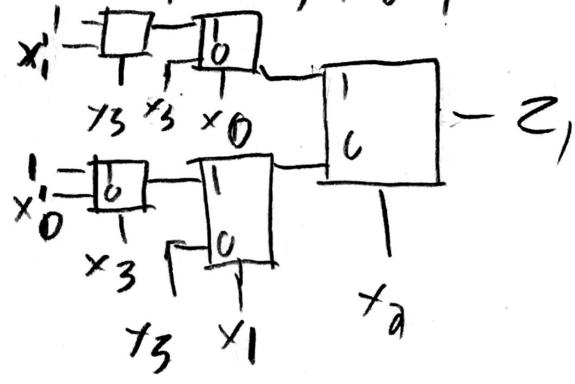


**Problem 5) Extra Page**

$$Z_0 : r_a x_1' x_0' + r_a x_1 x_0 + r_a' x_1' x_0$$

$$f_{x_2} = x_1' x_0' + x_1 x_0$$

$$f_{x_2'} = x_1' x_0$$

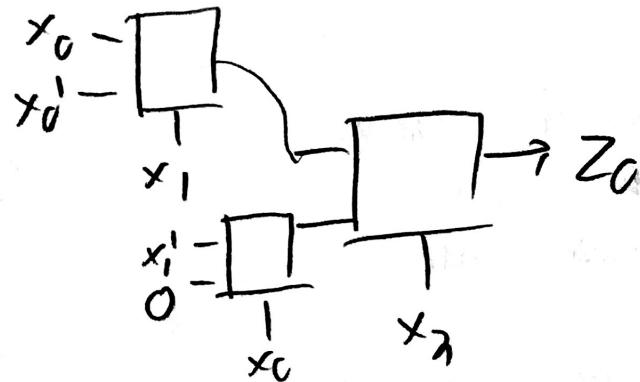

Name \_\_\_\_\_

Student ID # \_\_\_\_\_

University of California

Los Angeles

Computer Science Department

CSM51A/EEM16 Midterm Exam

Winter Quarter 2016

February 8<sup>th</sup> 2016

This is a closed book exam. Absolutely nothing is permitted except pen, pencil and eraser to write your solutions. Any academic dishonesty will be prosecuted to the full extent permissible by university regulations.

**Time allowed 100 minutes.**

Problem (possible points)	Points
1 (20)	20
2 (20)	20
3 (20)	16
4 (20)	20
5 (20)	20
Total (100)	96