

(Iza)
Name Hanna

Say

First

Last

Student ID # XXXXXXXXXX

University of California
Los Angeles
Computer Science Department

CSM51A/EEM16 Midterm Exam
Winter Quarter 2016
February 8th 2016

This is a closed book exam. Absolutely nothing is permitted except pen, pencil and eraser to write your solutions. Any academic dishonesty will be prosecuted to the full extent permissible by university regulations.

Time allowed 100 minutes.

Problem (possible points)	Points
1 (20)	20
2 (20)	20
3 (20)	20
4 (20)	16
5 (20)	20
Total (100)	96

0 20 15 20 15 15 ✓

Egate

20

Problem 1 (20 points)

Use only the "E" gate defined below to implement Boolean function:

$$F = w'xy' + wxz + w'x'z + wx'y'z'$$

You may also use constants 0 and 1 as inputs.

a	b	c	E(a,b,c)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


$$E = (a+b+c)(a'+b'+c') = ab' + ac' + a'b + bc' + a'c + bc$$

$$E(a,a,a) = (a)(a') = 0$$

$$E(a,1,1) = (a+1+1)(a'+0+0) = (1)(a') = a'$$


NOT
gate

MODULES

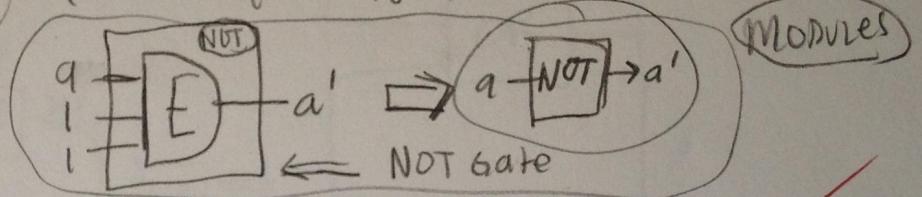

$$\begin{array}{ccccc} & ab & & b \\ & \diagdown & & \diagup \\ c & 00 & 01 & 11 & 10 \\ \diagup & 0 & 0 & 1 & 1 \\ \diagdown & 1 & 1 & 1 & 0 \\ & 1 & 1 & 0 & a \end{array}$$

$$E = bc' + ab' + a'c$$


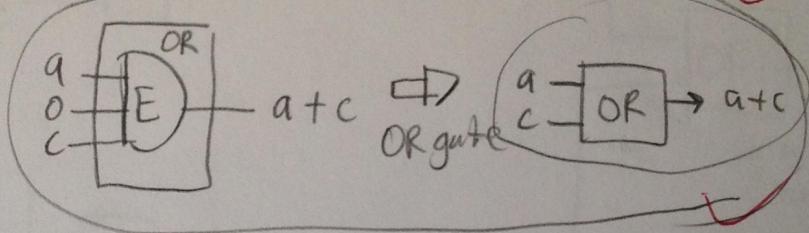


$$\text{OR } E(a,0,c) = 0 + a + a'c = a + c$$



$$\text{AND } E() = bc + 0ab + 1ac$$

$$(a'+b')' = ab$$

$$\text{NOT}(\text{OR}(\text{NOT}(a), \text{NOT}(b))) \Rightarrow \text{AND}$$

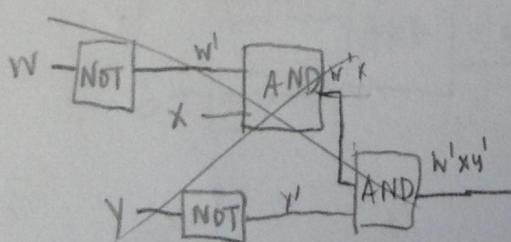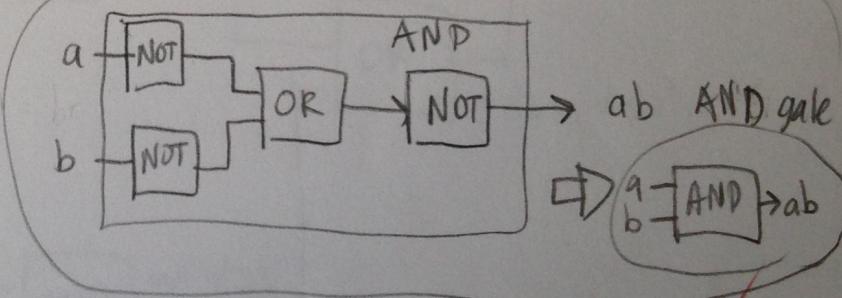

Problem 1) Extra Page

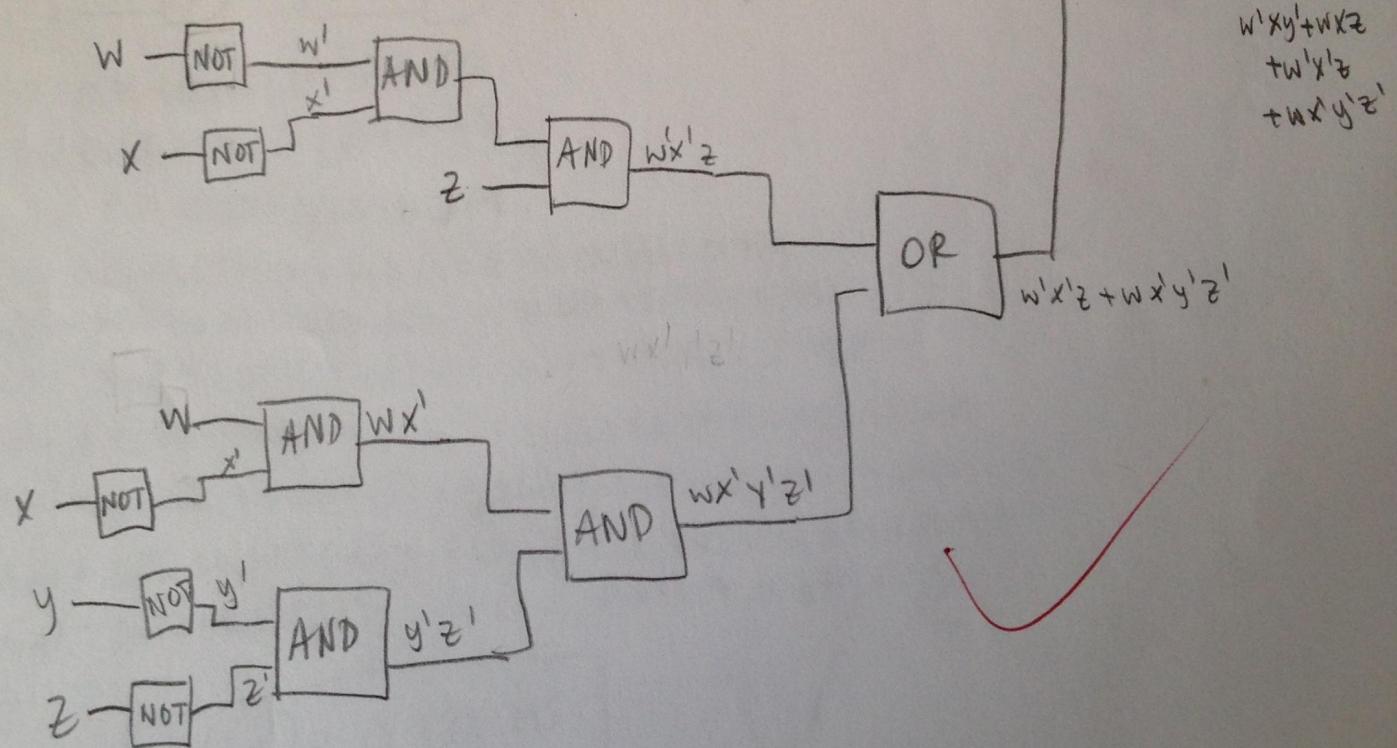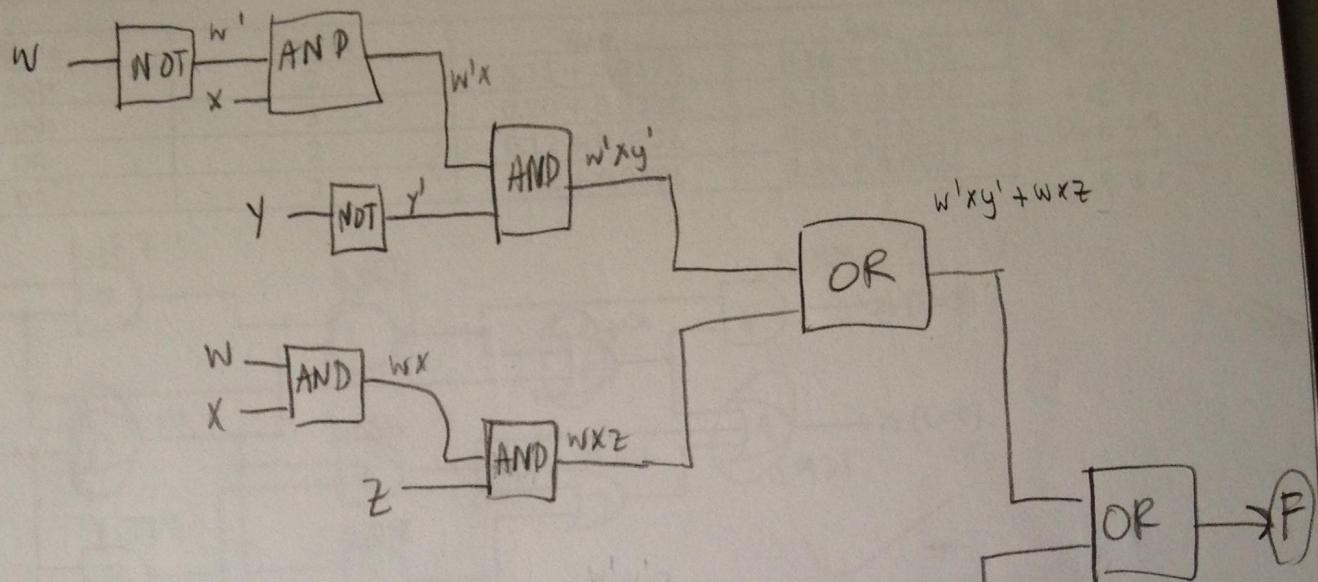


0.074	0.037	$\frac{0.637}{3}$	$\frac{0.111}{0.120}$	$\frac{0.150}{0.037}$	$\frac{0.187}{0.231}$	0.074	0.120
0.150	$\frac{0.037}{2}$	$\frac{0.637}{3}$	$\frac{0.111}{0.231}$	$\frac{0.150}{0.037}$	$\frac{0.187}{0.418}$	0.120	$\frac{0.037}{0.157}$
0.224	0.074	$\frac{0.111}{0.111}$	$\frac{0.231}{0.261}$	$\frac{0.150}{0.187}$	$\frac{0.187}{0.418}$	0.194	$\frac{0.157}{0.455}$
0.231		$\frac{0.111}{0.150}$	$\frac{0.261}{0.261}$	$\frac{0.150}{0.187}$	$\frac{0.187}{0.418}$	0.455	$\frac{0.455}{0.649}$
0.455		$\frac{0.111}{0.261}$	$\frac{0.261}{0.910}$			0.649	$\frac{0.649}{0.649}$

Problem 2 (20 points)

Given the network below, calculate the critical path delay. Consider L → H delay when calculating the critical path.

Gate	Fan-in	t_{PLH}	t_{PHL}
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$
AND	3	$0.20 + 0.038L$	$0.18 + 0.018L$
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$
OR	3	$0.12 + 0.038L$	$0.34 + 0.022L$
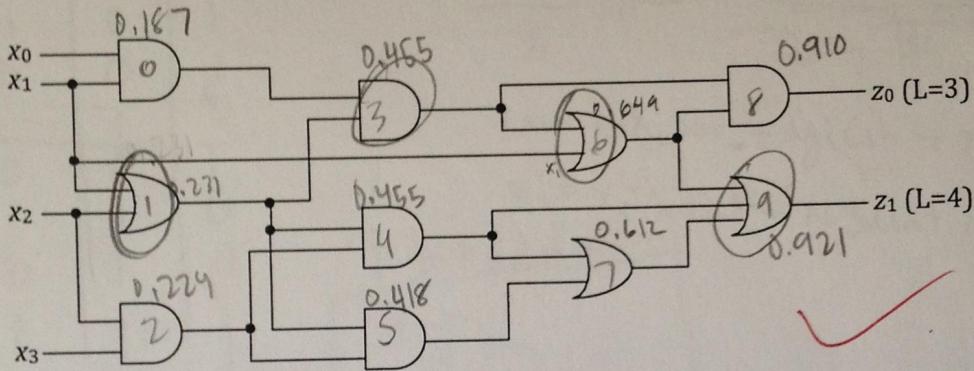
$$\begin{array}{r} 0.15 \\ 0.120 \\ \hline 0.272 \\ 0.649 \\ \hline 0.921 \end{array}$$



AND $d(G_0) = 0.15 + 0.037(1) = 0.187$

OR $d(G_1) = 0.12 + 0.037(3) = 0.231$

AND $d(G_2) = 0.15 + 0.037(2) = 0.224$

AND $d(G_3) = 0.15 + 0.037(2) + d(G_1) = 0.224 + 0.231 = 0.455$

OR $d(G_4) = 0.15 + 0.037(2) + d(G_5) = 0.224 + 0.231 = 0.455$

OR $d(G_5) = 0.15 + 0.037(1) + d(G_6) = 0.187 + 0.231 = 0.418$

OR $d(G_6) = 0.12 + 0.037(2) + d(G_3) = 0.12 + 0.074 + 0.455 = 0.649$

OR $d(G_7) = 0.12 + 0.037(1) + d(G_4) = 0.157 + 0.455 = 0.612$

AND $d(G_8) = 0.15 + 0.037(3) + d(G_6) = 0.261 + 0.649 = 0.910$

OR $d(G_9) = 0.12 + 0.038(4) + d(G_6) = 0.272 + 0.649 = 0.921$

$d(CP) = 0.921 \text{ ns}$

CP = G₁, G₃, G₆, G₉

$$10^2(11110)_2 \\ \text{adding 4-bit #} \\ \text{max } 1111 = 15$$

$$\frac{30}{2}=15 \\ \frac{15}{2}=7R1 \\ \frac{7}{2}=3R1 \\ \frac{3}{2}=1R1 \\ \frac{1}{2}=0R1 \\ \text{Problem 3 (20 points)} \quad \text{max } 15+15=30$$

$$(11110)_2 \rightarrow 5\text{bit}$$

1. 1-bit adder
2. 4-bit adder

3. have 2 + 4-bit adders for E, F



4. 1 bit cmp \rightarrow 5 bit cmp

5. 5 cmp for E & F \rightarrow selector (mux)

Four 4-bit numbers A, B, C, and D are given as inputs. E = A + B, F = C + D. Design a system that outputs the larger number between E and F. If E = F, output either E or F. You can use any type of gates to implement your design.

① 1-bit adder





x_i	y_i	c_{in}	c_{out}	z_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

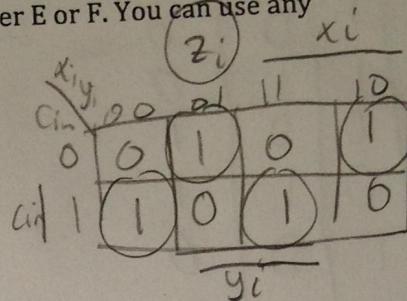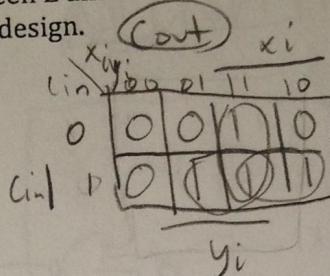

$$Cout = x_i c_{in} + y_i c_{in} + x_i y_i$$

$$z_i = x_i y_i' c_{in}' + x_i y_i c_{in} + x_i' y_i c_{in}' + x_i' y_i c_{in}$$



1-bit adder

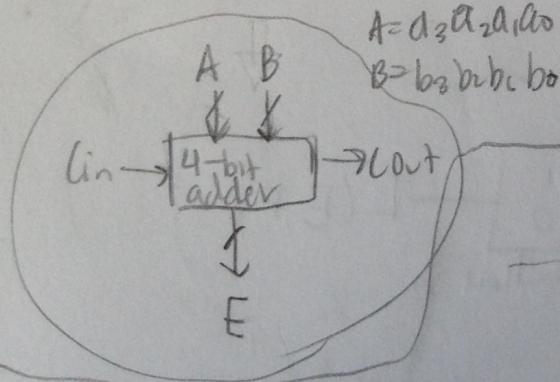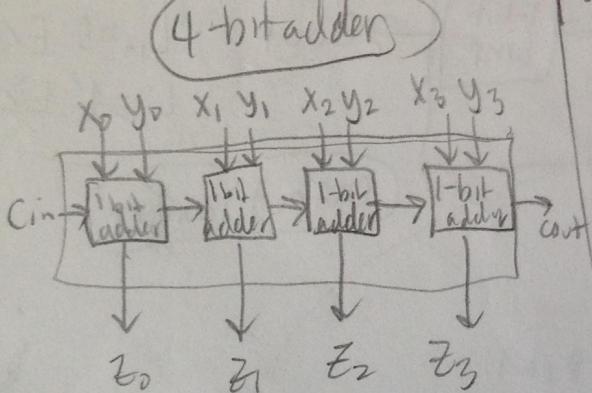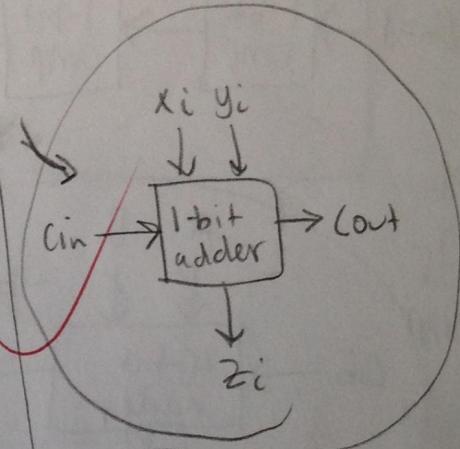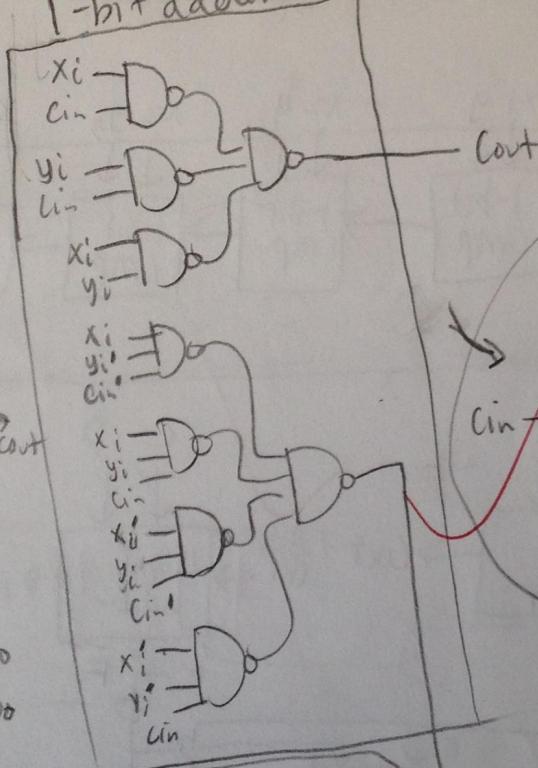

4. 1-bit comparator $X_1 Y = 4\text{ bit numbers}$


x_i	y_i	L_{in}	L_{out}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1
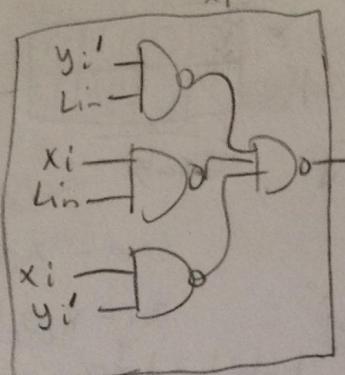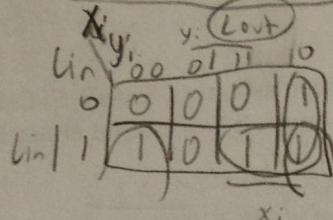
$$\begin{cases} L_{in=0} : X < Y \\ L_{in=1} : X \geq Y \end{cases}$$




least sig to most
sig bit
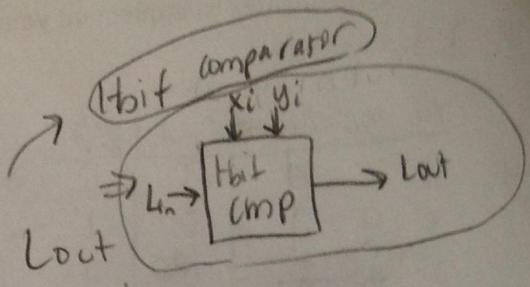
$$L_{out} = y_i' L_{in} + x_i L_{in} + x_i y_i'$$




5-bit cmp

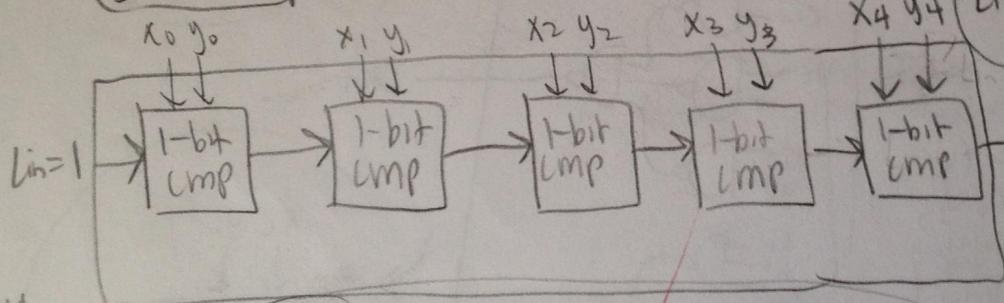

$$\begin{cases} L_{in}=0 : E < F \\ L_{in}=1 : E \geq F \end{cases}$$

Output trigger

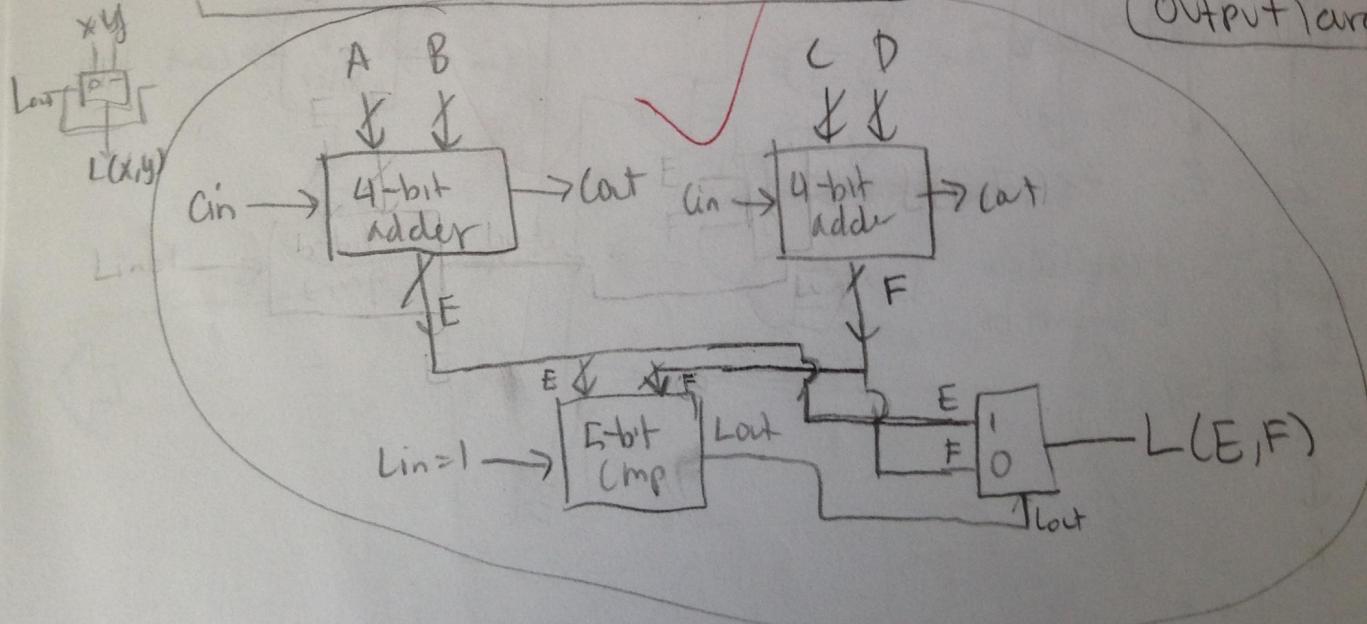

Problem 4 (20 points)

1b

M: PI
N: EPI



easier to not
don't care

value of $P = M - N$ among all the 4×4 K-maps.
= more
most #PI > EPI


For a K-map, M denotes the number of prime implicants of the K-map, and N denotes the number of essential prime implicants of the K-map. Draw a 4×4 K-map that has the largest value of $P = M - N$ among all the 4×4 K-maps.

For example, in the following 4×4 K-map, $M=3$, $N=2$, $P=M-N=1$.



		x_0	
		00	01
x_3	00	0	0
	01	1	0
x_2	10	1	1
	11	0	0
		x_1	

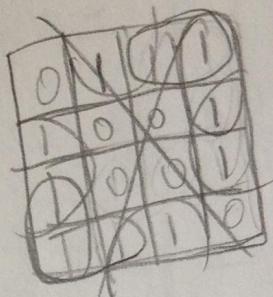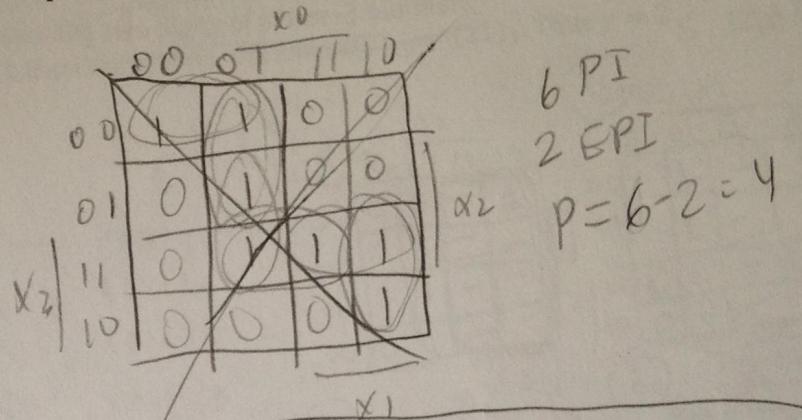



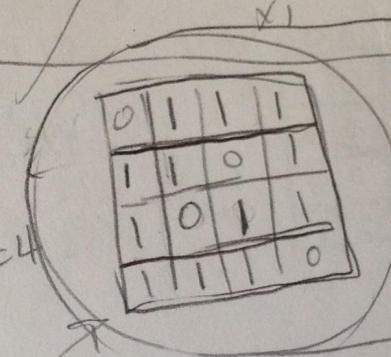
PI: (00, 01)
EPI: (01, 11)
 $P = 6 - 2 = 4$



10PI
0 EPI
 $P = 10 - 10 = 0$

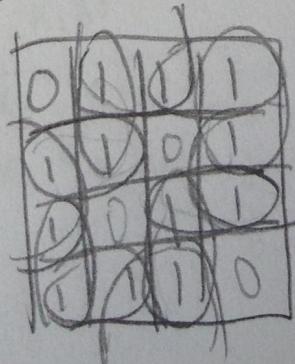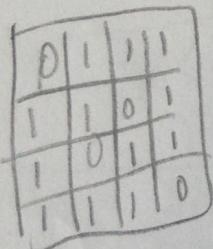

10 PI
0 EPI
 $P = 10 - 0 = 10$

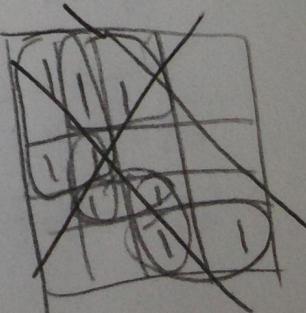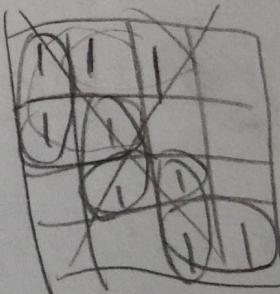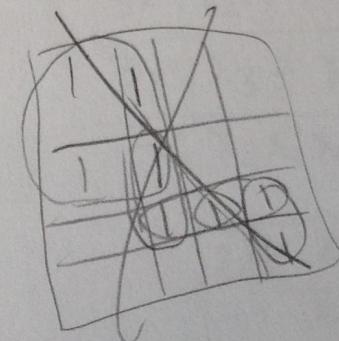

$0 \leq X \leq 8$

20 $y \leq 2 \neq 3$
 $z \leq 2 \neq 3$

Problem 5 (20 points)

Use only multiplexers to design a system with input $x \in \{0, 1, 2, \dots, 8\}$ outputs y and z that implements the following equation

$$(x)_{10} = (yz)_3$$

In the system, x is encoded as $x_3x_2x_1x_0$ in binary. y is encoded as y_1y_0 in binary, and z is encoded as z_1z_0 in binary.

Note that the outputs y and z represent the two digits of a base-3 number.

For example, if $x=7$ ($x_3x_2x_1x_0=0111$), then the system will solve: $(7)_{10} = (21)_3$. Thus $y = 2$ ($y_1y_0=10$) and $z = 1$ ($z_1z_0=01$).

	$x_3x_2x_1x_0$	y_1y_0	z_1z_0
0	0000	00	00
1	0001	00	01
2	0010	00	10
3	0011	01	00
4	0100	01	01
5	0101	01	10
6	0110	10	00
7	0111	10	01
8	1000	10	10
9	1001	—	—
10	1010	—	—
11	1011	—	—
12	1111	—	—
13	1111	—	—
14	1111	—	—
15	1111	—	—

$$y_1 < y_1x_3 = 1 + x_2x_1 = 1$$

$$y_1x_3' = y_2x_1$$

$$y_0 < y_0x_2 = x_1'$$


$$y_0x_2' = x_1x_0$$

$$z_1 < z_1x_1 = x_3 + x_2'x_0' \quad [z_1x_1x_3 = 1 + x_1'x_0' = 1]$$

$$z_1x_1x_3' = x_2'x_0$$

$$z_1 < z_1x_1 = x_3 + x_2x_0 \quad [z_1x_1x_3 = 1 + x_2x_0 = 1]$$

$$z_1x_1x_3' = x_2x_0$$

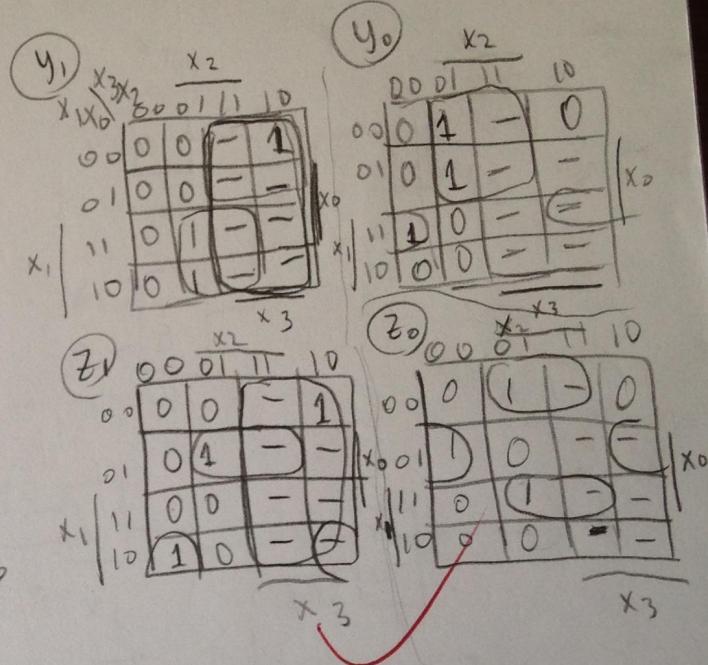

$$y_1 = x_3'x_1 + x_2x_1$$

$$y_0 = x_2x_1' + x_2'x_1x_0$$

$$z_1 = x_3 + x_2'x_1x_6' + x_2x_1'x_0$$

$$z_0 = x_2x_1'x_0' + x_2'x_1'x_0 + x_2x_1x_0$$

$$z_0 < z_0x_2 = x_1'x_0' + x_1x_0$$

$$z_0x_2' = x_1'x_0$$

$$z_0x_2x_1 = x_0$$

$$z_0x_2x_1' = x_0'$$

5 | 15 | 15 | 10 | 100

$$C = aS + bS'$$

$$aS + b - ANP$$

Problem 5) Extra Page

