

Name Megan Williams
First Last
Student ID #

University of California
Los Angeles
Computer Science Department

CSM51A/EEM16 Midterm Exam
Winter Quarter 2016
February 8th 2016

This is a closed book exam. Absolutely nothing is permitted except pen, pencil and eraser to write your solutions. Any academic dishonesty will be prosecuted to the full extent permissible by university regulations.

Time allowed 100 minutes.

Problem (possible points)	Points
1 (20)	20
2 (20)	20
3 (20)	16
4 (20)	16
5 (20)	20
Total (100)	92

Problem 1 (20 points)

Use only the "E" gate defined below to implement Boolean function:

$$F = w'xy' + wxz + w'x'z + wx'y'z'$$

You may also use constants 0 and 1 as inputs.

a	b	c	E(a,b,c)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0



$$E = (a+bc)(a'+b'+c')$$

$$E = ab' + ac' + a'b + bc' + a'c + b'c + b' + 0$$

$$(ab) \quad (ab)'' + c''$$

$$F = w'xy' + wxz + w'x'z + wx'y'z'$$

$$w'y'(x+x'z')$$

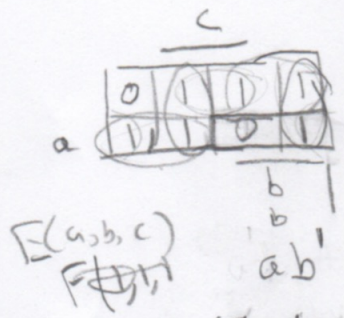
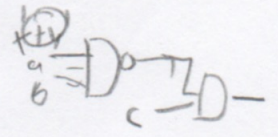


$$(ab)' = w'xy' + w'y'z' + wxz + w'x'z$$

NAND gate

$$E(a, 1, 1) = 0 + a' + 0 = a'$$
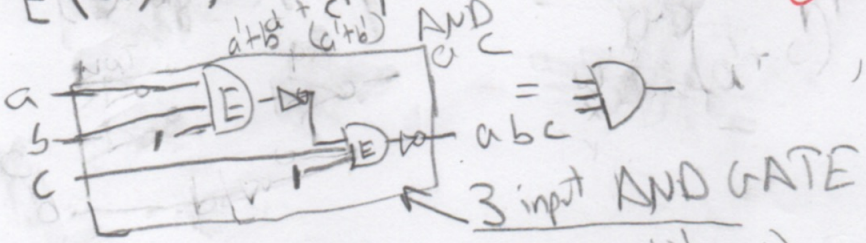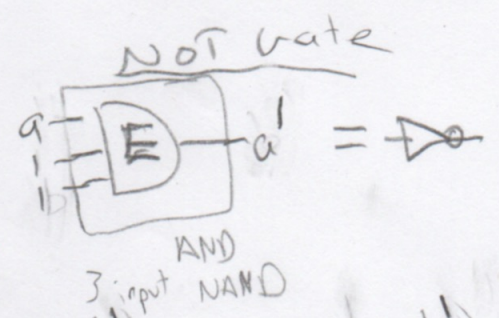
$$E(a', b', 1) = a'b + a + 0 = a + b \rightarrow \text{OR}$$





$$(a+b)(c'+b')$$

$$= (a+b)(c'+b')$$

$$= (a'+c') + b'$$

$$= (a'+c')b'$$


$$= ac'b'$$

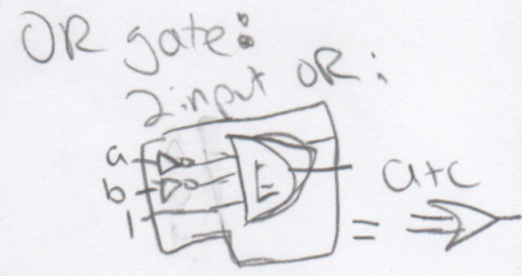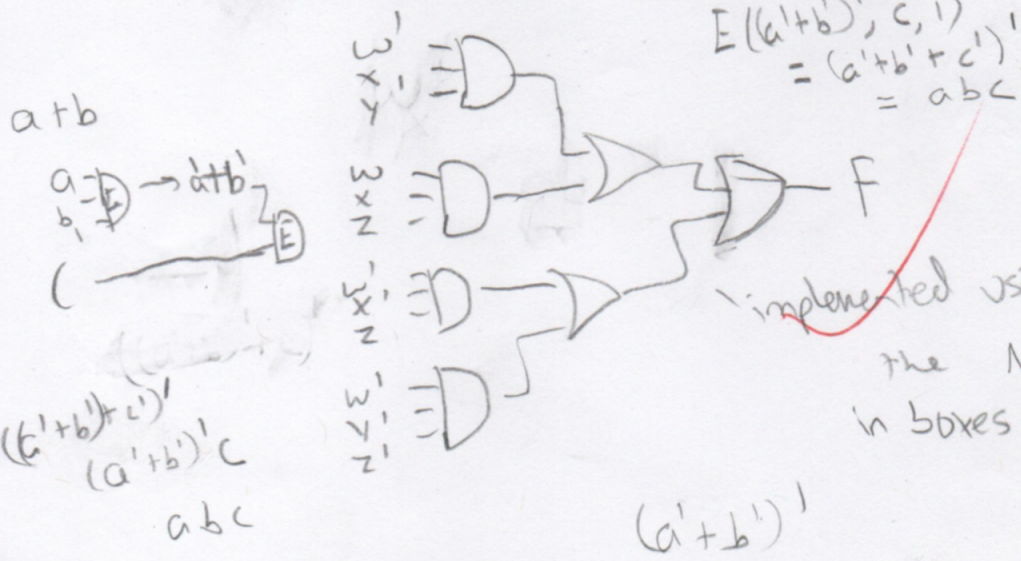

Problem 2 (20 points)

Given the network below, calculate the critical path delay. Consider L → H delay when calculating the critical path.

Gate	Fan-in	t_{pLH}	t_{pHL}
AND	2	$0.15 + 0.037L$	$0.16 + 0.017L$
AND	3	$0.20 + 0.038L$	$0.18 + 0.018L$
OR	2	$0.12 + 0.037L$	$0.20 + 0.019L$
OR	3	$0.12 + 0.038L$	$0.34 + 0.022L$

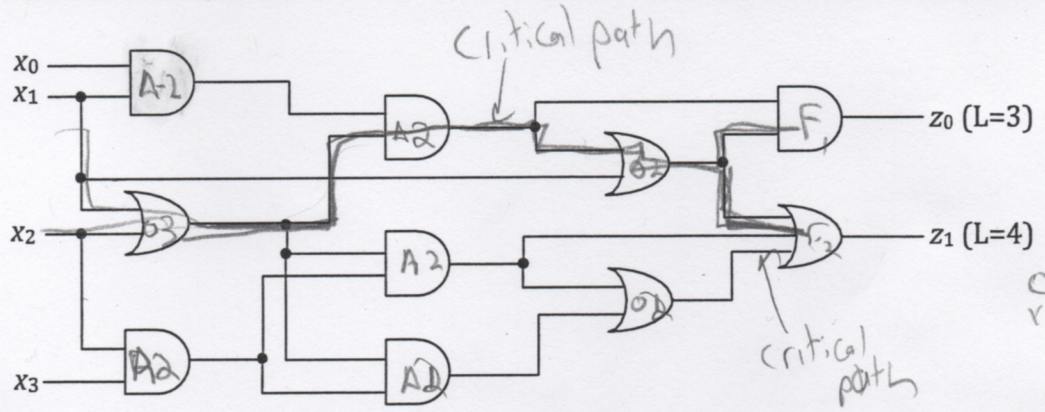

z_0 : critical path:

either $A_2 \rightarrow A_2 \rightarrow O_2 \rightarrow F$,

OR $O_3 \rightarrow A_2 \rightarrow O_2 \rightarrow F$,

O_3 - 3 outputs > A_2 - 1 output, so

$$\begin{array}{r} .24 \\ .15 \\ \hline .39 \end{array}$$

$$\begin{array}{r} .037 \\ .15 \\ \hline .261 \end{array}$$

$$\begin{array}{r} .037 \\ \times 7 \\ \hline .259 \\ + .396 \\ \hline .649 \end{array}$$

$$t_{z_0} = 0.12 + 0.037(3) + 0.15 + 0.037(2) + 0.12 + 0.037(2) + F$$

$$= 0.649 + 0.261$$

$$= 0.910$$

$$F = 0.15 + 0.037(3)$$

t_{z_1}

critical path: $A_2 \rightarrow A_2 \rightarrow O_2 \rightarrow F_2$

or: $O_3 \rightarrow A_2 \rightarrow O_2 \rightarrow F_2 \rightarrow \text{critical}$

$$t_{z_1} = 0.649 + 0.12 + 0.038(4)$$

$$= 0.921$$

$$\begin{array}{r} .038 \\ \times 4 \\ \hline .152 \\ + .649 \\ \hline .801 \\ + .12 \\ \hline .921 \end{array}$$

$$\begin{array}{r} .649 \\ .261 \\ \hline .910 \end{array}$$



16

Problem 3 (20 points)


Four 4-bit numbers A, B, C, and D are given as inputs. $E = A + B$, $F = C + D$. Design a system that outputs the larger number between E and F. If $E = F$, output either E or F. You can use any type of gates to implement your design.

$a_3 a_2 a_1 a_0$ $b_3 b_2 b_1 b_0$ $c_3 c_2 c_1 c_0$ $d_3 d_2 d_1 d_0$

Output is 5 bit $z_3 z_2 z_1 z_0$

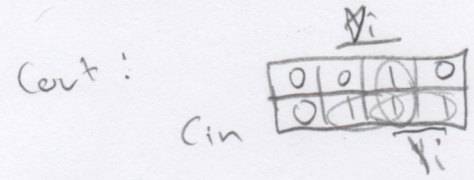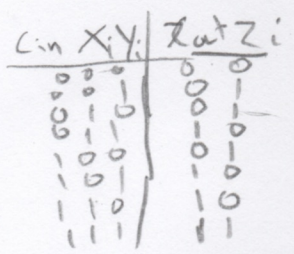


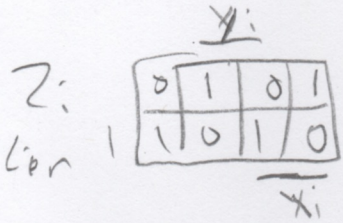$C_{out} = C_{in} Y_i + C_{in} X_i + X_i Y_i$




$Z = C_{in} Y_i' X_i' + C_{in} Y_i X_i + C_{in}' Y_i X_i' + C_{in}' X_i Y_i'$


2 bit adder

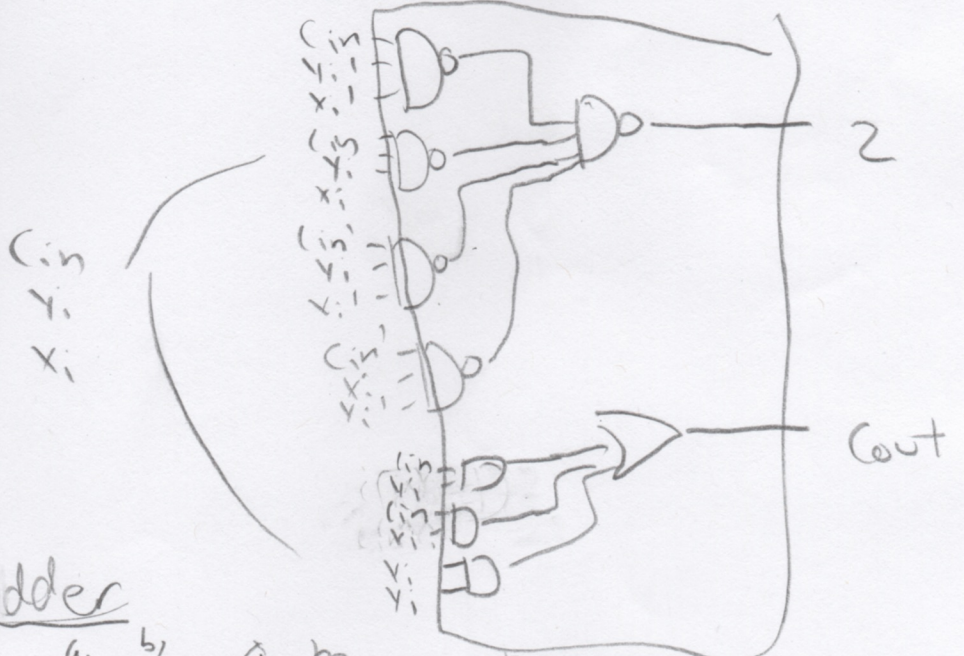

4 bit Adder


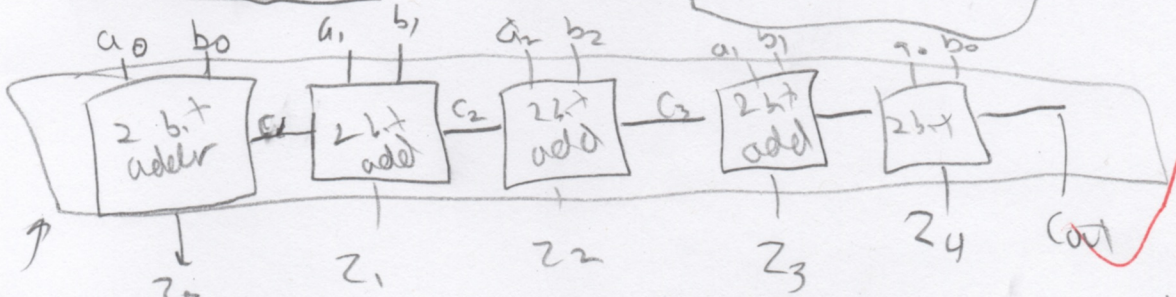


Let A, B, E be represented as

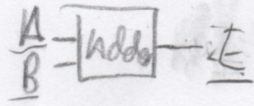

where A, B, E are 4 bit numbers

Problem 3) Extra Page

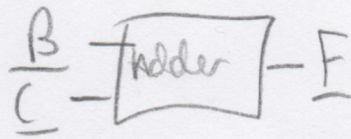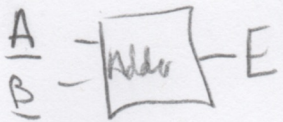

to compare $E \geq F$

E: 01010
F: 10110 → output 1011





2 bit sorter

cin	x	y	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

will output of bit that is higher

Must sort from highest bit to lowest bit

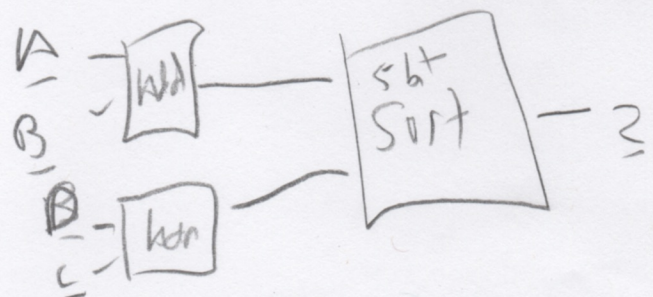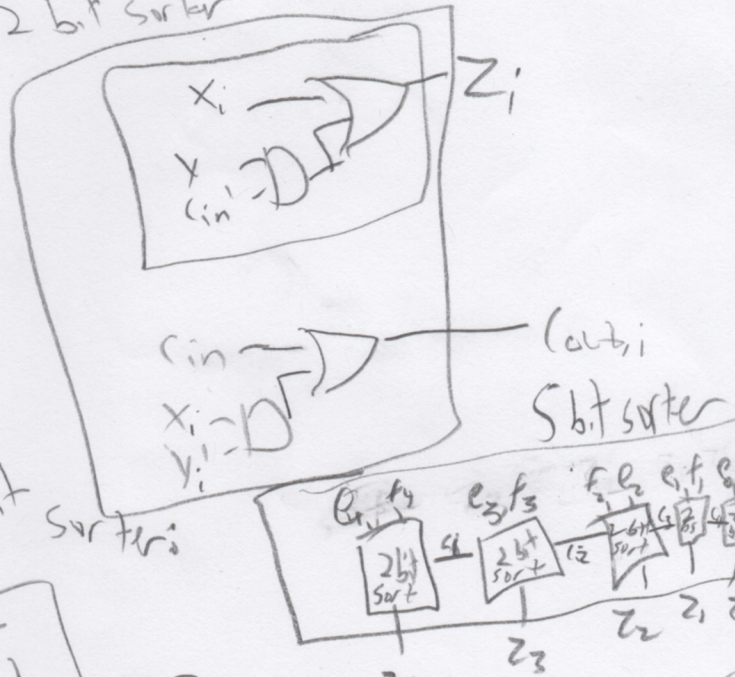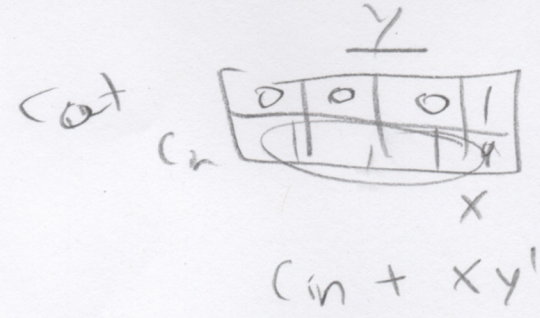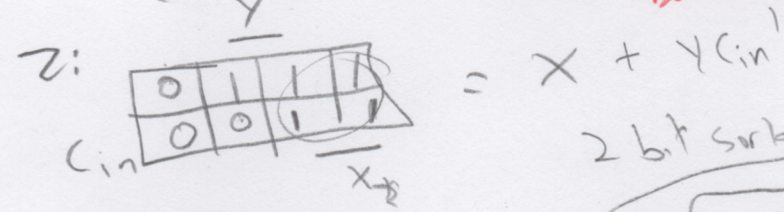1 bit because if bit is set, then we know 4 bit x is greater than 4 bit y. Not overlap the longer between each bit.



output Z is the greater of E or F


16

Problem 4 (20 points)


For a K-map, M denotes the number of prime implicants of the K-map, and N denotes the number of essential prime implicants of the K-map. Draw a 4×4 K-map that has the largest value of $P=M-N$ among all the 4×4 K-maps.

For example, in the following 4×4 K-map, $M=3$, $N=2$, $P=M-N=1$.

	x_0				
	0	0	0	0	
	1	1	0	0	x_2
x_3	1	1	1	0	
	0	0	1	0	
	x_1				

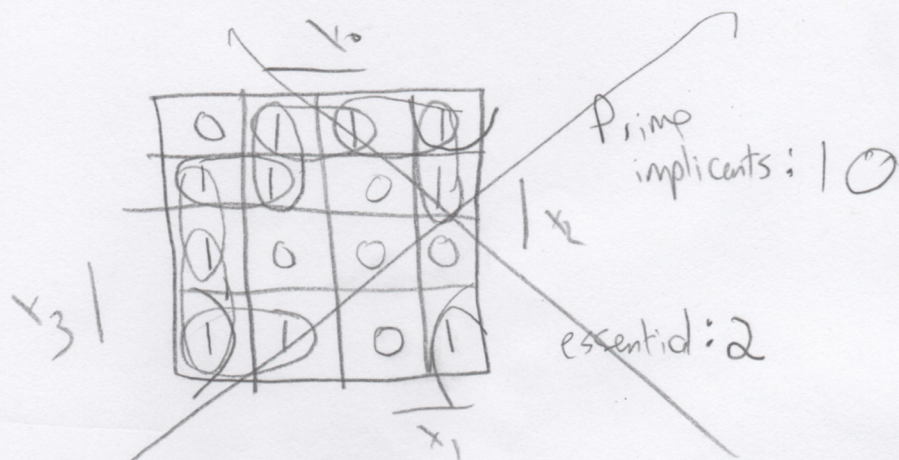

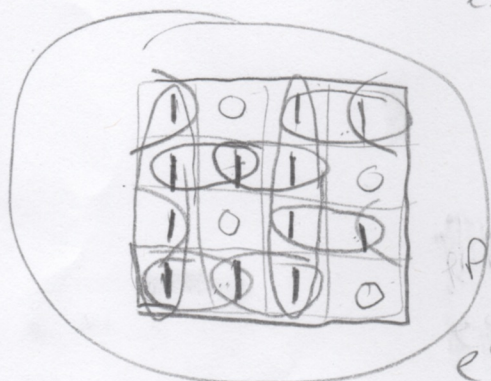Minimize SS. Prime
 maximize prime imp \rightarrow use 2×2 , 1×2 prime implicants



$M-N=8$

Prime imp: 10
 essential prime imp: 0

$P=10$

Problem 5 (20 points)

Use only multiplexers to design a system with input $x \in (0,1,2, \dots, 8)$, outputs y and z that implements the following equation


$$(x)_{10} = (yz)_3$$

In the system, x is encoded as $x_3x_2x_1x_0$ in binary. y is encoded as y_1y_0 in binary, and z is encoded as z_1z_0 in binary.

Note that the outputs y and z represent the two digits of a base-3 number.


For example, if $x=7$ ($x_3x_2x_1x_0=0111$), then the system will solve: $(7)_{10} = (21)_3$. Thus $y = 2$ ($y_1y_0=10$) and $z = 1$ ($z_1z_0=01$).

x	x_3	x_2	x_1	x_0	y_1	y_0	z_1	z_0
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	0
3	0	0	1	1	0	1	0	0
4	0	1	0	0	1	0	0	0
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	1	0
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	0

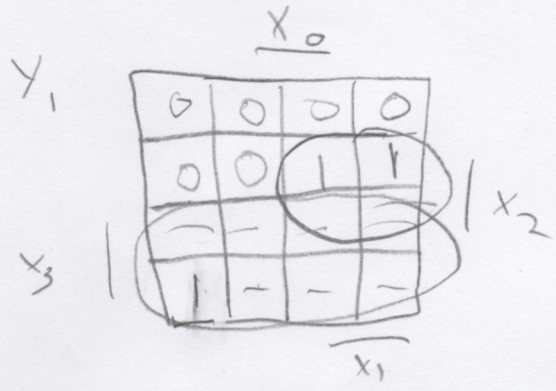


$$y_1 = x_2x_3 + x_3$$


→ don't care

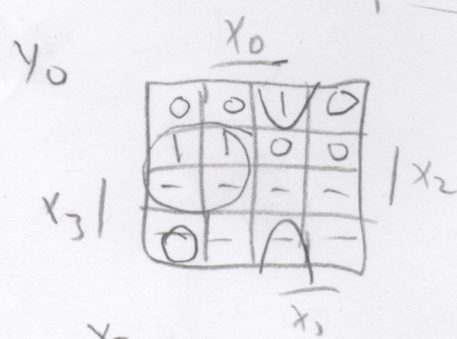

$$y_0 = x_2x_1' + x_2'x_1x_0$$

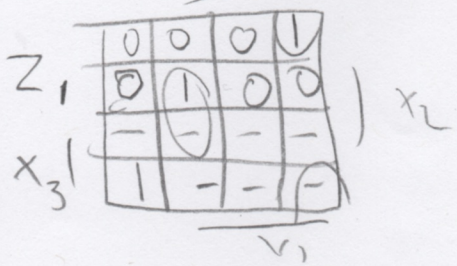

$$z_1 = x_3 + x_2x_0x_1' + x_2'x_0x_1'$$

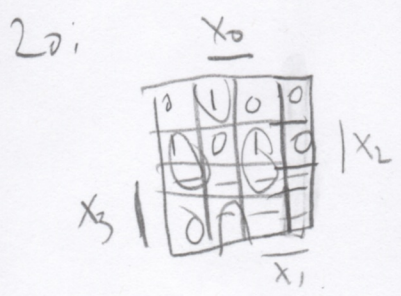


$$z_0 = x_2x_1x_0 + x_2x_1'x_0' + x_2'x_0x_1'$$

Problem 5) Extra Page

$$Y_1 = x_2 x_1 + x_3$$

NOT gate:

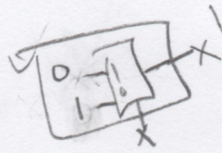

$$f_{x_3} = 1$$

$$f_{x_3'} = x_2 x_1$$

$$f_{x_3' x_2} = x_1$$

$$f_{x_3' x_2'} = 0$$

$$Y_0 = x_2 x_1' + x_2' x_1 x_0$$

$$f_{x_2} = x_1'$$

$$f_{x_2'} = x_1 x_0$$

$$f_{x_2' x_1} = x_0$$

$$f_{x_2' x_1'} = 0$$

$$Z_1 = x_3 + x_2 x_0 x_1' + x_2' x_1 x_0'$$

$$f_{x_3} = 1$$

$$f_{x_3'} = x_2 x_0 x_1' + x_2' x_1 x_0'$$

$$f_{x_3' x_2} = x_0 x_1'$$

$$f_{x_3' x_2 x_1} = 0$$

$$f_{x_3' x_2'} = x_1 x_0$$

$$f_{x_3' x_2 x_1'} = x_0$$

$$f_{x_3' x_2' x_1} = x_0'$$

$$f_{x_3' x_2' x_1'} = 0$$

$$Z_0 = x_2 x_1 x_0 + x_2 x_1' x_0' + x_2' x_0 x_1'$$

$$f_{x_2} = x_1 x_0 + x_1' x_0'$$

$$f_{x_2 x_0} = x_1$$

$$f_{x_2'} = x_0 x_1'$$

$$f_{x_2 x_0'} = x_1'$$

$$f_{x_2' x_0} = x_1'$$

$$f_{x_2' x_0'} = 0$$

