

Name Kevin

Huynh

First

Last

Student ID #

University of California

Los Angeles

Computer Science Department

CSM51A/EEM16 Midterm Exam #2

Winter Quarter 2015

February 23rd 2015

This is a closed book exam. Absolutely nothing is permitted except pen, pencil and eraser to write your solutions. Any academic dishonesty will be prosecuted to the full extent permissible by university regulations.

Time allowed 100 minutes.

Problem (possible points)	Points
1 (20)	19
2 (20)	20
3 (20)	20
4 (20)	2
5 (20)	12
Total (100)	73

59


14

19

$$Q(t+1) = Q(t)K'(t) + Q'(t)J(t)$$

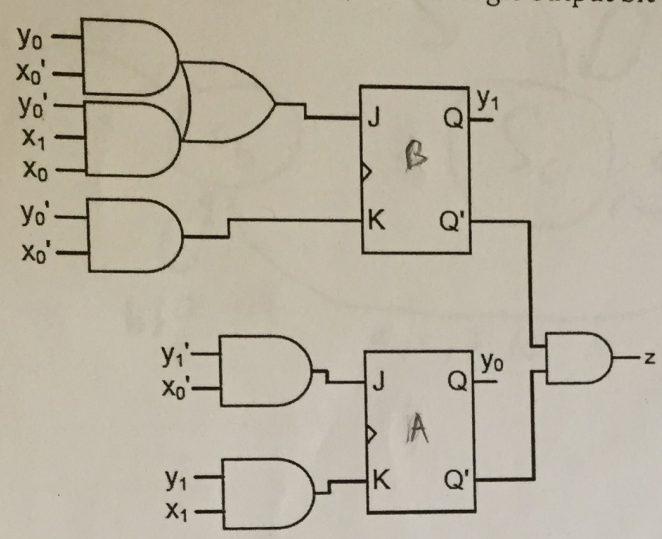Problem 1 (20 points)

Obtain a high-level description (state transition table) of the network shown in the figure below. The system has two input bits x_1 and x_0 , with a single output bit z .



PS	J(t)		K(t)	
	00	01	10	11
0	0	0	1	1
1	1	0	1	0

$$J_B = y_0 x_0' + y_0' x_1 x_0 \quad K_B = y_0' x_0'$$

$$Q_B(t+1) = Q_B (y_0' x_0')' + Q_B' (y_0 x_0' + y_0' x_1 x_0)$$

$$= y_1 (y_0' x_0')' + y_1' (y_0 x_0' + y_0' x_1 x_0)$$

$$J_A = y_1' x_0' \quad K_A = y_1 x_1$$

$$Q_A(t+1) = Q_A (y_1 x_1)' + Q_A' (y_1' x_0')$$

$$= y_0 (y_1 x_1)' + y_0' (y_1' x_0')$$


$$z = y_1' y_0'$$

PS $y_1 y_0$	NS, z $x_1 x_0$				z
	$x=00$	$x=01$	$x=10$	$x=11$	
00	01	01	01	10	1
01	11	01	11	11	0
10	00	10	00	10	0
11	11	11	10	10	0

PS	a	00	PS	x=a	NS, z	x=b	x=c	x=d
b	01	S_a	S_b	S_a	S_b	S_c		
c	10	S_b	S_d	S_b	S_d	S_d		
d	11	S_c	S_a	S_c	S_a	S_c		

next page

Problem 1) Extra Page

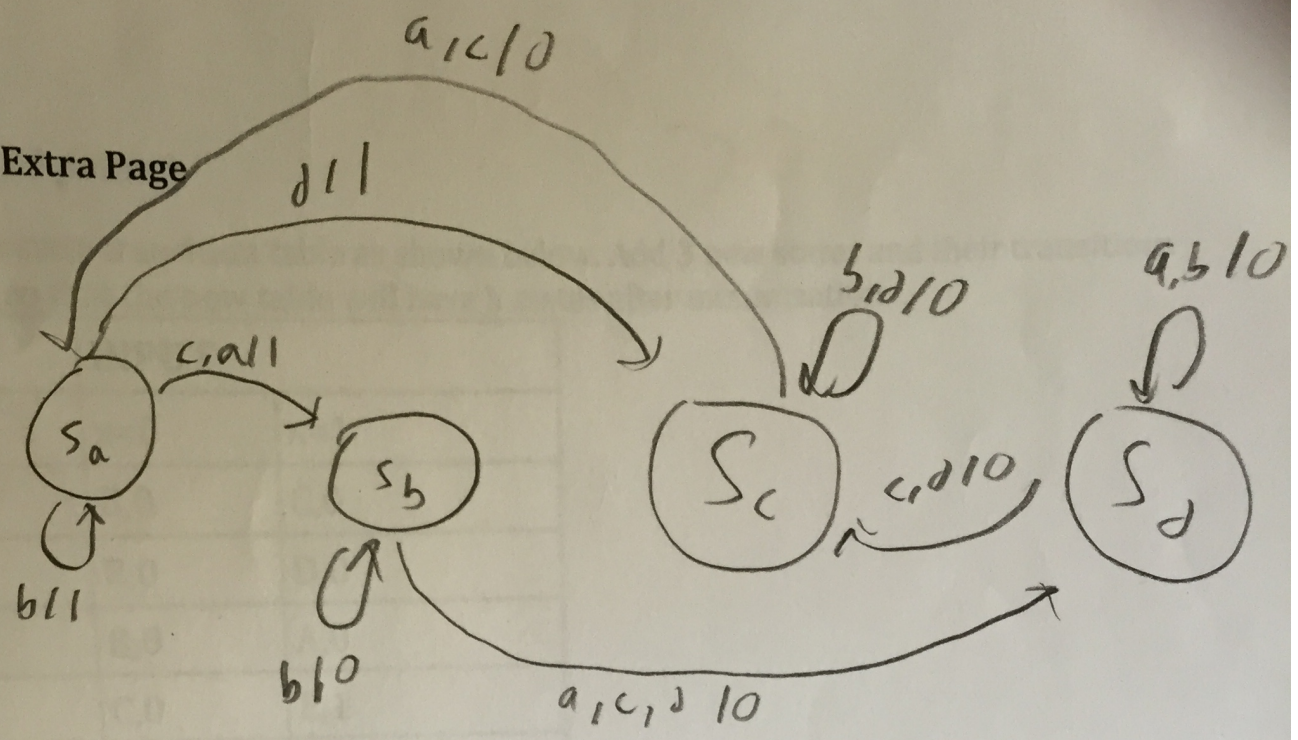

Problem 2 (20 points)

70

Consider the state transition table as shown below. Add 3 new states and their transitions to the table, so that the new table will have 5 states after minimization.

PS	INPUT	
	x=0	x=1
A	B,0	C,0
B	B,0	D,0
C	B,0	A,0
D	C,0	E,1
E	E,1	F,1
F	F,1	E,1

Handwritten notes and diagrams:

G, H, J are circled. Below them are handwritten labels: P_1 and P_2 .

Diagram 1 (under P_1):

	A	B	C
A	1	1	1
B	1	2	1
C	1	2	3

Diagram 2 (under P_2):

	A	C	B	D	E	F	G	H	I
A	2	2			4	4	5	5	5
C	1	1			4	4	5	5	5

PS	INPUT	
	x=0	x=1
A	B,0	A,0
B	B,0	D,0
D	A,0	E,1
E	E,1	E,1

G	G,1	H,0
H	G,1	I,0
I	G,1	G,0

3 new states

I will add G, H, I

next page

Problem 2) Extra Page

~~original~~ table with 3 new states

G	G, 1	H, 0
H	G, 1	T, 0
I	G, 1	G, 0

fully minimized table after adding 3 states

PS	Input	
	x=0	x=1
A	B, 0	A, 0
B	B, 0	D, 0
D	A, 0	E, 1
E	E, 1	E, 1
G	G, 1	G, 0

Problem 3 (20 points)

Using RD flip-flops as defined below, design a system as described below. Use only multiplexers to implement your combinational logic.

Input set: {a, b, c}


Output: 1, if $x(t-n, t) = a[b|c]^*d^+a$
 0, otherwise

abbcabc
ac

Note: * denotes a character can appear 0 to infinite number of times.
 + denotes a character can appear 1 to infinite number of times.
 b|c denotes b or c.
 For example, given abcbbdda, the output should be 1.

abcbbdda

	RD			
PS, Q(t)	00	01	10	11
0	1	0	0	1
1	1	0	1	0
	NS, Q(t+1)			

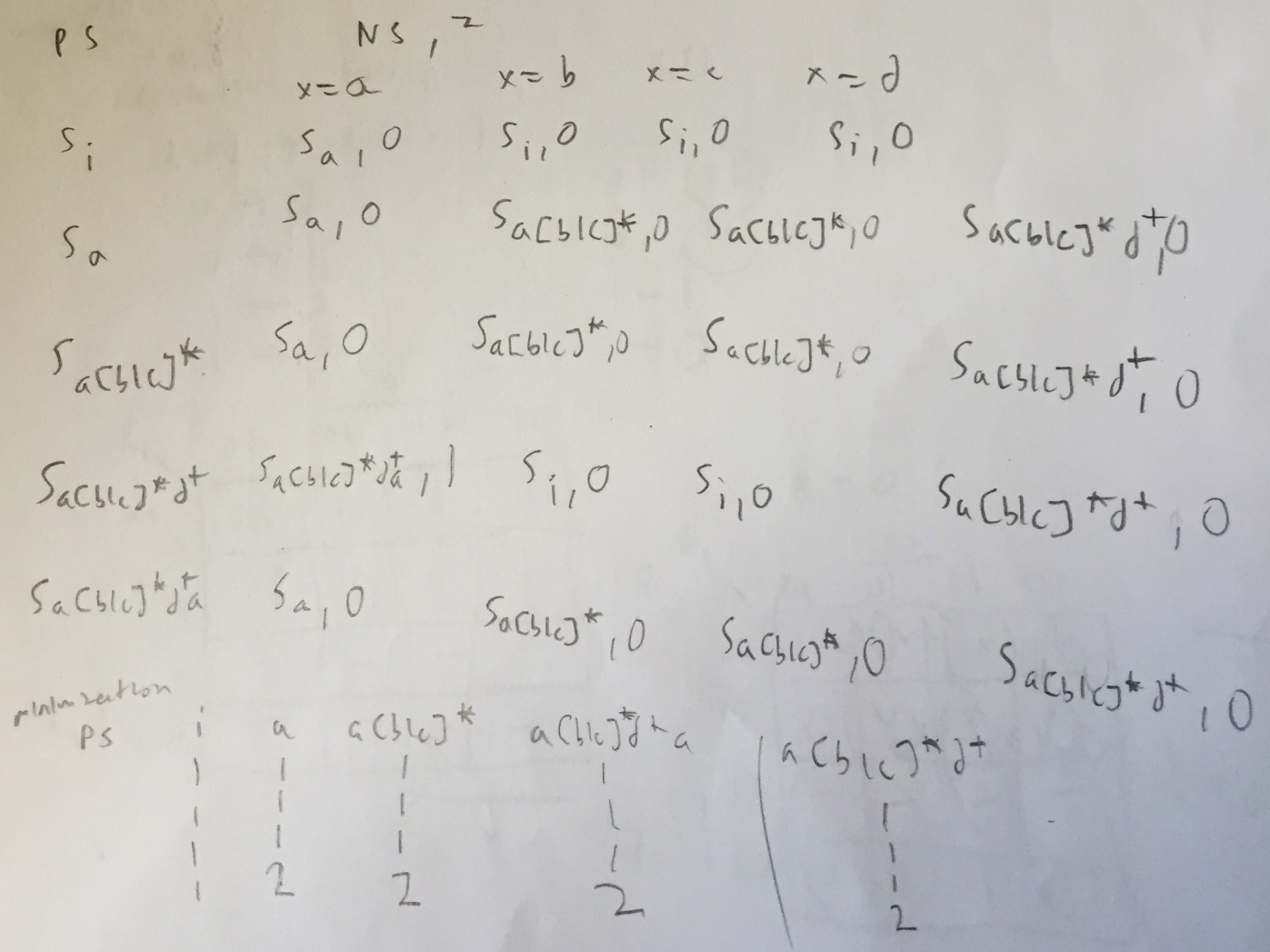

Problem 3) Extra Page

	1	2	3
i	a	$a(blc)^*$	$a(blc)^*d^+a$
2	2	2	2
1	2	2	2
1	3	3	3
1			

minimized $x = a$ $x = b$ $x = c$ $x = d$

PS

S_i	00	01, 0	00, 0	00, 0	00, 0
$S_{a(cbc)^*d}$	1	01, 0	01, 0	01, 0	10, 0
$S_{a(cbc)^*d^+a}$	10	01, 1	00, 0	00, 0	10, 0

excitation table

$a(t) \rightarrow a(t+1)$

- 0 \rightarrow 0
- 0 \rightarrow 1
- 1 \rightarrow 0
- 1 \rightarrow 1 x_0

RD

- 01
- 10
- 00
- 11
- 1
- 0

R_1	00	01	10	11
00	0	1	1	1
01	0	1	1	1
11	-	-	-	-
10	-	-	-	-

$R_i = Q_i'$

Q_0	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	-	-	-	-
10	1	1	0	1

$D = Q_1 x_1' + Q_0 y_1 x_0 + Q_1 y_1 x_0' x_1$

		x_0			
		00	01	11	10
Q_0	00	1	1	1	1
	01	-	-	-	-
	11	-	-	-	-
Q_1	10	1	1	1	1

Q_0


$$P_0 = Q_0'$$

		x_0	x_1		
		00	01	11	10
Q_0	00	1	0	0	0
	01	0	0	1	0
	11	-	-	-	-
Q_1	10	1	0	0	0

Q_0

x_1

$$D_0 = Q_0 x_1 x_0 + Q_0' y_1' y_0'$$

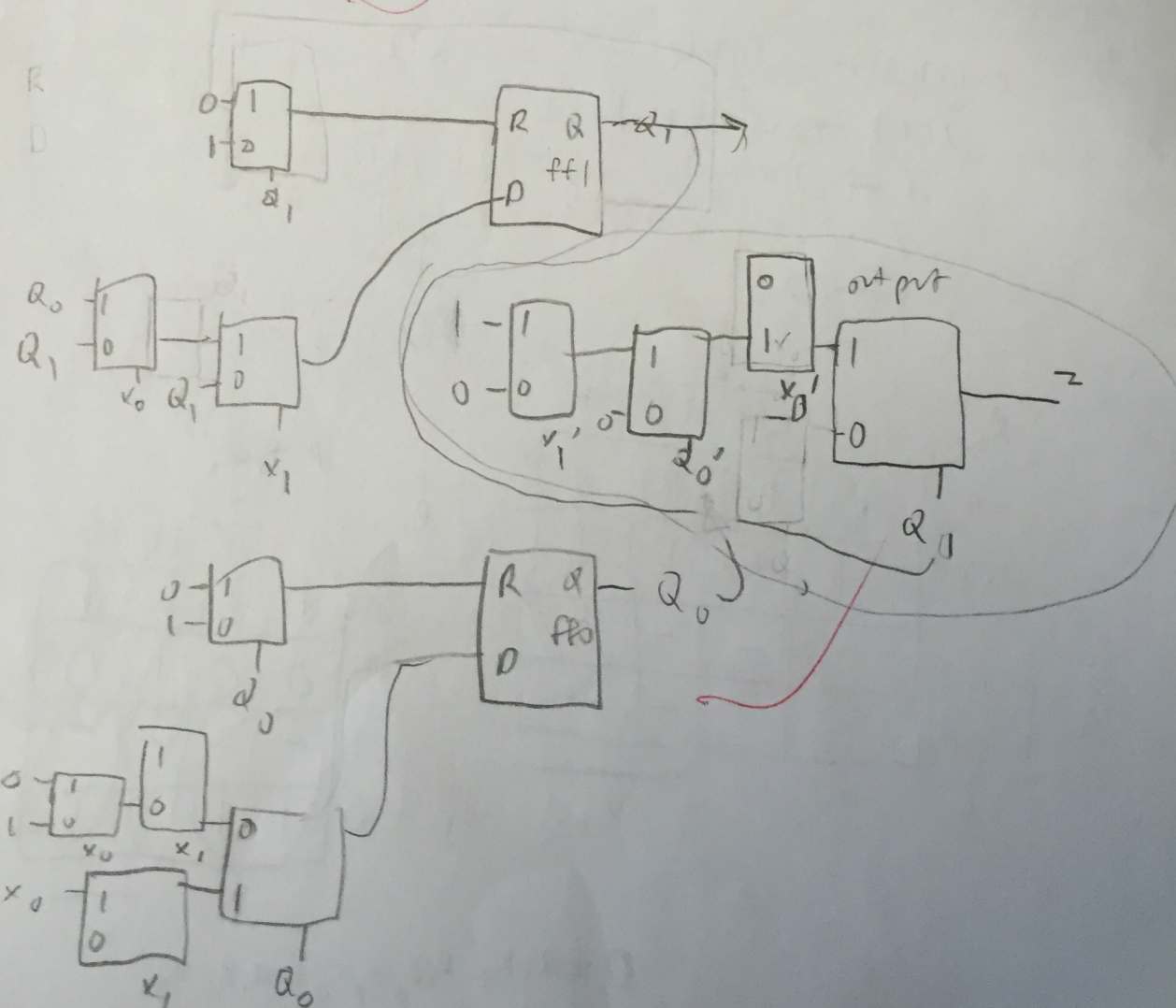

Problem 4 (20 points)


10011001
100110
1001

2



Given an input stream of 0s and 1s, design a system that outputs the length, Z , of the largest palindrome found in the last 7 inputs, along with the parity, P , of the length of that palindrome. A palindrome is a string that is spelled the same forwards as it is backwards. For example, the following strings are palindromes: 10101, 11, 1001, 0000. P is equal to 1 when the length of the palindrome is odd, and 0 when its length is even. Your system should only consider palindromes of length 2 to 7.

For example, given the following input stream, 1010101, the output should be $Z=7$ and $P=1$. For the input stream, 1010000, the output should be $Z=4$ and $P=0$.

Use any type, any number of flip-flops and combinational gates of your choosing to implement this system.

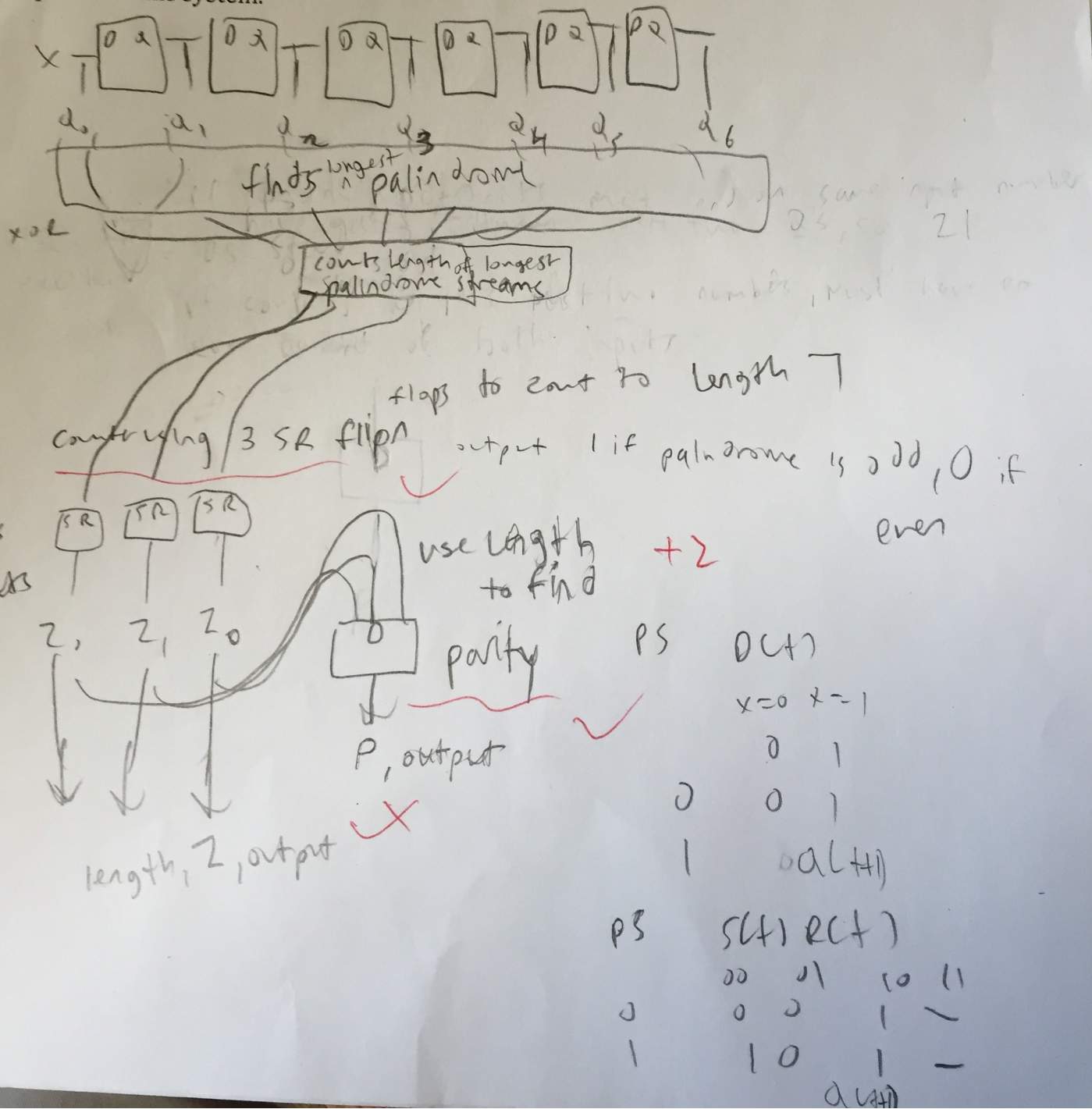

Problem 5) Extra Page

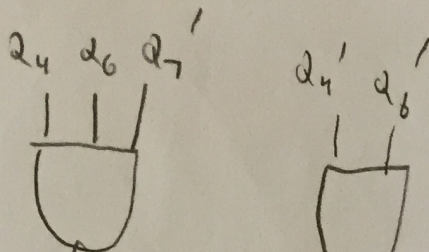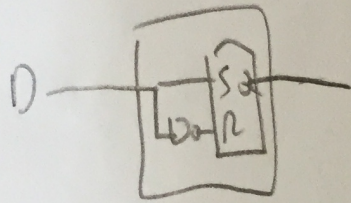

these 3's come from
between the
D flip flops
using NOT gate

