

Name Kristen Chui

First Last

Student ID # 104289172

University of California
Los Angeles
Computer Science Department

CSM51A/EEM16 Midterm Exam #2

Winter Quarter 2015

February 23rd 2015

This is a closed book exam. Absolutely nothing is permitted except pen, pencil and eraser to write your solutions. Any academic dishonesty will be prosecuted to the full extent permissible by university regulations.

Time allowed 100 minutes.


Problem (possible points)	Points
1 (20)	18
2 (20)	20
3 (20)	17
4 (20)	17
5 (20)	12
Total (100)	84

38

46

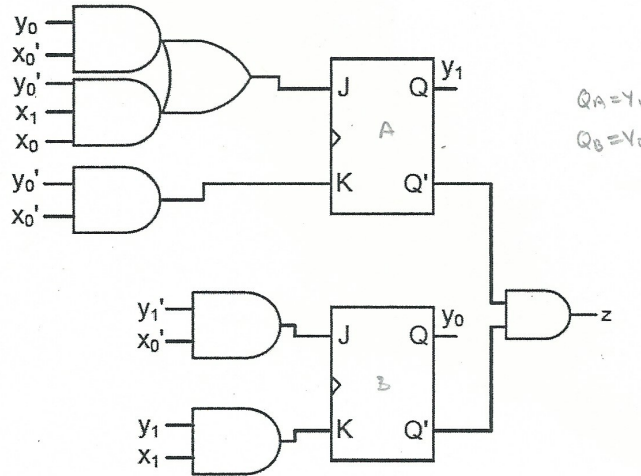Problem 1 (20 points)

Obtain a high-level description (state transition table) of the network shown in the figure below. The system has two input bits x_1 and x_0 , with a single output bit z .



$Q_A = y_1$
 $Q_B = y_0$

$Q(t+1) = Q_A K' + Q_A' Z$

$J_A = x_0' y_0 + x_0 x_1 y_0'$
 $K_A = x_0' y_0'$
 $J_B = x_0' y_1'$
 $K_B = x_1 y_1$
 $Z = y_0 y_1 + Q_A'$

$Q_A(t+1) = Q_A (x_0' y_0') + Q_A' (x_0' y_0 + x_0 x_1 y_0')$
 $= Q_A (x_0 + y_0) + Q_A' (x_0' y_0 + x_0 x_1 y_0')$
 $= Q_A x_0 + Q_A y_0 + Q_A' x_0' y_0 + Q_A' x_0 x_1 y_0'$
 $= Q_A x_0 + y_0 (Q_A + Q_A' x_0') + Q_A' x_0 x_1 y_0'$
 $= Q_A x_0 + Q_A y_0 + x_0' y_0 + Q_A' x_0 x_1 y_0'$

$Q_B(t+1) = Q_B (x_1 y_1) + Q_B' (x_0' y_1')$
 $= Q_B (x_1 + y_1) + Q_B' x_0' x_1'$
 $= Q_B x_1 + Q_B y_1 + Q_B' x_0' x_1'$
 $= x_1 (Q_B + Q_B' x_0') + Q_B y_1$
 $= Q_B x_1 + x_1' x_0' + Q_B y_1$

$Q_A(t+1) = x_0 y_1 + y_1 y_0 + x_0' y_0 + x_1' x_0 x_1 y_0'$

$Q_B(t+1) = y_0 x_1' + x_1' x_0' + y_0 y_1$

$Z = y_1 y_0'$

-2

y_1, y_0	x_1, x_0			
PS	00	01	10	11
s_1	01, 1	00, 1	00, 1	10, 1
s_2	01, 0	01, 0	11, 0	01, 0
s_3	00, 0	10, 0	00, 0	10, 0
s_4	11, 0	11, 0	10, 0	10, 0

bring

PS	Next	Input	Output
00	s_1	00	a
01	s_2	01	b
10	s_3	10	c
11	s_4	11	d

PS	a	b	c	d
s_1	s_2, Y	s_1, Y	s_1, Y	s_3, Y
s_2	s_2, N	s_2, N	s_4, N	s_2, N
s_3	s_1, N	s_3, N	s_1, N	s_3, N
s_4	s_4, N	s_4, N	s_3, N	s_3, N

High level state transition table

20

Problem 2 (20 points)

Consider the state transition table as shown below. Add 3 new states and their transitions to the table, so that the new table will have 5 states after minimization.

PS	INPUT	
	x=0	x=1
A	B,0	C,0
B	B,0	D,0
C	B,0	A,0
D	C,0	E,1
E	E,1	F,1
F	F,1	E,1

Current table

1 eq: {A, B, C} ①

{D} ②

{E, F} ③

2 eq:

PS	x=0	x=1
A	1	1
B	1	2
C	1	1

{A, C} ① {B} ② {D} ③ {E, F} ④

PS	x=0	x=1
E	3	3
F	3	3

3 eq:

PS	x=0	x=1
A	2	1
C	2	1

PS	x=0	x=1
E	4	4
F	4	4

To make 5 states after minimization by adding 3 new states:

minimized \Rightarrow {A, C} {B} {D} {E, F} = 4 states table

minimized = {A, C} {B} {D} {E, F} {G, H, I}

PS	x=0	x=1
A	B,0	C,0
B	B,0	D,0
C	B,0	A,0
D	C,0	E,1
E	E,1	F,1
F	F,1	E,1
G	H,1	G,0
H	G,1	G,0
I	I,1	I,0

NS, Z

1 eq: {A, B, C} ①
 2 eq: {D} ②
 3 eq: {E, F} ③
 4 eq: {G, H, I} ④

2 eq:

PS	x=0	x=1
A	1	1
B	1	2
C	1	1

PS	x=0	x=1
G	4	4
H	4	4
I	4	4

\Rightarrow {A, C} {B} {D} {E, F} {G, H, I}

3 eq:

PS	x=0	x=1
A	2	1
C	2	1

PS	x=0	x=1
E	4	4
F	4	4

PS	x=0	x=1
G	5	5
H	5	5
I	5	5

Problem 3 (20 points)

Using RD flip-flops as defined below, design a system as described below. Use only multiplexers to implement your combinational logic.

Input set: $\{a, b, c\}$ $\{0, 1, \dots\}$
 Output: 1, if $x(t-n, t) = a[b|c]^*d^+a$
 0, otherwise

Note: * denotes a character can appear 0 to infinite number of times.
 + denotes a character can appear 1 to infinite number of times.
 b|c denotes b or c.
 For example, given abcddda, the output should be 1.


	RD			
PS, Q(t)	00	01	10	11
0	1	0	0	1
1	1	0	1	0
	NS, Q(t+1)			

	RD			
PS	00	01	10	11
0	1	0	0	1
1	1	0	1	0

NS

	RD	
0	01	10
1	00	11
1	-1	-0

State transition diagram:

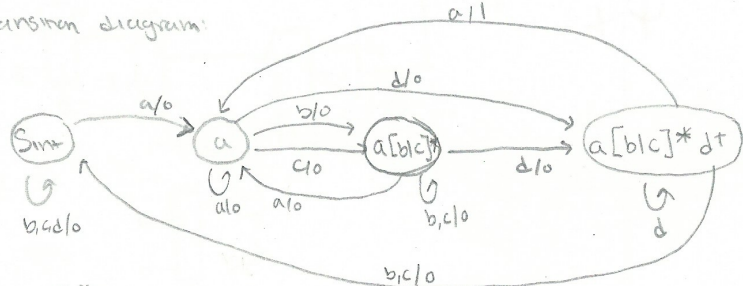

PS
 $S_{init} = 00$
 $a = 01$
 $a[b|c]^* = 10$
 $a[b|c]^*d^+ = 11$

$x_1 x_0$
 $a = 00$
 $b = 01$
 $c = 10$
 $d = 11$

+5

	$x_1 x_0$			
PS	00	01	10	11
S_{init}	01,0	00,0	00,0	00,0
a	01,0	10,0	10,0	11,0
$a[b c]^*$	00,0	10,0	10,0	11,0
$a[b c]^*d^+$	01,1	00,0	00,0	11,0

NS, Z

+3



	x_0			
Q_1	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

	x_0			
Q_0	00	01	10	11
0	0	0	0	0
1	0	0	0	0
0	0	0	0	0
0	0	0	0	0

use
 $0 \rightarrow 1 : 00$
 $0 \rightarrow 0 : 01$

+5

	x_0			
Z	00	01	10	11
0	0	0	0	0
1	1	0	0	0
0	0	0	0	0
0	0	0	0	0

use
 10 when $0 \rightarrow 0$
 &
 11 when $0 \rightarrow 1$


	x_0			
Q_1	00	01	10	11
0	0	0	0	0
1	1	1	1	1
0	0	0	0	0
1	0	0	0	0

	x_0			
Q_0	00	01	10	11
0	0	1	1	1
1	0	1	0	1
0	0	0	0	0
1	1	1	0	1

$R_1 = Q_1 = 1$
 $D_1 = Q_1 x_1 x_0' + Q_0 x_0 + Q_1' Q_0 x_1$
 $R_0 = 0$
 $D_0 = x_0 x_1' + x_1 x_0' + Q_1' Q_0' x_0 + Q_1 Q_0' x_1'$



Problem 3) Extra Page

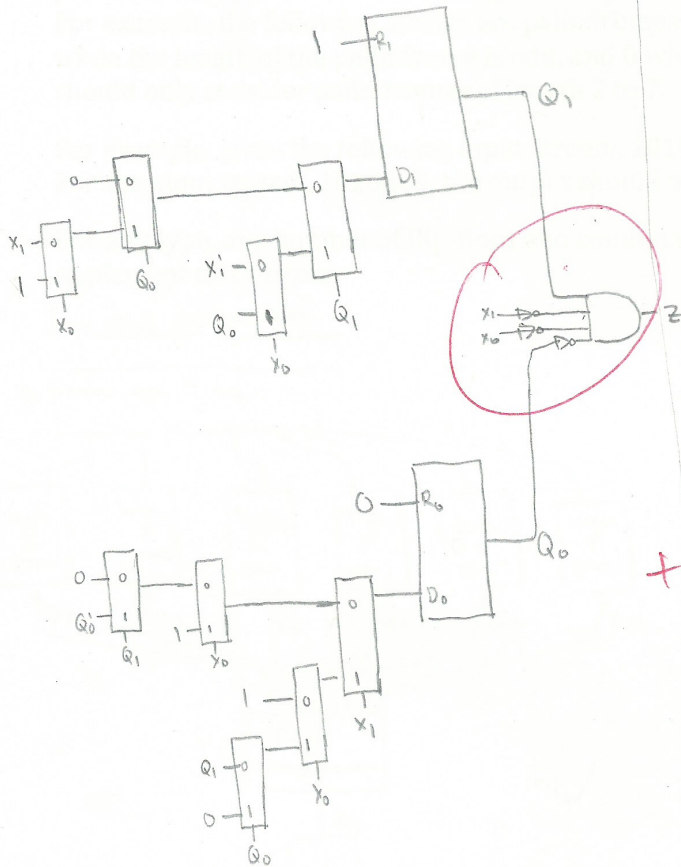

$$R_1 = 1$$

$$D_1 = Q_1 x_1' x_0' + Q_0 x_0 + Q_1' Q_0 x_1$$

$$R_0 = 0$$

$$D_0 = x_0 x_1' + x_1 x_0' + Q_1' Q_0' x_0 + Q_1 Q_0' x_1$$

$$D_1 = Q_1 x_1' x_0' + Q_0 x_0 (Q_1 + Q_1') + Q_1' Q_0 x_1$$

$$Q_1 (x_1' x_0' + Q_0 x_0) + Q_1' (Q_0 x_0 + Q_0 x_1)$$

$$\downarrow \qquad \qquad \qquad \downarrow$$

$$x_0 (Q_0) + x_0' (x_1') \qquad Q_0 (x_0 + x_1) + Q_0' (0)$$

$$\qquad \qquad \qquad \downarrow$$

$$x_0 (1 + x_0' (x_1'))$$

$$D_0 = x_0 x_1' + x_1 x_0' + Q_1' Q_0' x_0 + Q_1 Q_0' x_1$$

$$x_0 x_1' + x_1 x_0' + Q_1' Q_0' x_0 (x_1 + x_1') + Q_1 Q_0' x_1$$

$$x_1 (x_0' + Q_1' Q_0' x_0) + x_1' (x_0 + Q_1' Q_0' x_0 + Q_1 Q_0')$$

$$\downarrow \qquad \qquad \qquad \downarrow$$

$$x_0 (Q_1' Q_0') + x_0' (1) \qquad x_0 (1 + Q_1' Q_0' x_0 + Q_1 Q_0')$$

$$\downarrow \qquad \qquad \qquad \downarrow$$

$$Q_0 (0) + Q_0' (Q_1')$$

$$\qquad \qquad \qquad \downarrow$$

$$Q_1 (Q_0') + Q_1' (0)$$



Problem 4 (20 points)

Given an input stream of 0s and 1s, design a system that outputs the length, Z , of the largest palindrome found in the last 7 inputs, along with the parity, P , of the length of that palindrome. A palindrome is a string that is spelled the same forwards as it is backwards. For example, the following strings are palindromes: 10101, 11, 1001, 0000. P is equal to 1 when the length of the palindrome is odd, and 0 when its length is even. Your system should only consider palindromes of length 2 to 7.

For example, given the following input stream, 1010101, the output should be $Z=7$ and $P=1$. For the input stream, 1010000, the output should be $Z=4$ and $P=0$.




Use any type, any number of flip-flops and combinational gates of your choosing to implement this system.

high level implementation

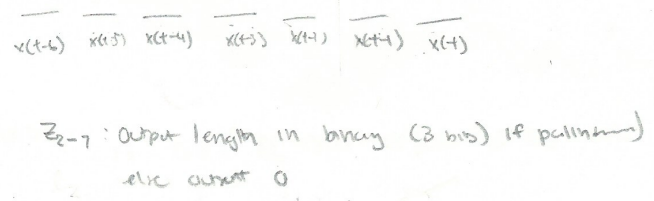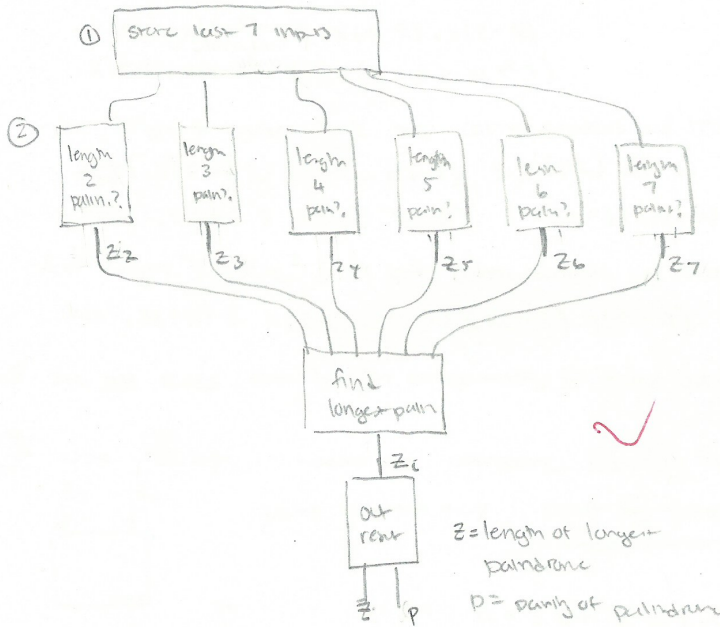


$X'Y = L$ $(X'Y + XY')' = E$ $XY' = G$

How to implement 1 bit comparator?

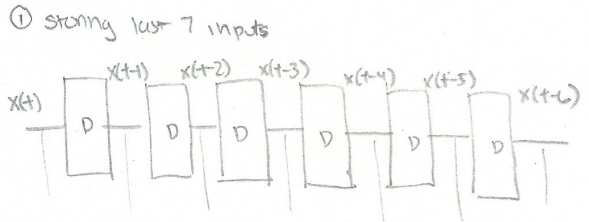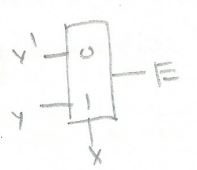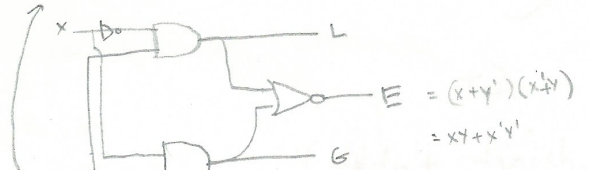

② length 2 palin?

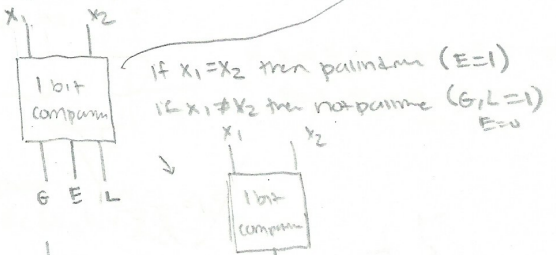

X_1 & X_2 must cycle through 6 times using these as inputs:

- $x(t), x(t+1)$
- $x(t-4), x(t-5)$
- $x(t+1), x(t-2)$
- $x(t-5), x(t-6)$
- $x(t-2), x(t-7)$
- $x(t-3), x(t-4)$

← If $E=1 \rightarrow Z_2 = 010$ else $Z_2 = 000$

t t-1 t-2 t-3 t-4 t-5 t-6

Problem 4) Extra Page

② cont for length 3, use 1 bit comparator to compare first and last digits of length 3 str.
 need to cycle 4 times.

inputs = $x(t), x(t-2)$ $x(t-2), x(t-4)$ $x(t-4), x(t-6)$
 $x(t+1), x(t-3)$ $x(t-3), x(t-5)$

if $E=1$ $Z_3=011$ otherwise $Z_3=000$

for length 4: use 2 1 bit comparators with inputs

• $x(t), x(t-3)$ & $x(t-1), x(t-2)$ $x(t-2), x(t-5)$ & $x(t-3), x(t-4)$
 • $x(t+1), x(t-4)$ & $x(t-2), x(t-3)$ $x(t-3), x(t-6)$ & $x(t-4), x(t-5)$

if $E=1$, $Z_4=100$
 otherwise $Z_4=000$

for length 5: use 2 1 bit comparators w/ inputs:

• $x(t), x(t-4)$ & $x(t-1), x(t-3)$
 • $x(t+1), x(t-5)$ & $x(t-2), x(t-4)$
 • $x(t-2), x(t-6)$ & $x(t-3), x(t-5)$

if $E=1$ $Z_5=101$ otherwise $Z_5=000$

for length 6: use 3 1 bit comparators w/ inputs:

• $x(t), x(t-5)$ & $x(t-1), x(t-4)$ & $x(t-2), x(t-3)$
 • $x(t+1), x(t-6)$ & $x(t-2), x(t-5)$ & $x(t-3), x(t-4)$

if $E=1$ $Z_6=110$ otherwise $Z_6=000$


for length 7: use 3 1 bit comparators w/ inputs:

• $x(t), x(t-6)$ & $x(t+1), x(t-5)$ & $x(t-2), x(t-4)$

if $E=1$ $Z_7=111$ otherwise $Z_7=000$

★ In all cases for length comparators, if ever output 1, constantly output 1 afterwards

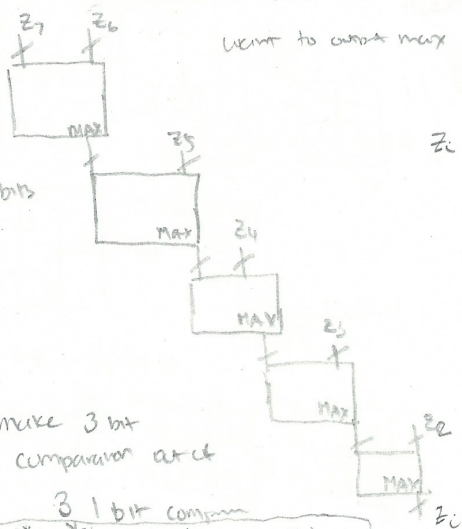③ Use 3 bit comparator to compare $Z_2, Z_3, Z_4, Z_5, Z_6, Z_7$



Want to output max: start by comparing $\max(Z_7, Z_6)$
 then compare $\max(\dots), Z_5$

$Z_i = 3$ bit # of longest length of palindrome

$Z_i = \frac{\quad}{x_2} \frac{\quad}{x_1} \frac{\quad}{x_0}$

+2
 (didn't finish the implementation)


④ parity generator



if $x_0=0 \rightarrow$ even $\Rightarrow P=0$
 $x_0=1 \rightarrow$ odd $\Rightarrow P=1$

final output:
 $Z = Z_i(x_2, x_1, x_0)$ & $P = x_0$

+5

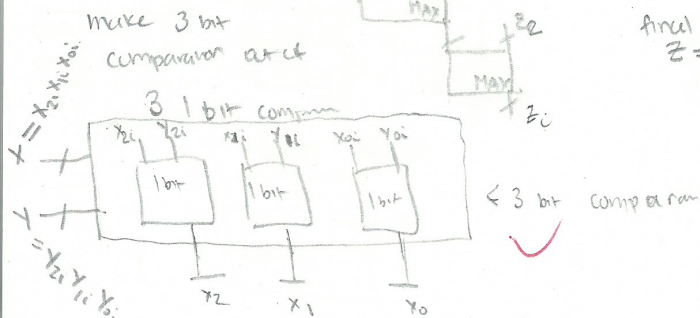

Problem 5 (20 points)

12

Using at most 1 JK flip-flop, at most 1 SR flip-flop, and at most 8 D flip-flops, design a system as specified below. You may use any gates to implement your combinational logic.

Input set: {0,1}



Output: 1, if $x(t, t-3)=11-0$, $x(t-4, t-7)=1-10$ or $0-0-$, $x(t-8, t-11)=1001$

0, otherwise

For example, for the given input sequence $x(t, t-11)=110010101001$, output is 1. For the input sequence $x(t, t-11)=101001011001$, output is 0.



high level design

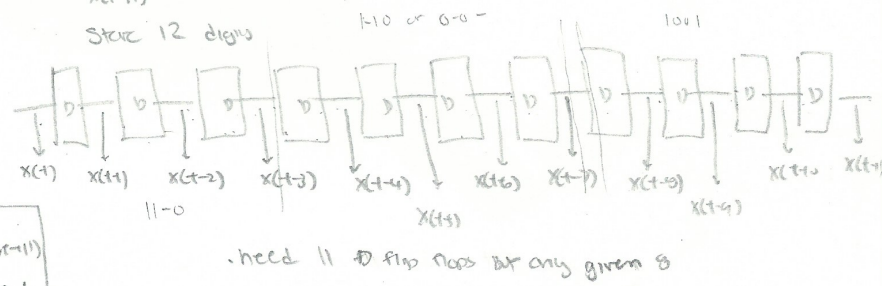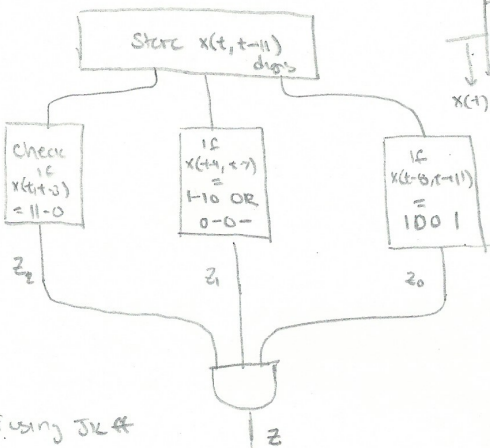


$z_2, z_1, z_0 = 1$ if recognize pattern, else = 0

To store 4 values need 3 flip flops


Make D ff using JK ff

D_2	0	1
D_1	0	1
D_0	1	0

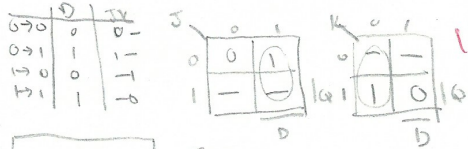

Make D ff using SR ff

D	0	1
S	0	1
R	0	1

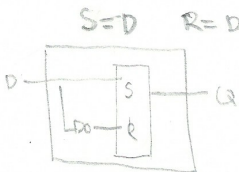

need 11 D-FFs

