
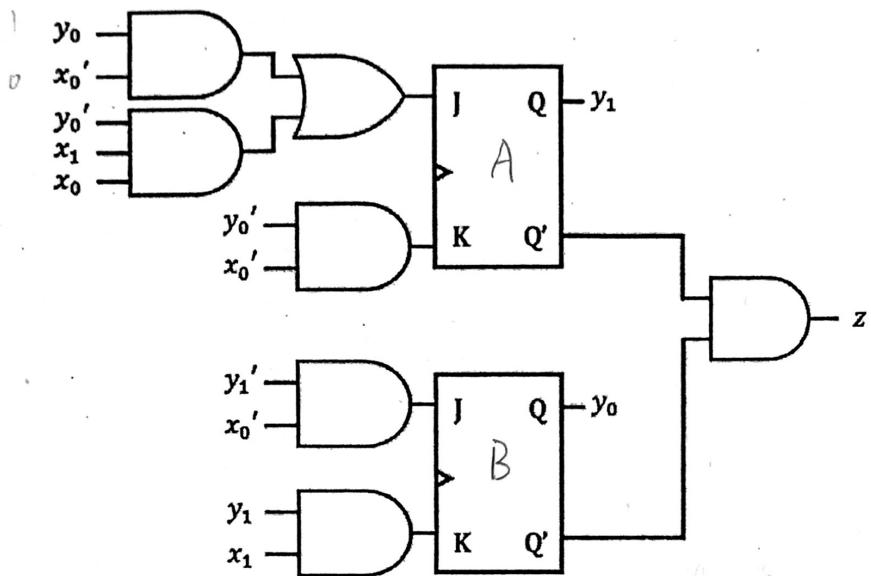


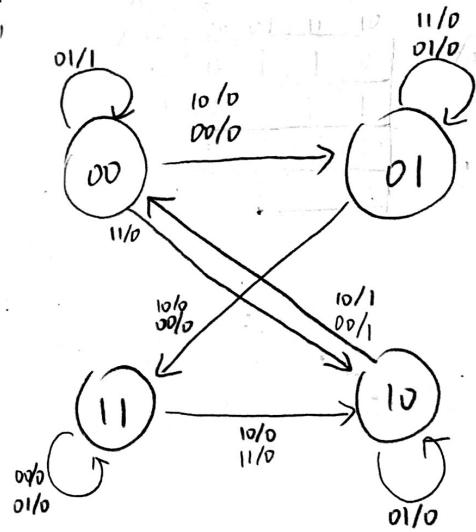Problem 1 (20 points)

Obtain a high level description (state transition table) of the network shown in the figure below. The system has two input bits x_1 and x_0 with output bit z .



X_1	X_0	$y_1 y_0$	$J_A K_A$	$Q_A(y_1)$	$J_B K_B$	$Q_B(y_0)$	$Z = Q_A' Q_B'$
0	0	00	(0 1)	0	(1 0)	1	0
0	0	01	(1 0)	1	(1 0)	1	0
0	0	10	(0 1)	0	(0 0)	0	1
0	0	11	(1 0)	1	(0 0)	1	0
0	1	00	(0 0)	0	(0 0)	0	1
0	1	01	(0 0)	0	(0 0)	1	0
0	1	10	(0 0)	1	(0 0)	0	0
0	1	11	(0 0)	1	(0 0)	1	0
1	0	00	(0 1)	0	(1 0)	1	0
1	0	01	(1 0)	1	(1 0)	1	0
1	0	10	(0 1)	0	(0 1)	0	1
1	0	11	(1 0)	1	(0 1)	0	0
1	1	00	(1 0)	1	(0 0)	0	0
1	1	01	(0 1)	1	(0 0)	1	0
1	1	10	(1 0)	1	(0 0)	0	0
1	1	11	(0 0)	1	(0 1)	0	0



PS	input=00	input=01	input=10	input=11
(00) A	B, 0	A, 1	B, 0	C, 0
(01) B	D, 0	D, 0	B, D	B, D
(10) C	A, 1	C, 0	A, 1	C, 0
(11) D	D, 0	D, 0	C, 0	C, 0

Problem 2 (20 points)

20

Design a state transition table such that it initially has 8 states, and after minimization, reduces down to 3 states.

	⁽¹⁾ A, B, C	⁽²⁾ D, E	⁽³⁾ F, G, H
A	2D 3F	D 2D 1A	F 1A 3F
B	2E 3G	E 2E 1B	G 1B 3G
C	2D 3H		H 1C 3H

PS	input=0	input=1
A	D, 0	F, 0
B	E, D	G, 0
C	D, 0	H, 0
D	D, 0	A, 1
E	E, 0	B, 1
F	A, 1	F, D
G	B, 1	G, 0
H	C, 1	H, 0

Problem 3 (20 points)

14

Given two 1-bit input streams A and B, output 1 if the difference between the number of times the pattern "001" appears in stream A and "101" appears in stream B is 3. If the difference between the number of their appearances is not 3, then the output is 0. You may use any type of flip flops or logical units of your choosing.

0

For example:

A: 001000000

¹⁰¹
max 4


A - 0 or 1

B: 101010101

B - 3 or 4

¹⁰⁰ ¹⁰¹

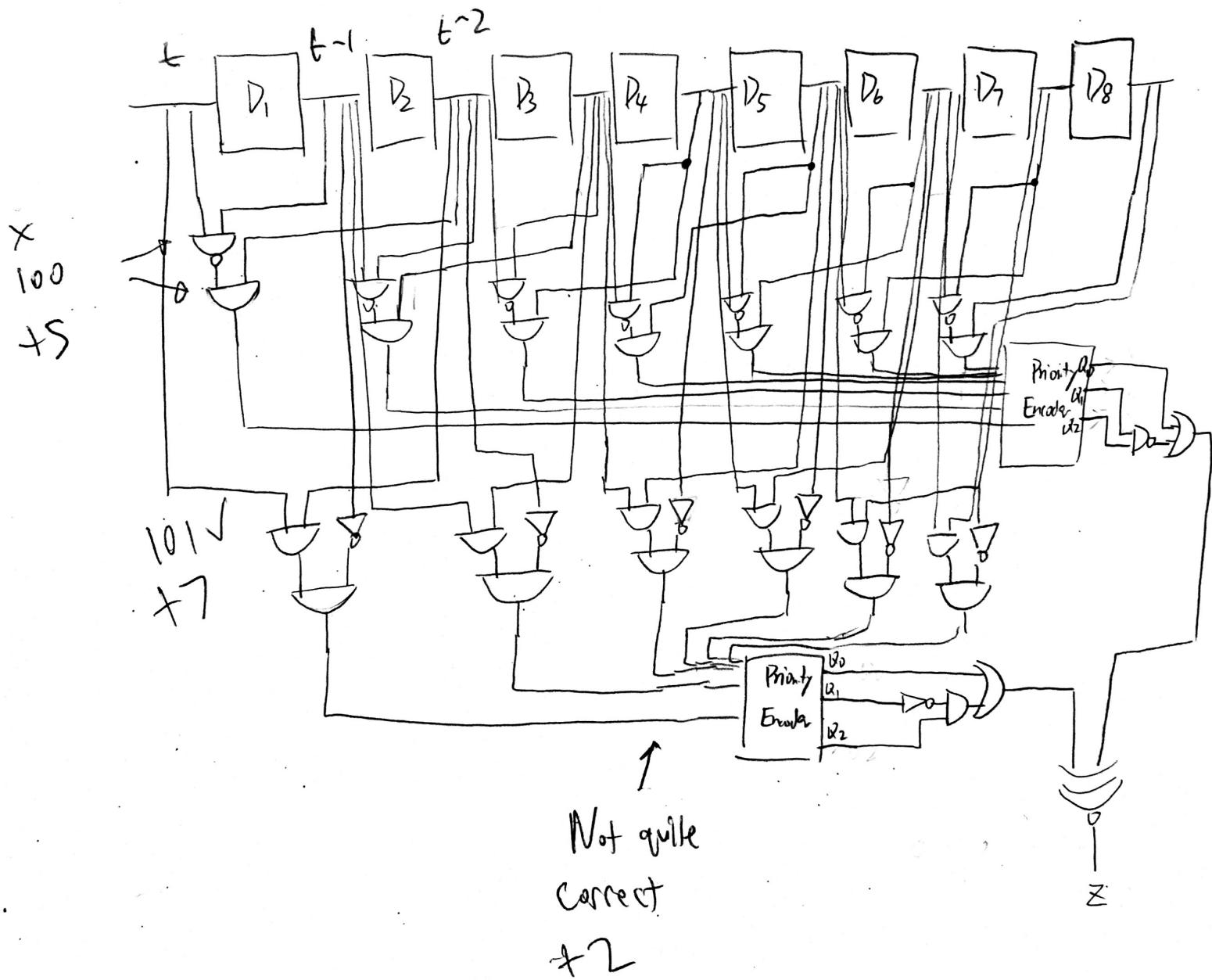Would output: 000000001. Notice that the B pattern overlaps.



$$\begin{array}{r} 7 \\ + 7 \\ \hline 14 \end{array}$$

problem 4 (20 points)

Using OK flip-flops as designed below and multiplexers for logic, design a minimum system which has the following behaviors:

Input set: $\{a, b, c\} d$

Output: 1 if $x(t-n, t) = a[b|c] + d^*a$

0 otherwise

Notes:

ababa

Overlaps can occur. For example *adada* would output 00101


| means OR

* means 0 or more of the previous character

+ means 1 or more of the previous character

you are using
4 states.
however,
you are
recognising
abcdabc
as well.

Prev State Q(t)	OK			
	00	01	10	11
0	1	1	0	-
1	-	1	0	0
	Nxt State Q(t+1)			-

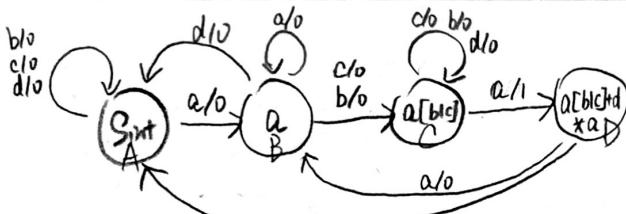

	input=a	input=b	input=c	input=d
A	B,0	A,0	A,0	A,0
B	B,0	C,0	C,0	A,0
C	D,1	C,0	C,0	(C,D)
D	B,0	A,0	A,0	(A,D)

D ₁ , K ₁	00	01	10	11	D ₂ , K ₂	00	01	10	11
00	10	10	10	10	00	0-	10	10	10
01	10	0-	0-	10	01	01	1-	1-	1-
10	1-	01	01	01	10	10	10	10	10

D ₁ , X ₁ X ₀	00	01	11	10
Q _A Q _B	1	1	1	1
Q _B	1	0	1	0
X ₁ X ₀	-	-	-	-
Q _A	1	0	0	0

$$U_1 = Q_A' Q_B' + X_1' X_0' + Q_B X_1 X_0$$

K ₁ , X ₁ X ₀	00	01	11	10
Q _A Q _B	0	0	0	0
Q _B	0	-	0	-
X ₁ X ₀	0	-	-	-
Q _A	-	1	1	1

$$K_1 = Q_A$$

	input=a	b	c	d
00 A	B,0	A,0	A,0	A,0
01 B	B,0	C,0	C,0	A,0
10 C	A,1	C,0	C,0	C,0
	Q _A	b	c	d
00	01	00	00	00
01	01	10	10	00
10	00	10	10	10

Reduction
states



D ₂ , X ₁ X ₀	00	01	11	10
Q _A Q _B	0	1	1	1
Q _B	0	1	1	1
X ₁ X ₀	-	-	-	-
Q _A	1	1	1	1

$$D_2 = Q_A + X_0 + X_1$$

K ₂ , X ₁ X ₀	00	01	11	10
Q _A Q _B	-	0	0	0
Q _B	1	-	-	-
X ₁ X ₀	-	-	-	-
Q _A	0	0	0	0

you
can
use
large
grp

Extra Page

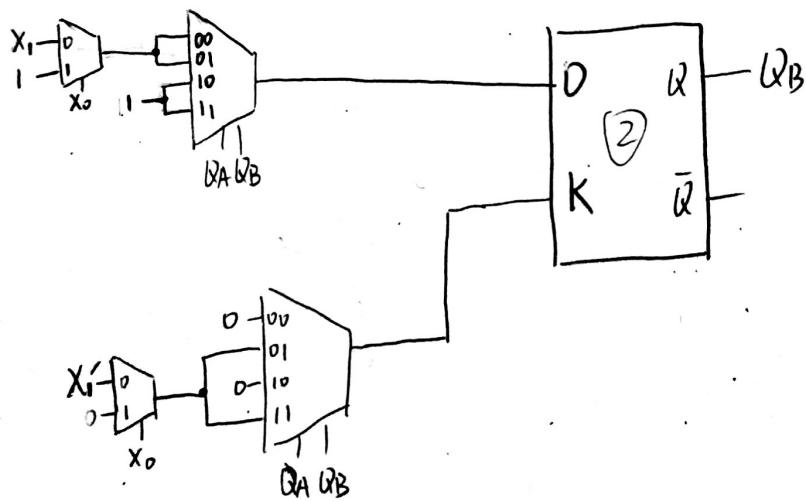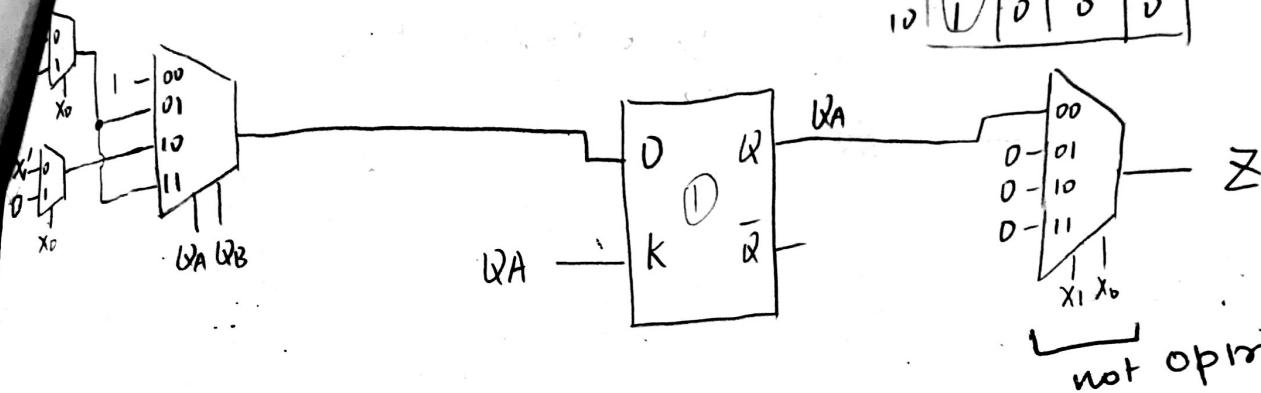


Problem 5 (20 points)

Given 6 2-bit numbers as input, $\{A, B, C, D, E, F\}$, design a system such that the system finds the maximum sum between any of the 2 inputs. You may only use multiplexers to implement this system.

$$\begin{array}{ll} \text{min: } 0 & 000 \\ \text{max: } 6 & 110 \end{array}$$

For example, if all the inputs are 01, then the maximum sum output should be 010.

2+3

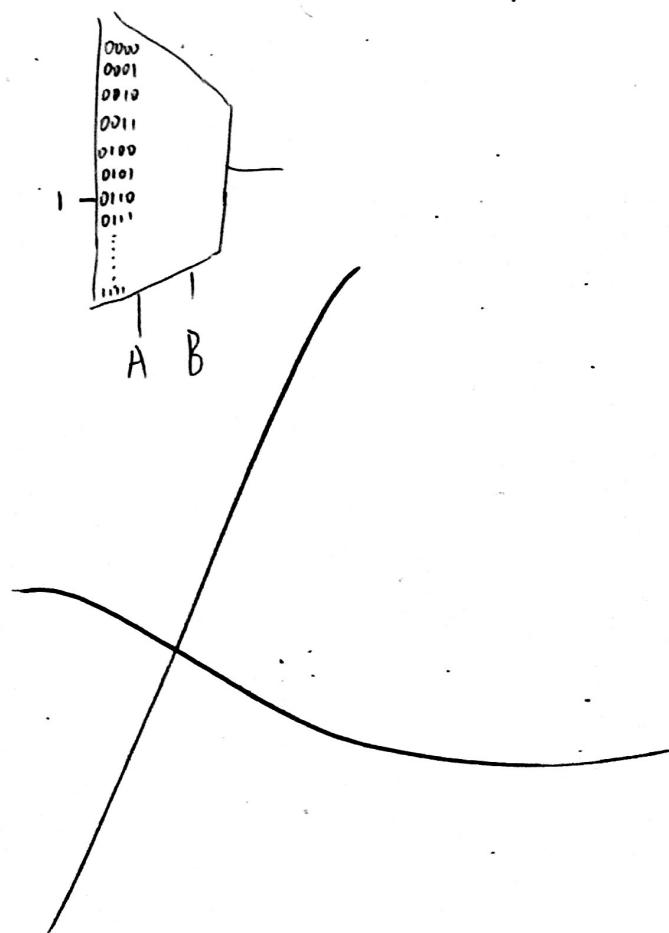

Time Allowed: 100 Minutes

Problem(Possible Points)	Points
1 (20)	18
2 (20)	20
3 (20)	14
4 (20)	14
5 (20)	6
Total (100)	66