

Midterm November 5, 2020
Deadline October 6, 2020 by 2pm Pacific Time

Problem 1 (10 points)

How many bits are required to encode a color spectrum capable of supporting 16 million colors using:

- a: Decimal digits in BCD
- b: Hexadecimal representation

which representation is more efficient and why?

Problem 2 (10 points)

Fill in the missing entries

Radix	Value	Value in decimal
16	(5 1 7)	
8	(5 1 7)	

True or False:

- a: A bubble on the output of a logic gate indicates that the output is active HIGH
- b: Bubbles on the input lines of logic gates indicate that these inputs are active LOW
- c: The Boolean expression for a logic circuit is $A' + B' = X$ (A' is complement A)
This tells us both inputs are active LOW and the output is active HIGH.

Problem 3 (10 points)

Given $E(a, b, c, d) = (ab + c)'(ac + (b' + c' + a'cd)') + a((b + c)(b + d) + c)'$, which of the following represents the same function as $E(a, b, c, d)$? Show all your work.

- 1. $a+b+c+d'$
- 2. $a' + b + c$
- 3. $b + c' + d$
- 4. $a'b'c'd$
- 5. $ab'c'$
- 6. $b'cd'$

Problem 4: (10 points)

- a: Explain Gray Codes and their characteristics and explain conversion of GC to Binary with an example
- b: What is X-3 code and explain the self complementary property of it.
- c: Subtract $(-25)_8$ from $(25)_{10}$ using 2's complement and explain the results in octal and decimal

d: realize XOR gate using NOR gates only.

Problem 5: (10 points)

Given the following simplification of a boolean expression, answer the following.

$$\begin{aligned} & (ab' + c')'(b' + c)(a + bc') & (1) \\ = & (ab')'c'(b' + c)(a + bc') & (2) \\ = & (a' + b)c'(b' + c)(a + bc') & (3) \\ = & (a' + b)c'(ab + ac + bb'c' + bcc') & (4) \\ = & (a' + b)c'(ab + ac) & (5) \\ = & (a' + b)(ab + ac)c' & (6) \\ = & (aa'b + abb + aa'c + abc)c' & (7) \\ = & abc' + abcc' & (8) \\ = & abc' & (9) \end{aligned}$$

a: (4 points) There is at least one mistake in this simplification. Find all steps that are derived incorrectly from its previous step (for example, write (8)→(9) if equation (9) is derived incorrectly from (8)).

b: (6 points) Show the correct simplification of (1)

Problem 6: (20 points)

a: Express the given expression in a product of maxterms:

$$F = xy + x'z$$

b: simplify the following boolean function and realize it using NOR gates

$$\begin{aligned} F(A,B,C,D) &= A'B'D' + A'CD + A'BC \\ d(A,B,C,D) &= A'BC'D + ACD + AB'D' \end{aligned}$$

c: simplify the Boolean function in SOP and POS form

$$F = \sum (0,1,2,5,8,9,10)$$

Problem 7: (20 points)


a: Draw the logic diagram for a four-bit comparator and explain the \geq block.

b: explain the BCD-to-7-segment decoding logic for “g” segment

c: explain Decimal to BCD priority encoder, draw it partially and show the truth table for inputs 3 and 6.

Problem 8: (10 points)

Consider the following gate network:

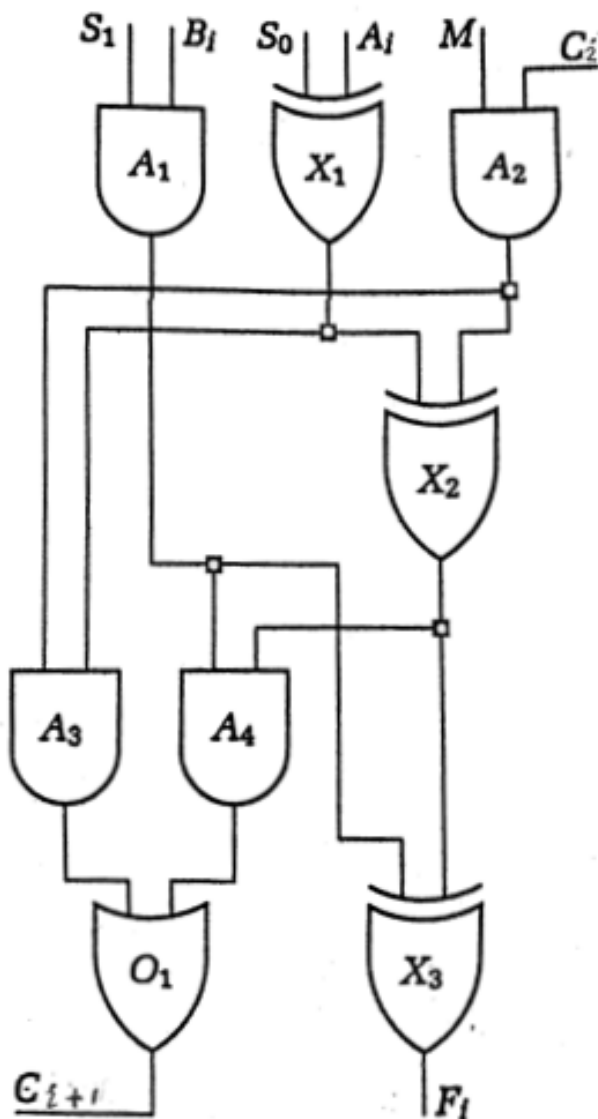

Determine the switching expressions for the outputs F_i and C_{i+1} . Using AND, OR, NOT, XOR expressions as appropriate fill in the following table:

M	S_1S_0	Expression for F_i	Expression for $CI + 1$
0	00		
0	01		
0	10		
1	10		
1	11		