



1. Find  $i_s$ ,  $i_1$ , and  $i_2$  in the circuit Fig. 1.



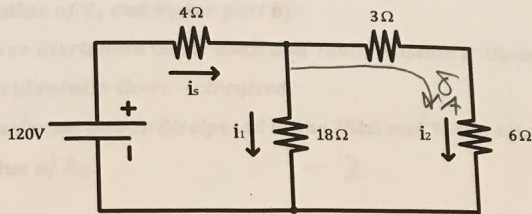


Figure 1

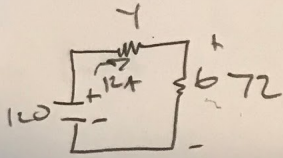

$$i_s = \frac{V_s}{R_{eq}}$$

$$i_s = 12A$$

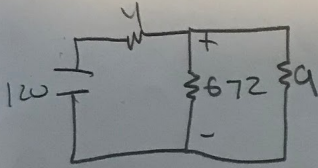

$$V_1 = I_2 R_3 + 6$$

$$\frac{72}{9} = 8 \quad I_2 = 8A$$

$$I_s = i_1 + i_2$$

$$12 - 8 = i_1 = 4A$$



2. a) Find no load value of  $V_o$  in the circuit Fig. 2.  
 b) Find  $V_o$  when  $R_L = 150 \text{ k}\Omega$ .  
 c) What are the value of  $V_1$  and  $V_2$  for part b).  
 d) How much power dissipated in the  $25 \text{ k}\Omega$  and  $75 \text{ k}\Omega$  resistors if the load terminals are accidentally short - circuited.  
 e) What is the maximum power dissipated in the  $25 \text{ k}\Omega$  and  $75 \text{ k}\Omega$  resistors, and for what value of  $R_L$ .

-2

$P = VI$

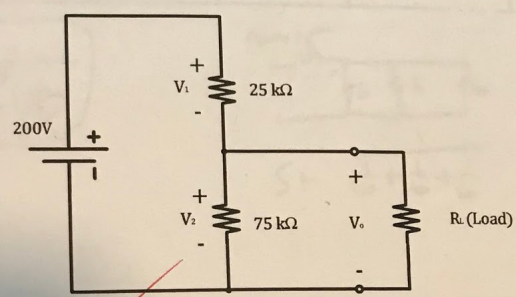


Figure 2

a)  $V = IR_{eq}$   
 $V = I \cdot 100$   
 $\frac{200}{100,000} = 2 \times 10^{-3} \text{ A}$   
 $V_o = 2 \times 10^{-3} \cdot 75 \times 10^3$

$V_o = 150 \text{ V}$

b)  $R_{2L} = \frac{1}{75} + \frac{1}{150}$   
 $= \frac{2}{150} + \frac{1}{150} = \frac{3}{150} = \frac{1}{50}$   
 $= 50 \Omega$   
 $V = IR: \frac{200}{75 \times 10^3} = 2.667 \times 10^{-3} = I$   
 $V_L = 133 \text{ V}$

c)  $V_1 = 200 - 133$   
 $= 67 \text{ V}$

$V_L = V_2 = 133 \text{ V}$


d) No Power in  $75 \text{ k}\Omega$ .  
 $P = VI = 1.6 \text{ W}$

$I = \frac{200}{25 \times 10^3}$

3. The ladder network has infinite number of resistors.


a) Find  $R_{eq}$  of the circuit and  $I_s$  in terms of  $V_s$  and  $R$ .

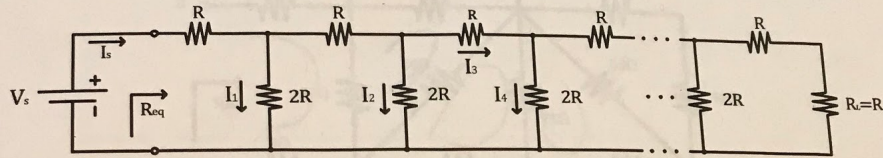b) If  $V_s = 10V$  and  $R = 1k\Omega$ , what are  $I_1, I_2, I_3$ , and  $I_4$ .



a)  $R_{eq} = R + \sum_{i=1}^{\infty} \frac{1}{2R}$

Figure 3

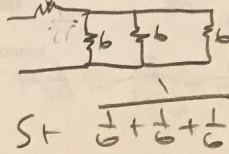

b)

-10



4. Find  $R_{ab}$  for the circuit.

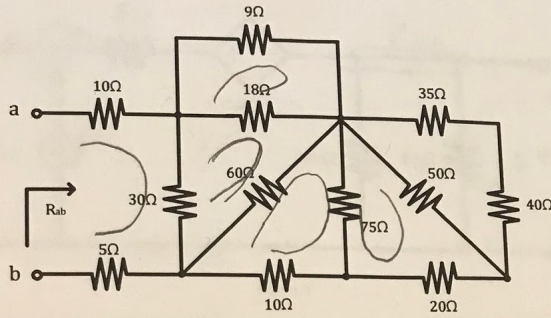


Figure 4

$$\frac{1}{75} + \frac{1}{50} = \frac{2}{150} + \frac{3}{150} = \frac{5}{150} = \frac{1}{30} = 30$$

$$\frac{1}{30} + \frac{1}{75} = 30$$


$$\frac{1}{40} + \frac{1}{60} =$$

$$\frac{6}{240} + \frac{4}{240} = \frac{10}{240} = \frac{240}{24} = 24$$

$$\frac{1}{9} + \frac{1}{18} =$$

$$\frac{3}{18} = 6$$

$$\frac{1}{30} + \frac{1}{30} = 15$$

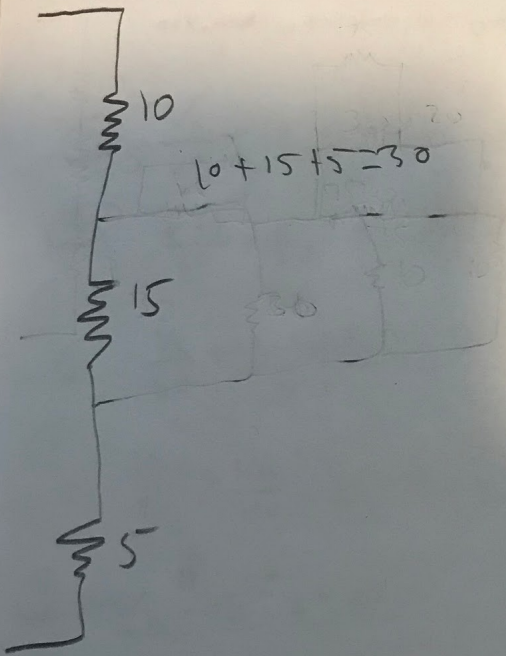

~~30Ω~~

30Ω

I redraw circuit, then erased  
95 went along

5. Find the THEVENIN equivalent circuit with respect to the terminals a, b.

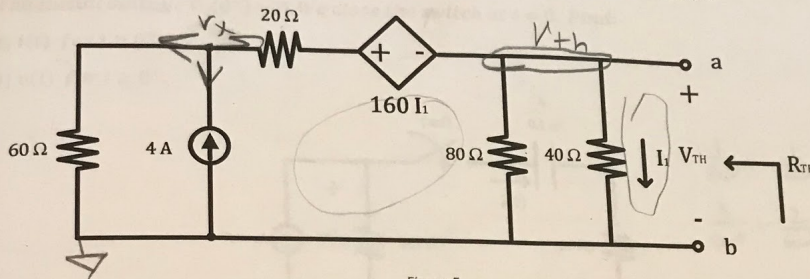


Figure 5

(Hint: define the voltage at the left most node as  $V_x$ , then write two nodal equations as  $V_x$  and  $V_{TH}$ , and then find  $V_{TH}$  and  $R_{TH}$ .)

$$\textcircled{1} \frac{V_x}{60} - 4 + \frac{V_x - 160I_1}{20} = 0$$

$$\textcircled{2} \frac{V_{th}}{80} + \frac{V_{th}}{40} - \frac{V_x - 160I_1}{20} = 0$$

$$\textcircled{1} \frac{V_x}{60} + \frac{V_x - 160I_1}{20} = 4$$

$$\frac{V_x}{60} + \frac{V_x}{20} - \frac{160I_1}{20} = 4 \Rightarrow V_x + 3V_x - 480I_1 = 240$$

$$\textcircled{2} \frac{V_{th}}{80} + \frac{V_{th}}{40} + \frac{160I_1 - V_x}{20} = 0$$

$$\begin{aligned} 4V_x - 480I_1 &= 240 \\ -4V_x + 600I_1 &= 0 \end{aligned}$$

$$I_1 = 120 \text{ A}$$

$$\textcircled{1} = 4V_x - 480I_1 = 240$$

$$4V_x - 57600 = 240$$

$$\textcircled{2} \frac{40I_1}{80} - \frac{40I_1}{40} + \frac{160I_1 - V_x}{20} = 0$$

$$V_{th} = 120 \cdot 40$$

$$= 4800 \text{ V}$$

-13

$$40I_1 - 80I_1 + (40I_1 - V_x) = 0$$

$$600I_1 - 4V_x = 0$$

$$R_{th} = \frac{V_{th}}{I_1}$$

Pract  
istor has  $KP$   
=  $160 \mu\text{m}$ ,  
he value for  
en, comput  
ice, and out  
ommon-ga  
on page 58  
cise 11.13  
is  $KP = 5$   
n,  $V_{io} = 1$   
es are  $V_I$   
resistan  
, and  $R_D$   
point and  
nput res

ates  
diagram  
quival  
; if th  
low.  
agra  
Hint:  
n in  
agra  
b. D  
d s  
ea



6. The switch in the circuit shown has been open for a long time. The initial voltage  $V_c(0^-) = 0$ . We close the switch at  $t = 0$ . Find:

- a)  $i(t)$  for  $t \geq 0^+$ .  
 b)  $v(t)$  for  $t \geq 0^+$ .

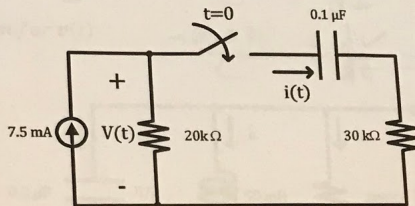


Figure 6

$$\frac{1}{20} + \frac{1}{30} = \frac{3}{60} + \frac{2}{60} = \frac{5}{60} = \frac{1}{12}$$

$$i(\infty) = 0$$

$$i(0^+) = 3 \times 10^{-3} \text{ A}$$

$$\tau = RC \quad R_{th} = 50 \text{ k}\Omega$$

$$= 5 \times 10^{-3} \text{ s}$$

$$i(t) = i(\infty) + (i(0) - i(\infty))e^{-t/\tau}$$

$$= 0 + (3 \times 10^{-3} \text{ A} - 0)e^{-t/5 \times 10^{-3}}$$

$$i(t) = (3 \times 10^{-3})e^{-t/5 \times 10^{-3}} \text{ A}$$


$$V(\infty) = 150 \text{ V}$$

$$V(t) = V(\infty) + (V(0) - V(\infty))e^{-t/\tau}$$

$$V(0^+) = 90 \text{ V}$$

$$150 + (90 - 150)e^{-t/5 \times 10^{-3}}$$

$$90e^{-t/5 \times 10^{-3}} \text{ V}$$

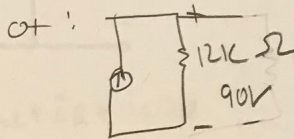

$$V = IR$$

$$\frac{90}{30 \text{ k}} = I$$

$$I = 3 \times 10^{-3} \text{ A}$$

$$= 3 \text{ mA}$$

7. For the circuit in figure below,  $v(0^+) = 12\text{ V}$  and  $i_L(0^+) = 30\text{ mA}$ .  
 $C = 0.2\ \mu\text{F}$ ,  $L = 50\text{ mH}$ , and  $R = 200\ \Omega$ .

a) Find the initial current in each branch of the circuit.

b) Find the initial value of  $\frac{dv}{dt}$ .

c) Write an expression for  $v(t)$ .

$$\dot{i}_C = C \frac{dv}{dt}$$

$$\frac{-0.091}{0.2 \times 10^{-6}} = \frac{dv}{dt} = \frac{-0.091}{2 \times 10^{-7}} = -45000$$

$$i_C = 0.091\text{ A}$$

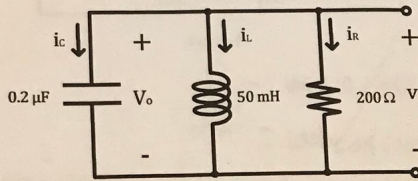


Figure 7

$$v(0^+) = 12\text{ V}$$

$$i_L(0^+) = 30\text{ mA}$$

$$= 0.03\text{ A}$$

$$i_R(0^+) = \frac{V}{R}$$

$$= \frac{12}{200}$$

$$= 0.06\text{ A}$$

$$i_L + i_R + i_C = 0$$

$$i_L + i_R = -i_C$$

$$\frac{d^2 v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = 0$$

$$\alpha = \frac{1}{2RC} = 5 \times 10^5 = 12500$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 0.00632 = 158.11$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = -1.000$$

$$s_2 = -24499$$

$$v(t) = A_1 e^{-1.0t} + A_2 e^{-24499.0t}$$

$$\alpha^2 \gg \omega_0^2 \text{, overdamped}$$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


$$12 = A_1 + A_2$$

$$45000 = -A_1 - 24499 A_2$$

→



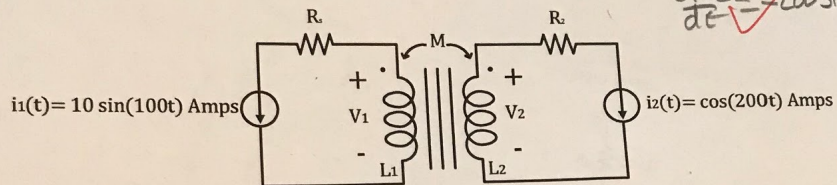8. For figure below,  $L_1 = 10 \text{ mH}$ ,  $L_2 = 20 \text{ mH}$  and  $M = 5 \text{ mH}$ . Find an expression for  $v_1(t)$  and  $v_2(t)$ .



$$\frac{di_2}{dt} = -200 \sin(200t)$$

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

Figure 8

$$\frac{di_1}{dt} = 1000 \cos(100t)$$

$$= 1000 \cos(100t)$$

$$V_1 = (10 \times 10^{-3})(1000 \cos(100t)) + (5 \times 10^{-3})(-200 \sin(200t))$$

$$= \cos(100t) - 0.2 \sin(200t)$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

$$= (5 \times 10^{-3})(1000 \cos(100t)) + (20 \times 10^{-3})(-200 \sin(200t))$$

$$= 5 \cos(100t) - 4 \sin(200t)$$