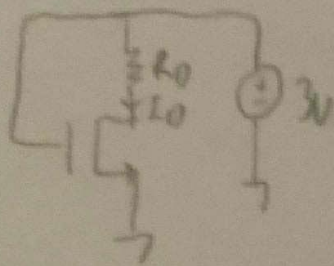


ECE 100 Final Exam Solutions



$$V_G = 3V$$

$$V_S = 0V$$

$$V_{GS} = V_{GS} - V_T \text{ (Edge of saturation)} \quad (1)$$

$$= 3 - 0.5 = 2.5V$$

$$I_D = K (V_{GS} - V_{TH})^2 \quad (1)$$

$$= 0.3 \cdot 10^{-3} (2.5)^2$$


$$= 1.875mA$$

$$V_D = V_{GS} - V_{TH} = 3V - I_D R_D \quad (1)$$

$$2.5 = 3V - I_D R_D$$

$$0.5 = I_D R_D$$
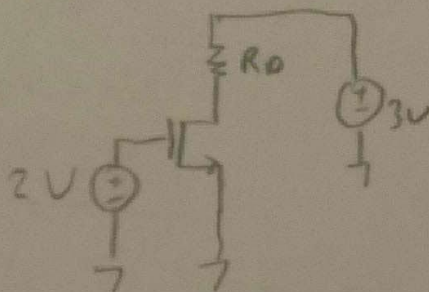
$$\frac{0.5}{1.875 \cdot 10^{-3}} = R_D \Rightarrow R_D = 266.67 \Omega \quad (2)$$



$$V_G = 2V$$

$$V_S = 0V$$

$$V_D = V_{GS} - V_T \text{ (Edge of saturation)} \quad (1)$$

$$= 2 - 0.5 = 1.5V$$

$$I_D = K (V_{GS} - V_{TH})^2 \quad (1)$$

$$= 0.3 \cdot 10^{-3} (1.5)^2$$


$$= 6.75 \cdot 10^{-4} A$$

$$V_D = V_{GS} - V_{TH} = 3 - I_D R_D \quad (1)$$

$$1.5 = 3 - I_D R_D$$

$$1.5 = I_D R_D$$
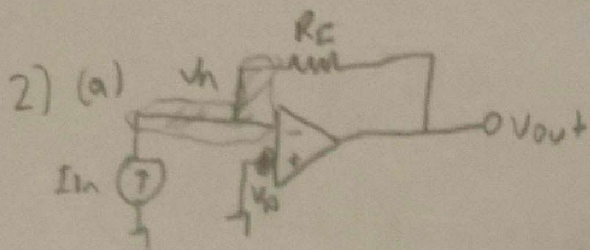
$$R_D = \frac{1.5}{6.75 \cdot 10^{-4}} = 222.22 \Omega = R_D \quad (2)$$



Node eqn at V_n

$$-I_{in} + \frac{V_n - V_{out}}{R_F} = 0$$


$$V_p = 0$$

$$V_n = V_p = 0$$

$$-I_{in} - \frac{V_{out}}{R_F} = 0$$

$$V_{out} = -I_{in} R_F$$

(2)

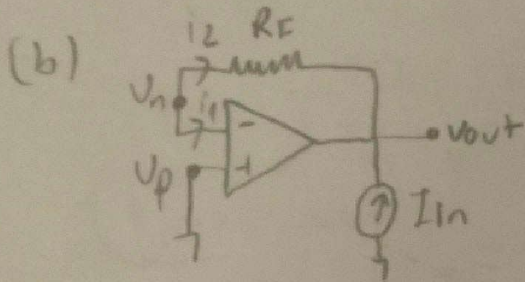

$$V_p = 0$$

$$V_n = V_p = 0$$

Node eq. at V_n

$$i_1 + i_2 = 0$$


$$i_1 = 0 \text{ due to ideal opamp}$$

$$i_2 = 0 \Rightarrow \frac{V_n - V_{out}}{R_F} = 0$$

$$V_n = V_{out}$$

$$0 = V_{out}$$

(2)

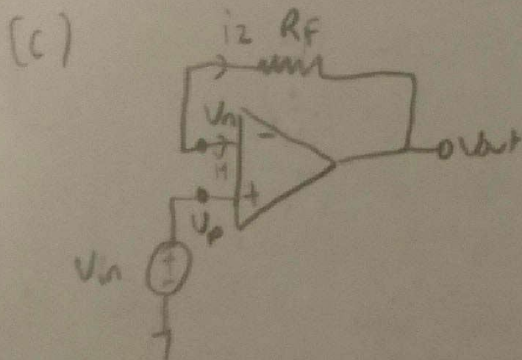

$$V_p = V_n$$

$$V_p = V_n = V_n$$

Node eq. at V_n

$$i_1 + i_2 = 0$$

$$i_1 = 0 \text{ due to ideal opamp}$$


$$i_2 = 0 \Rightarrow \frac{V_n - V_{out}}{R_F} = 0$$

$$V_n = V_{out}$$

$$V_{in} = V_{out}$$

(2)

d)

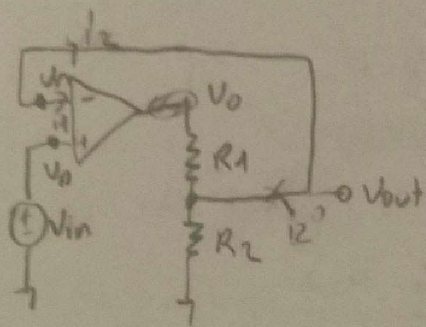

$$V_p = V_{in}$$


$$V_n = V_p = V_{in}$$

$$i_1 = i_2 = 0 \Rightarrow V_n = V_{out} = V_{in} \quad (2)$$

$$i_1 = i_2 = 0$$

$i_1 = 0$ due to ideal op-amp

e)

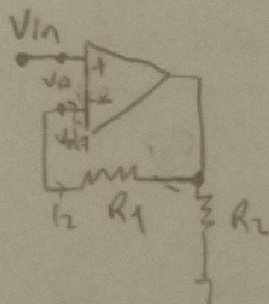

$$V_p = V_n = V_{in}$$


$i_1 + i_2 = 0$ (Node eqn at V_n)

$i_1 = 0$ due to ideal op-amp

$$i_2 = 0 = \frac{V_n - V_{out}}{R_1}$$

$$V_n = V_{out} = V_{in} \quad (2)$$

f)

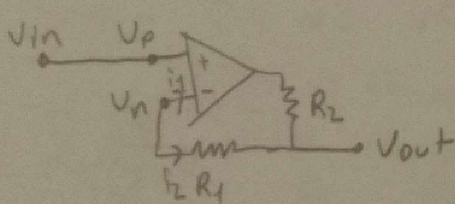

$$V_p = V_{in}$$

$$V_n = V_p = V_{in}$$


Node eqn at V_n

$$i_1 + i_2 = 0$$

$i_1 = 0$ due to ideal op-amp

$$i_2 = 0 = \frac{V_n - V_{out}}{R_1} \Rightarrow V_n = V_{out} = V_{in} \quad (2)$$

g)

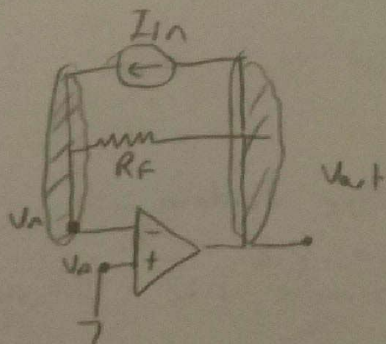

$$V_p = 0$$

$$V_p = V_n = 0$$


Node eqn at V_n :

$$-I_{in} + \frac{V_n - V_{out}}{R_F} = 0$$

$$V_n - V_{out} = I_{in} R_F$$

$$V_{out} = -I_{in} R_F \quad (2)$$

h)

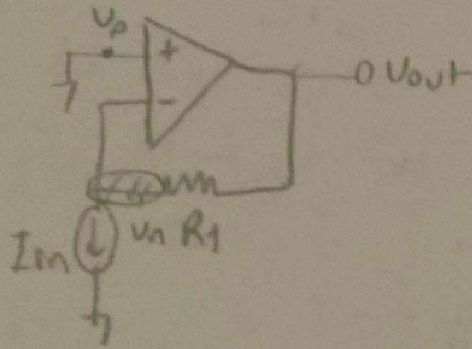

$$V_p = 0$$


$$V_n = V_p = 0$$

Node eqn at V_n :

$$\frac{V_n - V_{out}}{R_1} + I_{in} = 0$$

$$I_{in} \cdot R_1 = V_{out} \quad (2)$$

3) a)

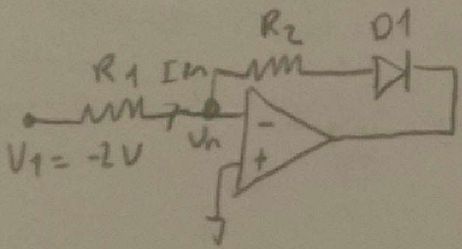

$$V_n = V_p = 0$$


$$I_{in} = \frac{-2 - V_n}{R_1} = \frac{-2}{R_1}$$

For $D1$ to be ON $I_{in} > 0$ however

$$I_{in} = \frac{-2}{R_1}$$

Therefore it is OFF (4)

b)

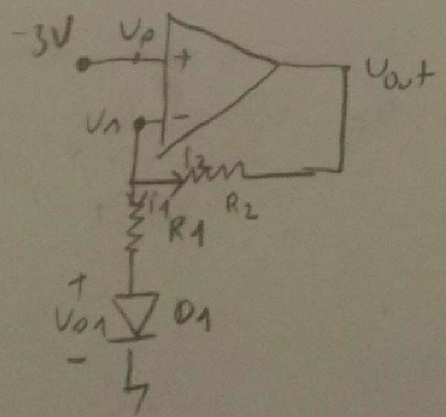

$$V_p = -3V$$

$$V_p = V_n = -3V$$

Assume off for diode

Node eq at V_n :

$$i_1 + i_2 = 0$$

$i_1 = 0$ because diode is off


$$i_2 = 0 \Rightarrow \frac{V_n - V_{out}}{R_2} = 0 \quad V_n = V_{out} = -3V$$

$$V_{D1} = V_n - i_1 R_1 = -3 - 0 = -3V < 0$$

Diode is OFF

$$(4)$$

4)

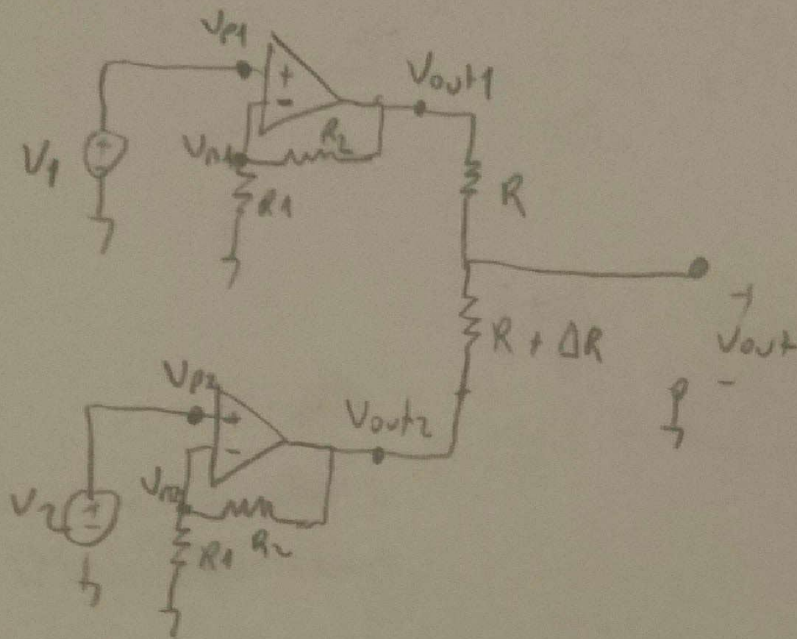

$$V_1 = V_2$$

$$V_{p1} = V_1 \quad V_{p1} = V_{n1} = V_1$$

Node eqn at V_{n1}

$$\frac{V_{n1} - V_{out1}}{R_2} + \frac{V_{n1}}{R_1} = 0$$

$$\frac{V_{out1}}{R_2} = V_1 \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$

$$V_{out1} = V_1 \left(\frac{R_1 + R_2}{R_1} \right) \quad (2)$$

Similarly $V_{out2} = V_2 \left(\frac{R_1 + R_2}{R_1} \right)$

Node eqn at V_{out}

$$\frac{V_{out} - V_{out1}}{R} + \frac{V_{out} - V_{out2}}{R + \Delta R} = 0$$

$$V_{out} (R + \Delta R) - V_{out1} (R + \Delta R) + V_{out} R - V_{out2} R = 0$$

$$V_{out} (2R + \Delta R) = V_{out1} (R + \Delta R) + V_{out2} R$$


$$V_{out} (2R + \Delta R) = V_1 \left(\frac{R_1 + R_2}{R_1} \right) (R + \Delta R) + V_2 \left(\frac{R_1 + R_2}{R_1} \right) R$$

$$V_{out} = \frac{\left(\frac{R_1 + R_2}{R_1} \right) [V_1 (R + \Delta R) + V_2 R]}{2R + \Delta R}$$

For an expired patient $V_1 = V_2$ (2)

$$V_{out} = \left(\frac{R_1 + R_2}{R_1} \right) V_1, (2)$$

Extra clarification for 3a)

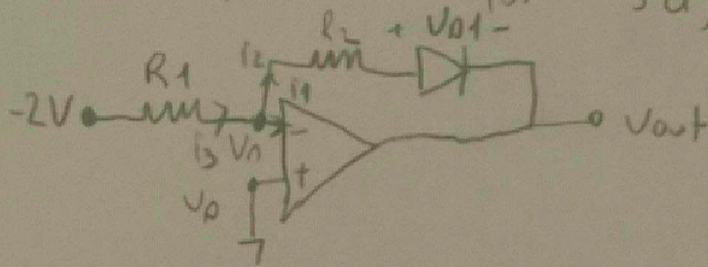

$$V_p = 0$$

If the diode is OFF, eventually $V_n \neq 0$

If $V_n = 0$ then there would be some I_3 which needs to flow somewhere. Since the diode is OFF, I_2 must be zero. T

$$I_3 = I_1 + I_2$$

$$I_1 = 0 \text{ because ideal op-amp}$$

$$I_2 = 0 \text{ because diode is OFF}$$

$$I_3 = 0$$

For $I_3 = 0$ $V_n = -2V \Rightarrow$ If $V_n = -2V$

$$V_{out} = A(V_p - V_n) = \lim_{A \rightarrow \infty} A(0 - (-2)) = \infty$$

The diode will have a voltage $\Rightarrow V_{D1} = -2 - \infty = -\infty < 0$

So the diode is OFF

\therefore Kirchhoff rests peacefully in his heaven!