

22W-EC ENGR-100-LEC-1 Midterm Exam



TOTAL POINTS

92.5 / 100

QUESTION 1

1 Q1 4 / 4

- ✓ - **0 pts** Correct
- **2 pts** 1.1 wrong
- **2 pts** 1.2 wrong
- **4 pts** wrong
- **0.5 pts** one blank of a part wrong

QUESTION 2

2 Q2 3 / 6

- **0 pts** Correct
- **1 pts** Part 1: Partially incorrect node - voltage or mesh analysis
- ✓ - **1 pts** Part 2: Rth wrong, Partially Incorrect Thevenin equivalent circuit
- ✓ - **1 pts** Part 2: Vth calculation wrong, Partially Incorrect Thevenin equivalent circuit
- ✓ - **1 pts** Part 3: R_N calculation wrong, Partially Incorrect Norton equivalent circuit
- **1 pts** Part 3: I_N calculation wrong, Partially Incorrect Norton equivalent circuit
- **2 pts** Part 1 solution missing
- **2 pts** Part 2 solution missing
- **2 pts** Part 3 solution missing

QUESTION 3

3 Q3 6 / 6

- ✓ - **0 pts** Correct
- **1 pts** Part 1: partially incorrect - incorrectly identified series and parallel combinations or calculation mistake
- **1 pts** Part 2: partially incorrect - incorrectly identified series and parallel combinations or calculation mistake
- **1 pts** Part 3: partially incorrect - incorrectly

identified series and parallel combinations or calculation mistake

- **2 pts** Part 1 solution missing
- **2 pts** Part 2 solution missing
- **2 pts** Part 3 solution missing

QUESTION 4

4 Q4 10 / 10

- ✓ - **0 pts** Correct
- **10 pts** solution missing
- **5 pts** incorrect KVL / KCL analysis
- **2 pts** partially incorrect : calculation mistake, wrong input

QUESTION 5

5 Q5 10 / 10

- ✓ - **0 pts** Correct
- **10 pts** No submission
- **3 pts** incorrect KCL / KVL application
- **1 pts** incorrect or not determined relation between V1 and V2 : $V1 - V2 = 10V$
- **1 pts** minor mistake, not calculated the final ans
- **5 pts** incomplete

QUESTION 6

6 Q6 10 / 10

- ✓ - **0 pts** Correct
- **10 pts** no submission
- **2 pts** Part 1: $i(0)$ wrong or missing
- **2 pts** Part 2: $i(\infty)$ wrong or missing
- **2 pts** Part 3: partially incorrect or incomplete
- **4 pts** Part 3: completely incorrect or missing major steps
- **6 pts** Part 3: no submission

QUESTION 7

7 Q7 10 / 10

✓ - 0 pts Correct

- 10 pts no submission
- 2 pts Part 1: incorrect or incomplete KCL / KVL analysis
- 2 pts Part 2: incorrect or missing expression of i_s
- 2 pts Part 3: Incorrect or missing expression of power absorbed by R3
- 3 pts Part 1: no work shown
- 3 pts Part 2: no work shown
- 3 pts Part 3: no work shown

QUESTION 8

8 Q8 14 / 14

✓ - 0 pts Correct

- 14 pts no submission or wrong
- 4 pts Part 1: incorrect DC steady state circuit
- 2 pts Part 2: incorrect voltage across C1
- 2 pts Part 2: incorrect voltage across C2
- 2 pts Part 3: incorrect current through L1
- 2 pts Part 3: incorrect current through L2
- 5 pts Part 2 missing
- 5 pts Part 3 missing
- 2 pts Part 1 partially incorrect
- 1 pts minor mistake

QUESTION 9

9 Q9 12 / 14

- 0 pts Correct
- 2 pts incorrect or missing value for V_c for $t < 1$ sec (steady state capacitance)
- 2 pts incorrect or missing value of $i(t)$ for $t < 1$ sec
- 2 pts incorrect value of V_c at $t \rightarrow \infty$
- 2 pts incorrect total expression of $V_c(t)$
- ✓ - 2 pts incorrect or incomplete expression for $i(t)$ for $t > 1$
- 1 pts minor mistake in the final expression of current $i(t)$
- 14 pts solution missing (no equation or calculation)

QUESTION 10

10 Q10 13.5 / 16



- 0 pts Correct
- 1.5 pts incorrect $v(0^+)$ or missing
- ✓ - 1.5 pts incorrect $dv(0^+)/dt$ or missing
- 0.5 pts Part 2: incorrect differential equation, KCL equation correct
- ✓ - 1 pts incorrect or missing general solution for underdamped system
- 3 pts Part 3) damping type incorrect or solution missing
- 3 pts Part 2: no solution
- 16 pts no solution : no steps shown
- 3 pts major mistakes in $v(t)$ expression or missing major steps
- 2 pts minor mistake in $v(t)$ expression or missing final expression
- 1.5 pts Part 2: KCL equation incorrect
- 7 pts Part 4: no solution
- 4 pts Part 4: no calculation of α , ω , A_1 , A_2 (or all four incorrect)

Question#1 (4 points, 2 points for each subquestion). Fill in the blanks:

1. The Voltage of a capacitor and the Current of an inductor don't permit a sudden jump.
2. The Voltage of a current source and the Currents of a voltage source are undetermined.

Question#2 (6 points, 2 points for each subquestion).

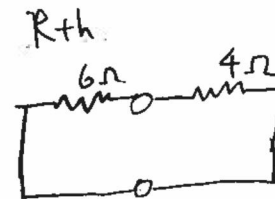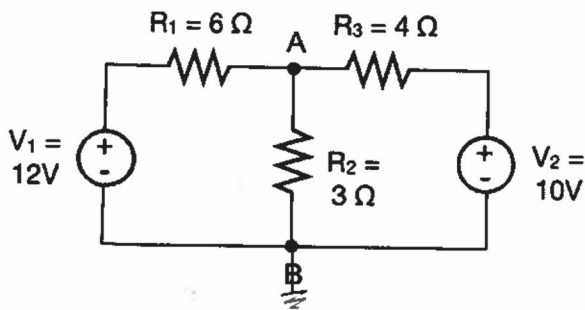1. Solve for the current I_{AB}
2. Find the Thévenin equivalent circuit between A and B
3. Find the Norton equivalent circuit between A and B



$$R_{th} = 6 // 4 = \frac{6 \cdot 4}{6 + 4} = \boxed{2.4 \Omega}$$

D

$$\frac{(12 - V_a)}{6} + \frac{(10 - V_a)}{4} = \frac{V_a}{3}$$


$$24 - 2V_a + 30 - 3V_a = 4V_a$$

$$9V_a = 54$$

$$V_a = 6V$$

$$V_{ab} = 6V$$
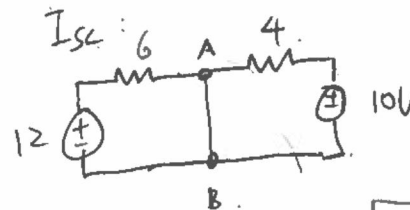
$$I_{ab} = \frac{V_{ab}}{3} = \frac{6V}{3} = \boxed{2A}$$



$$I_{sc} = \frac{12}{6} + \frac{10}{4} = \boxed{4.5A}$$

$$V_{oc} = I_{sc} \cdot R_{th} = 4.5A \cdot 2.4\Omega = \boxed{10.8V}$$


$$V_{oc} = \frac{12 - V_a}{6} = \frac{10 - V_a}{4}, \quad 24 - 2V_a = 30 - 3V_a$$

$$V_a = \frac{54}{5} = 10.8V \quad \checkmark$$

2) Thévenin




3) Norton

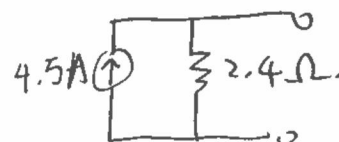



Question#3 (6 points, 2 points for each subquestion)

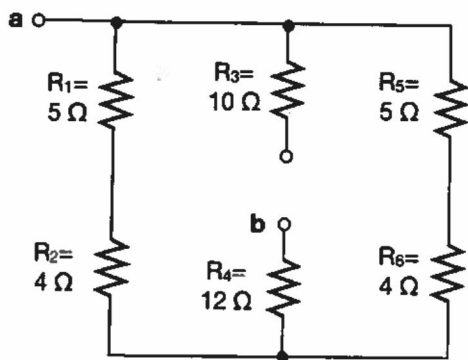1. Find the equivalent resistance R_{ab} between points a and b
2. Replace all resistors with inductors (replace Ω with mH too), find the equivalent inductance L_{ab} between points a and b
3. Replace all resistors with capacitors (replace Ω with μF too), find the equivalent inductance C_{ab} between points a and b




1).

$$9/9 = \frac{9 \cdot 9}{9+9} = 4.5 \Omega$$

$$R_{ab} = 12 + 4.5 = 16.5 \Omega$$

2). 16.5 mH (same maths as R)

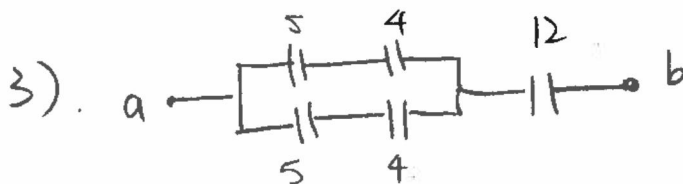

$$\left(\frac{5 \cdot 4}{5+4} \right) + \left(\frac{5 \cdot 4}{5+4} \right) = \frac{40}{9} \Omega$$

$$\frac{\frac{40}{9} \cdot 12}{\frac{40}{9} + 12} = \frac{120}{37} \approx 3.24 \mu\text{F}$$




5

-

5

5

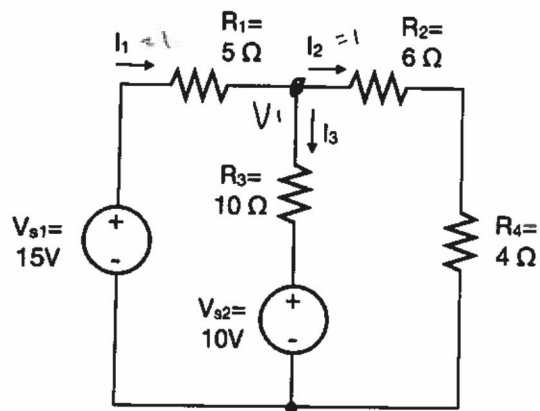Question#4 (10 points). Find I_3 

$$I_1 = \frac{15 - V_1}{5}$$

$$I_2 = \frac{V_1}{6 + 4}$$

$$I_3 = \frac{V_1 - 10}{10}$$

$$\frac{15 - V_1}{5} = \frac{V_1}{10} + \frac{V_1 - 10}{10}$$

$$2(15 - V_1) = 2V_1 - 10$$

$$30 - 2V_1 = 2V_1 - 10$$


$$4V_1 = 40$$

$$V_1 = 10$$

$$I_3 = \frac{10 - 10}{10} = \boxed{0A}$$




Question#5 (10 points). Find i_1

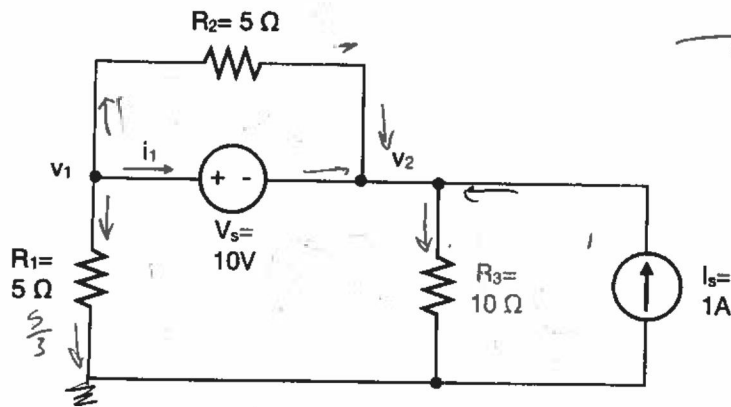

~~Mesh-Current~~
Superposition


zero out Voltage source

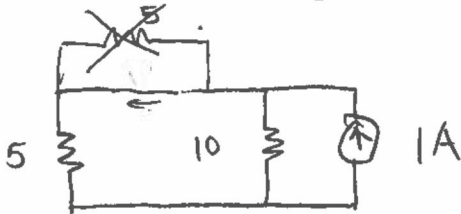

$$i_1 = 0 \text{ A}$$

$$\hat{i}_1 = -1 \cdot \frac{10}{10+5} = -\frac{2}{3} \text{ A}$$

zero out current source

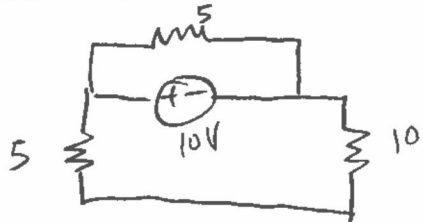

$$15 \parallel 5 = \frac{15 \cdot 5}{15+5} = \frac{75}{20} = 3.75 \Omega$$

$$\hat{i}_1 = -\frac{10 \text{ V}}{3.75 \Omega} = -\frac{8}{3} \text{ A}$$

$$\Sigma i = -\frac{2}{3} - \frac{8}{3} = \boxed{-\frac{10}{3} \text{ A}}$$

check: $i_1 + \frac{(V_1 - V_2)}{5} + \frac{V_1}{5} = 0$

$$i_1 + \frac{(V_1 - V_2)}{5} + 1 = \frac{V_2}{10}$$

$$V_1 - V_2 = 10 \text{ V}$$

$$i_1 + 2 + \frac{4}{3} = 0$$

$$i_1 + 3 = -\frac{4}{3}$$

$$i_1 = -\frac{10}{3} \text{ A} \checkmark$$

$$i_1 + 2 + \frac{V_1}{5} = 0$$

$$i_1 + 4 = \frac{V_1}{10}$$

$$\frac{V_1}{10} - 4 = -\frac{V_1}{5} - 2$$

$$V_1 - 40 = -2V_1 - 20$$

$$3V_1 = 20 \text{ V}$$


$$V_1 = \frac{20}{3} \text{ V}$$

$$V_2 = -\frac{10}{3} \text{ V}$$




Question#6 (10 points). The switch shown in the circuit has been closed for a long time prior to $t = 0$, then it opens at $t = 0$.

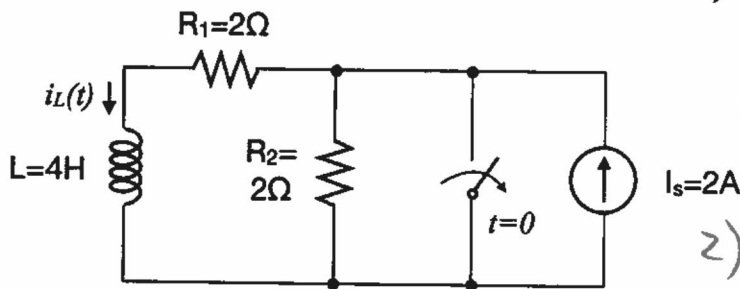1. Find $i_L(0^-)$ (2 points)
2. Find $i_L(\infty)$ (2 points)
3. Find $i_L(t)$ for $t > 0$ (6 points)




1) $i_L(0^-) = 0A$.
 current doesn't reach inductor due to short

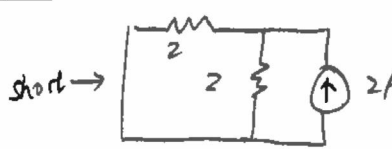2) $i_L(\infty) = 2 \cdot \frac{2}{2+2} = 1A$
 current division
 L acts as short in steady state.



5) src. transformation.

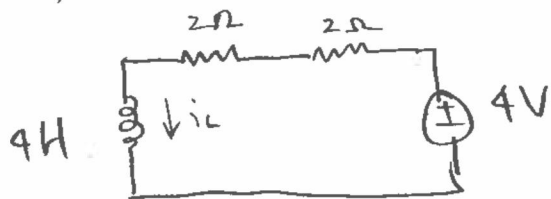

$$i_L(t) = K_1 + K_2 e^{st}$$

$$4V = 4i_L(t) + 4 \frac{di_L(t)}{dt}$$

$$4V = 4K_1 + 4K_2 e^{st} + 4s K_2 e^{st}$$

$$K_1 = 1$$

$$(4s+4) K_2 e^{st} = 0$$

$$s = -1$$

$$i_L(t) = 1 - e^{-t}$$

$$i_L(0) = 0A$$


$$K_1 + K_2 \cdot 1 = 0$$

$$K_2 = -1$$



Question#7 (10 points).

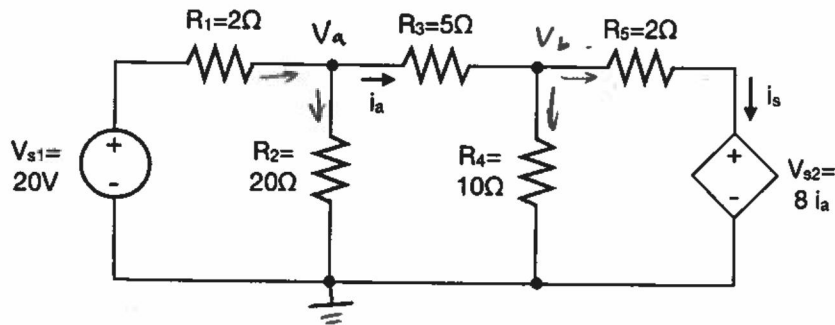1. Find the voltage across R_2 (3 points)
2. Find i_s (3 points)
3. Find the power absorbed by R_3 (4 points)



$$\begin{cases} \frac{20 - V_a}{2} = \frac{V_a}{20} + \frac{V_a - V_b}{5} \\ \frac{V_a - V_b}{5} = \frac{V_b}{10} + \frac{(V_b - 8i_a)}{2} \end{cases}$$

$$\begin{aligned} \rightarrow 2V_a - 2V_b &= V_b + 5V_b - 40i_a \\ 2V_a &= 8V_b - 8(V_a - V_b) \\ 10V_a &= 16V_b \\ V_a &= 1.6V_b \end{aligned}$$

$$\rightarrow \frac{20 - 1.6V_b}{2} = \frac{1.6V_b}{20} + \frac{0.6V_b}{5}$$

$$200 - 16V_b = 1.6V_b + 2.4V_b$$

$$20V_b = 200$$

$$V_b = 10V$$

$$V_a = 1.6V_b = 16V$$

$$i_a = \frac{V_a - V_b}{5} = \frac{16 - 10}{5} = 1.2A$$

$$1) R_2 = V_a = \boxed{16V}$$

$$\begin{aligned} 2) i_s &= \frac{V_b - 8i_a}{2\Omega} \\ &= \frac{10 - 9.6}{2\Omega} \\ &= \boxed{0.2A} \end{aligned}$$



$$\begin{aligned} 3) P_{R_3} &= VI = I^2R \\ &= 1.2^2 \cdot 5 \\ &= \boxed{7.2W} \end{aligned}$$



1
2
3
100

Question#8 (14 points). The circuit below is operating in DC steady state.

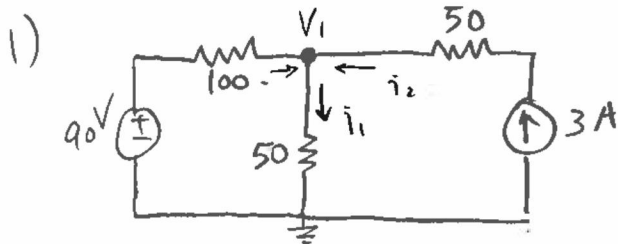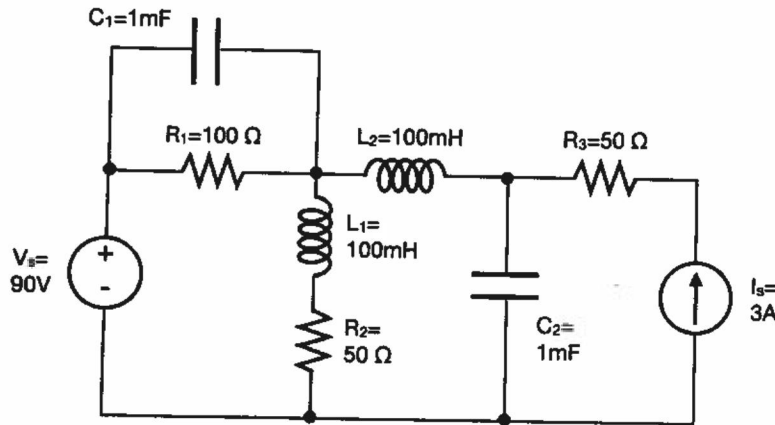1. Draw its equivalent circuit in DC steady state (4 points)
2. Find the total energy in all capacitors (5 points)
3. Find the total energy in all inductors (5 points)



2) Solving the s.s. circuit from

$$\frac{(90 - V_1)}{100} + 3 = \frac{V_1}{50}$$

$$90 - V_1 + 300 = 2V_1$$

$$3V_1 = 390$$

$$V_1 = 130V$$

$$V_{C1} = 130 - 90 = 40V$$

$$V_{C2} = 130V$$

$$\Sigma E_C = \frac{1}{2} \cdot 1mF \cdot 40V^2 + \frac{1}{2} \cdot 1mF \cdot 130V^2$$

$$= 9.25 J$$

3) $E = \frac{1}{2} L i^2$

$$i_1 = \frac{130V}{50\Omega} = 2.6A$$


$$i_2 = 3A$$

$$\Sigma E_L = \frac{1}{2} \cdot 100mH \cdot 2.6^2 + \frac{1}{2} \cdot 100mH \cdot 3^2$$

$$= 0.788 J$$




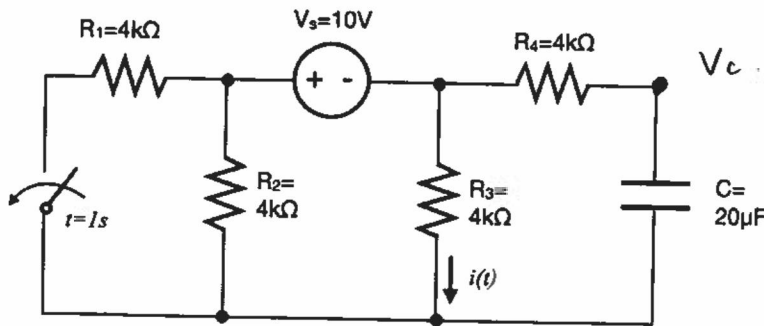Question#9 (14 points). The switch in the circuit has been open for a long time before closing at $t=1s$. Find $i(t)$ for $t>0$.




$$V(0) = 1.25 \cdot 4 = 5V$$

$t < 0, t \leq 1$, steady state

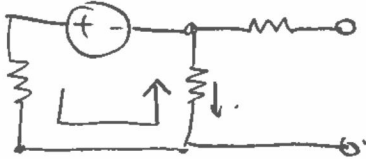


$$i(t) = \frac{-10V}{4k + 4k} = -\frac{10}{8000} = -1.25 \text{ mA}$$

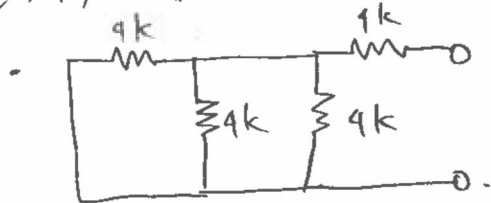$t > 1$, Transient state, use thevenin to simplify



$$4k // 4k = 2k$$
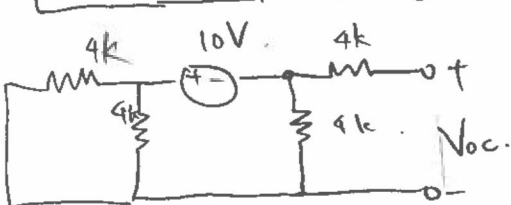
$$2k // 4k = \frac{2000 \cdot 4000}{6000} = \frac{4000}{3} \Omega$$




$$R_{th} = \frac{16000}{3} \Omega$$

$$V_{oc} = \frac{10 \cdot 4k}{2k + 4k} = \frac{20}{3} V$$

$$I_{sc} = \frac{10V}{2k + 4k} = 2.5 \text{ mA}$$

$$\frac{2.5}{2} = 1.25 \text{ mA} \checkmark$$

Eq. Circuit.

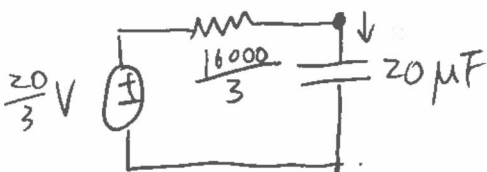

$$C \frac{dv}{dt} = \frac{V - \frac{20}{3}}{\frac{16000}{3}}$$

$$2 \cdot 10^{-5} \frac{dv}{dt} = \frac{3V - 20}{16000} \checkmark$$

Treating start of switch ($t=1$) as $t=0$. for now.

$$V_c(t) = K_1 + K_2 e^{st}$$

$$2 \cdot 10^{-5} K_2 e^{st} = \frac{3K_1 + 3K_2 e^{st} - 20}{16000}$$

$$K_1 = \frac{20}{3}, \quad \left(2 \cdot 10^{-5} s - \frac{3}{16000}\right) = 0 \quad s = -\frac{75}{8}$$


$$V(0) = k_1 + k_2 = 5$$

$$k_2 = 5 - \frac{20}{3}$$

$$= -\frac{5}{3}$$

$$V_c(t) = \frac{20}{3} - \frac{5}{3} e^{-\frac{75}{8}t}$$
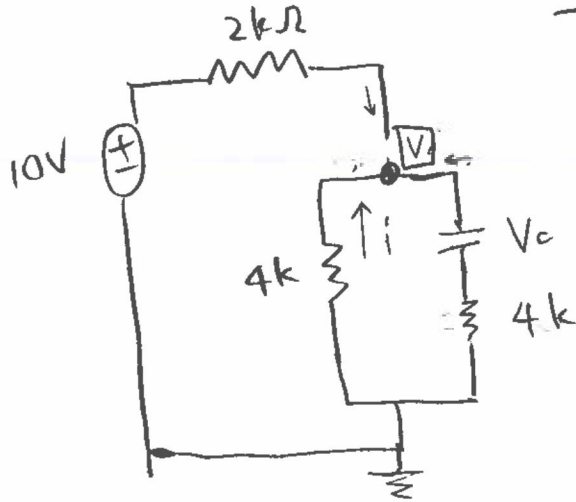
$$\frac{(10-V)}{2k} + \frac{-V_c - V}{4k} = -\frac{V}{4k}$$



$$20 - 2V - V_c - V = -V$$

$$V = 10 - \frac{V_c}{2}$$

$$i = \frac{-V}{4k} =$$


$$-\frac{10 - \frac{5}{3} + \frac{5}{6} e^{-\frac{75}{8}t}}{4000}$$

$$= -\frac{50 - 5 e^{-\frac{75}{8}t}}{24000}$$

$$\left\{ \begin{array}{ll} -1.25 \text{ mA} & 0 \leq t < 1 \\ -\frac{50 - 5 e^{-\frac{75}{8}(t-1)}}{24000} & t \geq 1 \end{array} \right.$$

Question#10 (16 points). Calculate the transient response $v(t)$ of the RLC circuit. The circuit stays in steady state before the switch turns off at $t=0$. $R = 1\Omega$, $L = \frac{1}{2\pi}H$, $C = \frac{1}{2\pi}F$. Assume no initial charge on L and C . Note that S_1 opens and S_2 closes at $t=0$.

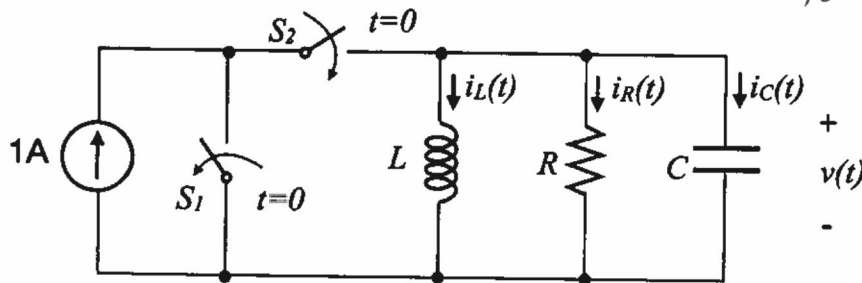1. Calculate $v(0^+)$ and $\frac{dv(0^+)}{dt}$ (3 points)
2. Write a differential equation with $v(t)$ as the variable (3 points)
3. What's the damping type? (3 points)
4. Calculate $v(t)$ (7 points)



$$i_C = C \frac{dv}{dt} \quad v_C = \frac{1}{C} \int_0^t i_C dt$$

$$I = \frac{1}{L} \int_0^t v dt$$

1) $v(0^+) = 1V$ ← no initial charge on L and C

$\frac{dv(0^+)}{dt} = 0V$ ← no instantaneous changes of voltage.

2) KCL. $i_L + i_R + i_C = 1A$

$$\frac{1}{L} \int_0^t v dt + \frac{v(t)}{R} + C \frac{dv}{dt} = 1A$$

$$\frac{1}{L} v + \frac{1}{R} \dot{v} + C \ddot{v} = 0$$

$$\ddot{v} + \frac{1}{RC} \dot{v} + \frac{1}{LC} v = 0$$

$$\ddot{v} + 2\pi \dot{v} + 4\pi^2 v = 0$$

3) $b^2 - 4ac = 4\pi^2 - 4 \cdot 4\pi^2 < 0$

Underdamped.

4) $s^2 V(s) - sV(0) - \dot{v}(0) + 2\pi(sV(s) - V(0)) + 4\pi^2 V(s) = 0$

$$(s^2 + 2\pi s + 4\pi^2) V(s) = (s + 2\pi) V(0) + \dot{v}(0)$$

$$V(s) = \frac{s + 2\pi}{s^2 + 2\pi s + 4\pi^2}$$

See next page!

$$= \frac{s + \pi}{(s + \pi)^2 + 3\pi^2} + \frac{\pi}{(s + \pi)^2 + 3\pi^2}$$

$$V(s) = \frac{s+\pi}{(s+\pi)^2 + 3\pi^2} + \frac{\pi\sqrt{3} \cdot \frac{1}{\sqrt{3}}}{(s+\pi)^2 + 3\pi^2}$$

$$V(t) = e^{-\pi t} \cos(\sqrt{3} \pi t) + \frac{1}{\sqrt{3}} e^{-\pi t} \sin(\sqrt{3} \pi t)$$

100 Midterm Exam (4-5:50pm, 10 questions)

Name:

UID:

