

UCLA

Department of Electrical Engineering

**EE10 – Spring 2010**

**Midterm**

April 28<sup>th</sup>, 2010

1. Exam is closed book. You are allowed **one 8 ½ x 11” double-sided cheat sheets**.
2. Calculators are allowed.
3. Show the intermediate steps leading to your final solution for each problem.
4. **There will be no partial credit for work done correctly using a wrong answer from a previous part of a question. For example, if part a) is wrong and part b) depends on part a), then part b) will be wrong. Therefore, be very careful and double check your work!**
5. You can use both sides of the sheets to answer questions.
6. Write your final answers in the BOX and use correct units for your answers.


Problem	Maximum Score	Your Score	Comments
1. a)	2	2	
1. b)	2	1	
1. c)	2	1	
1. d)	2	1	
1. e)	2	2	
2. a)	4	4	
2. b)	3	3	
2. c)	3	3	
3. a)	7	0	
3. b)	7	6	
3. c)	6	0	
4.	10	10	
	Total: 50		
		Total 33	

NAME: Angelina Hwang

UID: 803657204

1. The current  $i_o$  in the circuit is 2A.

[10 pts]

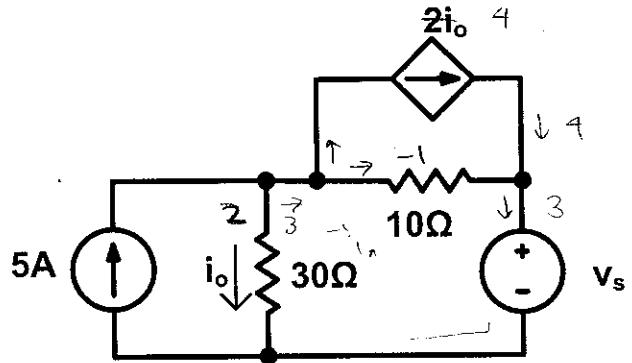

- a) Calculate  $v_s$  (2 pts)

$$3A = i_1 + 4 \\ i_1 = -1 \text{ A}$$

$$-5 - 4 + 1 = -8$$

$$i_A = -7 \\ I_A = 7$$

$$-v_s + 1A(10\Omega) + 2A(30\Omega) = 0$$

$$v_s = 10 + 60 = 70$$

2

$$v_s = 70V$$

- b) Calculate the power of the *independent VOLTAGE* source and circle if it is *absorbed OR delivered*. (2 pts)

$$P_{v_s} = IV$$

$$= (3A)(70V)$$

$$= 210 \text{ W}$$

1

$$\text{Power (absorbed, delivered)} = 210 \text{ W}$$

c) Calculate the power of the ***independent CURRENT*** source and circle if it is ***absorbed OR delivered.*** (2 pts)

$$P = 1V$$

$$V_S + V_{SA} - 1A \cdot 10\Omega = 0$$

$$70 + V_{SA} - 10 = 0$$

$$V_{SA} = -60$$

$$P = 5 \cdot (-60)$$

$$= -300 \text{ W}$$

$$\boxed{\text{Power (absorbed, delivered)} = -300 \text{ W}}$$

d) Calculate the power of the ***CONTROLLED current source*** and circle if it is ***absorbed OR delivered.*** (2 pts)

$$V_S - 2A(30\Omega) + V_{4A} = 0$$

$$V_{4A} = 60 - V_S = 60 - 70$$

$$V_{4A} = -10$$

$$P = 1V \cdot 4 \cdot (-10)$$

$$= -40$$

$$10 + V_4 = 0$$

$$V_4 = -10$$

$$\boxed{\text{Power (absorbed, delivered)} = -40 \text{ W}}$$

e) Calculate the total power dissipated in the ***two resistors.*** (2 pts)

$$P = I^2 R$$

$$= 2^2 \cdot 30$$

$$= 4 \cdot 30 = 120 \text{ W}$$

$$P = I^2 R$$

$$= (-1)^2 \cdot 10$$



$$= 10$$

$$P_{\text{total}} = 130$$

$$\boxed{\text{Total power} = 130 \text{ W}}$$

2. Find a)  $i_1$ , b)  $i_2$  and c)  $v_o$  in the circuit.

[10 pts]

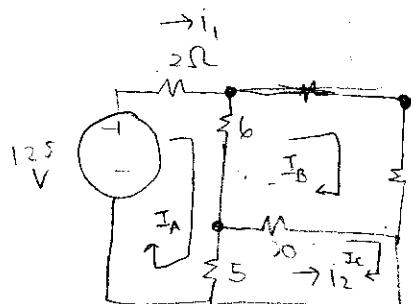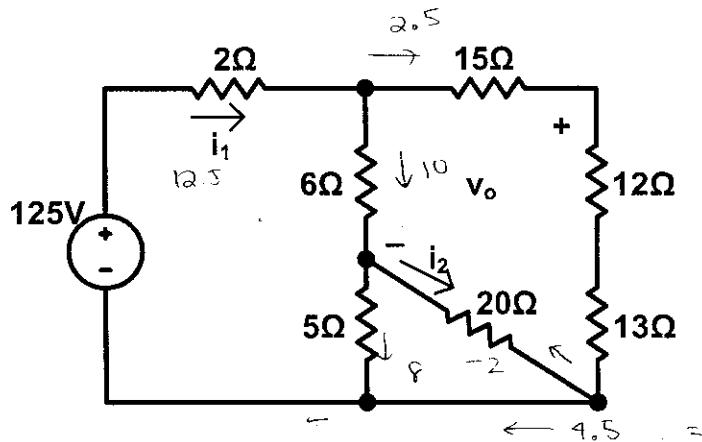

$$I_A = i_1$$

$$I_2 = I_C - I_B$$

$$125 = 13I_A - 6I_B - 5I_C$$

$$0 = 40I_B + 20(I_B - I_C) + 6(I_B - I_A)$$

$$0 = 60I_B - 6I_A - 20I_C$$

$$0 = *6I_A - 66I_B + 20I_C$$

$$0 = 6I_A - 66I_B + 20I_C$$

$$500 = 52I_A - 24I_B - 20I_C$$

$$500 = 58I_A - 80I_B$$

$$500 = 58I_A - 9(12I_A - 125)$$

$$500 = 58I_A - 108I_A + 1125$$

$$-625 = -50I_A$$

$$I_A = 12.5 \text{ A}$$

$$I_2 = 2 \text{ A}$$

$$V_o = 15 \cdot (-2.5) + 6 \cdot 10$$

$$= -37.5 + 60$$

$$= 22.5$$

$$I_C = 20(I_C - I_B) + 5(I_C - I_A) = 0$$

$$0 = 25I_C - 20I_B - 5I_A$$

$$625 = -25I_C - 30I_B + 65I_A$$

$$625 = -50I_B + 60I_A$$

$$125 = -10I_B + 12I_A$$

$$I_B = \frac{12I_A - 125}{10}$$


$$I_B = 2.5$$

$$I_C = 4.5$$

a) $i_1 = 12.5 \text{ A}$
b) $i_2 = 2 \text{ A}$
c) $v_o = 22.5 \text{ V}$

## 3. Node-voltage &amp; mesh-current method

[20 pts]

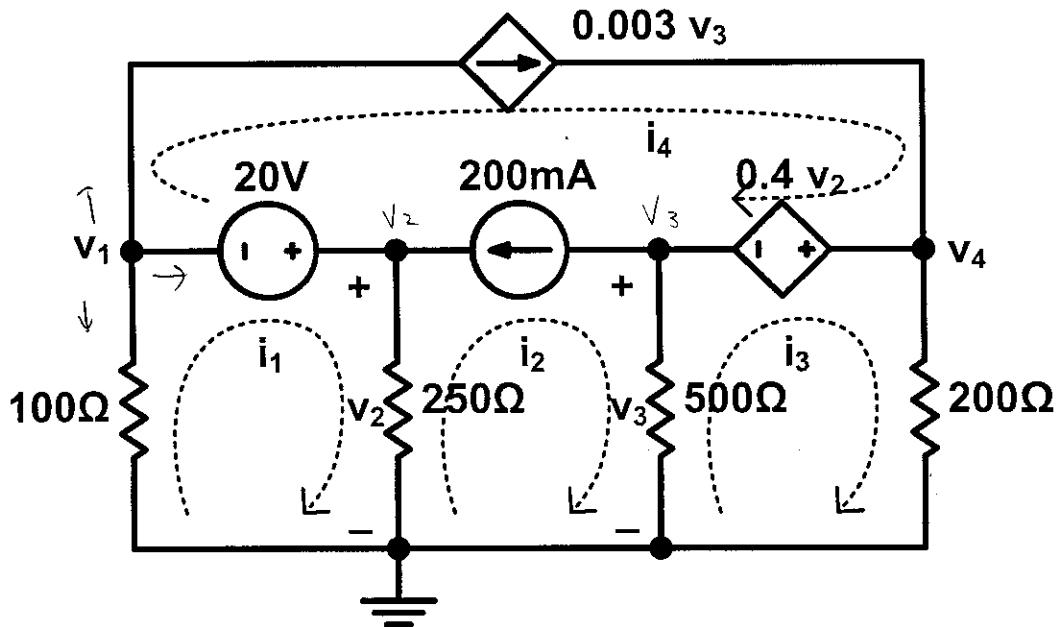

a) Make equations to find  $v_1$ ,  $v_2$ ,  $v_3$  and  $v_4$  using the node-voltage method. Use the reference node and the notation in the circuit. (7 pts)

$$\frac{v_1}{100} + 0.003v_3 = 0 \quad v_1 = -0.3$$

$$\frac{v_2}{250} - 0.002A = 0 \quad v_2 = 0.5 \text{ V}$$

$$0.002A + \frac{v_3}{500} = 0 \quad v_3 = -2.5 \text{ V}$$

$$-0.003v_3 + \frac{v_4}{200} = 0$$

$$-0.003(-2.5) + \frac{v_4}{200} = 0$$

$$v_4 = -1.5 \text{ V}$$

$$i_1 = 0.00063$$

EQN1:  $\frac{v_1}{100} + 0.003v_3 = 0$

EQN2:  $\frac{v_2}{250} - 0.002A = 0$

EQN3:  $0.002A + \frac{v_3}{500} = 0$

EQN4:  $-0.003v_3 + \frac{v_4}{200} = 0$

$$200 = i_4 - i_2$$

$$i_2 = i_4 - 0.2$$

b) Make equations to find  $i_1$ ,  $i_2$ ,  $i_3$  and  $i_4$  using the mesh-current method. Use the notation in the circuit. (7 pts)

$$i_1 \rightarrow : 100i_1 - 20 + 250(i_1 - i_2) = 0$$

$$v_2 = (i_1 - i_2)250$$

$$i_2 \rightarrow : 250(i_2 - i_1) + 500(i_2 - i_3) = 0$$

$$i_3 \rightarrow : 500(i_3 - i_2) - 0.4V_a + 200i_3 = 0$$

$$500i_3 - 500i_2 - 100(i_1 - i_2) + 200i_3 = 0$$

$$700i_3 - 400i_2 - 100i_1 = 0$$

$$7i_3 - 4i_2 - i_1 = 0$$

$$750i_2 - 250i_1 - 500i_3 = 0$$

$$-2i_3 + 3i_2 - i_1 = 0$$

$$v_3 = 500(i_2 - i_3)$$

$$20 = 350i_1 - 250i_2$$

$$-14i_3 - 8i_2 - 2i_1 = 0$$

$$2 = 35i_1 - 25i_2$$

$$-14i_3 - 2i_2 + 7i_1 = 0$$

$$2 = 35(29/5)i_2 - 25i_2$$

$$-29i_2 + 5i_1 = 0$$

$$i_2 = 2/178 = 0.01126$$

$$i_1 = 29/5i_2$$

$$\text{EQN1: } 100i_1 - 20 + 250(i_1 - i_2) = 0 \checkmark$$

$$\text{EQN2: } 250(i_2 - i_1) + 500(i_2 - i_3) = 0 \times$$

$$\text{EQN3: } 500(i_3 - i_2) - 0.4(i_1 - i_2) 250 + 200i_3 = 0 \checkmark$$

$$\text{EQN4: } i_4 = 0.003[500(i_2 - i_3)] \checkmark$$

c) Find power absorbed by 20V source by solving equations from a) or b). (6 pts)

$$i_4 = 1.5i_2 - 1.5i_3$$

$$i_1 \rightarrow : 20 = 350i_1 - 250i_2$$

$$i_2 \rightarrow : 750i_2 - 250i_1 - 500i_3 = 0$$

$$\Rightarrow 0.2 = i_4 - i_2$$

$$2 = 35i_1 - 25i_2$$

$$i_1 - 3i_2 + 2i_3 = 0$$

$$i_4 = 1.5(i_2 - 0.2) - 1.5i_3$$

$$i_3 \rightarrow : 700i_3 - 400i_2 - 100i_1 = 0$$

$$1.5i_3 + 0.3 = 0.5i_4$$

$$-i_1 + 4i_2 + 7i_3 = 0$$

$$\star \quad i_4 = 3i_3 + 0.6$$

$$i_1 - 3i_2 + 2i_3 = 0$$

$$\frac{2+25i_2}{35} + 3i_2 + \frac{14}{9}i_2 = 0$$

$$-7i_2 + 9i_3 = 0$$

$$i_1 = \frac{2+25i_2}{35}$$

$$i_3 = \frac{7}{9}i_2$$

$$18 + 225i_2 + 945i_2 + 150i_2$$

$$i_1 = 0.0494$$

~~$$18 = -1660i_2$$~~







~~$$i_2 = -0.0108$$~~

$$\boxed{\text{Power absorbed} = 0.988 \text{ W}}$$

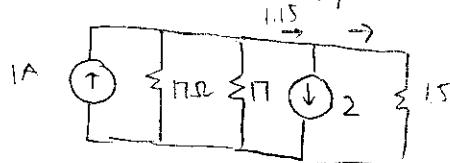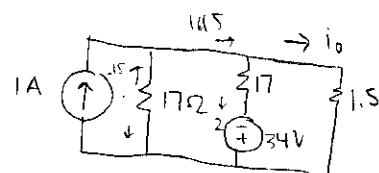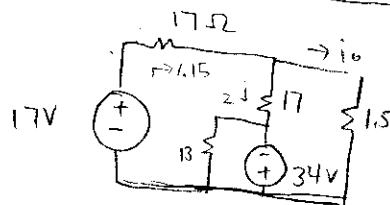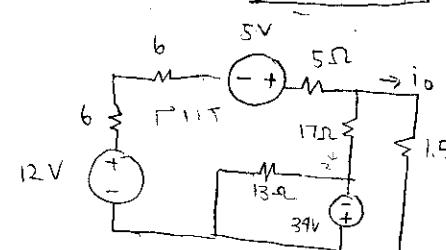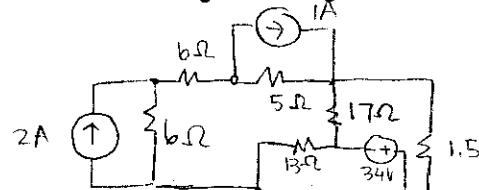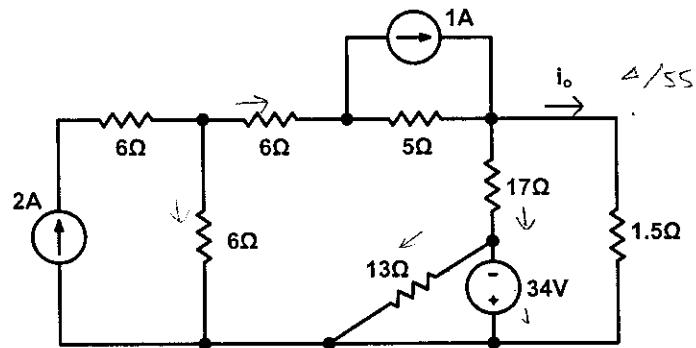4. Source transformation

[10 pts]


Use a series of source transformation to find the current  $i_o$  in the circuit.



$17||17$

$$R_{eq} = \frac{1}{\frac{1}{17} + \frac{1}{17}} = \frac{2}{17}$$

$$R_{eq} = 17/2$$

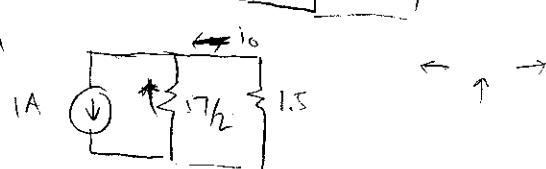

$$i_o = -\left(\frac{17/2}{17/2 + 17/2}\right) = -\left(\frac{17/2}{10}\right) = -(0.85)$$

$$i_o = -0.85 \text{ A}$$