

EE 10 Circuit Analysis I
Fall 2009

Midterm Examination

Closed Book

Name:

Student ID No.:



1) 10 / 10

2) 10 / 10

3) 10 / 10

4) 9 / 10

TOTAL 39 / 40

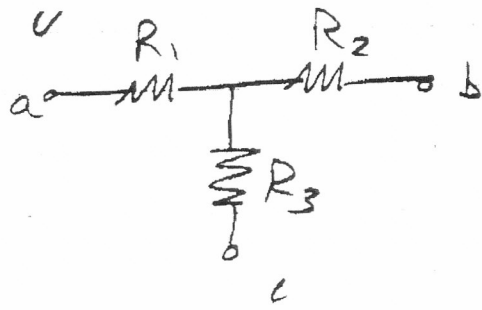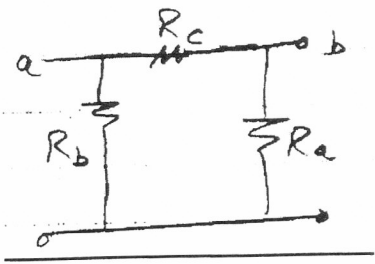

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$


$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

10 pts

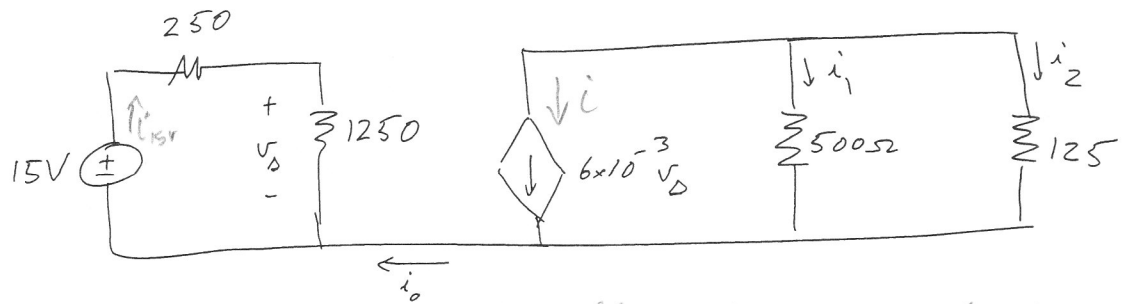Problem 1.Find the current i_o , i_1 , and i_2 .

$i_o = 0$ because current cannot flow in one conductor
 Current need to conductors to circulate between the
 two parts of the circuit.

$$i_{15V} = \frac{15}{250+1250} = 0.01 A.$$

$$V_{\Delta} = 0.01(1250) = 12.5 V.$$

$$i = 6 \times 10^{-3} (12.5) = 0.075 A.$$

(+10)


$$i_1 = -\frac{R_{eq}}{500\Omega} \cdot i = -\frac{500 \times 125}{500 + 125} \cdot 0.075 = -0.015 A \quad i_1$$

$$i_2 = -\frac{R_{eq}}{125} \cdot i = -\frac{500 \times 125}{500 + 125} \cdot 0.075 = -0.06 A \quad i_2$$

10 pts

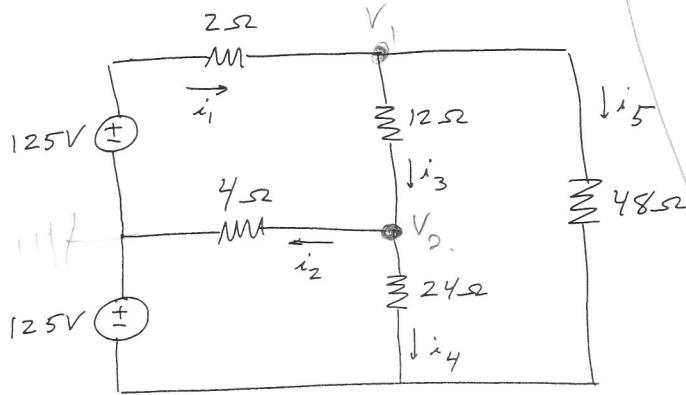Problem 2.

Use the node voltage method to find currents $i_1 - i_5$.



mesh current method to confirm
 $-125 + 2I_A + 12(I_A - I_C) + 4(I_A - I_B) = 0$
 $-125 + 4(I_B - I_A) + 24(I_B - I_C) = 0$
 $48I_C + 24(I_C - I_B) + 12(I_C - I_A) = 0$
 $I_A = 12.36$
 $I_B = 10.25$
 $I_C = 4.693$

$$\frac{V_1 - 125}{2} + \frac{V_1 - V_2}{12} + \frac{V_1 + 125}{48} = 0$$

$$\frac{V_2}{4} + \frac{V_2 - V_1}{12} + \frac{V_2 + 125}{24} = 0$$

$$V_1 \left(\frac{1}{2} + \frac{1}{12} + \frac{1}{48} \right) + V_2 \left(-\frac{1}{12} \right) - \frac{125}{2} + \frac{125}{48} = 0 \quad (+10)$$

$$V_1 \left(-\frac{1}{12} \right) + V_2 \left(\frac{1}{4} + \frac{1}{12} + \frac{1}{24} \right) + \frac{125}{24} = 0$$

$$0.6041666 V_1 - 0.08333 V_2 = 59.89583$$

$$-0.08333 V_1 + 0.375 V_2 = -5.20833$$

$$\Rightarrow V_1 = 100.29 V$$

$$V_2 = 8.399 V$$

$$i_1 = -\left(\frac{V_1 - 125}{2} \right) = -\left(\frac{100.29 - 125}{2} \right) = 12.355 A$$

$$i_2 = \frac{V_2}{4} = \frac{8.399}{4} = 2.01 A$$

see next page.

$$i_3 = \frac{V_1 - V_2}{12} = \frac{100.29 - 8.399}{12} = \boxed{7.66 \text{ A}} \checkmark i_3$$


$$i_4 = \frac{V_2 + 125}{24} = \frac{8.399 + 125}{24} = \boxed{5.558 \text{ A}} \checkmark i_4$$

$$i_5 = \frac{V_1 + 125}{48} = \frac{100.29 + 125}{48} = \boxed{4.69 \text{ A}} \checkmark i_5$$

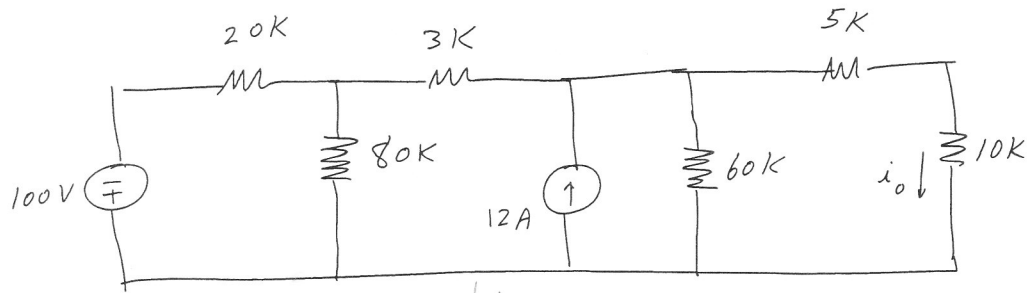
Problem 3.

10 pts


Find i_o using a series of source transformations. Be sure to redraw the circuit at each stage.




Same as.

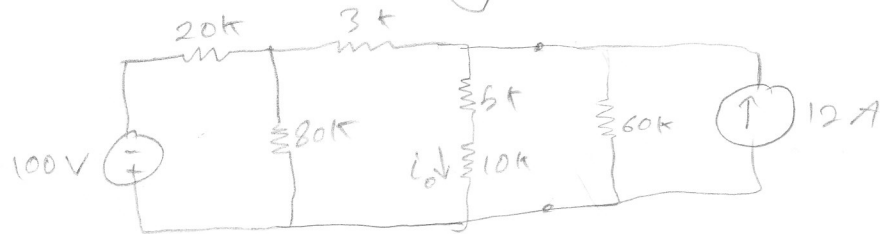

$\frac{100V}{20k} = 5mA$

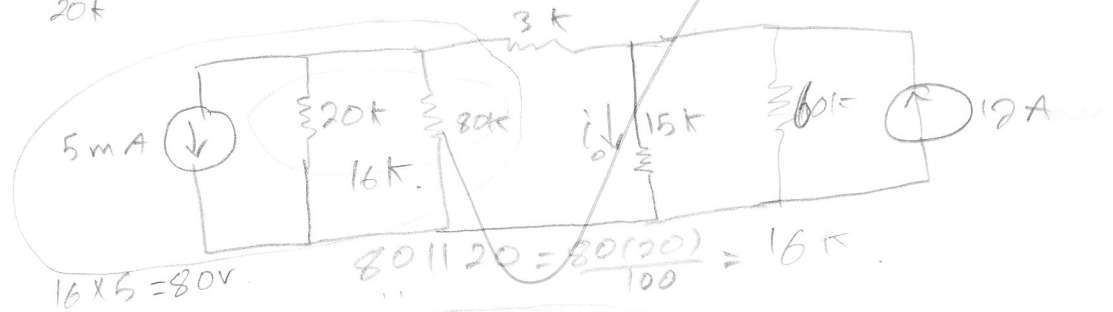


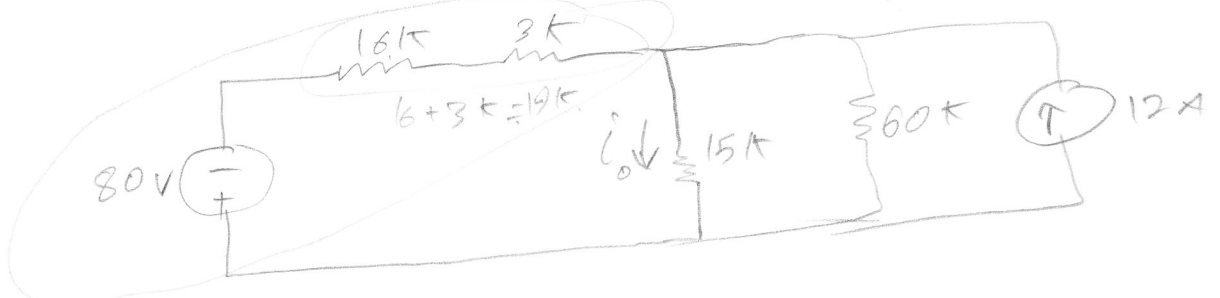$16 \times 80 = 80V$
 $80 \parallel 20 = \frac{80(20)}{100} = 16k$



$\frac{80}{13k} = 6.1538mA$

See next page.

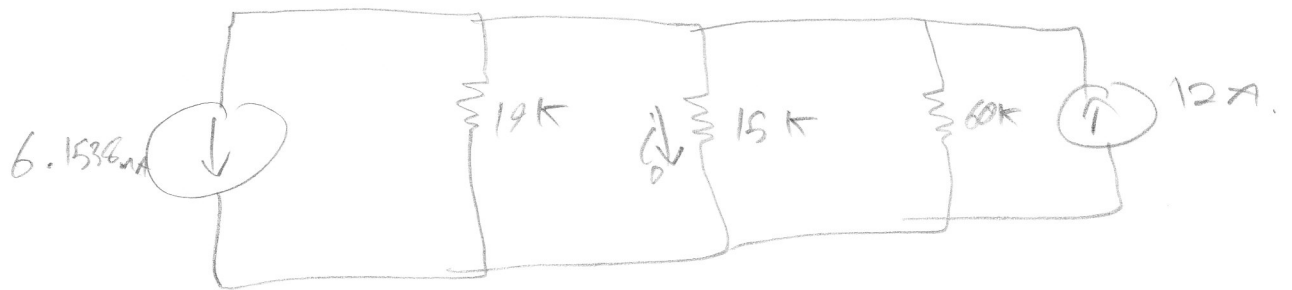

$$60 \parallel 19 = \frac{60 \times 19}{79} = 14.43 \text{ k}$$



+10

$$i_0 = \frac{R_{eq}}{15 \text{ k}} \cdot (11.9938)$$

$$= \frac{14.43}{14.43 + 15} \cdot (11.9938) = \boxed{5.88 \text{ A}}$$


Problem 4.

10 pts

5 pts

5 pts

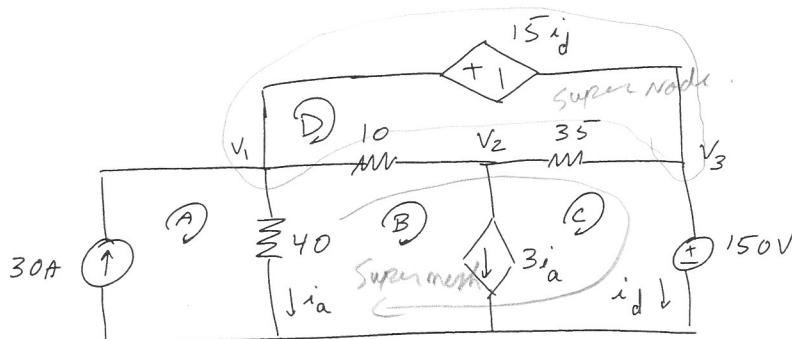- (a) For the circuit shown below, write but do not solve, the Mesh current equations in terms of I_A , I_B , I_C , and I_D . You should have 4 equations in all.
- (b) For the circuit shown below, write but do not solve, the Node voltage equations in terms of V_1 , V_2 , and V_3 . You should have 3 equations in terms of V_1 , V_2 , V_3 .



①

$$I_A = 30 \text{ A}$$

super mesh. $40(I_B - I_A) + 10(I_B - I_D) + 35(I_C - I_D) + 150 = 0$

$$10(I_D - I_B) + 15i_d + 35(I_D - I_B) = 0 \quad (1)$$

$$3i_a = I_B - I_C \quad (2)$$

$$i_a = \cancel{40}(I_A - I_B) \quad (3) ?$$

$$i_d = I_C \quad (4)$$

Substitute (4) into (1) and (3) into (2).

$$10(I_D - I_B) + 15I_C + 35(I_D - I_B) = 0$$

$$120(I_A - I_B) = I_B - I_C$$

Final mesh eqn:

$$I_A = 30 \checkmark$$

$$-40I_A + 50I_B + 35I_C - 45I_D = -150 \checkmark$$

$$-45I_B + 15I_C + 45I_D = 0 \checkmark$$

$$120I_A - 121I_B + I_C = 0 \checkmark$$

+4

b

From the
super node:

$$-30 + \frac{V_1}{40} + \frac{V_1 - V_2}{10} + \frac{V_3 - V_2}{35} + i_d = 0 \quad (1)$$

$$\frac{V_2 - V_1}{10} + \frac{V_2 - V_3}{35} + 3i_a = 0 \quad (4)$$

$$V_1 - V_3 = 15i_d \Rightarrow i_d = \frac{V_1 - V_3}{15} \quad (2)$$

(2) into (1).

$$\frac{V_1}{40} + \frac{V_1 - V_2}{10} + \frac{V_3 - V_2}{35} + \frac{V_1 - V_3}{15} = 30$$

$$i_a = \frac{V_1}{40} \checkmark \quad (3)$$

(3) into (4).

$$\frac{V_2 - V_1}{10} + \frac{V_2 - V_3}{35} + 3\frac{V_1}{40} = 0$$

$$\text{Also } V_3 = 150V$$

node voltage
eqns:

$$V_1 \left(\frac{1}{40} + \frac{1}{10} + \frac{1}{15} \right) + V_2 \left(-\frac{1}{10} - \frac{1}{35} \right) + V_3 \left(\frac{1}{35} - \frac{1}{15} \right) = 30$$

$$V_1 \left(-\frac{1}{10} + \frac{3}{40} \right) + V_2 \left(\frac{1}{10} + \frac{1}{35} \right) + V_3 \left(-\frac{1}{35} \right) = 0$$

$$V_3 = 150$$

+5