
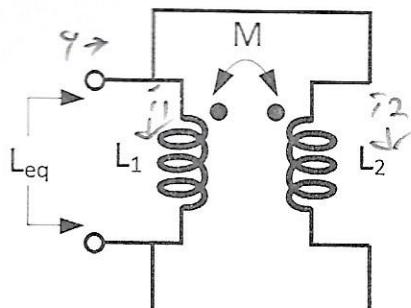


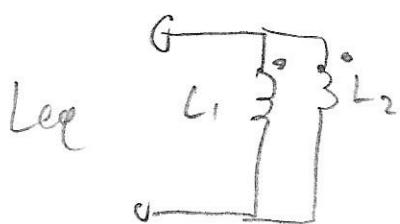1. Find the equivalent inductance of the circuit below. $L_1 = 5H$, $L_2 = 2H$, and $M = 3H$.



$$i = i_1 + i_2 \quad i' = i_1' + i_2'$$



$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \frac{di_1}{dt} = \frac{V_1 - M \frac{di_2}{dt}}{L_1}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$\frac{di_2}{dt} = \frac{V_2 - M \frac{di_1}{dt}}{L_2}$$

$$V_1 = V_2 = V$$

$$\frac{di_2}{dt} = \frac{V - M(V - M \frac{di_1}{dt})}{L_2}$$

$$L_1 L_2 \frac{\frac{di_2}{dt}}{dt} = L_1 V - M V + M^2 \frac{di_1}{dt}$$

$$\frac{di_2}{dt} (L_1 L_2 - M^2) = V(L_1 - M)$$

$$\frac{di_2}{dt} = \frac{V(L_1 - M)}{L_1 L_2 - M^2}$$

$$\frac{di_1}{dt} = \frac{V(L_2 - M)}{L_1 L_2 - M^2} + 30$$


$$i_1 + i_2 = i' = \frac{V}{L_{eq}}$$

$$\therefore L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = \frac{5 \cdot 2 - 3^2}{5+2-6} = \frac{10-9}{7-6} = 1H$$

2. In the circuit below, using node analysis,

a. Find the current i .

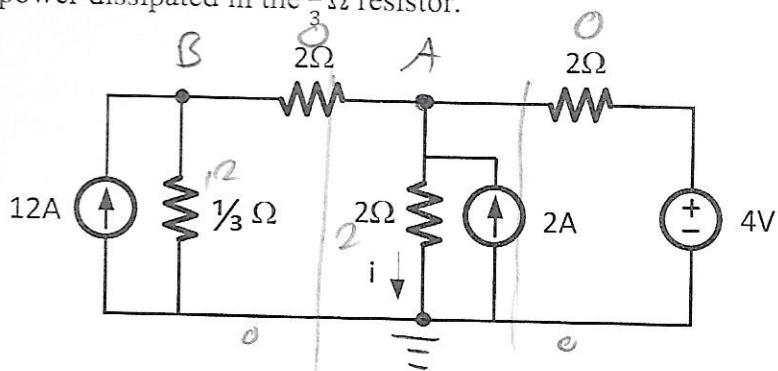b. Find the power dissipated in the $\frac{1}{3}\Omega$ resistor.



$$a) \frac{e_A}{2} + \frac{e_A - e_B}{2} + \frac{e_A - 4}{2} - 2 = 0$$

$$3e_B + \frac{e_B - e_A}{2} - 12 = 0$$

$$6e_B + e_B - e_A = 24$$

$$e_A = 7e_B - 24$$

$$e_A + e_A - e_B + e_A - 4 = 4$$

$$3e_A - e_B = 8$$

$$-e_A + 7e_B = 24$$

$$21e_A - 7e_B = 56$$

$$20e_A = 56 + 24 = 80$$

$$e_A = 4 \text{ V}$$

$$12 - e_B = 8$$

$$e_B = 4 \text{ V}$$

$$b) 3^2 \cdot 4^2 = 48 \text{ W}$$

$$+30$$

$$3e_B = 12$$


$$i^2 R = \frac{144}{3} = 48$$

$$V = 4 \quad i = 12 \\ 48$$

$$-3e_A + 2e_B = 72$$


$$20e_B = 80$$

$$e_B = 4$$

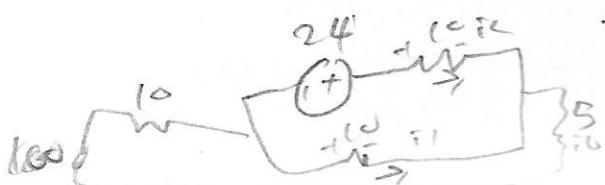


$$\begin{aligned}
 & -24 + 10i_L - 10i_L = 0 \\
 & 24 = 10i_L + 10i_L \\
 & 24 = 20i_L \\
 & i_L = 1.2 \text{ A} \\
 & 100 = 1.2i_L + 10i_L \\
 & 100 = 15.2i_L \\
 & i_L = 6.6 \text{ A}
 \end{aligned}$$

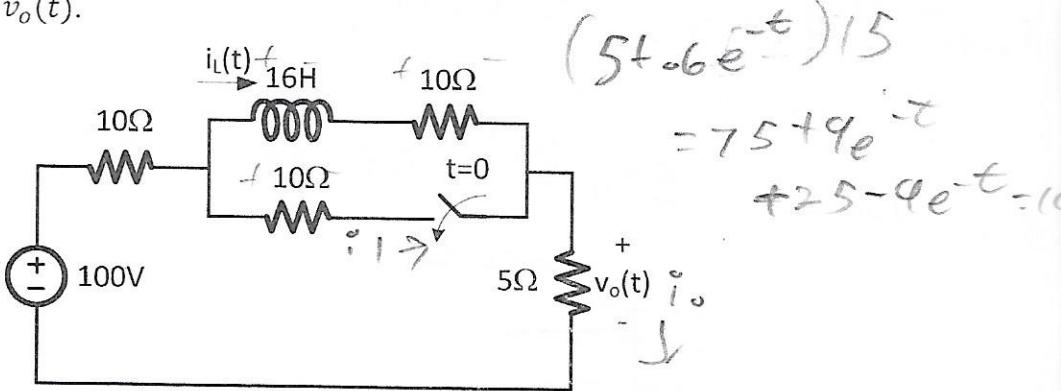3. The circuit below has been idle for a long time (switch is open). At $t = 0$, the switch is closed.
- Find the inductor current right before and after the switch is closed ($i_L(0^-)$, and $i_L(0^+)$).
 - Find v_o right before and after the switch is closed ($v_o(0^-)$, and $v_o(0^+)$).
 - Find and plot $v_o(t)$.


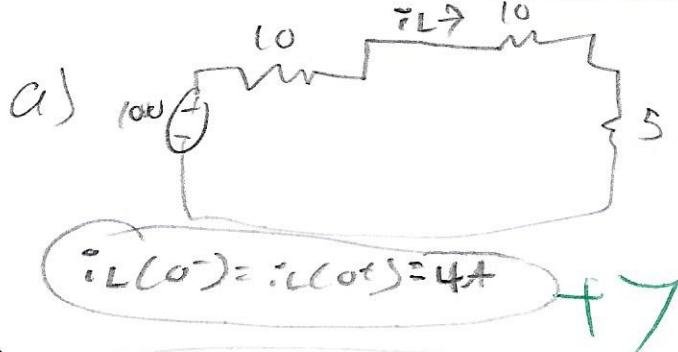
$$\begin{aligned}
 & (5t + 6e^{-t})/15 \\
 & = 75 + 9e^{-t} \\
 & + 25 - 9e^{-t} = 100
 \end{aligned}$$



$$i_L = \frac{100}{25} = 4 \text{ A} = i_L(0^-)$$


$i_L(0^+) = i_L(0^-) = 4 \text{ A}$
since infinite voltage
is not allowed (finite source)

b) $v_o(0^-) = 5 \cdot 4 = 20 \text{ V}$ $v_o(0^+) = 5 \cdot (5 + 6) = 28 \text{ V}$ +7

$$i_L(0^+) = 4 \text{ A}$$

$$i_L(0^-) = \frac{5}{2} \text{ A}$$


$R_{eq} = 5$

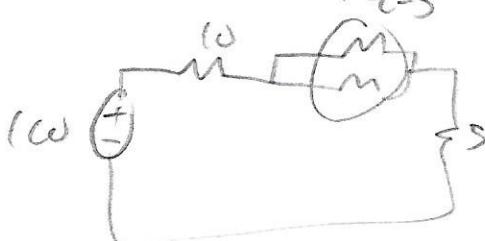

$$\begin{aligned}
 & \frac{100}{20} = 5 \text{ A} \\
 & 5 \cdot 10 = \frac{5}{2} \text{ A}
 \end{aligned}$$

$$i_L(t) = \frac{5}{2} + (4 - \frac{5}{2})e^{-\frac{16}{10}t} = \frac{5}{2} + \frac{3}{2}e^{-\frac{8}{5}t}$$
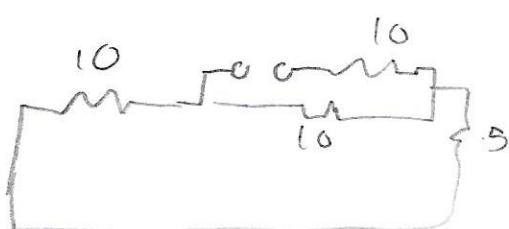
$$v_L(t) = L \frac{di_L}{dt} = 16 \left(-\frac{3}{2} e^{-\frac{8}{5}t} \right) = -24 e^{-\frac{8}{5}t}$$



$$\begin{aligned}
 & \frac{150}{25} = 6 \text{ A} \\
 & R_{eq} = 16 \Omega
 \end{aligned}$$