

Physics: \rightarrow Circuit Elements

Maxwell's Equations \rightarrow Resistor: $i-v$
 Capacitor: $q-v + i = \frac{dq}{dt}$
 Inductor: $\psi-i + v = \frac{d\psi}{dt}$
 (Mut ind): dot convention

\rightarrow ideal transformer $\begin{cases} \frac{V_1}{N_1} = \frac{V_2}{N_2} \\ i_1 N_1 + i_2 N_2 = 0 \end{cases}$

definition of power:

$P = i-v$
 $W = \int P dt$


Circuit Laws

Energy conservation \Rightarrow KVL \Rightarrow loop method

Charge conservation \Rightarrow KCL \Rightarrow node method.

\rightarrow Circuit solving techniques

• Source Shifting:

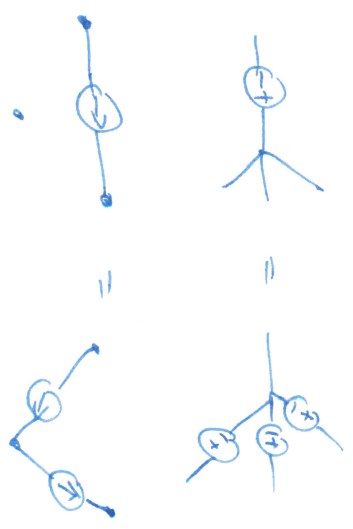

Special-case circuit:

• 1st order circuit: (1st order diff eqn)

- ① Write diff eqn based on Law + Technique
- ② Solve for ~~homogeneous~~ general
- ③ Solve for particular solution
- ④ Plug in initial condition

• 2nd order circuit: (2nd order diff eqn)

SSS: phasor:

$\begin{cases} L \rightarrow j\omega L \\ C \rightarrow \frac{1}{j\omega C} \\ R \rightarrow R \\ M \rightarrow j\omega M \end{cases}$

• Superposition: Keep ONE source at a time

~~Power~~

• Thevenin/Norton: V_{oc} I_{sc} R_{eq} (R_{th}) R_{no}



EE10 Final
Department of Electrical Engineering, UCLA
Winter 2014
Instructor: Prof. Gupta

1. Exam is closed book. Calculator and one double sided cheat-sheet is allowed.
2. Cross out *everything* that you don't want me to see. Points will be deducted for everything wrong!
3. Do NOT use Laplace Transforms to solve any problems.
4. No points will be given without proper explanations

Name:

Student ID:

Solution

Student on Left:

Student on Right:


Student in Front:

Time: 135 minutes

Problem	Maximum Score	Your Score
1	6	
2	4	
3	10	
4	10	
5	10	
Total	40	

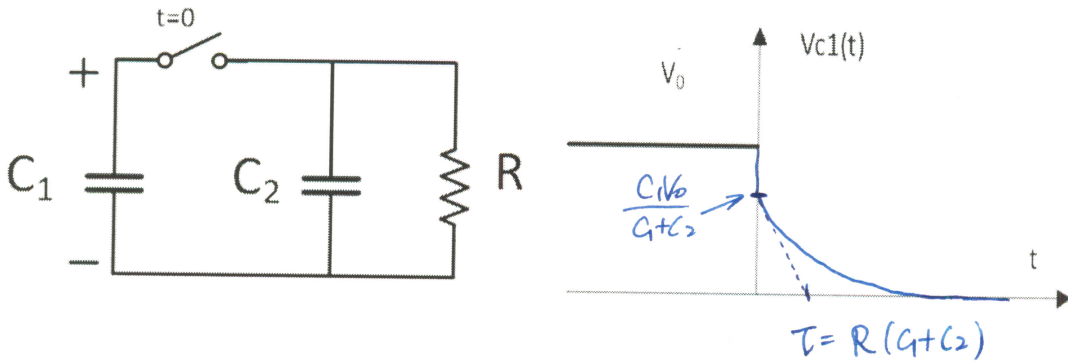Q1. (6 points) We connect charged capacitor C_1 to a discharged capacitor C_2 and a resistor R with a switch. The capacitor C_1 is charged to voltage V_0 .

We close the switch at $t=0$, derive v_{C_1} in terms of time and plot it.



At $t=0^+$, $v_{C_1} = v_{C_2} = v_R$

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

There is no charge going through R from $t=0^-$ to $t=0^+$,


otherwise: $i_R = \frac{dQ_R}{dt} = \infty \implies v_R = \infty \implies \underline{\underline{\text{contradiction}}}$

$$\begin{cases} Q_1 + Q_2 = C_1 \times V_0 \\ \frac{Q_1}{C_1} = \frac{Q_2}{C_2} \end{cases} \implies \begin{cases} Q_1 = C_1 V_0 \times \frac{C_1}{C_1 + C_2} \\ Q_2 = C_1 V_0 \times \frac{C_2}{C_1 + C_2} \end{cases} \implies \begin{aligned} v_{C_1} &= v_{C_2} \\ &= \frac{C_1 V_0}{C_1 + C_2} \end{aligned}$$

At $t > 0^+$, regular 1st-order circuit.

Q2. (4 points) In this circuit: $|V_1| = |V_2|$, V_s leads V_2 by 30°

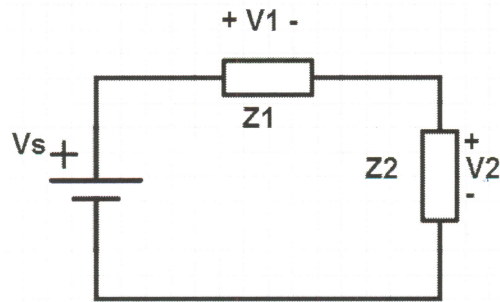For a $V_s(t) = 10 \cos 3t$ find $V_2(t)$ in steady state.



Or graphically:-

$$V_s = V_1 + V_2$$

$$10 = V_1 + V_2$$


$$= |V_1| e^{j\phi_1} + |V_2| e^{j\phi_2}$$

$$= |V_1| e^{j\phi_1} + |V_1| e^{j(-30^\circ)}$$

$$\phi_1 = 30^\circ \quad \phi_2 = -30^\circ$$





$$|V_1| = \frac{10}{\sqrt{3}} = \frac{10\sqrt{3}}{3}$$
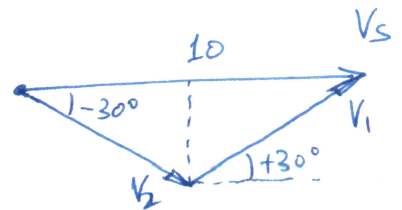
$$V_2(t) = \frac{10\sqrt{3}}{2} \cos(3t - 30^\circ)$$



Q3. (6 + 4 = 10 points)

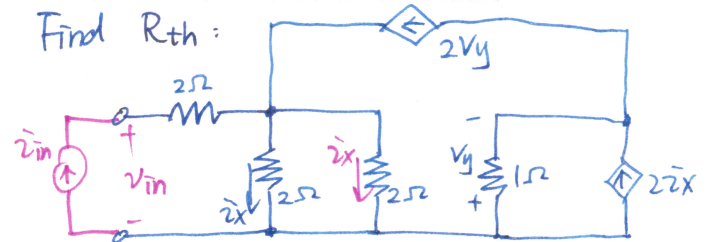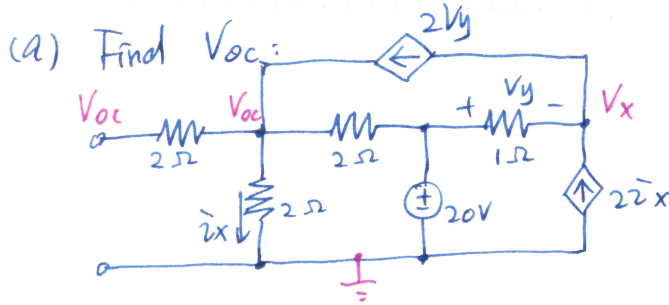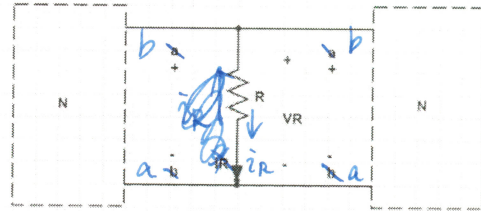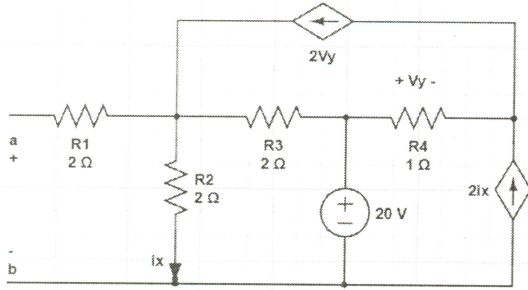- a) Find Thevenin equivalent of the circuit on the left (network N) looking from a & b
 b) If we use network N to implement the circuit on the right what is i_R if $V_R = \frac{5}{2}i_R + i_R^2$ (for $i_R > 0$)



$$\begin{cases} \frac{20 - V_{oc}}{2} + 2(20 - V_x) = \frac{V_{oc}}{2} \\ 2 \times \frac{V_{oc}}{2} + \frac{20 - V_x}{1} = 2(20 - V_x) \end{cases}$$

$$\Rightarrow V_{oc} = -10V$$




$$\frac{V_y}{1} + 2i_x = 2V_y \Rightarrow V_y = 2i_x$$

$$i_{in} + 2(2i_x) = i_x + i_x \Rightarrow i_{in} = -2i_x$$

$$V_{in} = i_{in} \times 2 + i_x \times 2 = (-2i_x) \times 2 + i_x \times 2 = -2i_x$$
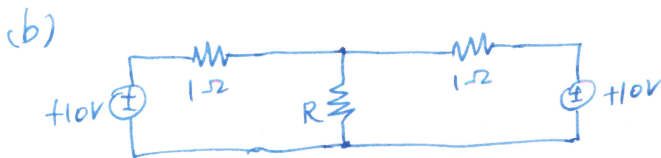
$$\Rightarrow R_{th} = \frac{V_{in}}{i_{in}} = 1$$



$$\frac{V_R}{0.5} + i_R = -20$$


$$5i_R + 2i_R^2 + i_R + 20 = 0$$

$$i_R = \boxed{2A} \text{ or } \boxed{-5A} \Rightarrow i_R = 2A$$



Q4. (5 + 3 + 2 = 10 points)

Assume $\omega = 10^4$ rad/sec.

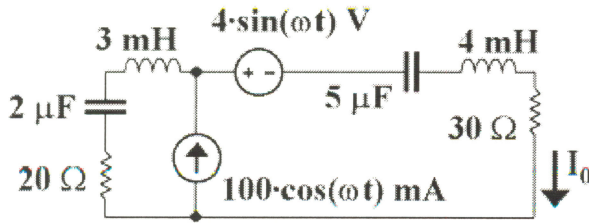- (a) Use source transformation to obtain the current I_0 . Express your answer in milliamps, both in the phasor notation (rectangular form) and in the time domain.
 (b) Draw a phasor diagram showing the voltage across 30ohm resistor, 4mH inductor, 5uF capacitor.
 (c) A complicated RLC circuit has a steady state current response of $10\cos(100t + 0.2)$ amperes when a voltage source of $10\cos(100t)$ volts is applied to it. Now, instead of the original source, a voltage source of $20\cos(100t + 0.1)$ volts is applied to the circuit. Can you find the new current response? Is this information enough to find it? If yes, find the new current response. If not, give reasons justifying your answer. In either case, explain your answer.




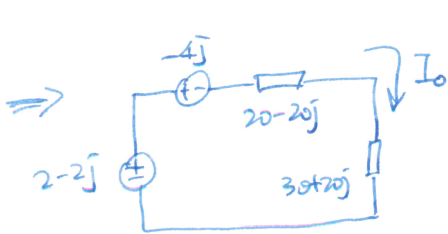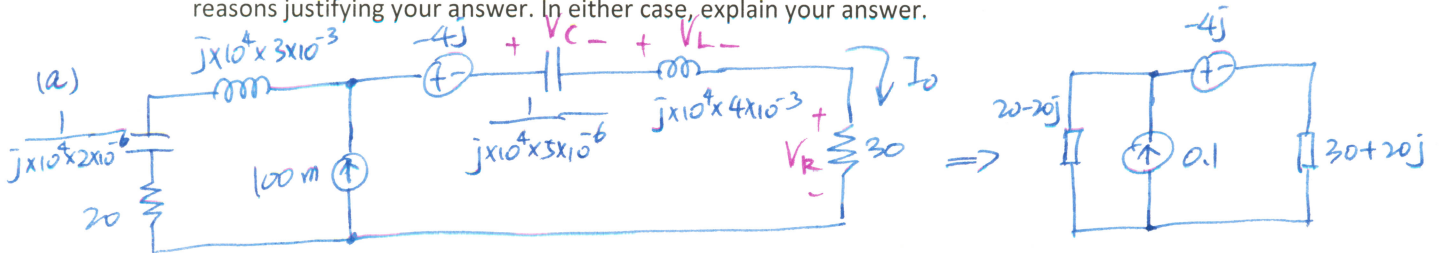- (c) A complicated RLC circuit has a steady state current response of $10\cos(100t + 0.2)$ amperes when a voltage source of $10\cos(100t)$ volts is applied to it. Now, instead of the original source, a voltage source of $20\cos(100t + 0.1)$ volts is applied to the circuit. Can you find the new current response? Is this information enough to find it? If yes, find the new current response. If not, give reasons justifying your answer. In either case, explain your answer.





$$I_0 = \frac{2+2j}{50} = 0.04 + 0.04j = (40 + 40j) \text{ mA}$$
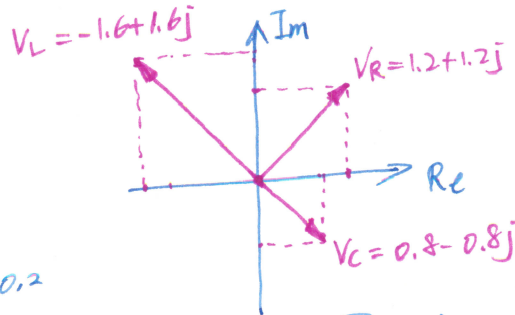
$$i_0(t) = 40\sqrt{2} \times \cos(10^4 t + 45^\circ) \text{ mA}$$



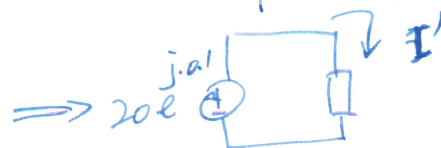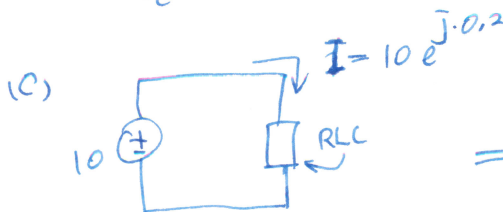(b) $V_R = 1.2 + 1.2j$
 $V_L = -1.6 + 1.6j$
 $V_C = 0.8 - 0.8j$




$$i'(t) = 20 \cos(100t + 0.3)$$

$$Z_{RLC} = \frac{10}{1 \cdot 0.2}$$

$$I' = \frac{20 \cdot e^{j \cdot 0.1}}{Z} = 20 \times e^{j \cdot 0.3}$$

Q5. (4 + 6 = 10 points)

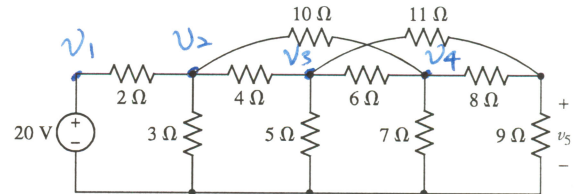- (a) Label the nodes in this circuit and write down the matrix equation to solve this circuit by node method. You don't need to solve the actual KCL equations.



$$\begin{bmatrix} 20 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ -\frac{1}{2} & \frac{1}{2} + \frac{1}{3} & -\frac{1}{4} & -\frac{1}{10} & 0 \\ 0 & -\frac{1}{4} & \frac{1}{4} + \frac{1}{5} & -\frac{1}{6} & -\frac{1}{11} \\ 0 & -\frac{1}{10} & -\frac{1}{6} & \frac{1}{6} + \frac{1}{8} & -\frac{1}{11} \\ 0 & 0 & -\frac{1}{11} & -\frac{1}{8} & \frac{1}{8} + \frac{1}{9} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}$$

(b)

Consider the circuit shown in Figure 1(a). The current $i(t)$, flowing through the inductor was found to obey the straight-line plot shown in Figure 1(b) for $0 < t < 4\text{ms}$. Find an expression for $v(t)$ for $0 < t < 4\text{ms}$ which satisfies the observation and draw a neat plot for it.

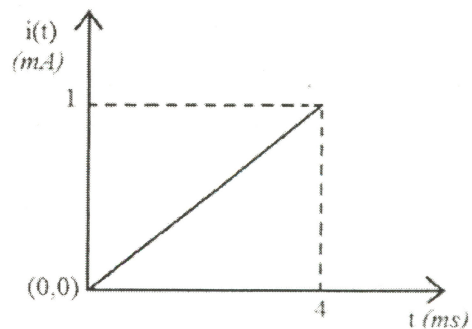
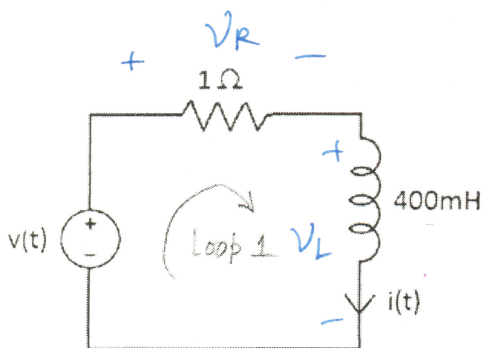


FIGURE 1(a)

FIGURE 1(b)

$$v_L = L \frac{di}{dt} = 0.4 \times \frac{1}{4} = 0.1 \text{ V}$$

$$v_R = R \cdot i = 1 \times i(t) = \frac{1}{4} t \text{ V}$$

$$v(t) = (0.1 + 0.25t) \text{ V} \quad t \text{ in ms}$$

$$= (100 + 0.25t) \text{ mV} \quad t \text{ in ms}$$

