

EE10 Midterm 1

February 8, 2012

Winter, 2012

Department of Electrical Engineering, UCLA

Instructor: Prof. Puneet Gupta

DURATION: 1 hour 15 minutes

1. Exam is closed book. You are allowed one 8.5" X 11" single-sided cheat sheet.
2. Calculators are allowed.
3. Cross out everything that you don't want evaluated. Points will be deducted for everything wrong!

NAME:

STUDENT ID:

SOLUTIONS

STUDENT ON LEFT:


STUDENT ON RIGHT:

STUDENT IN FRONT:


PROBLEM	MAXIMUM SCORE	YOUR SCORE
1	12	
2	5	
3	6	
4	3	
5	4	
TOTAL	30	

Question 1

12 points (2+2+6+2)

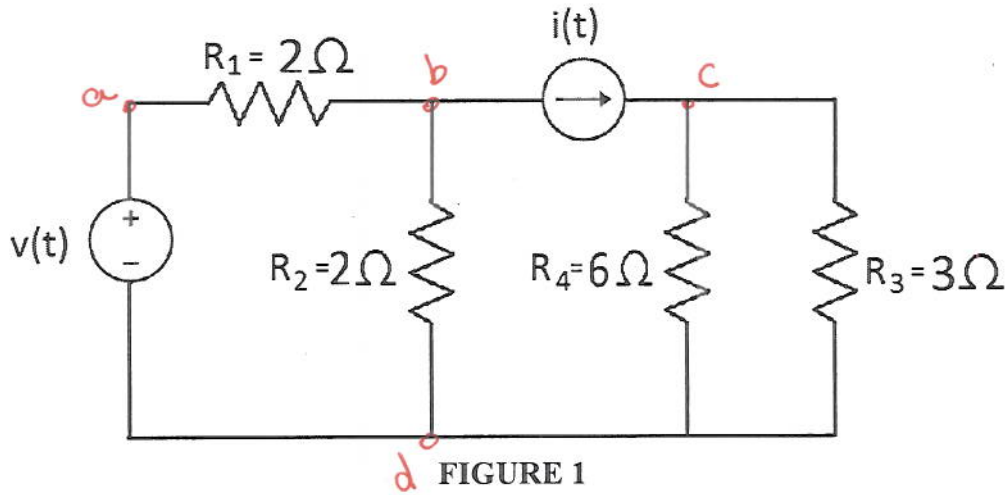

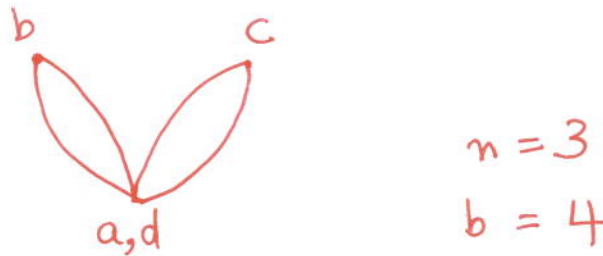(a) Draw the graph of the circuit in Figure 1 after zeroing out all sources.



(b) (i) What is the minimum number of node voltage equations needed to solve the circuit?


$$n - 1 = 2$$

(ii) What is the minimum number of loop current equations needed to solve the circuit?

$$b - (n - 1) = 4 - 2 = 2$$

(c) (i) Compute the power supplied by the voltage source. $\leftarrow P_v$

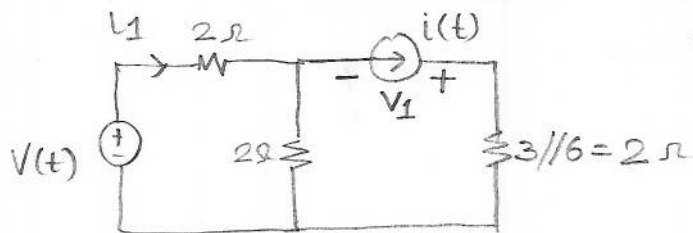(ii) Compute the power supplied by the current source. $\leftarrow P_i$



$$\Rightarrow v = 2i_1 + 2(i_1 - i)$$

$$\Rightarrow i_1 = \frac{v + 2i}{4}$$

$$\Rightarrow (i) P_v = v \cdot i_1 = \boxed{\frac{v^2}{4} + \frac{vi}{2}} \text{ (Watts)}$$

$$\text{Now, } V_1 = 2 \times i + 2 \times (i - i_1)$$

$$= 4i - 2i_1$$

$$= 4i - 2 \left(\frac{v + 2i}{4} \right)$$

$$= 3i - \frac{v}{2}$$

$$\therefore P_i = V_1 \times i = \boxed{3i^2 - \frac{vi}{2}} \text{ (Watts)}$$

(d) Compute the total power absorbed by all resistors. $\leftarrow P_R$

$P_R =$ Total power supplied by the two sources (v & i)

$$\therefore P_R = \left(\frac{v^2}{4} + \frac{vi}{2} \right) + \left(3i^2 - \frac{vi}{2} \right)$$

$$\boxed{P_R = \frac{v^2}{4} + 3i^2} \text{ (Watts)}$$

Question 2

5 points

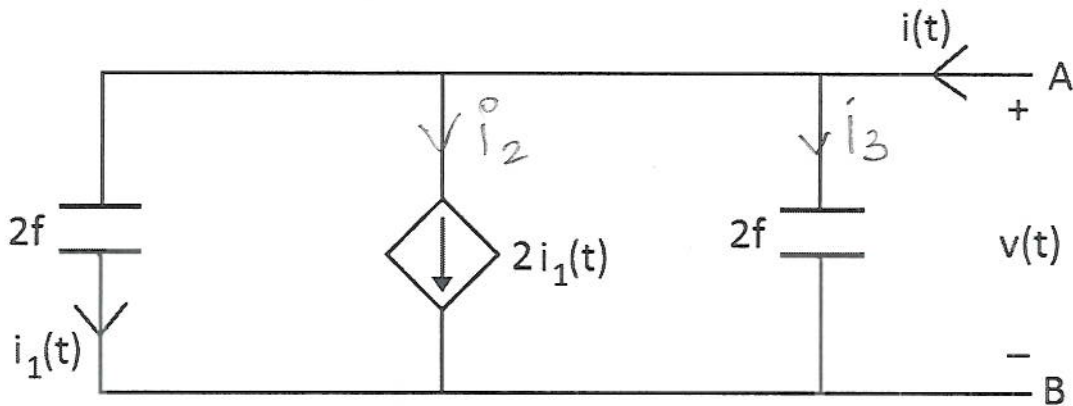


FIGURE 2

Show that the network in Figure 2 is equivalent to a single capacitor between terminals A and B. Find the value of the equivalent capacitance.

Using KCL,

$$i(t) = i_1(t) + i_2(t) + i_3(t)$$

$$i(t) = 2 \frac{dv}{dt} + 2 \left(2 \frac{dv}{dt} \right) + 2 \frac{dv}{dt}$$

$$i(t) = 8 \frac{dv(t)}{dt}$$

Expression for v & i resembles a capacitive relation
($i = C \frac{dv}{dt}$)
∴ Network is equivalent to a capacitor of value 8F between terminals A & B.

Question 3

(6 points)


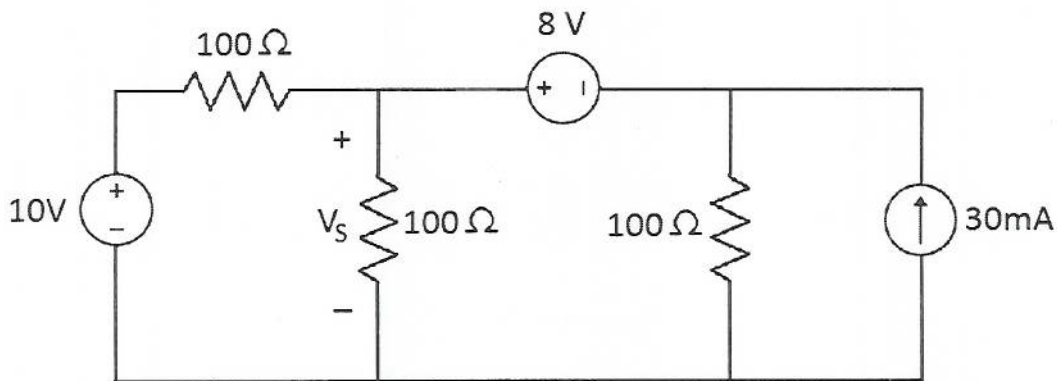


FIGURE 3

For the circuit in Figure 3, find the value of voltage V_s using source transformations. After doing the transformations, use exactly one KVL equation for finding V_s .

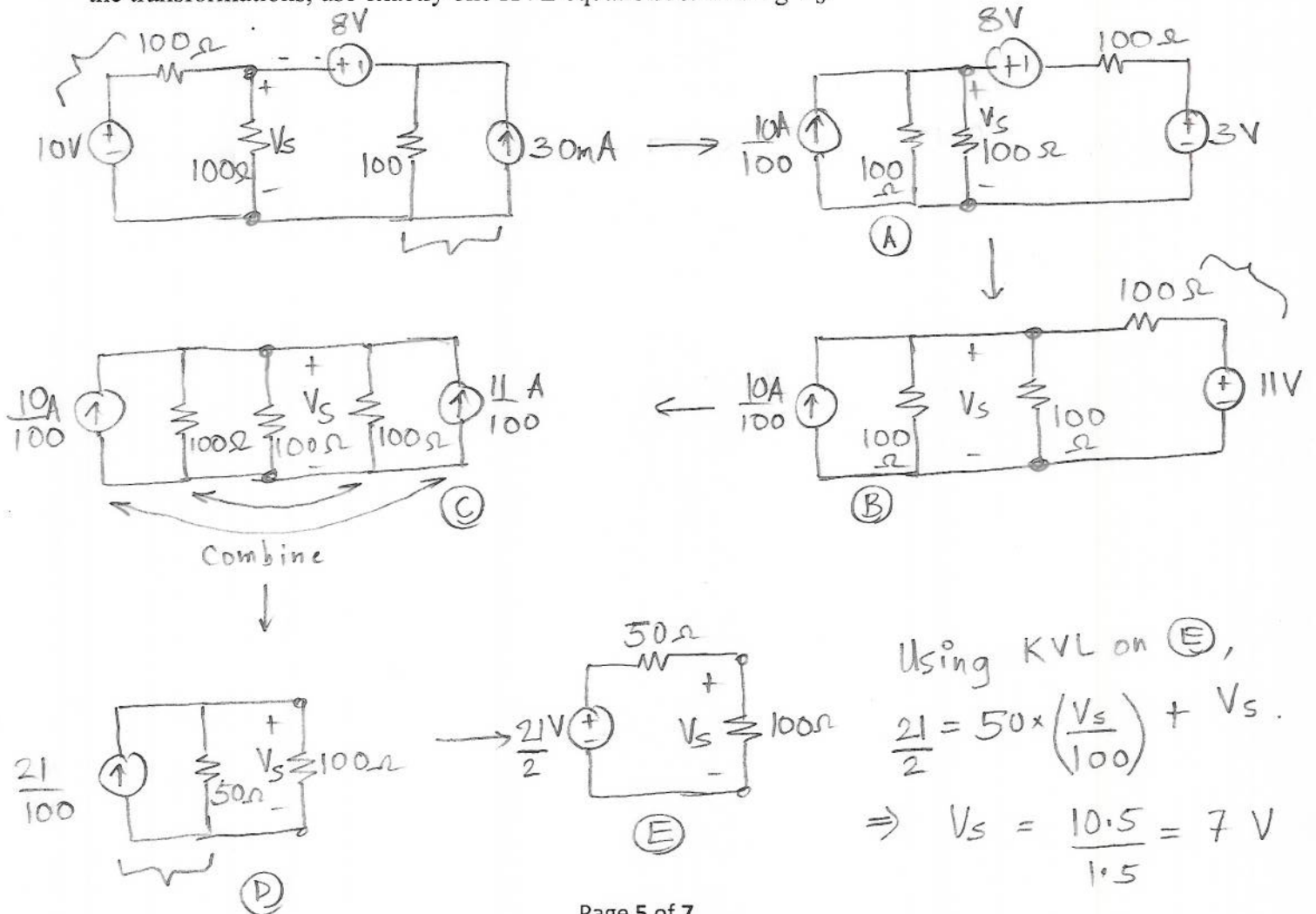

Question 4

(3 points)

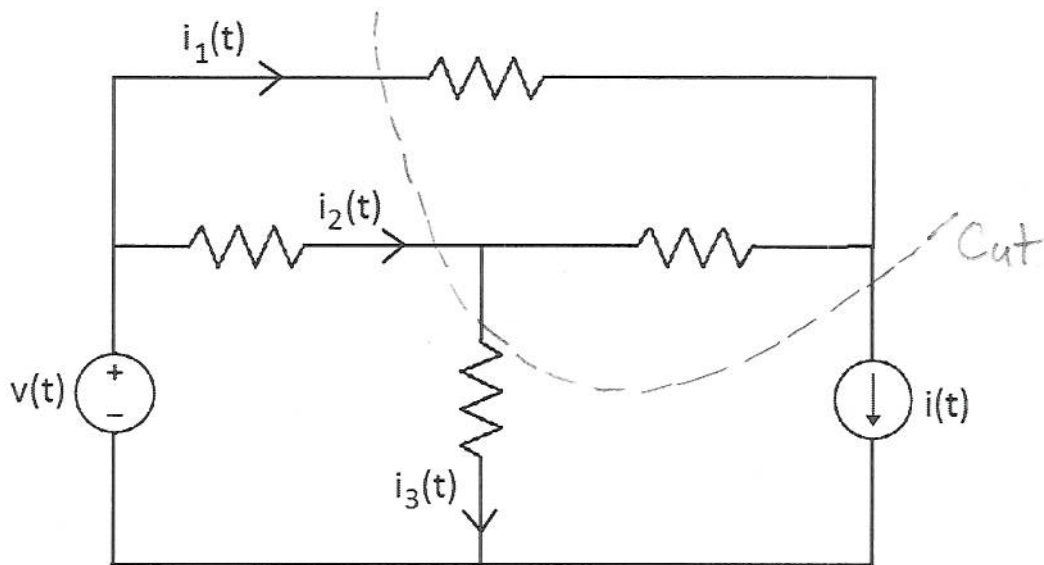


FIGURE 4

Draw a suitable cut-set on the above circuit to relate the currents $i_1(t)$, $i_2(t)$, $i_3(t)$ and $i(t)$ in only one KCL equation. Also write the resulting KCL equation relating the four mentioned currents.

Total Current through the cutset = 0.

$$\therefore i_1(t) + i_2(t) - i_3(t) - i(t) = 0.$$

Question 5

(4 points)

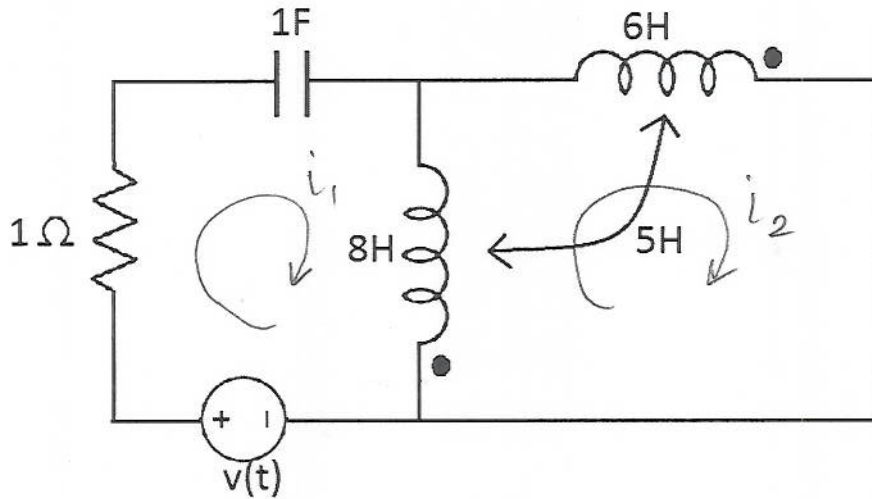


FIGURE 5

For the circuit shown in Figure 5, write the loop equations in matrix form by inspection. There is no need to solve them.

$$\begin{bmatrix} V(t) \\ 0 \end{bmatrix} = \begin{bmatrix} 1 + \frac{1}{s} + 8s & -5s \\ 5s - 8s & 6s + 8s - 5s - 5s \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$