

EE 10 : Circuit Analysis I

Winter 2012

Instructor: Prof. Puneet Gupta

Solutions to Practice Midterm 2

①

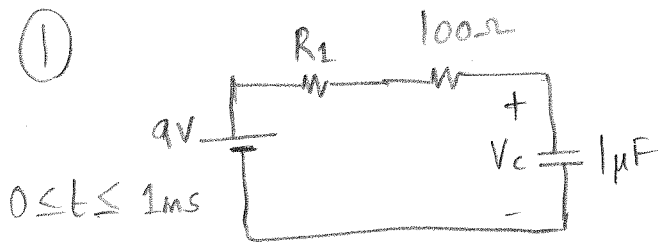


Fig. 1

Steady state voltage if the circuit connections remained as in Fig. 1 for ever.

$$V_c(t) = V_c(\infty) - [V_c(\infty) - V_c(0)] e^{-t/\tau_1}$$

$$V_c(\infty) = 9V$$

$$V_c(0) = 0V$$

$$\tau_1 = (R_1 + 100)C$$

$$\therefore V_c(t) = 9(1 - e^{-t/\tau_1}) \text{ for } 0 \leq t \leq 1ms$$

$$\text{Given } V_c(1ms) = 8 \Rightarrow 9(1 - e^{-1m/\tau_1}) = 8$$

$$\Rightarrow \tau_1 = \frac{1ms}{\ln 9} = (R_1 + 100) \times 10^{-6}$$

$$\therefore R_1 = \frac{10^3}{\ln 9} - 100 \approx 355.12 \Omega$$

For $1ms < t < \infty$

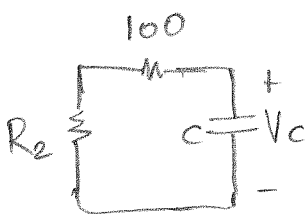


Fig. 2

$$V_c(t) = V_c(\infty) - [V_c(\infty) - V_c(1ms)] e^{-(t-1ms)/\tau_2}$$

↑
Timeshift!

Steady state voltage if the circuit connections remained as in Fig. 2 for ever.

$$V_c(\infty) = 0V$$

$$V_c(1ms) = 8V \text{ (Given)}$$

$$\tau_2 = (R_2 + 100)C$$

$$\therefore V_c(t) = 8e^{-(t-1ms)/\tau_2} \text{ for } 1ms < t < \infty$$




Given $V_c(2\text{ms}) = 1\text{V}$

$$\Rightarrow 1 = 8e^{-(2-1)\text{ms}/\tau_2} \Rightarrow \tau_2 = \frac{1\text{ms}}{\ln 8} = (R_2 + 100) \times 10^{-6}$$

$$\therefore R_2 = \frac{10^3}{\ln 8} - 100 \approx 380.89 \Omega$$

$$\therefore \boxed{\begin{matrix} R_1 = 355.12 \Omega \\ R_2 = 380.89 \Omega \end{matrix}}$$

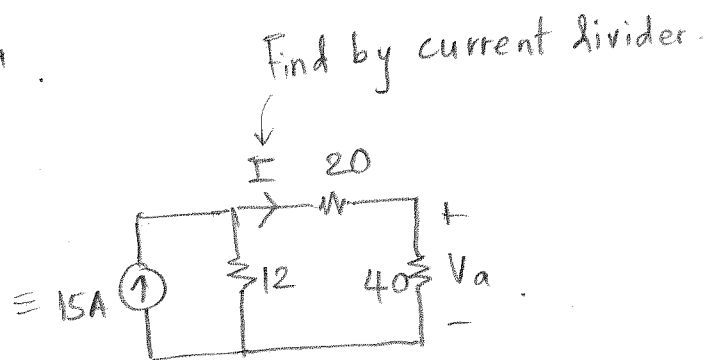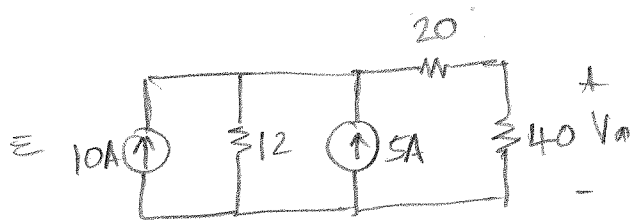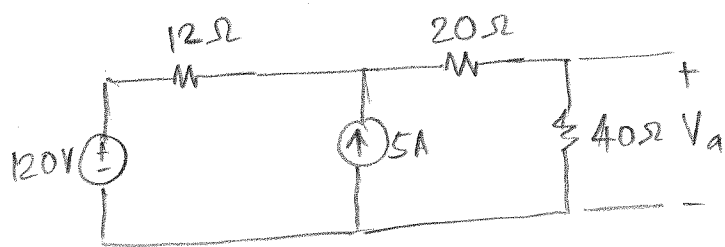
② In steady state, an inductor is equivalent to a short circuit, a capacitor is equivalent to an open circuit. Using this, the equivalent circuit to the given circuit becomes




$$\therefore V_a = \frac{12}{12 + (20 + 40)} \times 15 \times 40 = \frac{12}{72} \times 15 \times 40 = 100\text{V}$$

$$\therefore \boxed{V_a = 100\text{V}}$$

3

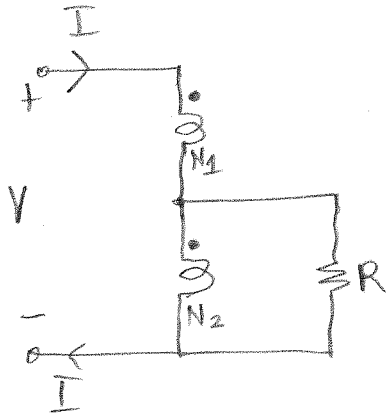

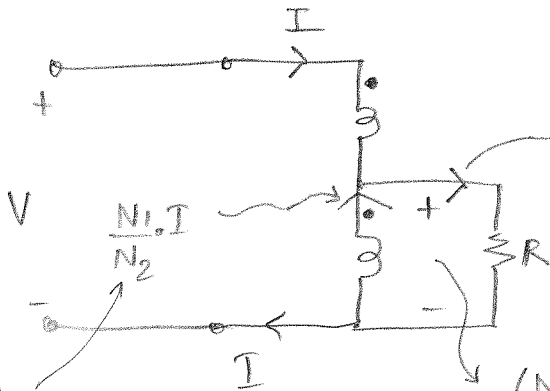Assuming V & I as the only variables, we will find all other voltages & currents in terms of these.




KCL \Rightarrow

$$\frac{N_1}{N_2} I + I = \left(\frac{N_1 + 1}{N_2}\right) I$$

$$\left(\frac{N_1 + 1}{N_2}\right) I \times R$$

Using transformer current equation.

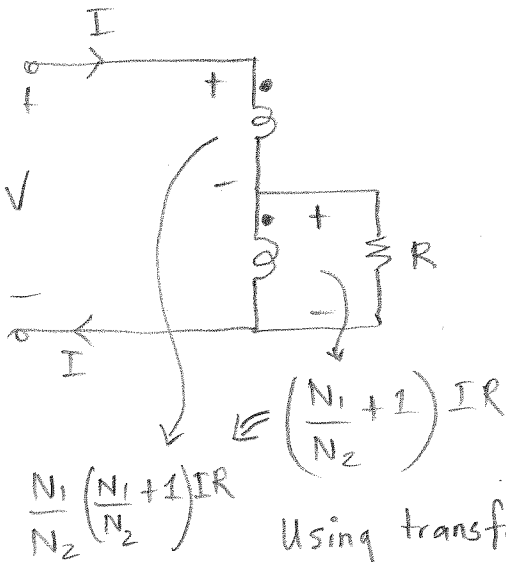

$$\frac{N_1}{N_2} \left(\frac{N_1 + 1}{N_2}\right) IR$$

Using transformer voltage equation.





$$V = \frac{N_1}{N_2} \left(\frac{N_1 + 1}{N_2}\right) IR + \left(\frac{N_1 + 1}{N_2}\right) IR$$

$$\Rightarrow \frac{V}{I} = \left(\frac{N_1 + 1}{N_2}\right) \left[\frac{N_1 + 1}{N_2}\right] R$$

$$\therefore \boxed{R_{eq} = \left(\frac{N_1 + 1}{N_2}\right)^2 R}$$

4

Possible network connections:

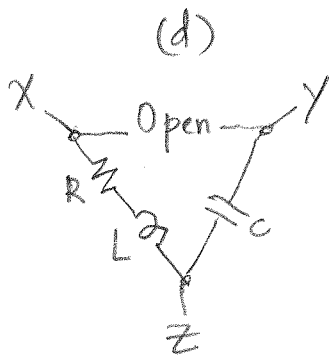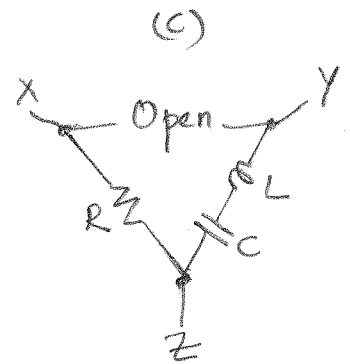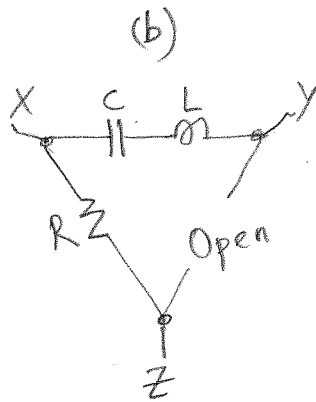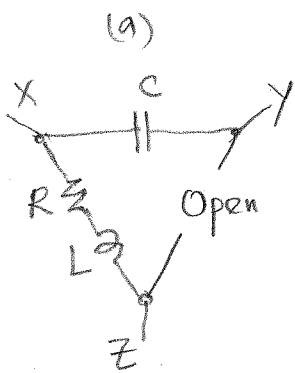

$R = 10\Omega$ in all the connections.
 L & C can be of any arbitrary values

Since the equivalent resistance between XY & YZ must be ∞ , there should be a DC open circuit between $(X \& Y)$ and $(Y \& Z)$ both. We know that elements that qualify for such a condition are a capacitor, a series LC or an actual open!

i.e. or or

Since the R_{eq} between $X \& Z$ has to be 10Ω DCwise, elements that qualify for this are an actual resistor of 10Ω or a series L-R with $R = 10\Omega$.

i.e. or