

EE10 Midterm 2

Department of Electrical Engineering, UCLA

Fall 2017

Instructor: Prof. Gupta

1. Exam is closed book. Calculator and one double sided cheat-sheet is allowed.
2. Cross out *everything* that you don't want me to see. Points will be deducted for everything wrong!
3. No points will be given without proper explanations
4. Time allotted: 75 minutes

Name: [REDACTED]

Student ID: [REDACTED]

Student on Left: [REDACTED]






Student on Right: [REDACTED]

Student in Front: [REDACTED]

Problem	Maximum Score	Your Score
1	6	6
2	6	4.5
3	10	10
4	8	4
Total	30	25

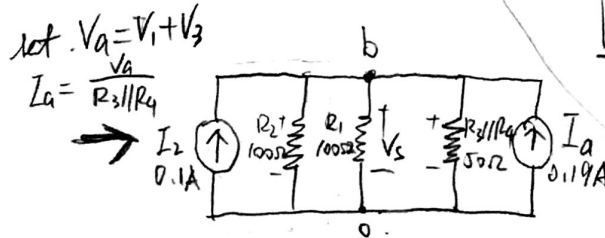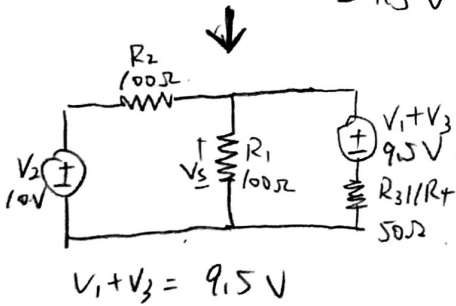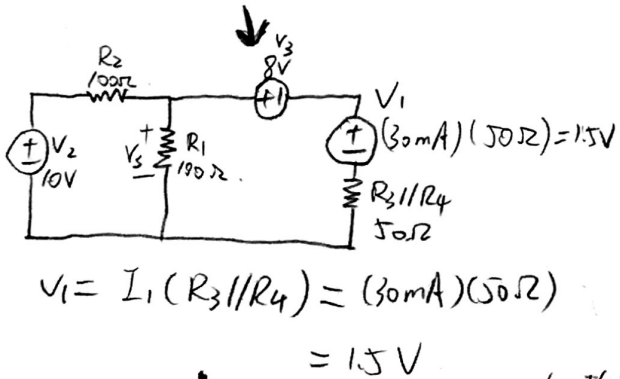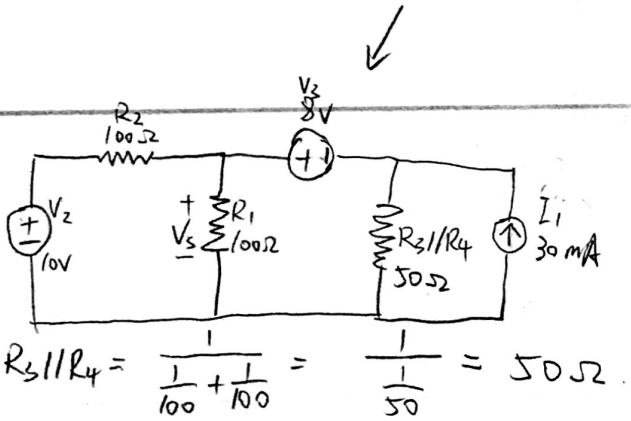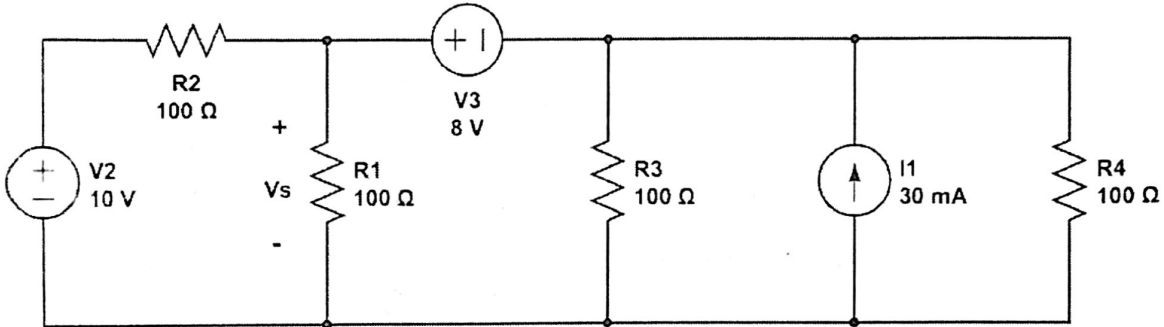Q1. (6 points)

Find V_s by repeating source transformations. Write as few KCL or KVL equations as possible.




$I_2 = \frac{10 \text{ V}}{100 \Omega} = 0.1 \text{ A}$
 $I_a = \frac{9.5 \text{ V}}{50 \Omega} = 0.19 \text{ A}$

Assume $V_b = 0$.
 write KCL:
 $\frac{V_b}{100} + \frac{V_b}{100} + \frac{V_b}{50} - 0.1 - 0.19 = 0$
 $\frac{V_b}{25} = 0.29$
 $V_b = 25 \cdot 0.29 = 7.25 \text{ V}$
 since $V_b = V_s$
 $V_s = 7.25 \text{ V}$

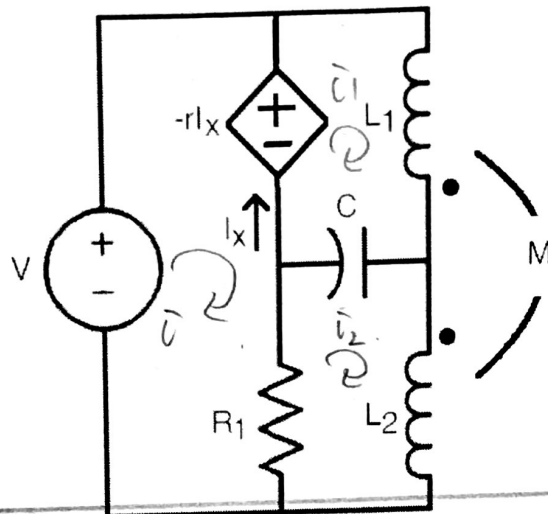Q2. (6 points)



Apply Loop Variable Analysis (Matrix KVL) to the circuit in the figure. The resulting system of equations should be presented in matrix form.



$$\begin{bmatrix} \checkmark \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} R_1 + r & -r & \cancel{rR_1} \\ -r & r + \frac{1}{C} \int dt + L_1 \frac{d}{dt} & \cancel{\frac{1}{C} \int dt - M \frac{d}{dt}} \\ -R_1 & \cancel{-\frac{1}{C} \int dt - M \frac{d}{dt}} & R_1 + \frac{1}{C} \int dt + L_2 \frac{d}{dt} \end{bmatrix} \begin{bmatrix} i \\ i_1 \\ i_2 \end{bmatrix}$$




Q3. 10 points

Use superposition to find V_x below.

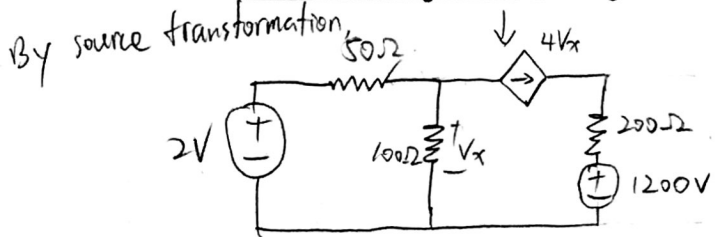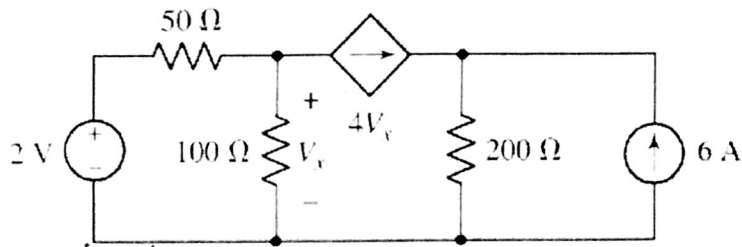

First

Second

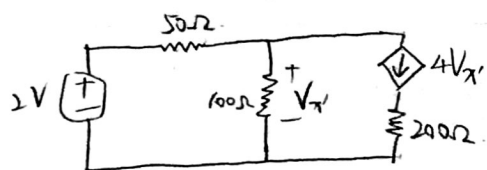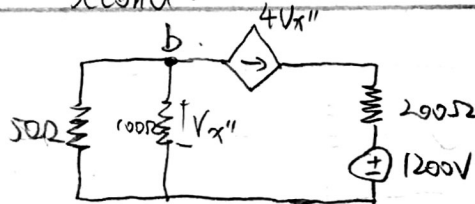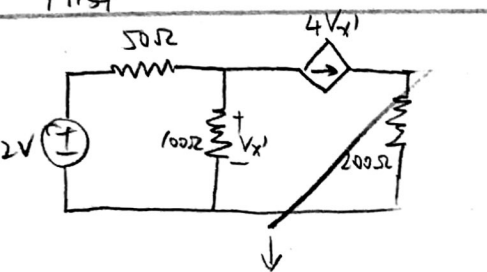

write KCL for b

$$\frac{V_b}{50} + \frac{V_b}{100} + 4V_{x''} = 0$$

since $V_b = V_{x''}$

$$\frac{V_{x''}}{50} + \frac{V_{x''}}{100} + 4V_{x''} = 0$$

$$\frac{3V_{x''}}{100} + \frac{400}{100} V_{x''} = 0$$

$$V_{x''} = 0 \text{ V}$$

Assume $V_o = 0$

write KCL:

$$\frac{V_a}{50} + \frac{V_a}{100} - 0.04 + 4V_x = 0$$

since $V_a = V_{x'}$

$$\frac{V_{x'}}{50} + \frac{V_{x'}}{100} + 4V_{x'} = 0.04$$


$$\frac{3V_{x'}}{100} + \frac{400}{100} V_{x'} = 0.04$$

$$V_{x'} = \frac{4}{403} \text{ V}$$


$$V_x = V_{x'} + V_{x''} = \frac{4}{403} + 0 = \frac{4}{403} \text{ V}$$

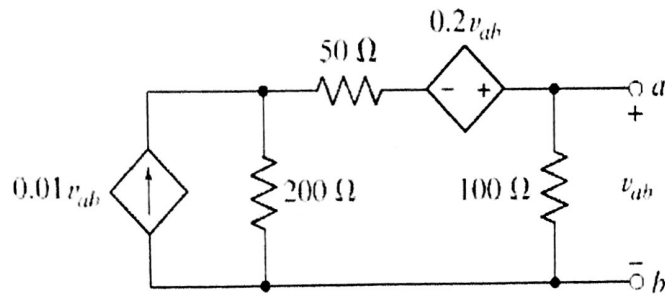Q4. 8 points

Find the Thevenin Equivalent between a and b .



By source transformation,

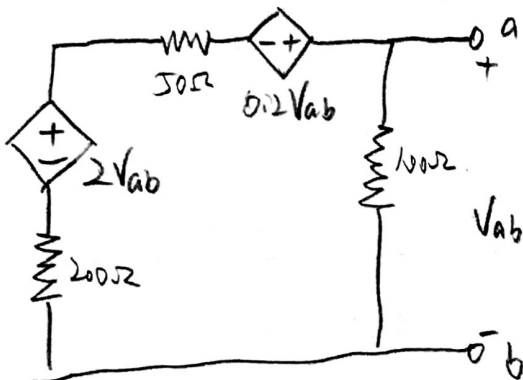


$$V_{ab} = \frac{22}{35} V_{ab}$$

$$V_{ab} = 0 \cdot V = V_T$$


zero out the dependent sources because they are supplying 0 volts.

we have

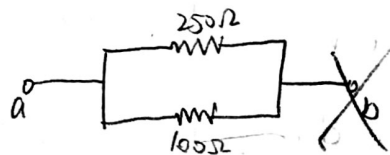

$$R_T = \frac{1}{\frac{1}{100} + \frac{1}{250}} = \frac{500}{7} \Omega$$


then the Thevenin Equivalent circuit is

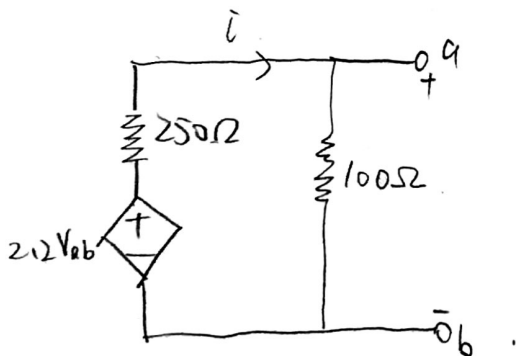

$$2.2V_{ab} - i \cdot 250 - i \cdot 100 = 0$$

$$i = \frac{2.2V_{ab}}{350}$$
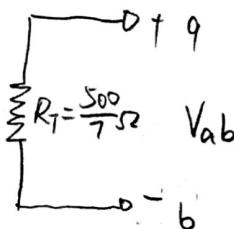
$$V_{ab} = \frac{2.2V_{ab}}{250 + 100} \cdot 100$$



$$V_T = 0 \text{ V}$$

$$R_T = \frac{500}{7} \Omega$$