

EE10 Midterm 2

Department of Electrical Engineering, UCLA

Fall 2017

Instructor: Prof. Gupta

1. Exam is closed book. Calculator and one double sided cheat-sheet is allowed.
2. Cross out *everything* that you don't want me to see. Points will be deducted for everything wrong!
3. No points will be given without proper explanations
4. Time allotted: 75 minutes

Name: Robert

Student ID: 30

Student on Left



Student on Right: Alex

Student in Front: Gezer Domingo

Problem	Maximum Score	Your Score
1	6	6
2	6	6
3	10	10
4	8	8
Total	30	30

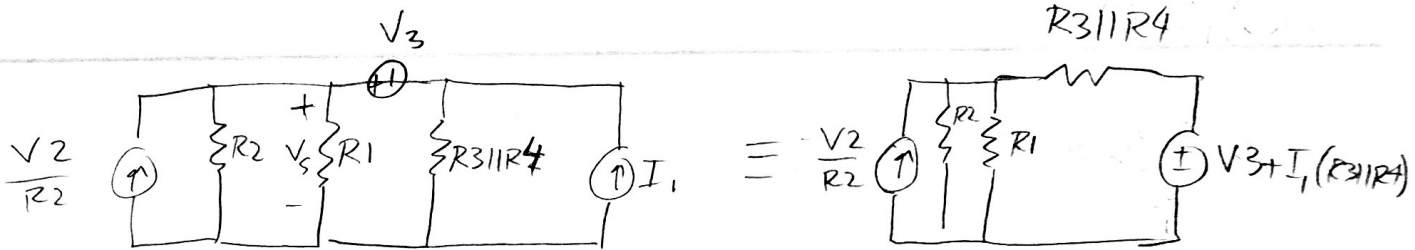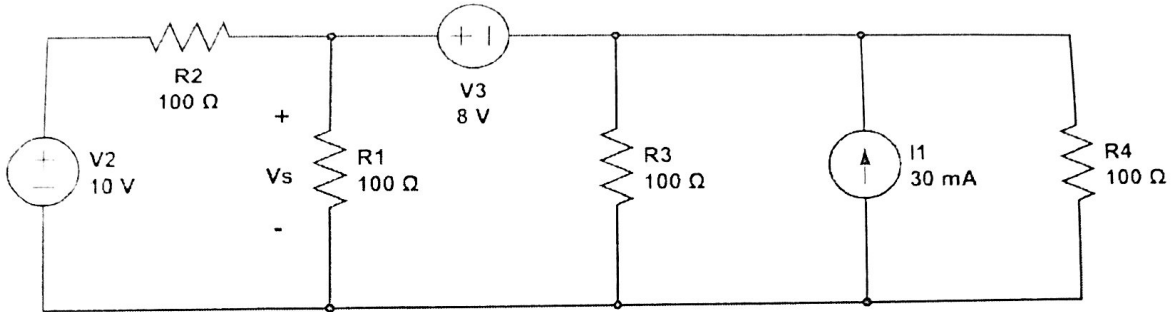Q1. (6 points)

Find V_s by repeating source transformations. Write as few KCL or KVL equations as possible.



$$V_s = R_1 \left(\frac{V_2}{R_2} + \frac{V_3 + I_1(R_3 \parallel R_4)}{R_3 \parallel R_4} \right) \left(\frac{R_2 \parallel (R_3 \parallel R_4)}{R_1 + R_2 \parallel (R_3 \parallel R_4)} \right)$$


$$V_s = 100 \left(\frac{1}{10} + \frac{8 + \frac{3}{100}(50)}{50} \right) \left(\frac{100/3}{400/3} \right)$$

$$V_s = 29 \left(\frac{1}{4} \right) = \frac{29}{4} \text{ V}$$



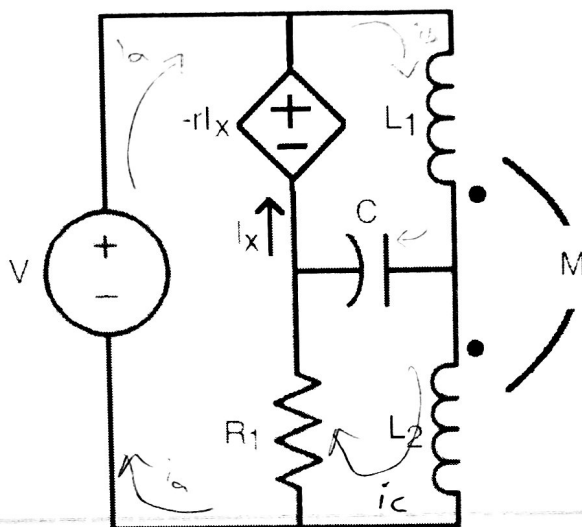Q2. (6 points)

Apply Loop Variable Analysis (Matrix KVL) to the circuit in the figure. The resulting system of equations should be presented in matrix form.



$$I_x = i_b - i_a$$

$$V = -r(i_b - i_a)$$



$$-r(i_b - i_a) = L_1 \frac{di_b}{dt} - i_b - i_c$$

$$\begin{bmatrix} r + R_1 & -r & -R_1 \\ -r & r + L_1 \frac{d}{dt} + \frac{1}{C} \int dt & -M \frac{d}{dt} - \frac{1}{C} \int dt \\ -R_1 & -M \frac{d}{dt} - \frac{1}{C} \int dt & R_1 + L_2 \frac{d}{dt} + \frac{1}{C} \int dt \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} V \\ 0 \\ 0 \end{bmatrix}$$

6

Q3. 10 points

Use superposition to find V_x below.

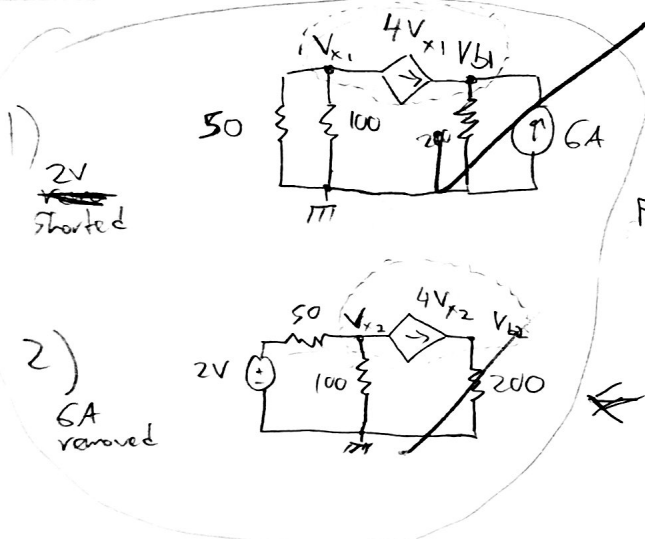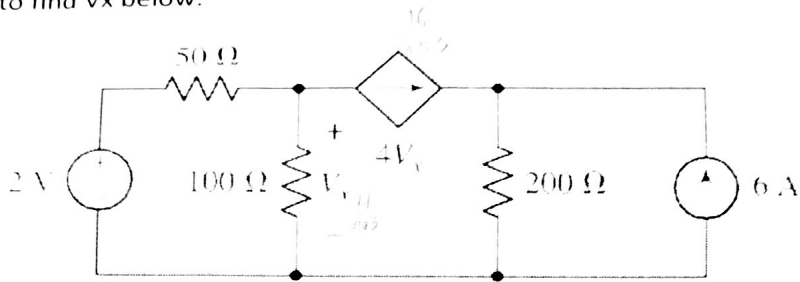

$$V_{x1} = \frac{100}{3} \left(6 - \frac{V_{b1}}{200} \right)$$

$$\frac{V_{x1}}{50} + \frac{V_{x1}}{100} + \frac{V_{b1}}{200} = 6A \quad \leftarrow \text{cutset around dependent source}$$

$$\frac{V_{x2} - 2}{50} + \frac{V_{x2}}{100} + \frac{V_{b2}}{200} = 0$$

$$V_{x2} = \frac{100}{3} \left(\frac{1}{25} - \frac{V_{b2}}{200} \right)$$

$$V_{x1} + V_{x2} = V_x = \frac{100}{3} \left(\frac{1}{25} - \frac{V_{b1}}{200} + 6 - \frac{V_{b2}}{200} \right)$$

$$V_x = \frac{100}{3} \left(\frac{151}{25} - \frac{V_b}{200} \right)$$

from here I proceeded to lower left box. Using that answer, I tested w/ the above equation

$$V_b = \left(\frac{16}{403} + 6 \right) 200 = 1207.94 \sim$$

$$\frac{100}{3} \left(\frac{151}{25} - \frac{1207.94}{200} \right) = \frac{4}{403} V$$

They converge.

1) $\frac{V_{x1}}{50} + \frac{V_{x1}}{100} + 4V_{x1} = 0 \quad V_{x1} \checkmark$




2) $\frac{V_{x2} - 2}{50} + \frac{V_{x2}}{100} + 4V_{x2} = 0$

$$V_{x2} = \frac{1}{25} \left(\frac{100}{403} \right) = \frac{4}{403} V$$

$V_x = \frac{4}{403} V$

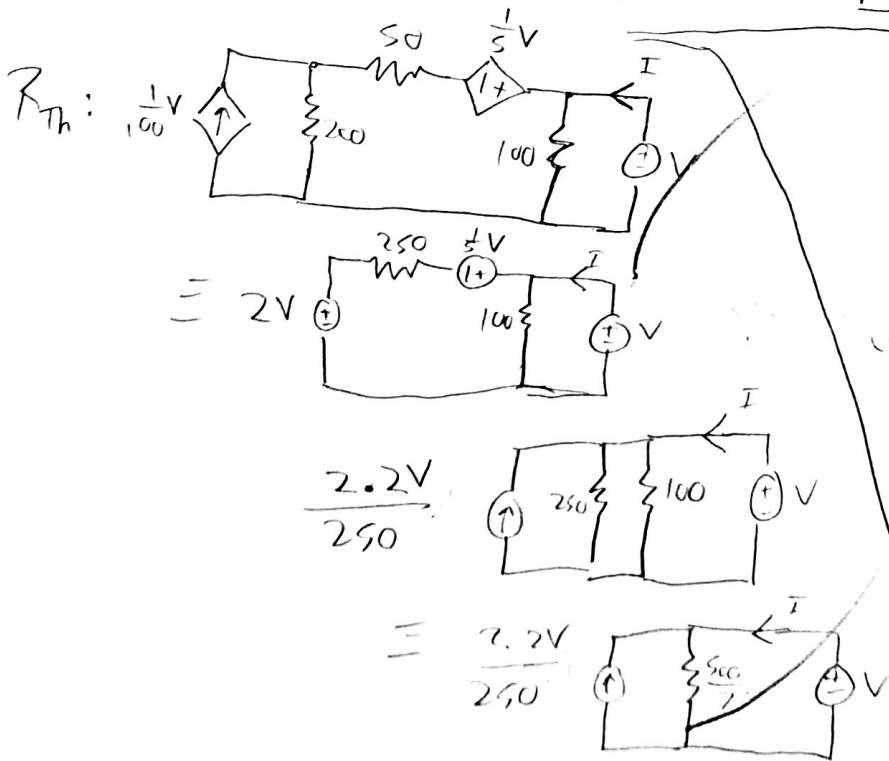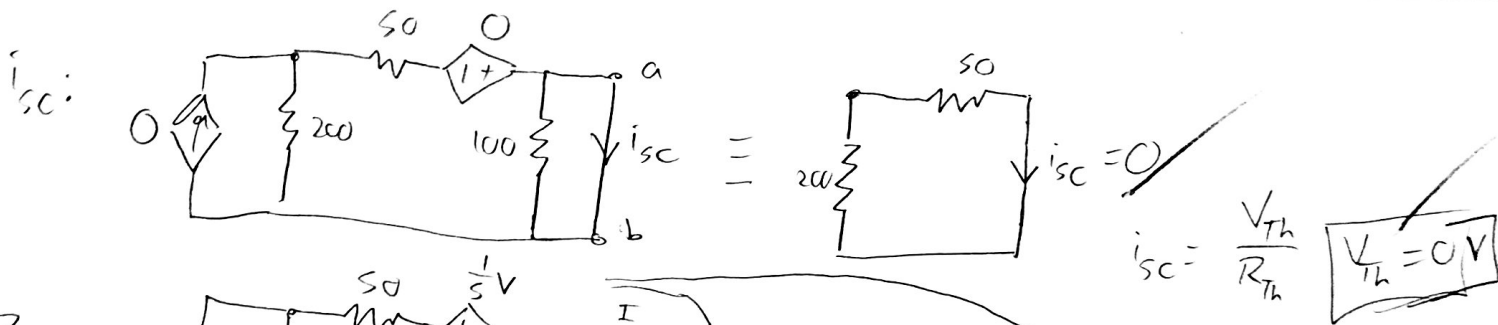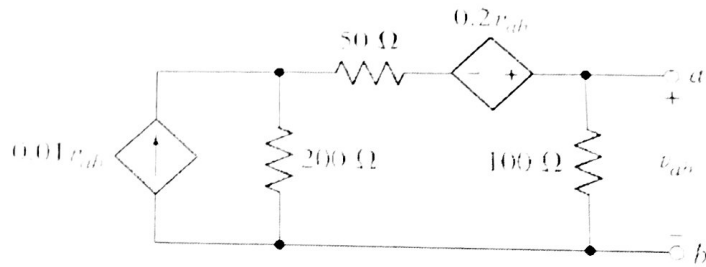Q4. 8 points

Find the Thevenin Equivalent between a and b .



$$V = \frac{500}{7} \left(I + \frac{2.2V}{250} \right)$$

$$V = \frac{500}{7} I + \frac{22}{35} V$$

$$V = \frac{2500}{13} I \quad \text{R}_{TH} = \frac{2500}{13} \Omega$$

