

EE10 Midterm 2

Department of Electrical Engineering, UCLA

Winter 2016

Instructor: Prof. Gupta

1. Exam is closed book. Calculator and one double sided cheat-sheet is allowed.
2. Cross out *everything* that you don't want me to see. Points will be deducted for everything wrong!
3. No points will be given without proper explanations
4. Time allotted: 75 minutes

Name:

Student ID:

Student on Left:

Student on Right:

Student in Front:


Problem	Maximum Score	Your Score
1	10	2
2	10	5
3	10	10
Total	30	17




**Q1. 10 points (5+5)**

Find the Thevenin equivalent circuit of each network at terminals x-y/A-B.

(a)

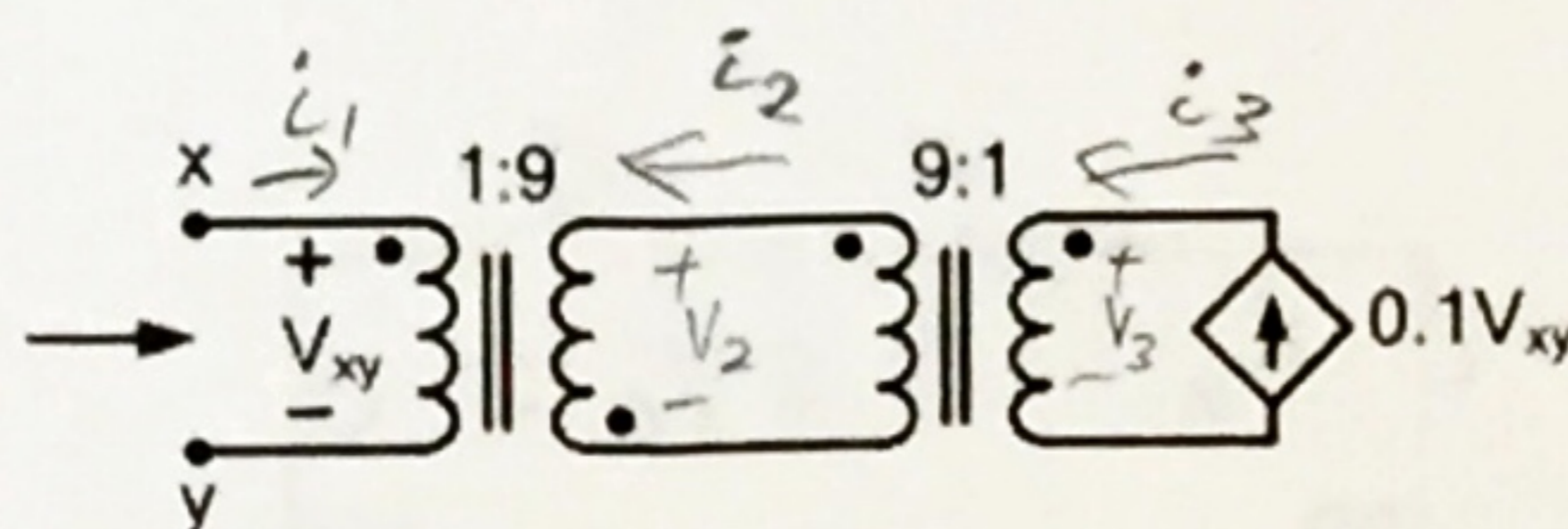

(b)

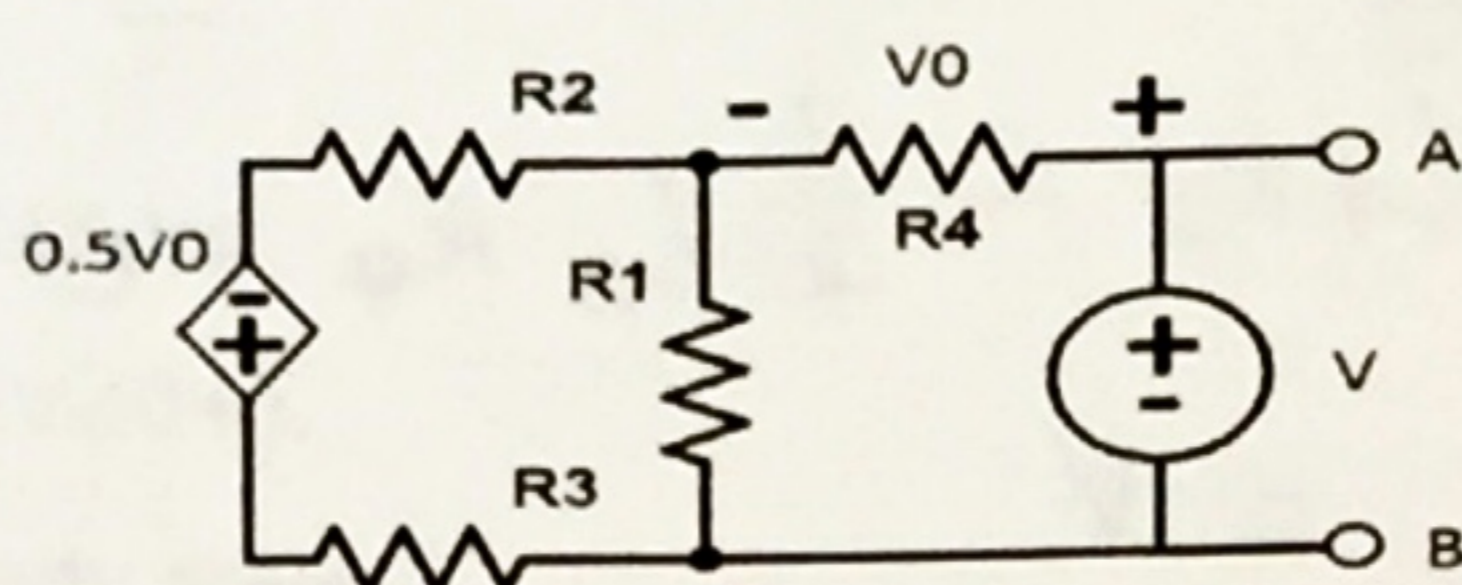

$$a) \quad i_2 = \frac{1}{n} i_1 \quad V_2 = -n V_{xy} \rightarrow i_2 = \frac{1}{9} i_1 \quad V_2 = -9 V_{xy}$$

$$-i_3 = -\frac{1}{n} i_2 \quad V_3 = n V_2 \rightarrow i_3 = 9 i_2 \quad V_3 = \frac{1}{9} V_2$$

$$i_3 = 0.1 V_{xy}$$

$$V_3 = \frac{1}{9} V_2$$


$$0.1 V_{xy} = 9 i_2 = 9 \left( \frac{1}{9} i_1 \right)$$

$$V_3 = -V_{xy}$$


$$0.1 V_{xy} = i_1$$

$$\frac{V_{xy}}{i_1} = 10 \Omega$$

$$R_{TH} = 10 \Omega$$

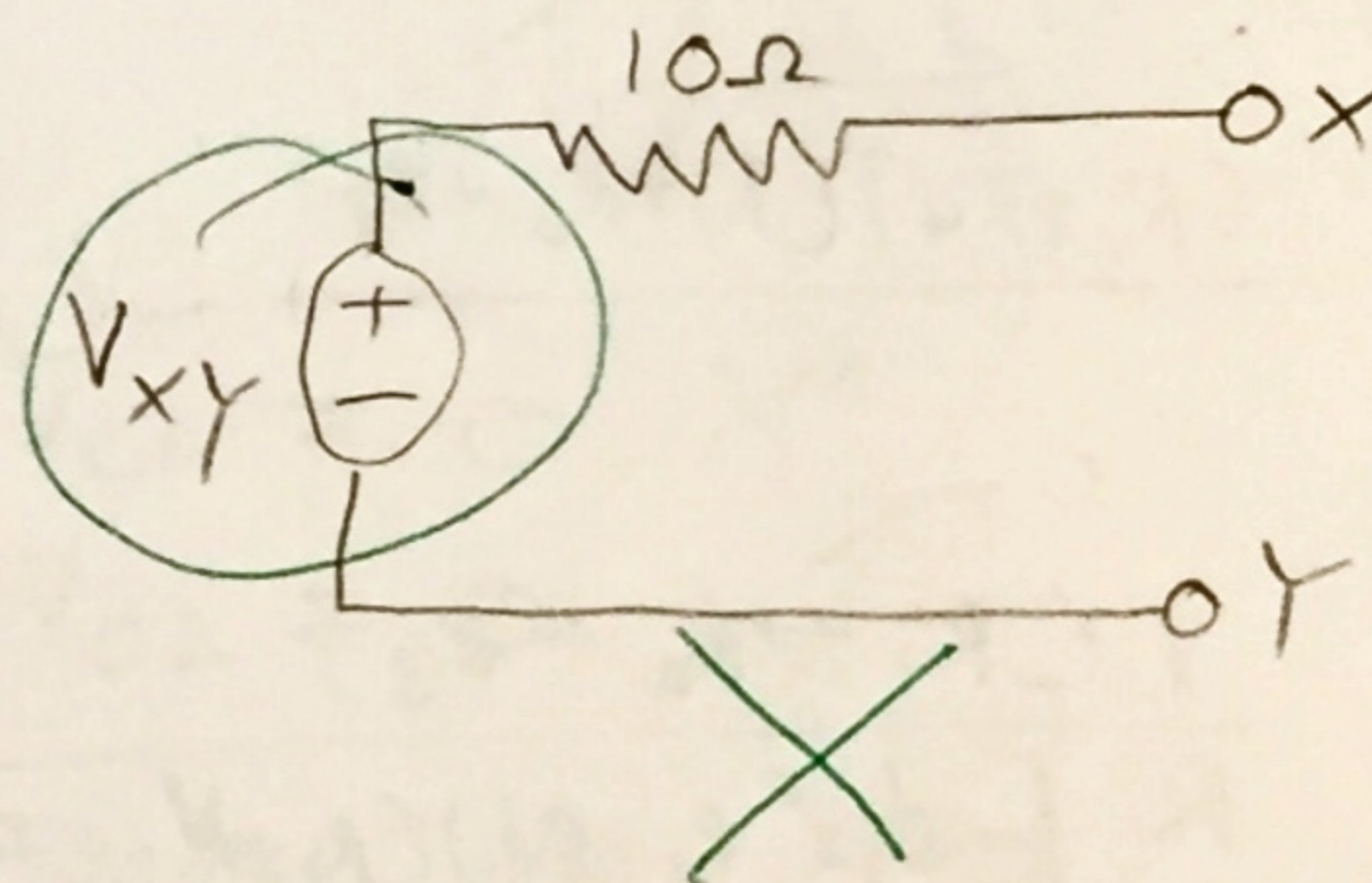



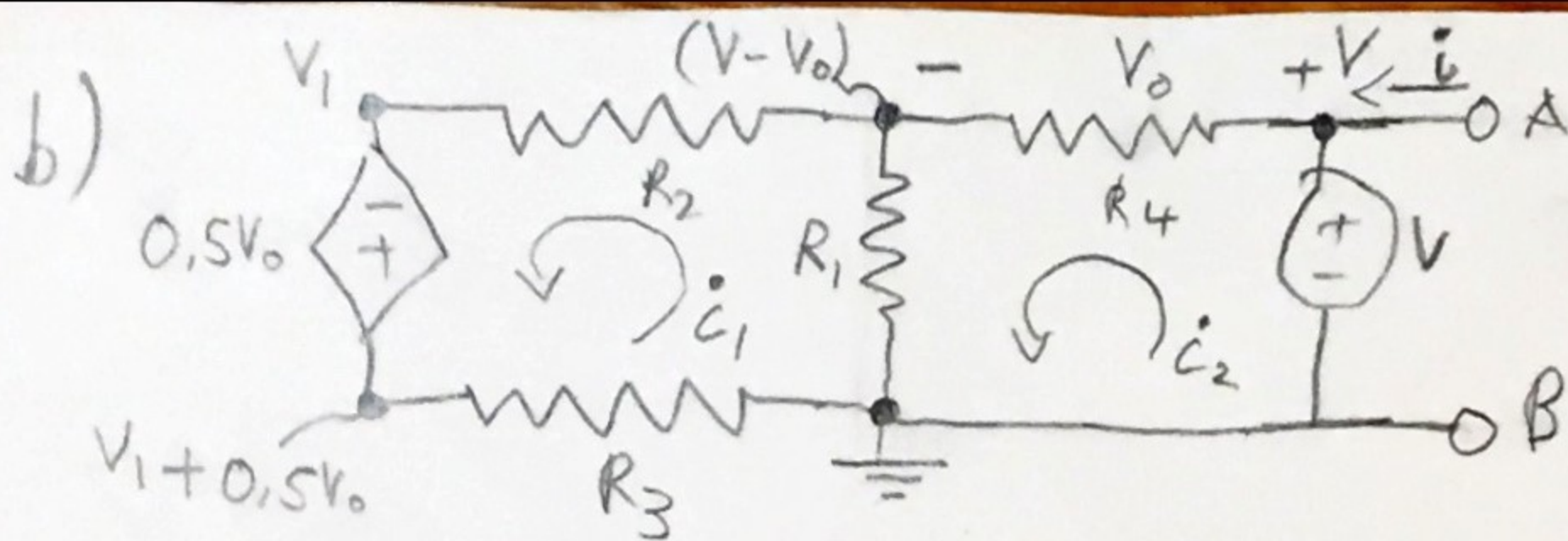

$$V_{OC} = V \checkmark$$

$$\textcircled{1} \dot{i}_1 R_3 + (\dot{i}_1 - \dot{i}_2) R_1 + \dot{i}_1 R_2 - 0.5V_0 = 0$$

$$V_0 = \dot{i}_2 R_4$$

$$\textcircled{2} -V + \dot{i}_2 R_4 + (\dot{i}_2 - \dot{i}_1) R_1 = 0$$

$$\textcircled{1} \dot{i}_1 R_3 + \dot{i}_1 R_1 - \dot{i}_2 R_1 + \dot{i}_1 R_2 - \frac{1}{2} \dot{i}_2 R_4 = 0$$

$$\textcircled{2} \dot{i}_2 R_4 + \dot{i}_2 R_1 - \dot{i}_1 R_1 = V$$

$$\textcircled{1} \dot{i}_1 (R_1 + R_2 + R_3) - \dot{i}_2 (R_1 + \frac{1}{2} R_4) = 0$$

$$\textcircled{2} -\dot{i}_1 R_1 + \dot{i}_2 (R_1 + R_4) = V$$

$$\dot{i}_1 = -\frac{V - \dot{i}_2 (R_1 + R_4)}{R_1} = \frac{\dot{i}_2 (R_1 + R_4)}{R_1} - \frac{V}{R_1}$$


$$\textcircled{1} \left[ \frac{\dot{i}_2 (R_1 + R_4)}{R_1} - \frac{V}{R_1} \right] (R_1 + R_2 + R_3) - \dot{i}_2 (R_1 + \frac{1}{2} R_4) = 0$$

$$\dot{i}_2 \left[ \frac{(R_1 + R_4)(R_1 + R_2 + R_3)}{R_1} - (R_1 + \frac{1}{2} R_4) \right] = \frac{V(R_1 + R_2 + R_3)}{R_1}$$

$$\dot{i}_2 = \frac{V(R_1 + R_2 + R_3)}{R_1 \left[ \frac{1}{R_1} (R_1 + R_4)(R_1 + R_2 + R_3) - (R_1 + \frac{1}{2} R_4) \right]}$$

$$\dot{i} = \dot{i}_2$$

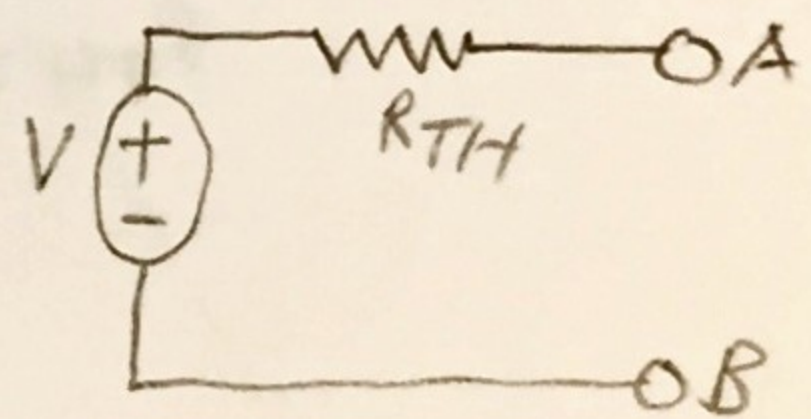
$$R_{TH} = \frac{V_{OC}}{\dot{i}} = \frac{V}{\dot{i}_2} = \frac{R_1 \left[ \frac{1}{R_1} (R_1 + R_4)(R_1 + R_2 + R_3) - (R_1 + \frac{1}{2} R_4) \right]}{(R_1 + R_2 + R_3)} \checkmark$$





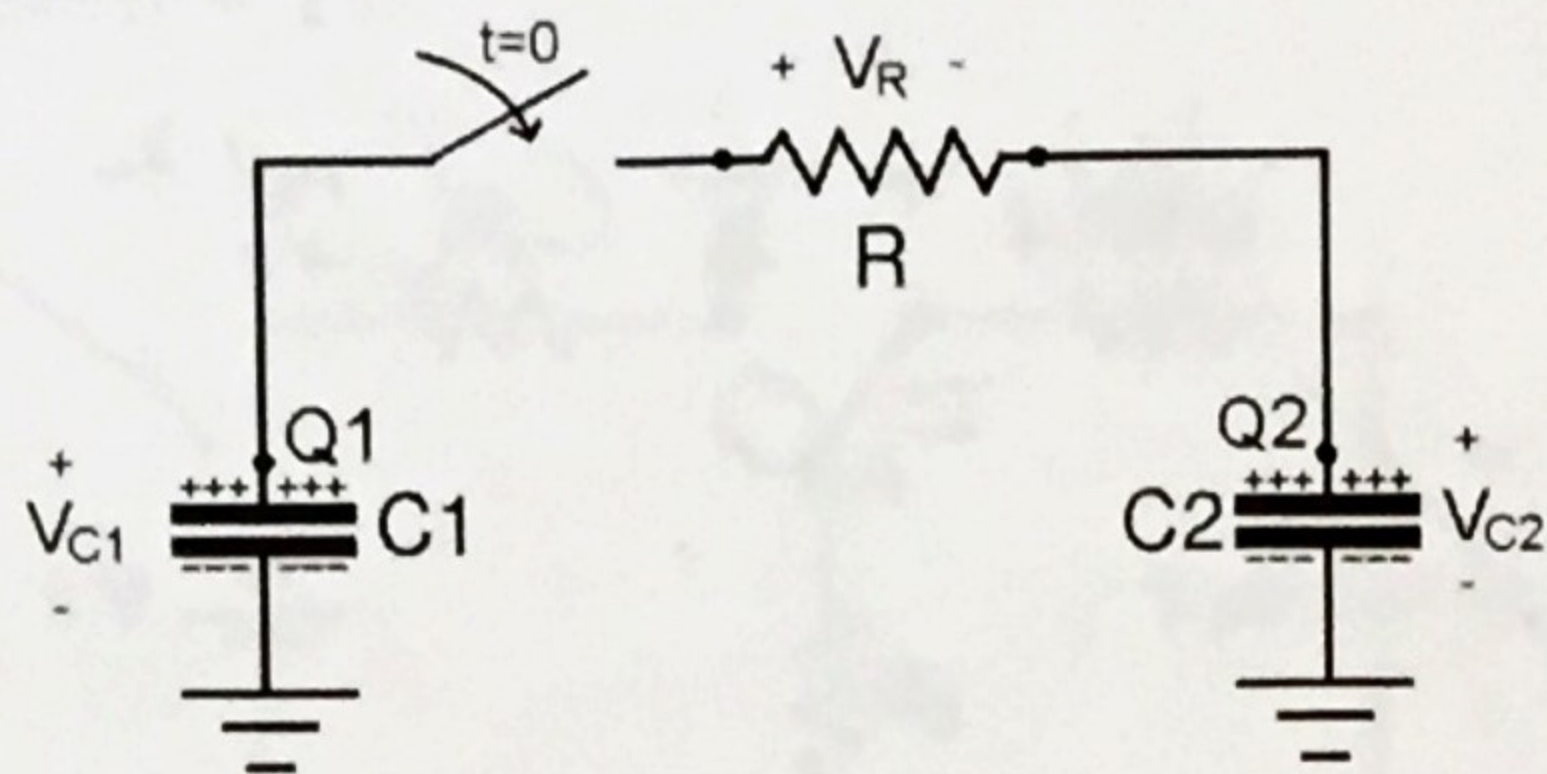**Q2. 10 points**

Capacitors C1 and C2 are initially charged with  $Q_1$  and  $Q_2$  Coulombs respectively. At  $t=0$  the switch closes.




- Find  $V_{C1}(0^-)$ ,  $V_{C2}(0^-)$  and  $V_R(0^-)$ .
- Find  $V_{C1}(0^+)$ ,  $V_{C2}(0^+)$  and  $V_R(0^+)$ .
- Find  $V_{C1}$ ,  $V_{C2}$  and  $V_R$  at steady state.
- For the case where  $Q_1=Q$ ,  $Q_2=0C$  and  $C_1=C_2=C$ . Calculate the total amount of energy dissipated by the resistor after the system reached its steady state.

a)  $V_{C1}(0^-) = \frac{Q_1}{C_1}$  ✓  $V_{C2}(0^-) = \frac{Q_2}{C_2}$  ✓  $V_R(0^-) = 0V$  ✓

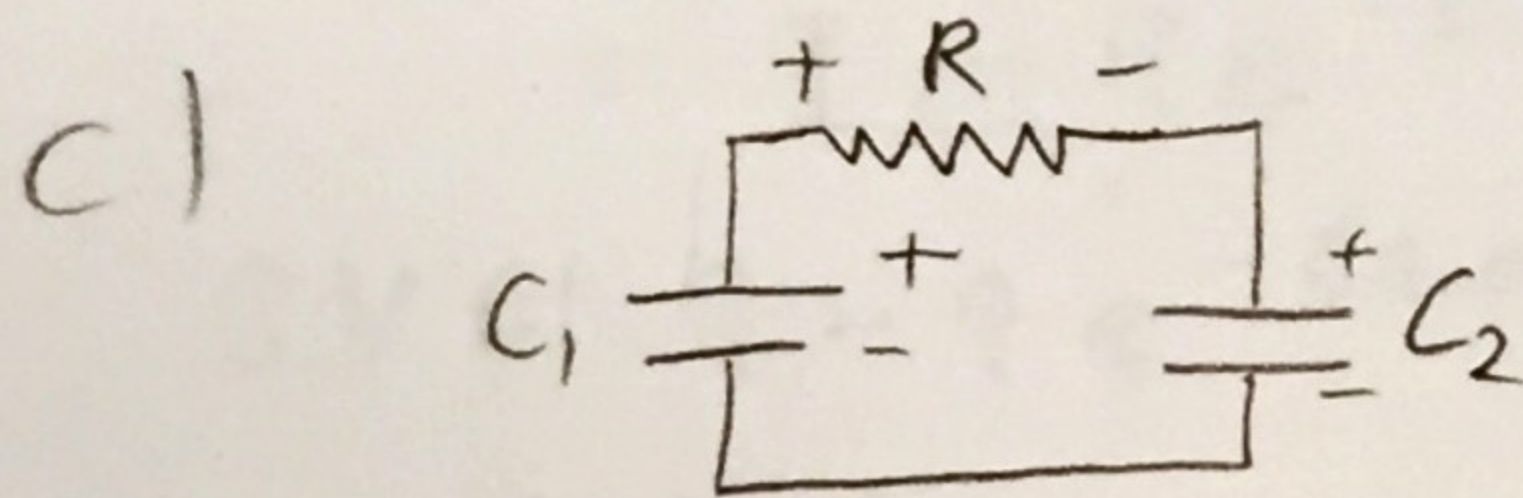b)  $V_{C1}(0^+) = V_{C1}(0^-) = \frac{Q_1}{C_1}$  ✓  
 $V_{C2}(0^+) = V_{C2}(0^-) = \frac{Q_2}{C_2}$  ✓

$V_R(0^+) = V_{C1}(0^+) - V_{C2}(0^+)$   
 $= \frac{Q_1}{C_1} - \frac{Q_2}{C_2}$  ✓



$V_{C1} = 0$  X  
 $V_{C2} = 0$  X

$V_R = V_{C1} - V_{C2} = 0$  ✓



$$d) Q_1 = Q \quad Q_2 = 0 \quad C_1 = C_2 = C$$

$$W_1 = \frac{1}{2} C_1 V_{C1}^2 \checkmark$$

$$W_2 = \frac{1}{2} C_2 V_{C2}^2 \checkmark$$

$$V_{C1} = \frac{Q_1}{C_1} = \frac{Q}{C} \checkmark$$

$$V_{C2} = \frac{Q_2}{C_2} = 0 \checkmark$$

$$W_1 = \frac{1}{2} C \left( \frac{Q}{C} \right)^2$$

$$W_2 = \frac{1}{2} C (0)^2$$

$$= \frac{1}{2} C \frac{Q^2}{C^2}$$

$$= 0$$

$$= \frac{1}{2} \frac{Q^2}{C}$$


$$E_{\text{tot dissipated}} = W_1 + W_2 \quad X$$

$$= \frac{1}{2} \frac{Q^2}{C}$$



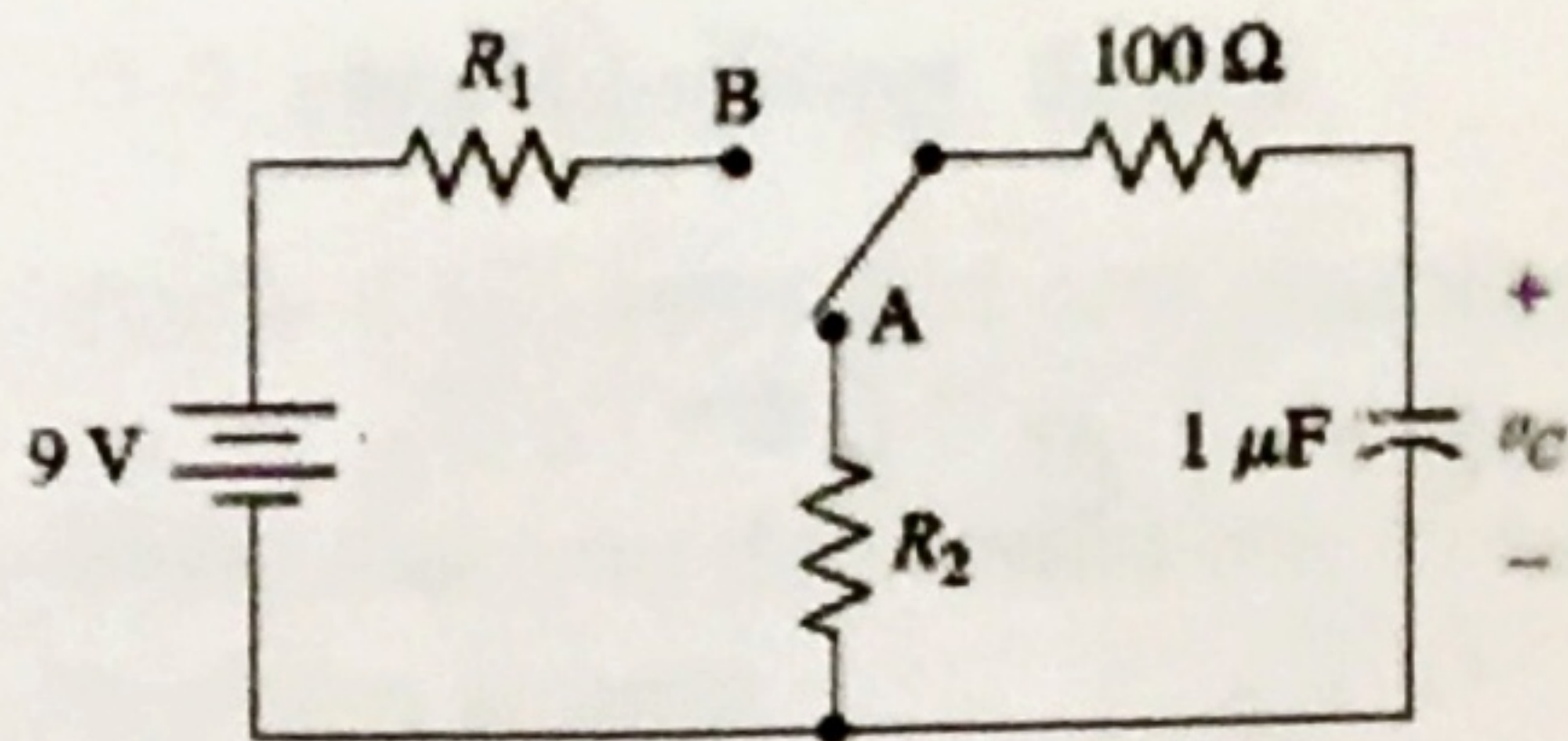**Q3. 10 points**


The switch in the circuit below has been in position A for long time. It is switched to position B at  $t=0$  and back to position A at  $t=1\text{ms}$ . Find  $R_1$  and  $R_2$  such that  $V_c(1\text{ms}) = 8\text{V}$  and  $V_c(2\text{ms}) = 1\text{V}$ .



$t < 0$ :

$$V_c(0^-) = V_c(0^+) = 0\text{V}$$

$0 \leq t \leq 1\text{ms}$ :

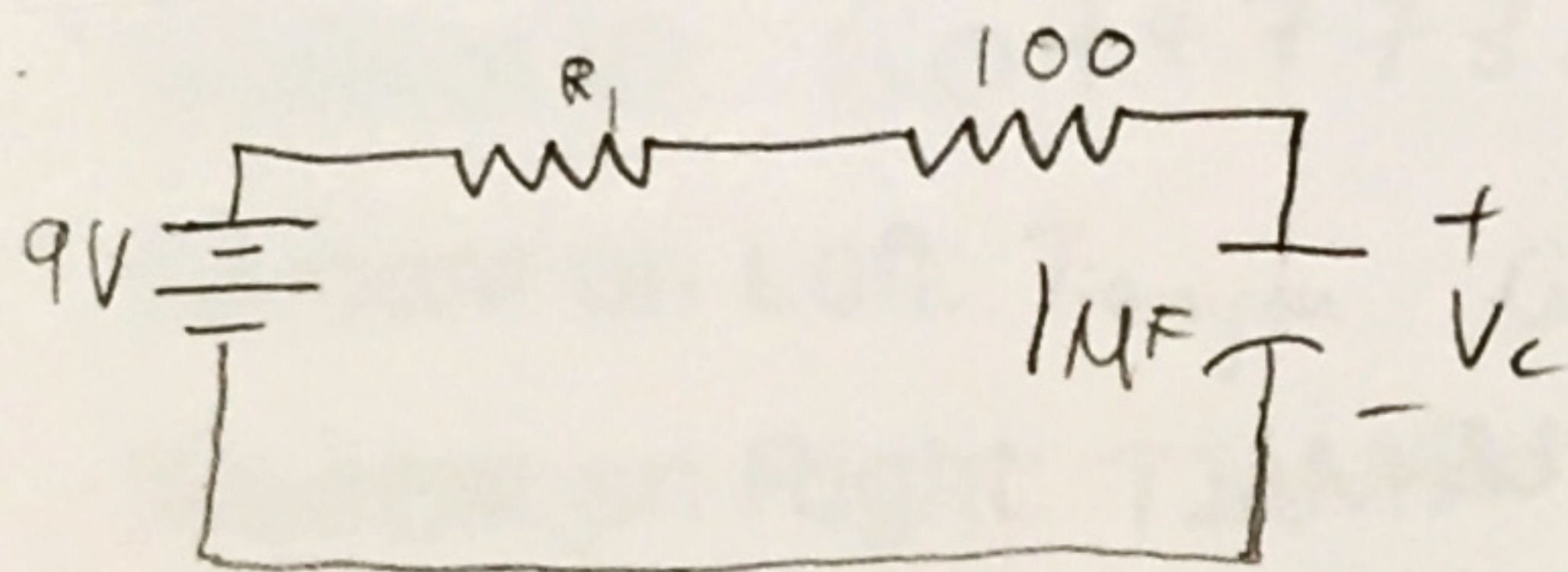

$$\begin{aligned} \tau_1 &= RC \\ &= (R_1 + 100)(1\mu\text{F}) \end{aligned}$$

$$V_c(0) = 0\text{V}$$

$$V_c(\infty) = 9\text{V}$$

$$\begin{aligned} V_c(t) &= 9\text{V} - [9\text{V} - 0]e^{-t/\tau_1} \\ &= 9 - 9e^{-t/\tau_1} \end{aligned}$$

$$8\text{V} = 9 - 9e^{-0.001/\tau_1}$$

$$-\frac{0.001}{\tau_1} = -2 \ln(3)$$


$$\tau_1 \approx 4.55 \times 10^{-4}\text{s}$$

$$(4.55 \times 10^{-4}\text{s}) = (R_1 + 100)(1\mu\text{F})$$

$$\boxed{R_1 \approx 355\Omega}$$



$$1 \leq t \leq \infty:$$

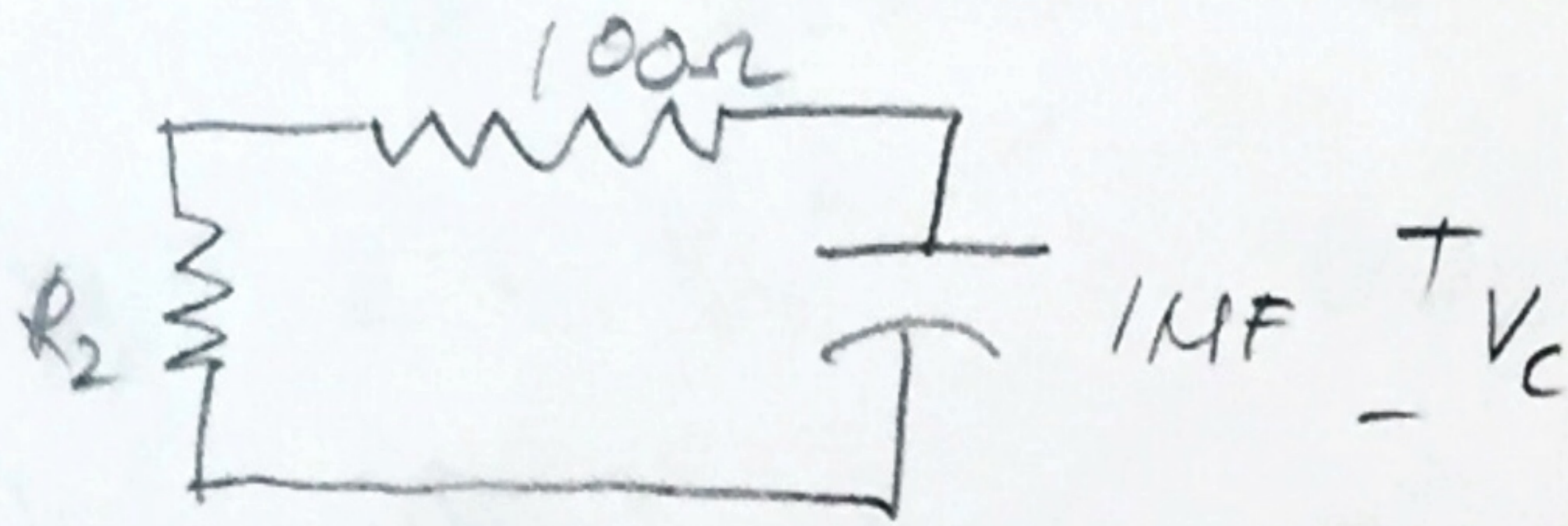

$$V_c(1\text{ms}) = 8\text{V}$$

$$V_c(\infty) = 0\text{V}$$

$$\tau_2 = RC$$

$$= (R_2 + 100)(1\text{MF})$$

$$V_c(t) = 0 - [0 - 8\text{V}] e^{-(t-1)/\tau_2}$$
$$= 8e^{-(t-1)/\tau_2}$$

$$1\text{V} = 8e^{-(2-1)/\tau_2}$$

$$-\frac{(1)}{\tau_2} = \ln \frac{1}{8}$$

$$\tau_2 = -\frac{1}{\ln \frac{1}{8}} \approx 0.481\text{ms}$$

$$\tau_2 = (R_2 + 100)(1\text{MF})$$

$$0.481 \times 10^{-3}\text{s} = (R_2 + 100)(1\text{MF})$$

$$\boxed{R_2 \approx 381\Omega}$$