

EE10 Midterm 2

Department of Electrical Engineering, UCLA

Winter 2016

Instructor: Prof. Gupta


1. Exam is closed book. Calculator and one double sided cheat-sheet is allowed.
2. Cross out *everything* that you don't want me to see. Points will be deducted for everything wrong!
3. No points will be given without proper explanations
4. Time allotted: 75 minutes

	Score	
1	10	10
2	10	10
3	10	10
Total	30	30


Q1. 10 points (5+5)

Find the Thevenin equivalent circuit of each network at terminals x-y/A-B.


(a)

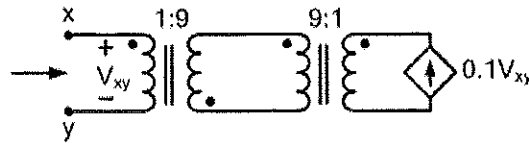

(b)

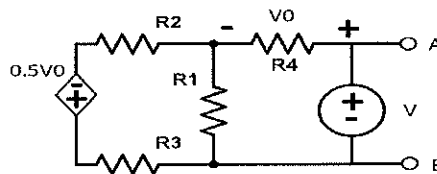

(a) We put a test voltage V_T at x and y

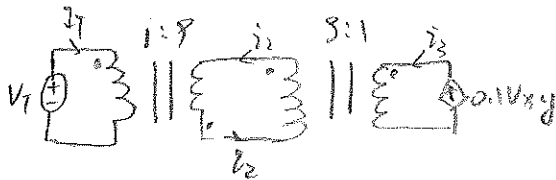


In this case $R_{TH} = \frac{V_T}{I_T}$
 $V_{xy} = V_T$
 $i_2 = \frac{1}{9} I_T$
 $i_3 = 0.1 V_T$
 $i_2 = \frac{1}{9} i_3$
 $I_T = i_3 = 0.1 V_T$

$I_T = 0.1 V_T$
 $R_{TH} = \frac{V_T}{I_T} = \frac{V_T}{0.1 V_T} = 10 \Omega$

Thevenin equivalent:



V_{TH} would be zero because there is no independent source.

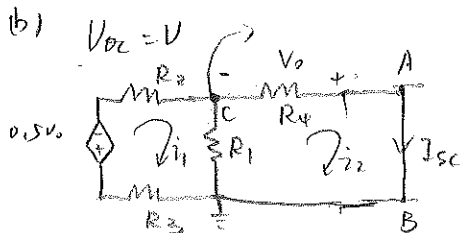

loop 1: $-R_2 i_1 - R_1 i_1 - R_3 i_1 - 0.5 V_0 + i_2 R_1 = 0$

loop 2: $-R_1 i_2 - R_4 i_2 + R_1 i_1 = 0$

$V_0 = -R_4 i_2$

$-i_1 (R_1 + R_2 + R_3) + i_2 (R_1 + \frac{1}{2} R_4) = 0$

$i_1 (R_1 + R_2 + R_3) = i_2 (R_1 + \frac{1}{2} R_4)$

$i_1 = \frac{(R_1 + \frac{1}{2} R_4)}{R_1 + R_2 + R_3} i_2$


loop 2: $-i_2 (R_1 + R_4) + R_1 i_1 = 0$

$[-(R_1 + R_4) + \frac{(R_1 + \frac{1}{2} R_4)}{R_1 + R_2 + R_3} \cdot R_1] i_2 = 0$

$i_2 = 0 = I_{SC}$
 $I_{SC} = \infty$

$V_A = 0 = V_B$
 $i_2 = I_{SC} = 0 \Rightarrow R_{TH} = \frac{V}{I} = \infty$

Thevenin equivalent:

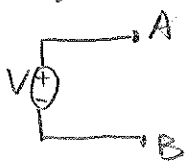

$$Q_{1f} + Q_{2f} = Q_1 + Q_2$$

$$V_{C1(0-)} = \frac{Q_1}{C_1}$$

$$V_{C2(0-)} = \frac{Q_2}{C_2}$$

$$\frac{Q_{1f}}{C_1} = \frac{Q_{2f}}{C_2}$$

$$(Q_1 + Q_2 - Q_{2f}) C_2 = C_1 Q_{2f}$$

$$V_{C2} = \frac{1}{C_2} \cdot \frac{C_2 Q_1 - C_1 Q_2}{C_1 C_2 R} \cdot \frac{C_1 C_2}{C_1 + C_2} \quad (10-1)$$

$$V_{C2} = \frac{C_2 Q_1 - C_1 Q_2}{C_2 (C_1 + C_2)} + \frac{Q_2}{C_2}$$

$$V_{C1} = \frac{-(C_2 Q_1 - C_1 Q_2) + (C_1 + C_2) Q_2}{C_1 (C_1 + C_2)}$$

Q2. 10 points

Capacitors C1 and C2 are initially charged with Q1 and Q2 Coulombs respectively. At t=0 the switch closes.


$$C_1 Q_1 + C_2 Q_2 - C_2 Q_{2f} = C_1 Q_{2f}$$

$$(C_1 + C_2) Q_{2f} = C_2 Q_1 + C_2 Q_2$$

$$Q_{2f} = \frac{C_2 (Q_1 + Q_2)}{C_1 + C_2}$$

$$V_{C2} = \frac{Q_1 + Q_2}{C_1 + C_2}$$

$$V_{C1} = \frac{Q_1 + Q_2}{C_1 + C_2}$$

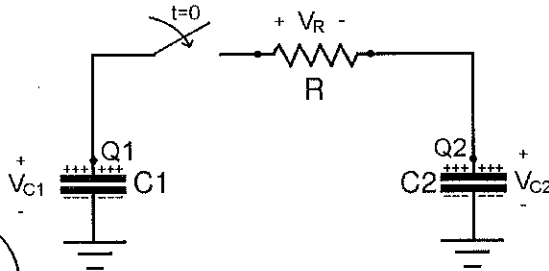

$$\frac{C_2 Q_1 - C_1 Q_2 + Q_2 C_1 + Q_2 C_2}{C_2 (C_1 + C_2)}$$

$$\frac{Q_2 (Q_1 + Q_2)}{C_2 (C_1 + C_2)}$$

$$\frac{Q_1 C_1 + Q_2 C_2 + Q_2 C_1 - Q_2 C_1}{C_1 (C_1 + C_2)}$$

a) Find $V_{C1}(0-)$, $V_{C2}(0-)$ and $V_R(0-)$.

b) Find $V_{C1}(0+)$, $V_{C2}(0+)$ and $V_R(0+)$.

c) Find V_{C1} , V_{C2} and V_R at steady state.

d) For the case where $Q_1=Q$, $Q_2=0C$ and $C_1=C_2=C$. Calculate the total amount of energy dissipated by the resistor after the system reached its steady state.

(a) $Q = CV$. $Q_1 = V_{C1} \cdot C_1$ $Q_2 = C_2 \cdot V_{C2}$

$$V_{C1} = \frac{Q_1}{C_1}$$

$$V_{C2} = \frac{Q_2}{C_2}$$

Since the switch is open, there is no current

$$V_{C1}(0-) = \frac{Q_1}{C_1}$$

$$V_{C2}(0-) = \frac{Q_2}{C_2}$$

$$V_R(0-) = 0$$

$$V_{C2} = \frac{1}{C_2} \int_0^{\infty} i_2 dt + V_{C2}(0+) \text{ at steady state.}$$

$$V_{C1} = V_{C1}(0+) - \frac{1}{C_1} \int_0^{\infty} i_1 dt$$

$$V_{C2} = \frac{C_2 Q_1 - C_1 Q_2}{C_2 (C_1 + C_2)} + \frac{Q_2}{C_2} = \frac{Q_1 + Q_2}{C_1 + C_2}$$

$$V_{C1} = \frac{Q_1}{C_1} + \frac{C_1 Q_2 - C_2 Q_1}{C_1 (C_1 + C_2)} = \frac{Q_1 + Q_2}{C_1 + C_2}$$

(b) Since the voltage across capacitors would not change instantaneously


Instantaneously

$$V_{C1}(0+) = \frac{Q_1}{C_1}$$

$$V_{C2}(0+) = \frac{Q_2}{C_2}$$

$$V_R = V_{C1} - V_{C2}$$
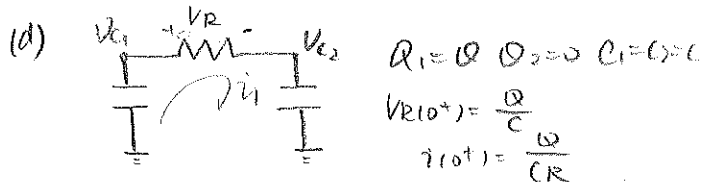
$$V_R(0+) = \frac{Q_1}{C_1} - \frac{Q_2}{C_2}$$



$$Q_1 = Q \quad Q_2 = 0 \quad C_1 = C_2 = C$$

$$V_R(0+) = \frac{Q}{C}$$

$$i(0+) = \frac{Q}{RC}$$

$$-\frac{1}{C} \int_0^t i_1 dt - i_1 \frac{R}{C} - \frac{1}{C} \int_0^t i_2 dt = 0$$

$$+\frac{1}{C} \dot{i}_1 + R \frac{d i_1}{d t} + \frac{1}{C} \dot{i}_2 = 0$$

$$+\frac{2}{C} \dot{i}_1 + R \frac{d i_1}{d t} = 0$$

$$\frac{2}{RC} \dot{i}_1 + \frac{d i_1}{d t} = 0$$


$$i_1 = k \cdot e^{-\frac{2t}{RC}}$$

$$i_1 = \frac{Q}{CR} \cdot e^{-\frac{2t}{RC}}$$

(on the back)

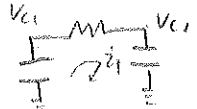(c) at steady state capacitors work as open circuit

no current through the resistor $V_R = 0$



$$\left(\frac{1}{C_1} + \frac{1}{C_2}\right) \dot{i}_1 + R \frac{d i_1}{d t} = 0$$

$$\dot{i}_1 = k \cdot e^{-\frac{(C_1 + C_2)t}{C_1 C_2 R}}$$


$$i_1 = \frac{C_2 Q_1 - C_1 Q_2}{C_1 C_2 R} \cdot e^{-\frac{(C_1 + C_2)t}{C_1 C_2 R}}$$

$$i_1(0+) = \frac{C_2 Q_1 - C_1 Q_2}{C_1 C_2 R} = k$$

(lifetime in top right)

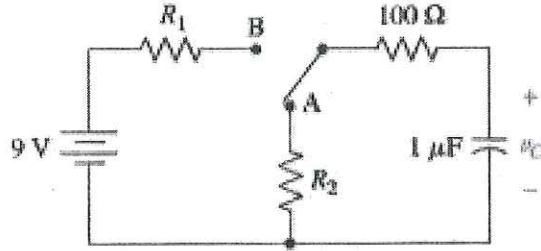Q3. 10 points

The switch in the circuit below has been in position A for long time. It is switched to position B at $t=0$ and back to position A at $t=1\text{ms}$. Find R_1 and R_2 such that $V_c(1\text{ms}) = 8\text{V}$ and $V_c(2\text{ms}) = 1\text{V}$.



$$V_c(2\text{ms}) = 8 \cdot e^{-\frac{(1\text{ms})}{\tau_2}} = 1$$

When $t < 0$
there is no current

$$\frac{1\text{ms}}{\tau_1} = -\ln \frac{1}{8}$$

$$e^{-\frac{(1\text{ms})}{\tau_2}} = \frac{1}{8}$$

$$V_c(0^-) = V_c(0^+) = 0\text{V}$$

$$\tau_1 = \frac{1\text{ms}}{-\ln \frac{1}{8}}$$

$$\frac{-(1\text{ms})}{\tau_2} = \ln \frac{1}{8}$$

Since voltage across capacitor

can't change instantaneously


$$\frac{1\text{ms}}{\tau_2} = -\ln \frac{1}{8}$$

$0 < t < 1$

$$\tau_1 = (R_1 + 100) \times 10^{-6}$$

$$\frac{\tau_2}{1\text{ms}} = \frac{1}{-\ln \frac{1}{8}}$$
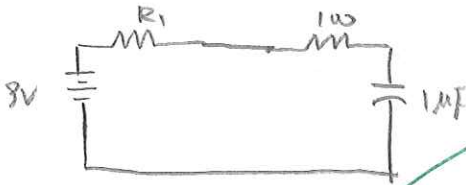
$$\tau_2 = \frac{1 \times 10^{-3}}{-\ln \frac{1}{8}}$$



$$R_1 + 100 = \frac{1 \times 10^{-3} \times 10^6}{-\ln \frac{1}{8}}$$

$$R_1 = 355.125 \Omega$$

$$R_2 + 100 = \frac{1 \times 10^{-3}}{-\ln \frac{1}{8}}$$

$$R_2 = 380.90 \Omega$$

$$R_{eq} = R_1 + 100$$

$$\tau_1 = R_{eq} \cdot C$$

$$V_c = 9(1 - e^{-t/\tau_1})$$

$t > 1$



$$R_{eq} = R_2 + 100$$

$$\tau_2 = R_{eq} \cdot C = (R_2 + 100) \times 10^{-6}$$

$$\begin{cases} R_1 = 355.125 \Omega \\ R_2 = 380.90 \Omega \end{cases}$$

$$V_c(1\text{ms}) = 8 = 9(1 - e^{-\frac{1\text{ms}}{\tau_1}})$$

$$1 - e^{-\frac{1\text{ms}}{\tau_1}} = \frac{8}{9}$$

$$e^{-\frac{1\text{ms}}{\tau_1}} = \frac{1}{9}$$

$$\frac{1\text{ms}}{\tau_1} = \ln \frac{1}{9}$$

$$V_c = k \cdot e^{-\frac{(t-1\text{ms})}{\tau_2}}$$

when $t = 1\text{ms}$

$$V_c = 8\text{V} \quad \text{so } k = 8$$

$$V_c = 8 \cdot e^{-\frac{(t-1\text{ms})}{\tau_2}}$$