



Name: _

UID: _

Total of 3 questions, 100 minutes.

P1 (30)	30
P2 (30)	30
P3 (40)	26
Total (100)	

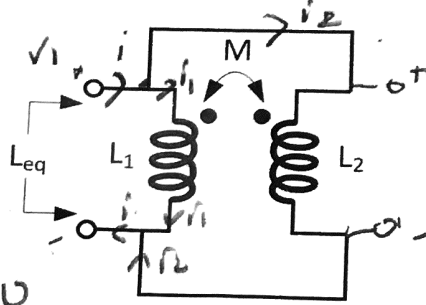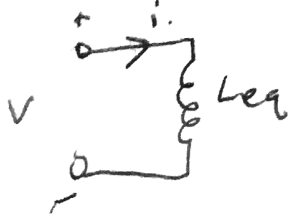1. Find the equivalent inductance of the circuit below. $L_1 = 5H$, $L_2 = 2H$, and $M = 3H$.



M should be added since currents enter inductors through dots.

By KVL $i - V_1 + V_2 = 0$

$V_2 = V_1 = V$ where V is some voltage.

$$V = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$L_2 \left(V = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \right) \Rightarrow L_2 V = L_1 L_2 \frac{di_1}{dt} + M L_2 \frac{di_2}{dt}$$

$$-M \left(V = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \right) \Rightarrow -M V = -M L_2 \frac{di_2}{dt} - M^2 \frac{di_1}{dt}$$

$$(L_2 - M) V = (L_1 L_2 - M^2) \frac{di_1}{dt}$$

$$\frac{di_1}{dt} = \frac{(L_2 - M) V}{L_1 L_2 - M^2}$$

$$-M \left(V = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \right) \Rightarrow -M V = -M L_1 \frac{di_1}{dt} - M^2 \frac{di_2}{dt}$$

$$L_1 \left(V = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \right) \Rightarrow L_1 V = L_1 L_2 \frac{di_2}{dt} + M L_1 \frac{di_1}{dt}$$

$$(L_1 - M) V = (L_1 L_2 - M^2) \frac{di_2}{dt}$$

$$\frac{di_2}{dt} = \frac{(L_1 - M) V}{L_1 L_2 - M^2}$$

By KCL $-i + i_1 + i_2 = 0 \Rightarrow i = i_1 + i_2$

$$\frac{d}{dt} (i = i_1 + i_2)$$

$$\frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$= \frac{(L_1 - M) V}{L_1 L_2 - M^2} + \frac{(L_2 - M) V}{L_1 L_2 - M^2} = \frac{(L_1 + L_2 - 2M) V}{L_1 L_2 - M^2}$$

$$V \propto \frac{1}{2t}$$

$$V \propto L_{eq} \left(\frac{(L_1 + L_2 - 2M) \omega}{L_1 L_2 - M^2} \right)$$

$$L_{eq} \propto \frac{1}{\frac{L_1 + L_2 - 2M}{L_1 L_2 - M^2}}$$

$$L_{eq} \propto \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

$$L_1 = 5H \quad L_2 = 2H \quad \text{and} \quad M = 3H$$


$$L_{eq} \propto \frac{(5H)(2H) - (3H)^2}{5H + 2H - 2(3H)}$$

$$\propto \frac{10H^2 - 9H^2}{7H - 6H} = \frac{1H^2}{1H} \propto 1H$$

$$L_{eq} = 1H$$

+30

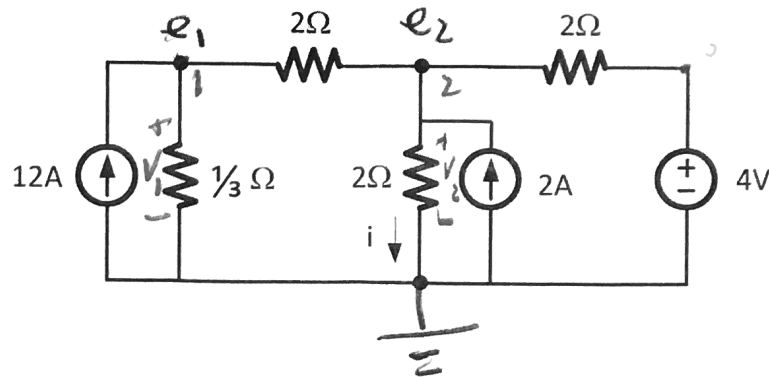2. In the circuit below, using node analysis,
- Find the current i .
 - Find the power dissipated in the $\frac{1}{3}\Omega$ resistor.



9. Node-voltage analysis

$$\text{node 1: } -12A + \frac{e_1 - 0}{1/3\Omega} + \frac{e_1 - e_2}{2\Omega} = 0$$

$$3e_1 + \frac{e_1}{2} - \frac{e_2}{2} = 12$$

$$\frac{7}{2}e_1 - \frac{e_2}{2} = 12$$

$$\text{node 2: } \frac{e_2 - e_1}{2\Omega} + \frac{e_2 - 0}{2\Omega} - 2A + \frac{e_2 - 4}{2\Omega} = 0$$

$$3\frac{e_2}{2} - \frac{e_1}{2} - 2 - 2 = 0$$

$$-\frac{e_1}{2} + 3\frac{e_2}{2} = 4$$

system of equations:

$$3\left(\frac{7}{2}e_1 - \frac{e_2}{2} = 12\right) \Rightarrow$$

$$-\frac{e_1}{2} + 3\frac{e_2}{2} = 4$$


$$\left(\frac{21}{2}e_1 - \frac{3e_2}{2} = 36\right)$$

$$+ \left(-\frac{e_1}{2} + 3\frac{e_2}{2} = 4\right)$$

$$\frac{20}{2}e_1 = 40 \quad 10e_1 = 40$$


$$e_1 = 4V$$

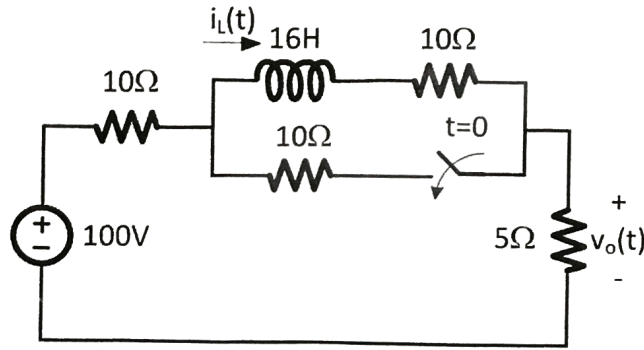3. The circuit below has been idle for a long time (switch is open). At $t = 0$, the switch is closed.
- Find the inductor current right before and after the switch is closed ($i_L(0^-)$, and $i_L(0^+)$).
 - Find v_o right before and after the switch is closed ($v_o(0^-)$, and $v_o(0^+)$).
 - Find and plot $v_o(t)$.



a. If circuit is idle for long time by $t=0^-$, then inductor acts as a short at $t=0^-$.

Equivalent circuit at $t=0^-$

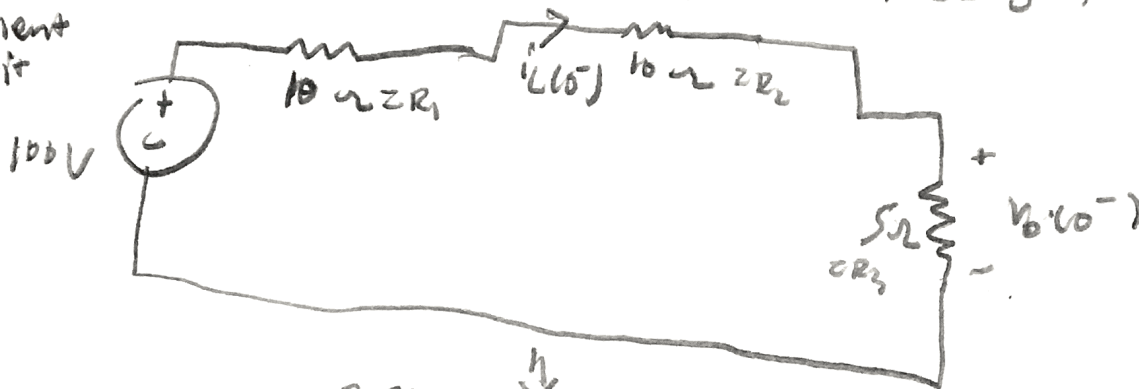

By KVL, voltage across the resistor is 100V

$$R_{eq} = R_1 + R_2 + R_3 = 10\Omega + 10\Omega + 5\Omega = 25\Omega$$

$$i_L(0^-) = \frac{100V}{25\Omega} = \frac{100V}{25\Omega} = 4A$$

$$i_L(0^-) = 4A \quad \text{f1}$$

At $t=0^+$, an infinite voltage can be applied to the inductor as the voltage supply is only 100V, so


$$i_L(0^+) = i_L(0^-)$$

$$i_L(0^+) = 4A \quad \text{f2}$$

b. Look at equivalent circuit at $t=0^-$, since $i_L(0^-) = 0$

$$v_o(0^-) = i_L(0^-) R_3 = (4A)(5\Omega) = 20V \quad \text{f2}$$

Equivalent circuit at $t=0^+$

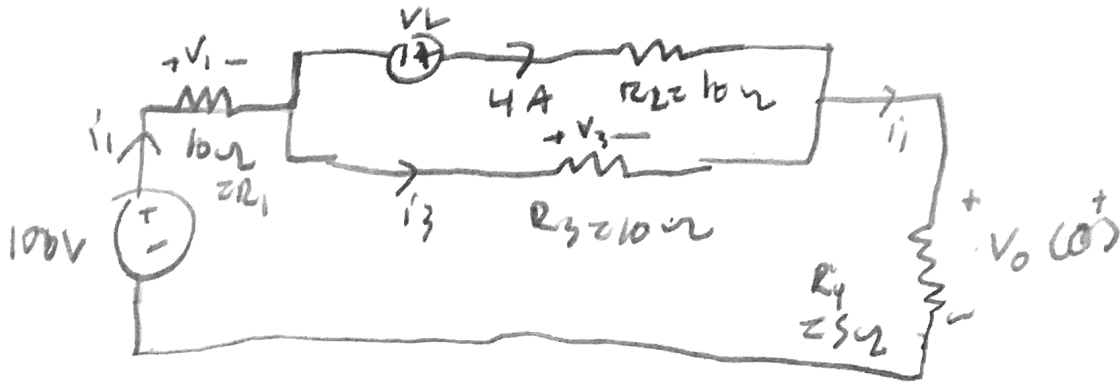

By KCL: $-i_1 + i_3 + 4A = 0 \Rightarrow i_2 = i_3 + 4A$

By KVL: $-100V + v_1 + v_3 + v_0(t) = 0$

$v_1 + v_3 + v_0(t) = 100V$

$i_1 R_1 + i_3 R_3 + i_1 R_4 = 100V$

$(i_3 + 4) R_1 + i_3 R_3 + (i_3 + 4) R_4 = 100$

$i_3 (R_1 + R_3 + R_4) = 100 + 4R_1 - 4R_4$

$i_3 = \frac{100 - 4R_1 - 4R_4}{R_1 + R_3 + R_4} = \frac{100 - 4(10\Omega) - 4(5\Omega)}{10\Omega + 10\Omega + 5\Omega} A$


$= \frac{100 - 60}{25} A = \frac{40}{25} A = \frac{8}{5} A$

$v_0(t) = i_1 R_4 = (i_3 + 4) R_4 = (\frac{8}{5} A + 4A)(5\Omega)$

$= 28V$ $v_0(t) = 28V$

+5

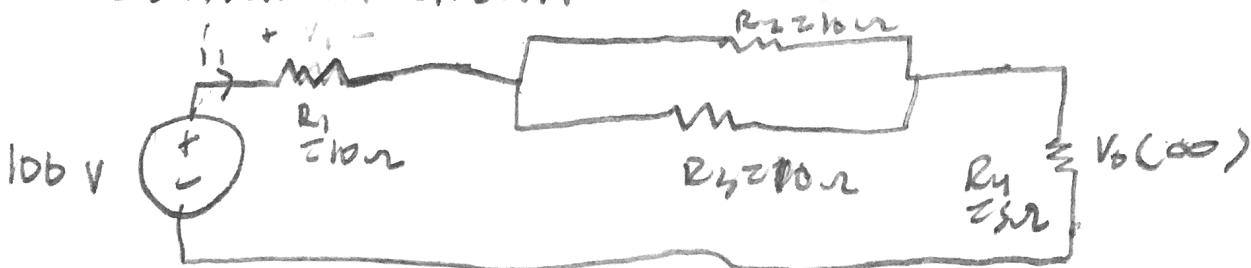c. at $t \rightarrow \infty$, inductor acts as short circuit
Equivalent circuit at $t \rightarrow \infty$



Equivalent to



$R_{eq} = R_1 + R_2 // R_3 + R_4$

$= R_1 + \frac{R_2 R_3}{R_2 + R_3} + R_4 =$

$= (10\Omega) + \frac{(10\Omega)(10\Omega)}{10\Omega + 10\Omega} + 5\Omega$

$= 10\Omega + 5\Omega + 5\Omega = 20\Omega$

By KVL voltage across $R_{eq} = 100V$

$$i_1 = \frac{100V}{R_{eq}} = \frac{100V}{20\Omega} = 5A$$

$$V_0(\infty) = i_1 R_4 = (5A)(9\Omega) = 25V + 5$$

Since this is a DC circuit! for $t < 0$; $V_0(t) = V_0(0^-) = 20V$
for $t \geq 0$; $V_0(t) = V_0(\infty) + (V_0(0^+) - V_0(\infty))e^{-\frac{t}{\tau}}$


In this case $\tau = \frac{L}{R_{eq}(t)}$ Note! $R_{eq}(t) = R_{eq}(\infty) = 20\Omega$ recall

$$\tau = \frac{16H}{20\Omega} = 0.8 \text{ s}$$

$$\begin{aligned} \text{So } V_0(t) &= 25V + (28V - 25V)e^{-\frac{t}{0.8}} \\ &= 25V + 3Ve^{-1.25t} \text{ for } t \geq 0 \end{aligned}$$

So
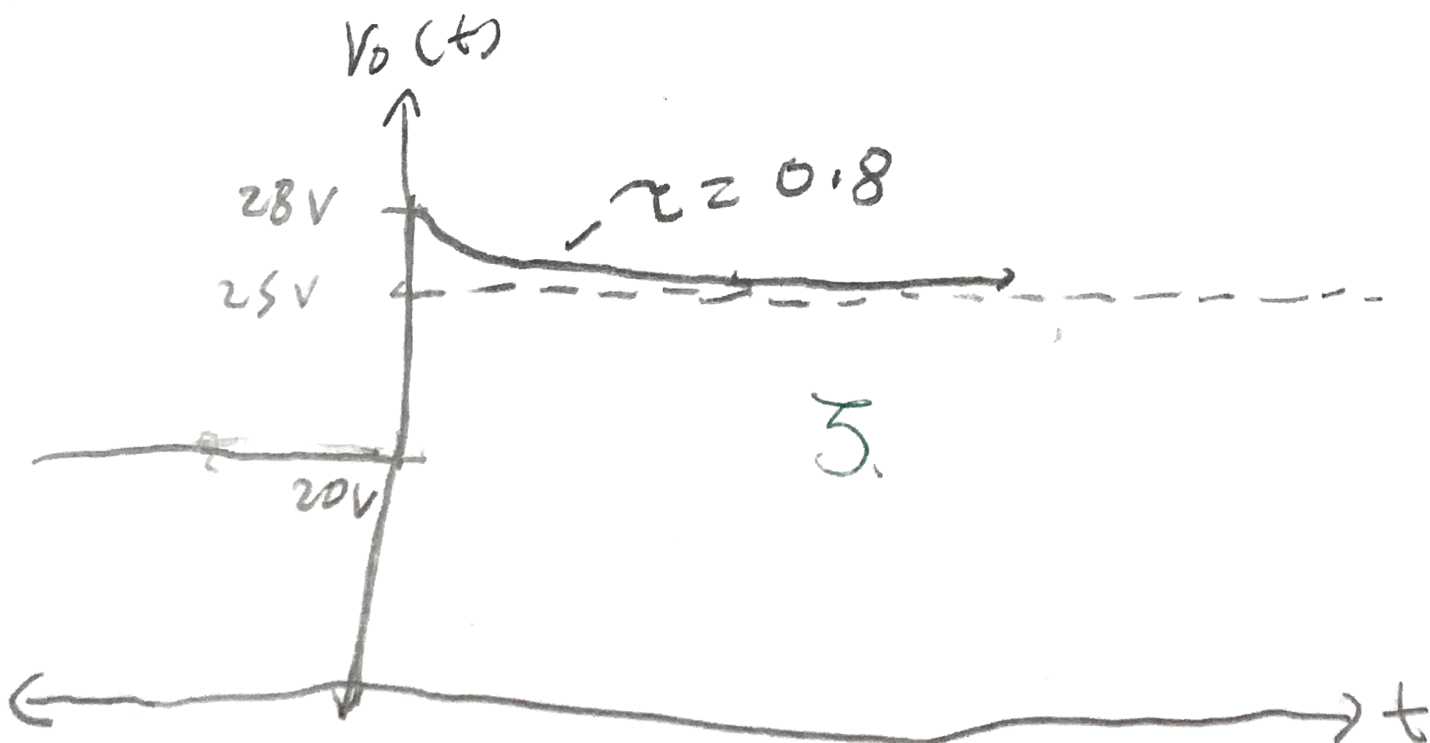
$$V_0(t) = \begin{cases} 20V & \text{for } t < 0 \\ 25V + 3Ve^{-1.25t} & \text{for } t \geq 0 \end{cases}$$



$$\frac{7}{2}(4V) - \frac{e_2}{2} = 12V$$

$$14V - \frac{e_2}{2} = 12V$$

$$-\frac{e_2}{2} = -2V \quad e_2 = 4V$$

$$i = \frac{v_2}{2\Omega} = \frac{e_2 - 0}{2\Omega} = \frac{4V - 0}{2\Omega} = 2A$$

$$\boxed{i = 2A}$$

b. $P_{233} = \frac{(v_1)^2}{1/3\Omega} = \frac{(e_1 - 0)^2}{1/3\Omega} = \frac{(4V - 0)^2}{1/3\Omega}$

$$= \frac{16V^2}{1/3\Omega} = 48W$$

$$\boxed{P_{233} = 48W}$$

t30