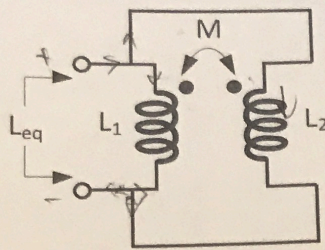



1. Find the equivalent inductance of the circuit below. $L_1 = 5H$, $L_2 = 2H$, and $M = 3H$.



$$L_{eq} = \frac{V_{ab}}{\frac{di_1}{dt}}$$


$$V = L \frac{di}{dt}$$

Inductors are in parallel

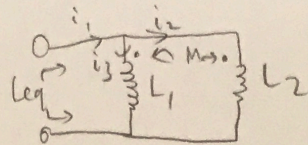

$$V_{ab} = M \frac{di_2}{dt} + L_1 \frac{di_3}{dt}$$
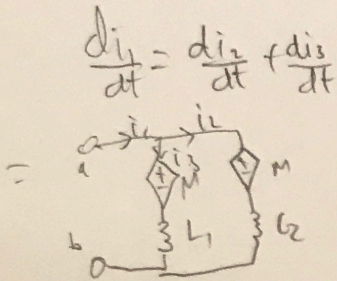
$$V_{ab} = \frac{M di_3}{dt} + \frac{L_2 di_2}{dt}$$



$$\frac{di_1}{dt} = \frac{di_2}{dt} + \frac{di_3}{dt}$$

$$V_{ab} = M \left(\frac{di_1}{dt} \right) \left(\frac{M-L_1}{M-L_2} \right) \left(\frac{M-L_2}{M-L_2+M-L_1} \right) + L_1 \left(\frac{di_1}{dt} \right) \left(\frac{M-L_2}{M-L_2+M-L_1} \right)$$

$$\frac{di_2}{dt} (M-L_2) = \frac{di_3}{dt} (M-L_1)$$

$$\frac{di_2}{dt} = \frac{di_3}{dt} \left(\frac{M-L_1}{M-L_2} \right)$$

$$V_{ab} = \frac{di_1}{dt} \left(M \left(\frac{M-L_1}{2M-L_2-L_1} \right) + L_1 \left(\frac{M-L_2}{2M-L_2-L_1} \right) \right)$$

$$\frac{di_1}{dt} = \frac{di_3}{dt} \left(1 + \frac{M-L_1}{M-L_2} \right)$$

$$L_{eq} = \frac{V_{ab}}{\frac{di_1}{dt}} = \frac{M^2 - L_1 M}{2M - L_2 - L_1} + \frac{L_1 M - L_1 L_2}{2M - L_2 - L_1}$$

$$\frac{di_1}{dt} = \frac{di_2}{dt} \left(\frac{M-L_2}{M-L_1} \right) \left(1 + \frac{M-L_1}{M-L_2} \right)$$

$$= \frac{M^2 - L_1 L_2}{2M - L_2 - L_1}$$

$$M=3H, L_1=5H, L_2=2H$$

$$\frac{9-10}{6-5-2} = \frac{-1}{-1} = 1$$

$$\begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}$$


$$= \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

$$\boxed{L_{eq} = 1H}$$

$$\frac{10-9}{7-6} = \frac{1}{1} \checkmark$$

f30

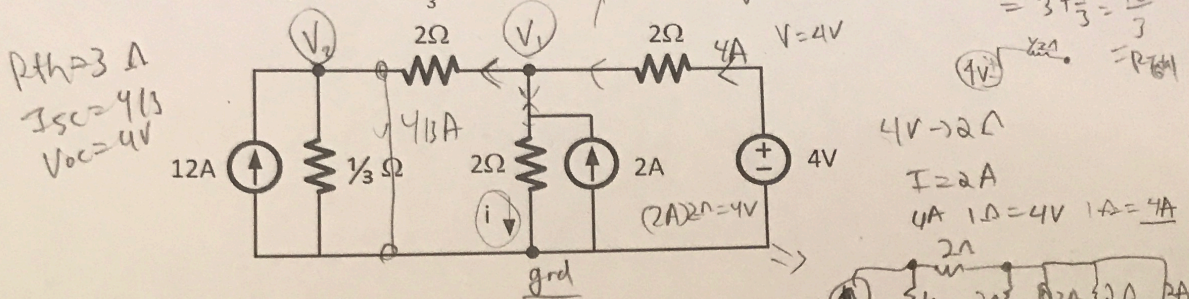2. In the circuit below, using node analysis, $V_1 = \frac{8}{3}$
- Find the current i .
 - Find the power dissipated in the $\frac{1}{3}\Omega$ resistor.



a) $(V_1): \frac{V_1 - V_2}{2} + \frac{V_1 - 4}{2} - 2 + \frac{V_1}{2} = 0$

$(V_2): \frac{V_2 - V_1}{2} - 12 + \frac{V_2}{1/3} = 0$

$V_1 - V_2 + V_1 - 4 + V_1 = 4$

$3V_1 - V_2 = 8$

$\frac{100}{3} = V$

$P_{th} = \frac{10}{3}$

$\frac{V_1}{2} + V_1 = 2$

$\frac{V_2 - V_1}{2} - 12 + 3V_2 = 0$

$V_2 - V_1 - 24 + 6V_2 = 0$

$7V_2 = V_1 + 24$

$V_1 = 7V_2 - 24$

$3(7V_2 - 24) - V_2 = 8$

$21V_2 - 72 - V_2 = 8$

$20V_2 = 80$


$V_2 = 4V$

$V_1 = (4)7 - 24$

$V_1 = 4V$

Find $R_{th} = 3\Omega$
 $I_{sc} = 4/3A$
 $V_{oc} = 4V$


from LHS

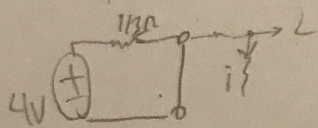

$I = 2A$

but, $\frac{V_1}{2} = \frac{4}{2} = 2A \Rightarrow 4A - 4/3A = 8/3A$

$I = 2A$

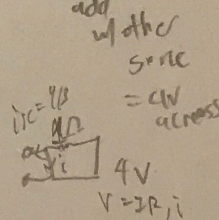

b) $V_2 = 4V$ $P = \frac{V^2}{R} = \frac{(4)^2}{1/3} = \frac{16}{1/3} = 48W$


$P = 48W$ in $\frac{1}{3}\Omega$ resistor

f30

$\begin{bmatrix} 3 & -1/2 \\ -1/2 & 7/2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4 \\ 8 \end{bmatrix}$

$i_L = \frac{100 + 0 i_L(t)}{25}$
 $\frac{15}{25} = \frac{2}{5} (100 + 0 i_L(t)) = 80 i_L(t) + 60$
 $\frac{1}{5} + \frac{1}{10} = \frac{15}{50} = \frac{50}{8}$

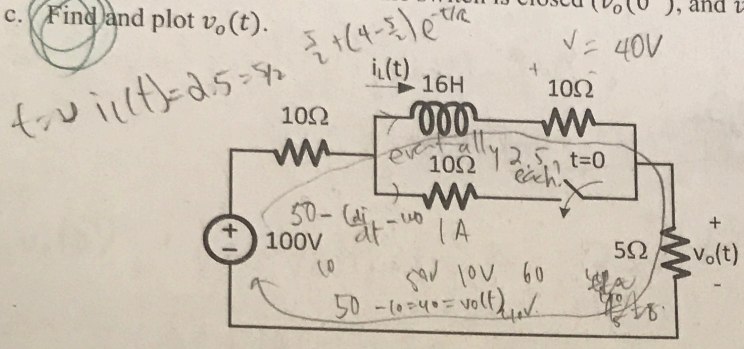3. The circuit below has been idle for a long time (switch is open). At $t = 0$, the switch is closed.
- Find the inductor current right before and after the switch is closed ($i_L(0^-)$, and $i_L(0^+)$).
 - Find v_o right before and after the switch is closed ($v_o(0^-)$, and $v_o(0^+)$).
 - Find and plot $v_o(t)$.




$R_{eq} = 10 + 5 + 5 = 20$
 $i = \frac{V}{R} = \frac{40}{20} = 2$
 at infinity, shorts again, we get
 $10\Omega \quad 5\Omega \quad 5\Omega = 20\Omega$
 $5A \text{ current output}$

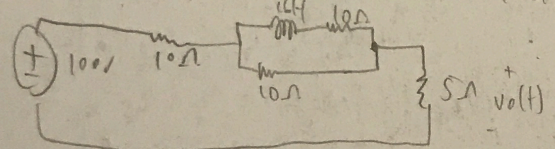a) KVL at $t=0^-$. Also, inductor is a short if idle for a long time b/c it's charged current.

$100V = 10(i_L(t)) + 10(i_L(t)) + 5(i_L(t)) \Rightarrow 25 i_L(t) = 100V$

at $t=0^+$, switch closes. Inductor doesn't want change in current. $i_L(0) = 4A$



$\frac{16 di_L}{dt} + 10 i_L = 10i_1 - 10i_2$
 $i_1 = i_2(t) + i_L(t)$
 $i_2(t) = i_1 - i_L(t)$

$100V = 10(i_1) + 16 \frac{di_L(t)}{dt} + 10 i_L(t) + 5(i_1)$
 $100V = 10(i_1) + 10(i_1 - i_L(t)) + 5(i_1)$
 $25 i_1 - 10 i_L(t) = 100V$
 $i_1 = \frac{100 + 10 i_L(t)}{25}$

$i_L(0^+) = 4$
 $\int (i_L(t) \cdot e^{+t})' = \int \frac{5}{2} e^t + C$
 $i_L(t) = \frac{5}{2} + C e^{-t}$
 $40 = 16 i_L(t) + 16 \frac{di_L(t)}{dt}$

$(0^+) = \frac{5}{2} + C$
 $i_L(0^+) = 4A$
 $i_L(t) = \frac{5}{2} + \frac{3}{2} e^{-t}$
 $u = e^{s \cdot t} = e^t$
 $\omega = 20, 4A$
 $100V = \frac{2}{5} \cdot 100 + 4 i_L(t) + 16 \frac{di_L(t)}{dt} + 10 i_L(t) + 20 + 2 i_L(t)$

b) before switch closes, $V_0?$

$$i(0^-) = 4A$$

$$100 - 4(10) - 4(10) - 4(5)$$

$$= 0V$$

$$\boxed{V_0(0^-) = 20V}$$

after switch closes?

if $i_L(0^+) = \frac{3}{2}A$

$$i_1 = \frac{100 + 10(i_L(t))}{25} = \frac{100 + 10(\frac{3}{2})}{25} = \frac{100 + 15}{25} = \frac{115}{25}$$


$$V_0(t) = (i_1)R_{5\Omega} = 23V = V_0(t) \text{ at } 0^+$$

For $V_0(0^+)$

$$V_0(t) = 5 \left(\frac{100 + 10(\frac{5}{2} + \frac{3}{2}e^{-t})}{25} \right) = \frac{1}{5} (100 + 10(\frac{5}{2})) = \frac{120}{5} = 24V = V_0(0^+) = 28V$$

c)


at infinity, we know inductor shorts and

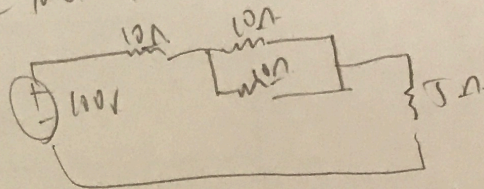

$$= R_{eq} = 20$$

$$I_{out} = 5A$$

$$(5)5\Omega = V_0(\infty)$$

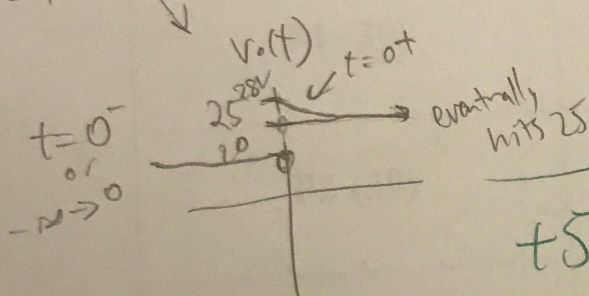

$V_0(t) = ?$