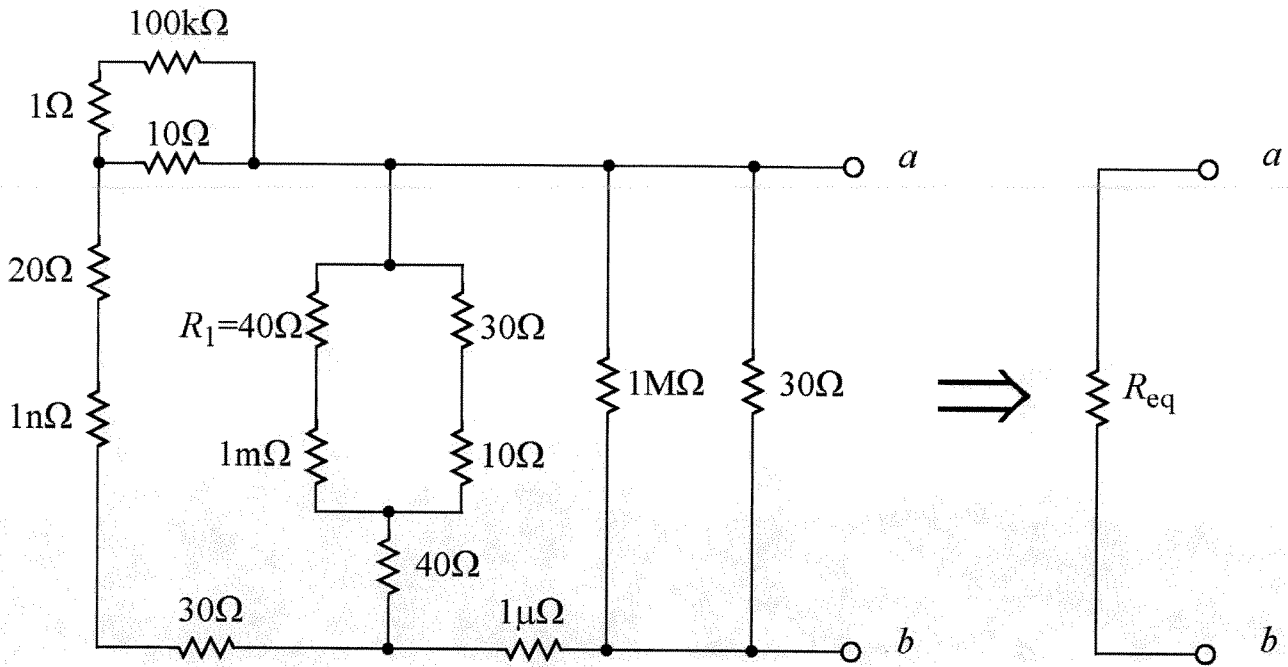



**Problem 1: Equivalent Resistance**

(15 points)



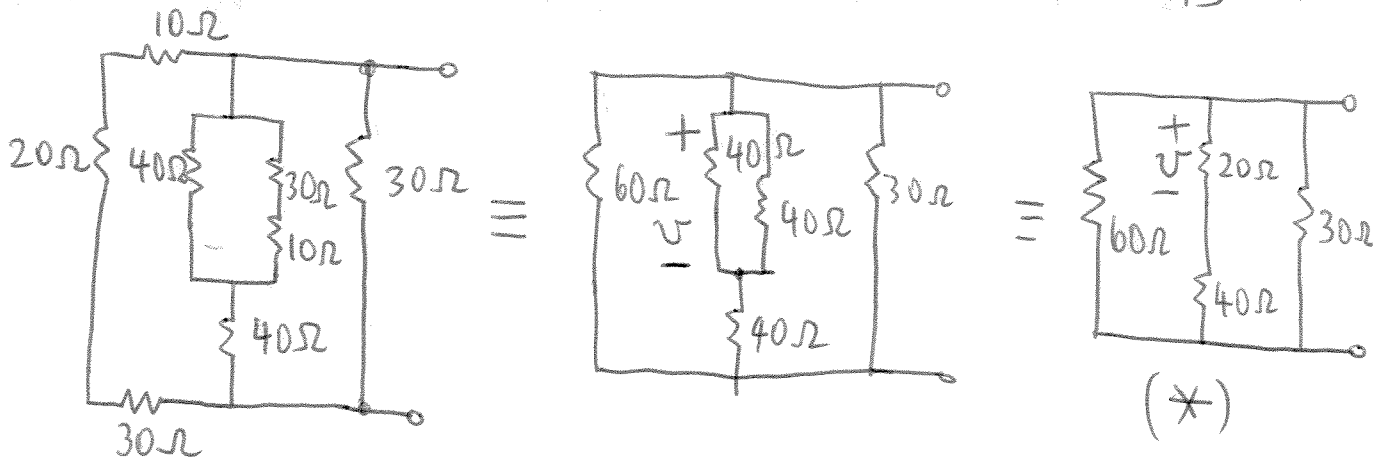- 1-1. Reduce the following resistor network to single resistor and find its approximate value (i.e., to two significant digits). Show your work in order to receive full and partial credit. Draw intermediate circuit diagrams as you simplify the resistor network. (5 points)

We remove the large resistors (compared to parallel resistors) to simplify the network. ( $1\text{M}\Omega$  &  $100\text{k}\Omega$ )  
 The  $1\Omega$  resistor also can be neglected when the  $100\text{k}\Omega$  is removed. The small value resistors ( $1\mu\Omega$ ,  $1\text{n}\Omega$ ,  $1\text{m}\Omega$ ) can be shorted out. The simplified network is




$$\equiv (60 \parallel 60) \parallel 30 = 30 \parallel 30 = 15 \Omega = R_{eq}$$

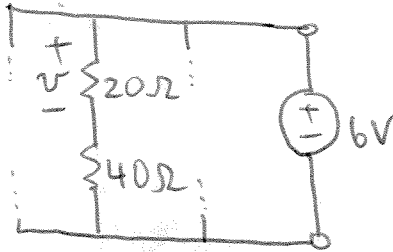- 1-2. If a 6-V source is attached to nodes  $a$  and  $b$  (i.e.,  $v_{ab} = 6$  V), calculate the approximate voltage across  $R_1$ . Show your work in order to receive full and partial credit. This includes re-drawing a portion of the circuit given on the previous page and showing your equations. (5 points)




Note the voltage across  $R_1$  is the same voltage across the  $20\Omega$  resistor in the last diagram from Prob 1-1.



$$v = 6V \cdot \frac{R_1}{R_{eq}} = 6 \cdot \frac{20}{60} = 2V$$

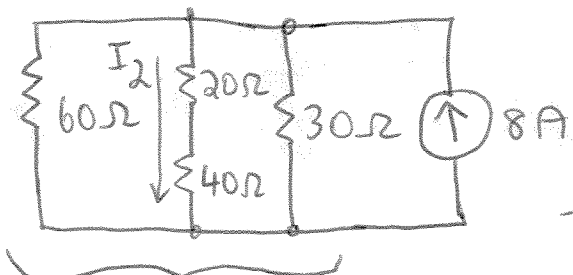- 1-3. If a 8-A source is attached to nodes  $a$  and  $b$  (i.e., 8 A flowing from  $b$  to  $a$ ), calculate the current passing through the 1-mΩ resistor. Show your work in order to receive full and partial credit. This includes re-drawing a portion of the circuit given on the previous page and showing your equations. (5 pt)


Again from 1-1, we see the current first splits into 3 branches. By current division



$$I_2 = 8A \cdot \frac{15}{20+40} \left( = \frac{R_{eq} \cdot I_{in}}{R_{branch}} \right) = 2A$$

From 1-1,  $R_{eq} = 15\Omega$


Then this current splits again

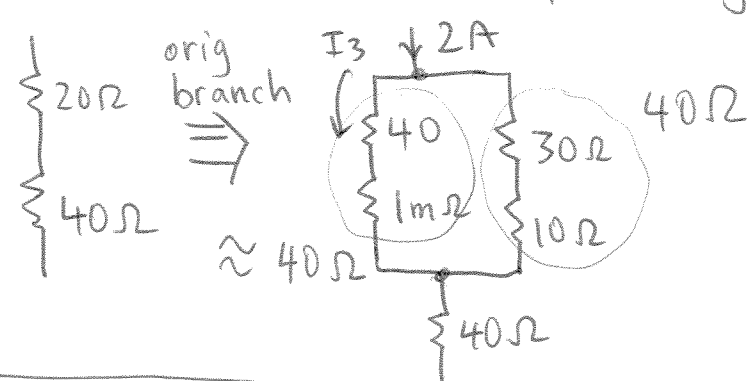

$$I_3 = 2A \cdot \frac{20\Omega}{40\Omega} = 1A = I \text{ through } 1m\Omega \text{ Res.}$$

**Problem 2: Node-Voltage or Mesh-Current Analysis**

(15 points)

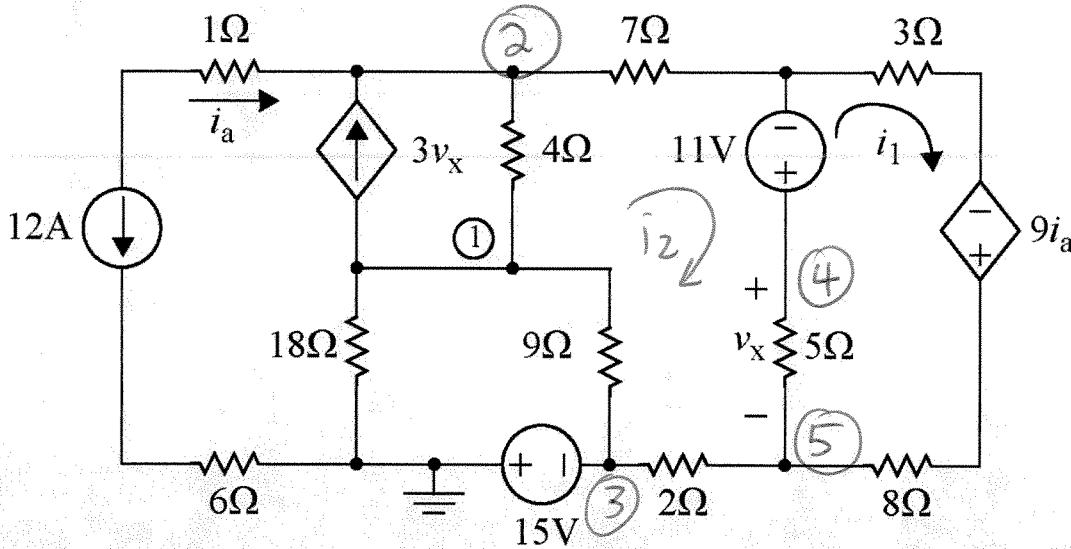

2-1. For the circuit above, would you prefer to use mesh or node-voltage analysis? Explain your choice. (5 points)

Mesh. There are less meshes than node voltages to find.

2-2. Write the node-voltage equation at node (1) in terms of only node voltages you define and numerical values. Simplify the equation by grouping node-voltage terms, but do not numerically evaluate fractions. Put a box around your final answer. (5 points)

Annotate diagram with node names.

$$\frac{V_1}{18} + \frac{V_1 - V_3}{9} + \frac{V_1 - V_2}{4} + 3(V_4 - V_5) = 0$$

But  $V_3 = -15$

$$V_1 \left( \frac{1}{18} + \frac{1}{9} + \frac{1}{4} \right) - \frac{V_2}{4} - \frac{V_3}{9} + 3V_4 - 3V_5 = -\frac{15}{9}$$

2-3. Write the mesh equation for  $i_1$  in terms of only mesh currents you define and numerical values (i.e., not in terms of dependent-source variables). Simplify the equation by grouping node-voltage terms, but do not numerically evaluate fractions. Put a box around your final answer. (5 points)


Define  $i_2$  mesh.  $i_a = -12A$

$$i_1(3) + (-9i_a) + 8i_1 + (i_1 - i_2)5 + 11 = 0$$

$$16i_1 - 5i_2 = -108 - 11 = -119$$

**Problem 3: Power Generation and Dissipation**

(32 points)

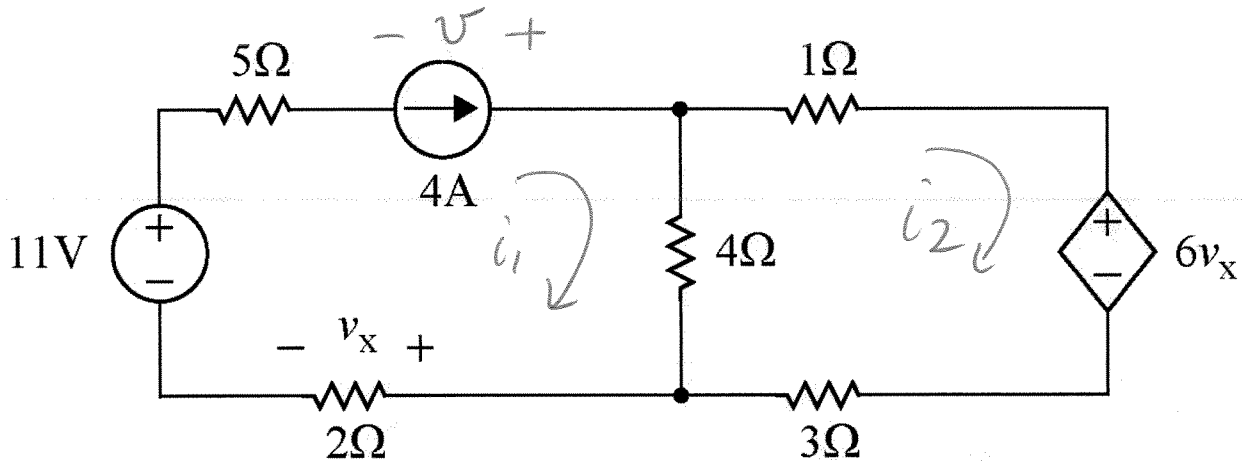

3-1. Calculate the power in each of the 8 components, and state whether it is generating or absorbing power. Show all intermediate calculations to receive full and partial credit.

$$i_1 = 4A \quad v_x = 8V$$

$$i_2 + 48 + 3i_2 + 4i_2 - 4i_1 = 0 \quad \neq$$


$$8i_2 = -32$$

$$i_2 = -4A$$

Find  $v$  across current source (KVL since we know all  $I$  in components)

$$32 + 8 - 11 + 20 - v = 0$$

$$v = 49V$$


Power in  $6v_x$    $\Rightarrow P = 192W$  Gen

Element (-)	Power (W)	Gen/Dis (-)
11 V	44	Gen
4 A	196	Gen
$6v_x$	192	Gen
$1\Omega$	16	Dis
$2\Omega$	32	Dis
$3\Omega$	48	Dis
$4\Omega$	256	Dis
$5\Omega$	80	Dis

} 432 W  
} 432 W

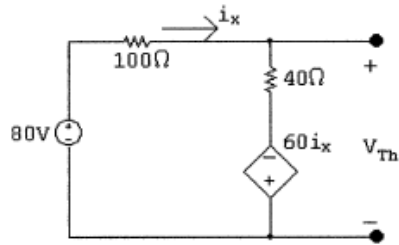Q4.


We begin by finding the Thévenin equivalent with respect to  $R_o$ . After making a couple of source transformations the circuit simplifies to



$$i_x = \frac{80 + 60i_x}{140}; \quad i_x = 1 \text{ A}$$

$$V_{Th} = 40i_x - 60i_x = -20i_x = -20 \text{ V}$$

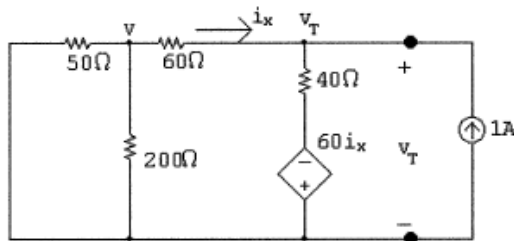Using the test-source method to find the Thévenin resistance gives



Use the node voltage method:

$$\frac{v}{50} + \frac{v - v_T}{60} + \frac{v}{200} = 0$$


$$\frac{v_T - v}{60} + \frac{v_T + 60i_x}{40} - 1 = 0$$

$$i_x = \frac{v - v_T}{60}$$

Solving,  $v_T = 50 \text{ V}$ .

$$R_{Th} = \frac{v_T}{1 \text{ A}} = 50 \Omega$$

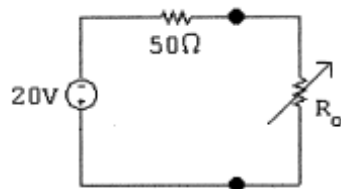Thus our problem is reduced to analyzing the circuit shown below.



$$\left( \frac{-20}{50 + R_o} \right)^2 R_o = 1.5$$

$$\frac{400R_o}{R_o^2 + 100R_o + 2500} = 1.5$$

$$1.5R_o^2 - 250R_o + 3750 = 0$$

$$\therefore R_o = 16.67 \Omega; \quad R_o = 150 \Omega$$