

Quiz 1 04/13/10

Allotted time: 1 hour (1pt/min delayed submission penalty). Total 20 points.

Calculator and one handwritten double-sided sheet of paper allowed


Name:

Student on right:

Student on left:

Student in front:

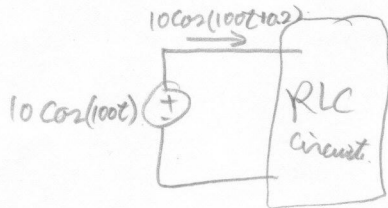Q1. A complicated RLC network has steady state current response of $10\cos(100t + 0.2)$ when a voltage source $10\cos(100t)$ is applied to it. Now a voltage source $20\cos(100t + 0.1)$ is applied to the circuit instead of the original source. Can you find the new current response? Is the information enough for you to find it? **5 points**



$V = ZI$
if we find the equivalent impedance of the circuit, we can find the new current response.

$$Z = \frac{V}{I} = \frac{10\angle 0}{10\angle 0.2} = 1\angle -0.2 \quad \left(\begin{array}{l} \text{Assuming that} \\ \text{phase is in} \\ \text{radians} \end{array} \right)$$
$$= \cos(-0.2) + j\sin(-0.2)$$
$$= 0.98 - j0.1987$$

Now if the voltage source is

$$20\cos(100t + 0.1) = 20\angle 0.1$$

$$I = \frac{V}{Z} = \frac{20\angle 0.1}{1\angle -0.2} = 20\angle 0.1 - (-0.2)$$
$$= 20\angle 0.3$$

5

$$= 20\cos(100t + 0.3)$$



is the new steady state current response of the new source.

Q2. You found a rather strange piece of circuitry which has three exposed terminals (x,y,z) and it has exactly one resistor, one inductor, and one capacitor, but you don't know how they are connected. The capacitor has a capacitance of $1 \mu\text{F}$. However, the other labels are not readable. The resistances (measured by applying a 1V DC source) between the terminals of the mystery circuit are as follows:

- x - y: infinity
- y - z: infinity
- z - x: 10

Next, you apply a 1 Volt, 100 Hz, square-wave signal from the x terminal to the y terminal. The plot below displays the voltage from z to y superimposed on the square wave, at the same scale as the square wave. As you can see, waveform from z to y follows the square wave, but there is ringing with a cycle time of about 1 ms.

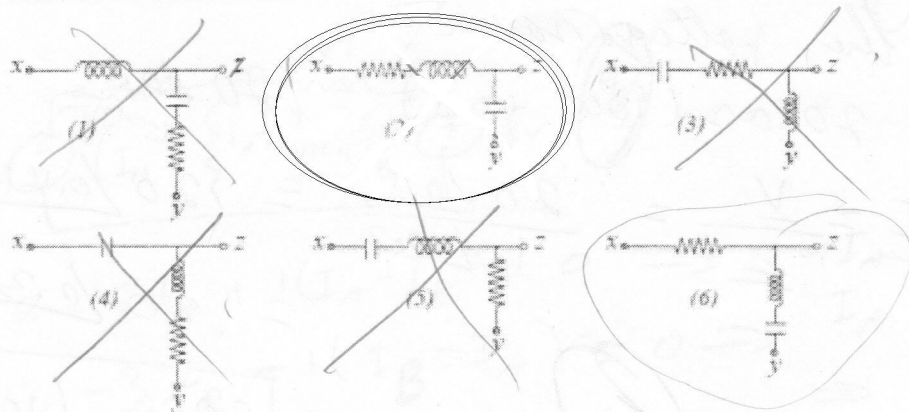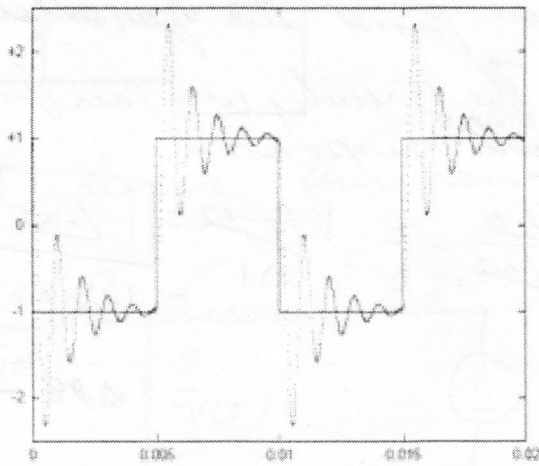Choose the likely circuit implementation from one of the following options. Also approximately find out the values of R and L. **10 points**




(2), (6)
leads to


Q3. Consider a two terminal network which have v-i relations as follows

$$N1: v_1(t) = 4i_1(t) - 8$$

$$N2: v_2(t) = 2i_2(t) + 3$$

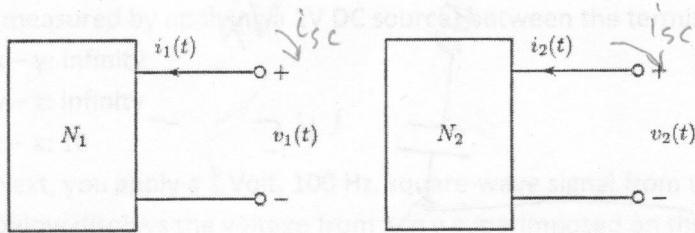

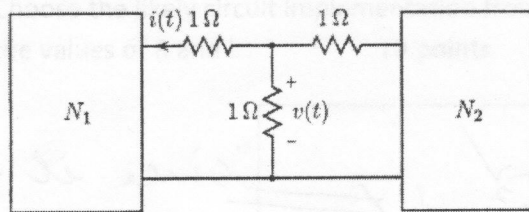Determine $v(t)$ and $i(t)$ if the two networks are connected as below.



5 points

EE-110 Quiz 1

A1 $V_{s1}(t) = 10 \cos(100t)$

$\Rightarrow P\{V_{s1}(t)\} = 10 \angle 0$

$I_1(t) = 10 \cos(100t + 0.2)$

$\Rightarrow P\{I_1(t)\} = 10 \angle 0.2$

$V_{s2}(t) = 20 \cos(100t + 0.1)$

$\Rightarrow P\{V_{s2}(t)\} = 20 \angle 0.1$

$I_2(t) = ?$

We have

$\frac{P\{V_s(t)\}}{P\{I(t)\}} = \frac{V}{I} = \frac{P\{V_s(t)\}}{Z}$

$\Rightarrow Z = \frac{P\{V_s(t)\}}{P\{I_1(t)\}}$

$\Rightarrow \frac{10 \angle 0}{10 \angle 0.2} = \frac{20 \angle 0.1}{I_{s2}(t)}$

$\Rightarrow \boxed{P\{I_{s2}(t)\} = 20 \angle 0.3}$

$\Rightarrow I_{s2}(t) = 20 \cos(100t + 0.3)$

Note

$P\{V(t)\}$ = phasor of $V(t)$

Z = resultant impedance of

the network

Question 1: Alternate Solution

Q1. A RLC network is a "Linear" System.

When

$$v_1(t) = 10 \cos(100t) \longrightarrow \boxed{\text{RLC}} \longrightarrow i_1(t) = 10 \cos(100t + 0.2)$$

and if $v_2(t) = 20 \cos(100t + 0.1)$,

$$v_2(t) = 2 \cdot v_1(t + \frac{1}{1000}) \quad (\leftarrow \text{time shifted by } \frac{1}{1000} \text{ \& scaled by a factor of } \times 2)$$

Applying $v_2(t)$ to RLC network.

$$v_2(t) \longrightarrow \boxed{\text{RLC}} \longrightarrow i_2(t).$$

$$\begin{aligned} i_2(t) &= 2 \cdot i_1(t + \frac{1}{1000}) \\ &= 20 \cos(100(t + \frac{1}{1000}) + 0.2) \\ &= 20 \cos(100t + 0.3) // \end{aligned}$$

Q2 We have

$$\underline{R(z-x)} = 10$$

⇒ (1), (4) and (5) are ruled out.

$$R(x-y) = \infty$$

$$R(y-z) = \infty$$

⇒ (3) is ruled out as it just has an inductor along $(z-y)$.

⇒ Possible choices:- (2) or (6)

Consider circuit (6)

Consider the time interval when ^{input} voltage goes from $-1V$ to $+1V$.

⇒ $V(x \rightarrow y)$ goes from $-1V$ to $+1V$ at $t = t_0$

In the series RLC circuit, current across the inductor cannot change instantaneously.

$$\Rightarrow I_L(t=t_0^+) - I_L(t=t_0^-) = 0$$

$$\Rightarrow V_R(t=t_0^+) - V_R(t=t_0^-) = 0$$

Also, voltage across the capacitor cannot change instantaneously

$$\Rightarrow V_C(t=t_0^+) - V_C(t=t_0^-) = 0$$

\Rightarrow from $t=t_0^-$ to $t=t_0^+$

$$\Delta V_R = 0$$

$$\Delta V_C = 0$$

$$\Rightarrow \Delta V_L = 2V \quad \left\{ \text{KVL} \right\}$$

$$\begin{aligned} \Rightarrow \Delta V(y-z) &= \Delta V_L + \Delta V_C \\ &= 2V \end{aligned}$$

Therefore in circuit 6, from $t=t_0^-$ to $t=t_0^+$, voltage across $(y-z)$ should bump up suddenly by 2V. However, in the waveform, it is seen that $V(y-z)$ lags a little and does not bump up instantaneously.

\Rightarrow (6) is not a solution

Consider (2).

Again, from $t = t_0^-$ to $t = t_0^+$

$$\left. \begin{aligned} \Delta V_R &= 0 \\ \Delta V_C &= 0 \\ \Delta V_L &= 2V \end{aligned} \right\} t_0^- \text{ to } t_0^+$$

$$\Rightarrow \Delta V(y-z) = \Delta V_C = 0$$

This is verified from the waveform where $V(y-z)$ lags a little compared to the squared input.

\Rightarrow Circuit implementation is (2).

We have

$$R(z-x) = 10 \Omega$$

$$\Rightarrow \boxed{R = 10 \Omega}$$

$$T = 1 \times 10^{-3} = \frac{2\pi}{\omega_d}$$

$$\Rightarrow \omega_d = 2\pi \times 10^3$$

$$\sqrt{\omega_0^2 - \alpha^2} = \omega_d$$

$$\Rightarrow \frac{1}{LC} - \frac{R^2}{4L^2} = 4\pi^2 \times 10^6$$

$$\Rightarrow 16\pi^2 L^2 - 4L + 10^{-4} = 0$$

$$\Rightarrow L = \frac{4 \pm \sqrt{16 - 4 \times 16\pi^2 \times 10^{-4}}}{2 \times 16\pi^2}$$


$$\Rightarrow \boxed{L = 0.025 \text{ H}}$$

Q3 We will find the Thevenin Equivalent circuits for blocks N_1 and N_2 .

I N_1 : $v_1(t) = 4i_1(t) - 8$
 $i_1(t) = 0 \Rightarrow v_1(t) = -8$
 $\Rightarrow V_{oc}(t) = -8V = V_{Th1}$

$v_1(t) = 0 \Rightarrow i_1(t) = 2A$
 $\Rightarrow i_{sc}(t) = -i_1(t) |_{v_1(t)=0}$
 $= -2A$

$\Rightarrow R_{Th1} = \frac{V_{Th1}}{i_{sc} |_{v_1=0}} = 4\Omega$

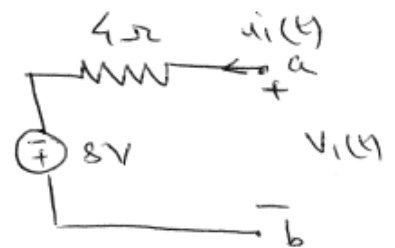


II N_2 : $v_2(t) = 2i_2(t) + 3$

$V_{oc}(t) = v_2(t) |_{i_2(t)=0}$
 $= 3V = V_{Th2}$


$i_2(t) |_{v_2(t)=0} = -\frac{3}{2}A$

$\Rightarrow i_{sc} = -i_2(t) |_{v_2(t)=0} = \frac{3}{2}A$

$\Rightarrow R_{Th2} = \frac{V_{Th2}}{i_{sc} |_{v_2=0}} = 2\Omega$

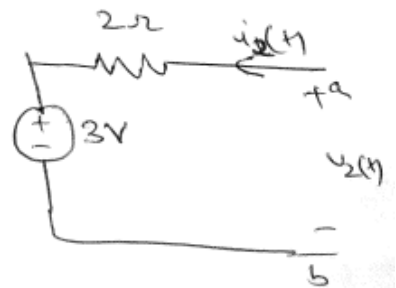

Then, we have

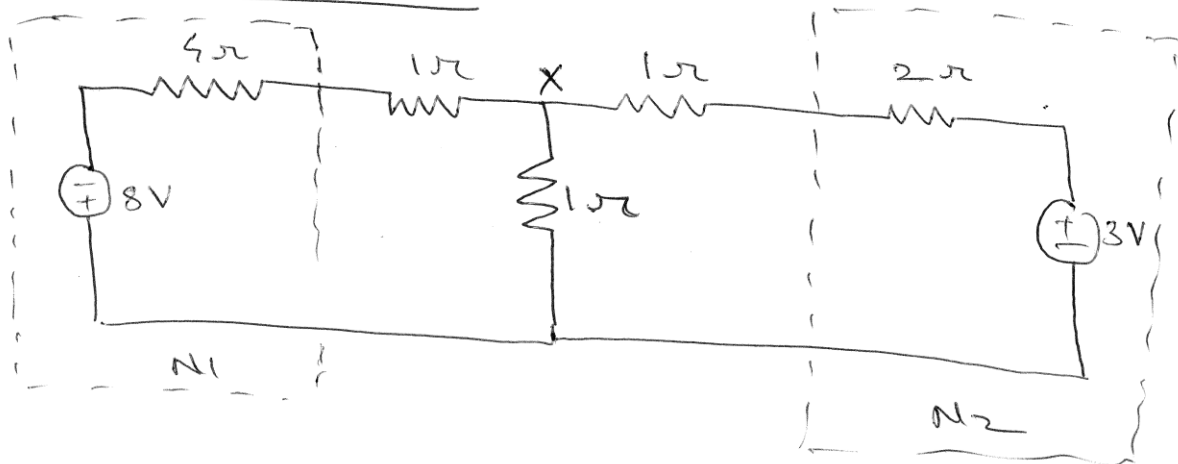

KCL at node X

$$\frac{V_x - (-8)}{4+1} + \frac{V_x}{1} + \frac{V_x - 3}{2+1} = 0$$

$$\Rightarrow \frac{V_x + 8}{5} + V_x + \frac{V_x - 3}{3} = 0$$

$$\Rightarrow 3V_x + 24 + 15V_x + 5V_x - 15 = 0$$

$$\Rightarrow 23V_x + 9 = 0$$

$$\Rightarrow \boxed{V_x = -\frac{9}{23} \text{ V}} = v(t)$$

$$i(t) = \frac{V_x + 8}{5} = \frac{8 - \frac{9}{23}}{5} = \boxed{\frac{35}{23} \text{ A}}$$