


Midterm Solutions

Prob. 1 For the following circuit (transformers are ideal), find

a) Input Impedance Z_{in}

b) Complex power supplied by the source?

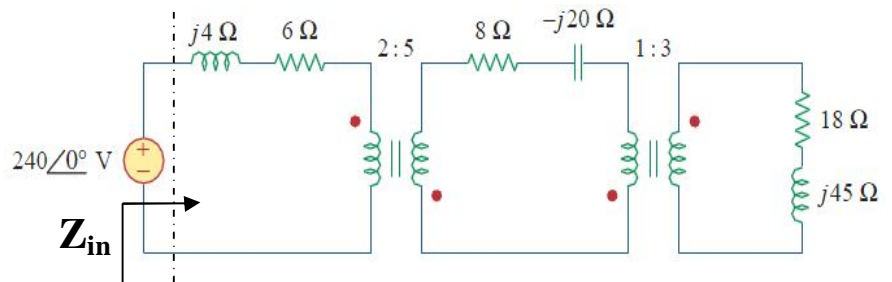c) Average power delivered to the 18 Ohm resistor



Solution:

(a) Reflect the load to the middle circuit.

$$Z_L' = 8 - j20 + (18 + j45)/3^2 = 10 - j15$$

We now reflect this to the primary circuit so that

$$Z_{in} = 6 + j4 + (10 - j15)/n^2 = 7.6 + j1.6 = 7.767 \angle 11.89^\circ, \text{ where } n = 5/2 = 2.5$$

(b) $I_1 = 240/Z_{in} = 240/7.767 \angle 11.89^\circ = 30.9 \angle -11.89^\circ$

$$S = 0.5 v_s I_1^* = (240 \angle 0^\circ)(30.9 \angle 11.89^\circ) = \underline{\underline{3708 \angle 11.89^\circ \text{ VA}}}$$

(c) $I_2 = -I_1/n, \quad n = 2.5$

$$I_3 = -I_2/n', \quad n' = 3$$

$$I_3 = I_1/(nn') = 30.9 \angle -11.89^\circ / (2.5 \times 3) = 4.12 \angle -11.89^\circ$$


$$P = 0.5 |I_3|^2 (18) = 9(4.12)^2 = \underline{\underline{152.77 \text{ watts}}}$$

Prob. 2 The switch in this circuit has been in position **a** for a long time. At $t = 0$, it moves instantaneously to position **b**.

a) Construct S-domain circuit for $t > 0$


b) Find $V_o(s)$?

c) Find $v_o(t)$?

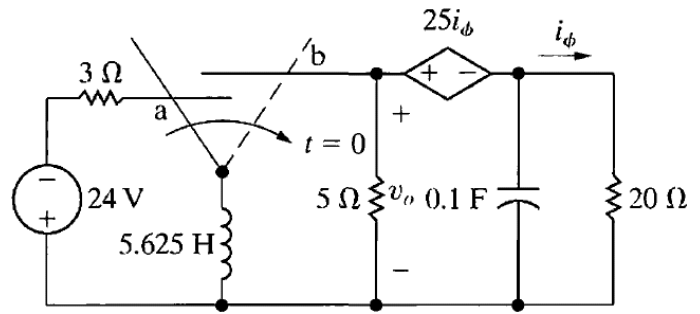

Solution:

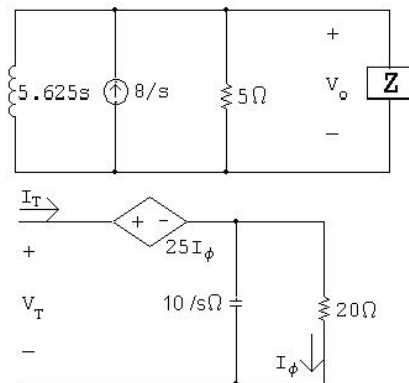[a] $i_L(0^-) = i_L(0^+) = \frac{24}{3} = 8\text{ A}$ directed upward



[b]
$$V_T = 25I_\phi + \left[\frac{20(10/s)}{20 + (10/s)} \right] I_T = \frac{25I_T(10/s)}{20 + (10/s)} + \left(\frac{200}{10 + 20s} \right) I_T$$

$$\frac{V_T}{I_T} = Z = \frac{250 + 200}{20s + 10} = \frac{45}{2s + 1}$$

$$\frac{V_o}{5} + \frac{V_o(2s + 1)}{45} + \frac{V_o}{5.625s} = \frac{8}{s}$$

$$\frac{[9s + (2s + 1)s + 8]V_o}{45s} = \frac{8}{s}$$

$$V_o[2s^2 + 10s + 8] = 360$$

$$V_o = \frac{360}{2s^2 + 10s + 8} = \frac{180}{s^2 + 5s + 4}$$


[c]
$$V_o = \frac{180}{(s + 1)(s + 4)} = \frac{K_1}{s + 1} + \frac{K_2}{s + 4}$$

$$K_1 = \frac{180}{3} = 60; \quad K_2 = \frac{180}{-3} = -60$$

$$V_o = \frac{60}{s + 1} - \frac{60}{s + 4}$$

$$v_o(t) = [60e^{-t} - 60e^{-4t}]u(t)\text{ V}$$

Prob. 3 In the following circuit,

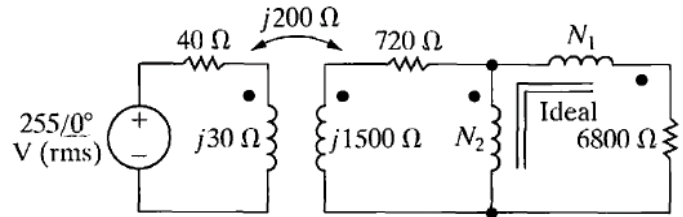

a) If $N_1 = 1000$ turns, how many turns should be placed on the N_2 winding of the ideal transformer so that Maximum Average Power is delivered to the 6800 ohm load ?

b) Find the Average Power delivered to the 6800 ohm load

c) What percentage of average power generated by voltage source is delivered to 6800 ohm load?

Solution:

$$[a] Z_{Th} = 720 + j1500 + \left(\frac{200}{50}\right)^2 (40 - j30) = 1360 + j1020 = 1700/36.87^\circ \Omega$$


$$\therefore Z_{ab} = 1700 \Omega$$

$$Z_{ab} = \frac{Z_L}{(1 + N_1/N_2)^2}$$

$$(1 + N_1/N_2)^2 = 6800/1700 = 4$$

$$\therefore N_1/N_2 = 1 \quad \text{or} \quad N_2 = N_1 = 1000 \text{ turns}$$
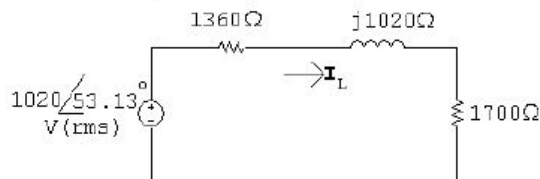
$$[b] V_{Th} = \frac{255/0^\circ}{40 + j30} (j200) = 1020/53.13^\circ \text{ V}$$




$$I_L = \frac{1020/53.13^\circ}{3060 + j1020} = 0.316/34.7^\circ \text{ A (rms)}$$

Since the transformer is ideal, $P_{6800} = P_{1700}$.

$$P = |I|^2 (1700) = 170 \text{ W}$$

[c]

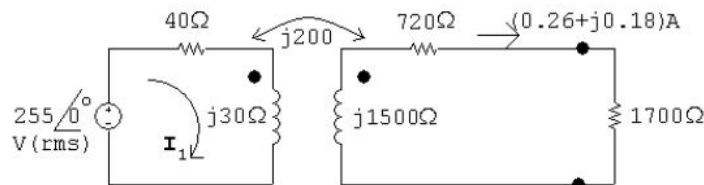

$$255/0^\circ = (40 + j30)I_1 - j200(0.26 + j0.18)$$


$$\therefore I_1 = 4.13 - j1.80 \text{ A (rms)}$$

$$P_{gen} = (255)(4.13) = 1053 \text{ W}$$

$$100 (170/1053) = 16.14 \%$$


Prob. 4

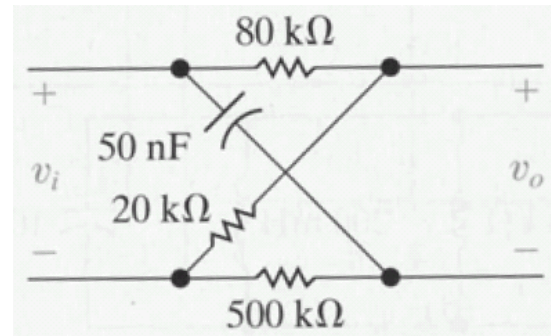- a) Find the numerical expression for the transfer function $H(s) = V_o/V_i$ for the circuit
- b) Give the numerical value of each pole and zero of $H(s)$.



Solution:

[a]

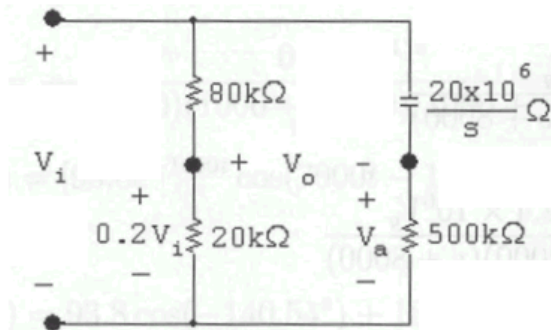

$$V_a = \frac{V_i}{500,000 + [(20 \times 10^6)/s]} (500,000) = \frac{s}{s + 40} V_i$$

$$0.2V_i = V_o + V_a$$

$$\therefore V_o = 0.2V_i - \frac{s}{s + 40} V_i$$

$$\frac{V_o}{V_i} = \frac{0.2(s + 40) - s}{s + 40} = \frac{-0.8s + 8}{s + 40} = \frac{-0.8(s - 10)}{s + 40}$$

[b] $-z_1 = 10 \text{ rad/s}$

$-p_1 = -40 \text{ rad/s}$