

EE110 – Circuit Analysis II
Spring 2017 – Dr. Shervin Moloudi
Mid-Term Exam – Thursday May 4, 2017

Instructions

- 1- You have 1 hour and 50 minutes.
- 2- Do not attach your own paper. Ask the proctors for extra paper
- 5- The exam is closed book. No formula sheets, electronic devices, tablets, smart phones/watches allowed. Regular wrist watches allowed.

Name: _____


UID: _____

Discussion Session: _____

Question	
1	7.5 / 10
2	30 / 30
3	30 / 30
4	30 / 30
Grade	97.5 / 100


Excellent!

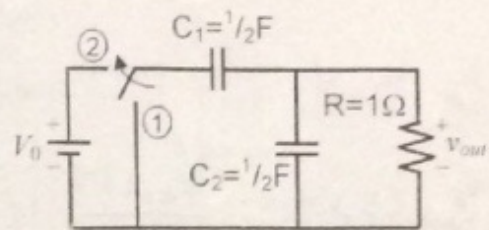2- Find $v_{out}(t)$ for all t if the switch goes from position 1 to position 2 to at $t = 0$ and back to position 1 at $t = 1$ sec. The circuit had been at rest for a long time before $t = 0$.



(30 points)

① For $t < 0$

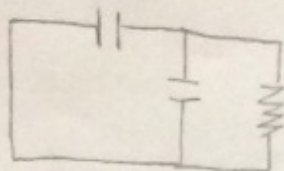


$$V_{C_1}(0^-) = 0$$

$$V_{C_2}(0^-) = 0$$

$$V_{out}(0^-) = 0$$

② For $0 < t < 1$

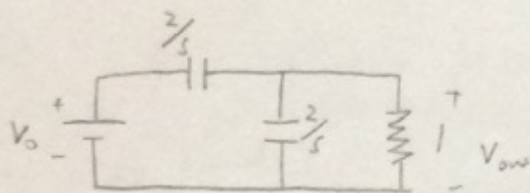


$$\begin{aligned} \frac{V_{out}(s)}{V_0(s)} &= \frac{1 // \frac{2}{s}}{1 // \frac{2}{s} + \frac{2}{s}} \\ &= \frac{\frac{2/s}{1 + 2/s}}{\frac{2/s}{1 + 2/s} + \frac{2}{s}} \end{aligned}$$

$$= \frac{\frac{2/s}{s+2}}{\frac{2/s}{s+2} + \frac{2}{s}} = \frac{2/s}{2/s + 2 + 2(s+2)/s} = \frac{2/s}{2/s + 2 + 2 + 4/s} = \frac{2/s}{4 + 4/s} = \frac{2/s}{4(1 + 1/s)} = \frac{1}{2} \frac{s}{s+1}$$

$$\therefore V_0(s) = \frac{1}{s} V_0 \Rightarrow V_{out}(s) = \frac{1}{2} \frac{1}{s+1} V_0$$

$$\therefore V_{out}(t) = V_0 \frac{1}{2} e^{-t} u(t) \quad \text{for } 0 < t < 1$$

③ For $t > 1$

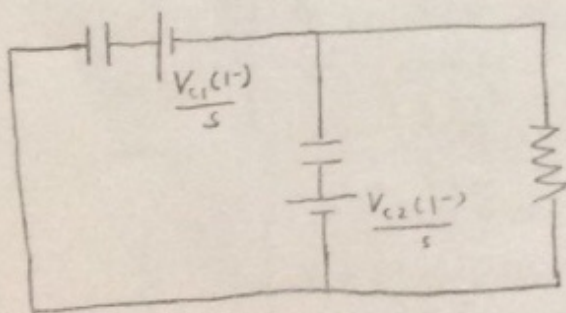

Using law of super position

$$V_{out}(s) = - \frac{V_{c1}(1^-)}{s} \cdot \left(\frac{1}{2} \frac{s}{s+1}\right) + \frac{V_{c2}(1^-)}{s} \cdot \left(\frac{1}{2} \frac{s}{s+1}\right)$$

$$V_{c2}(1^-) = V_{out}(1^-) = \frac{1}{2} V_0 e^{-1}$$

$$V_{c1}(1^-) = V_0 - V_{c2}(1^-) = V_0 \left(1 - \frac{1}{2} e^{-1}\right)$$

$$- V_{out}(s) = V_0 (-1 + e^{-1}) \frac{1}{2} \frac{1}{s+1}$$

$$- V_{out}(t) = \left[V_0 (-1 + e^{-1}) \frac{1}{2} e^{-t} \right] u(t)$$

However, for $t > 1$, time starts at $t = 1$

$$- V_{out}(t) = \left[V_0 (-1 + e^{-1}) \frac{1}{2} e^{-(t-1)} \right] u(t-1) \quad \text{for } t > 1$$


∴ overall,

$$V_{out}(t) = \begin{cases} \underline{V_0 \frac{1}{2} e^{-t}} & , 0 < t < 1 \\ \underline{V_0 \frac{1}{2} (-1 + e^{-1}) e^{-(t-1)}} & , t > 1 \\ \underline{0} & , t < 0 \end{cases}$$

$$= \begin{cases} V_0 \frac{1}{2} e^{-t} & , 0 < t < 1 \\ V_0 \frac{1}{2} (1 - e) e^{-t} & , t > 1 \\ 0 & , t < 0 \end{cases}$$

3- A) Without using the Laplace Transform, find the impulse response of a circuit, with input $f(t)$ and output $y(t)$, governed by this equation:

$$y' = f'' + f$$

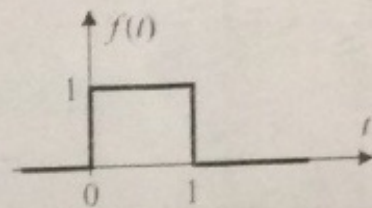

B) Without using the Laplace Transform, find the complete response of this circuit to the input $f(t)$ shown here, if $y(0^+) = 1$.

(10+20=30 points)

$$A) \quad y = A u(t) + B \delta(t) + C \delta'(t)$$

$$y' = A \delta(t) + B \delta'(t) + C \delta''(t)$$

$$y' = \delta''(t) + \delta(t)$$

$$\Rightarrow \begin{cases} A=1 \\ B=0 \\ C=1 \end{cases}$$

$$\therefore y = u(t) + \delta'(t) \quad \text{is the impulse response} \\ = h(t)$$

$$B) \quad f(t) = u(t) - u(t-1)$$

$$y_{zs}(t) = \int_{-\infty}^{\infty} f(\tau) h(t-\tau) d\tau$$

$$= \int_0^1 u(t-\tau) + \delta'(t-\tau) d\tau$$


$$= \int_0^1 u(t-\tau) d\tau + \int_0^1 \delta'(t-\tau) d\tau$$

$$= \begin{cases} 0, & t < 0 \\ t, & 0 \leq t \leq 1 \\ 1, & t > 1 \end{cases} + (\delta(t) - \delta(t-1))$$

$$= \begin{cases} 0, & t < 0 \\ t + \delta(t) - \delta(t-1), & 0 \leq t \leq 1 \\ 1, & t > 1 \end{cases}$$

3- A) Without using the Laplace Transform, find the impulse response of a circuit, with input $f(t)$ and output $y(t)$, governed by this equation:

$$y' = f'' + f$$

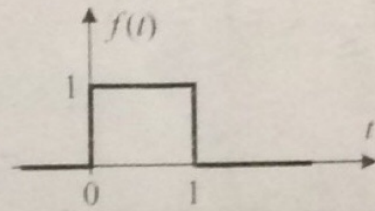

B) Without using the Laplace Transform, find the complete response of this circuit to the input $f(t)$ shown here, if $y(0^-) = 1$.

(10+20=30 points)

$$A) \quad Y = A u(t) + B \delta(t) + C \delta'(t)$$

$$Y' = A \delta(t) + B \delta'(t) + C \delta''(t)$$

$$Y' = \delta''(t) + \delta(t)$$

$$\Rightarrow \begin{cases} A=1 \\ B=0 \\ C=1 \end{cases}$$

$\therefore y = u(t) + \delta'(t)$ is the impulse response
 $= h(t)$

$$B) \quad f(t) = u(t) - u(t-1)$$

$$y_{zs}(t) = \int_{-\infty}^{\infty} f(\tau) h(t-\tau) d\tau$$


$$= \int_0^1 u(t-\tau) + \delta'(t-\tau) d\tau$$

$$= \int_0^1 u(t-\tau) d\tau + \int_0^1 \delta'(t-\tau) d\tau$$

$$= \begin{cases} 0, & t < 0 \\ t, & 0 \leq t \leq 1 \\ 1, & t > 1 \end{cases} + (\delta(t) - \delta(t-1))$$

$$= \begin{cases} 0, & t < 0 \\ t + \delta(t) - \delta(t-1), & 0 \leq t \leq 1 \\ 1, & t > 1 \end{cases}$$

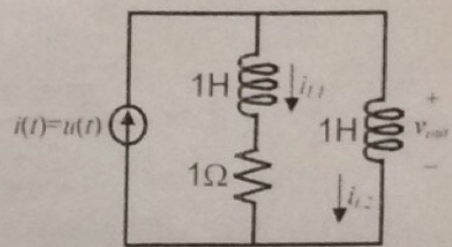
4- A) Find the complete response for $v_{out}(t)$ when the inductors have initial currents $i_{L1}(0^-)$ and $i_{L2}(0^-)$ at $t=0^-$. You can use the Laplace Transform if you choose to.
 B) Determine the condition for $i_{L1}(0^-)$ and $i_{L2}(0^-)$ for which the exponential part of the response becomes equal to 0.



(20+10=30 points)

$$A) \text{ at } t=0^-, \quad i(t) = 0$$
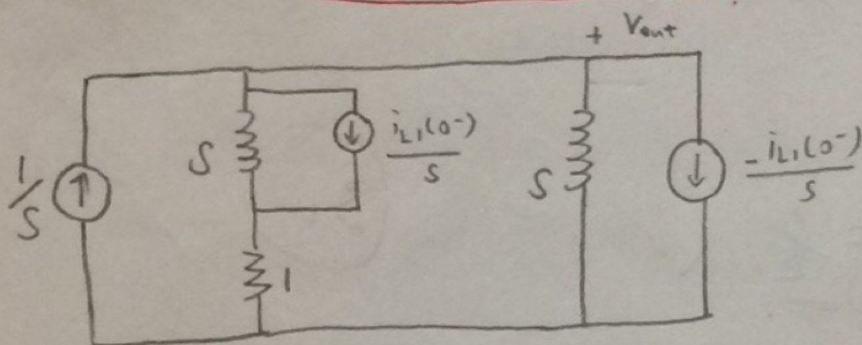
$$\therefore \underline{i_{L1}(0^-) = -i_{L2}(0^-)}$$



$$\frac{1}{s} = I_{L1}(s) + \frac{i_{L1}(0^-)}{s} + I_{L2}(s) + \frac{-i_{L1}(0^-)}{s}$$

$$= I_{L1}(s) + I_{L2}(s)$$

$$I_{L1}(s) \cdot s + \left[I_{L1}(s) + \frac{i_{L1}(0^-)}{s} \right] \cdot 1 = I_{L2}(s) \cdot s$$

$$\Rightarrow I_{L1}(s) (s+1) = -I_{L2}(s) \cdot s - \frac{i_{L1}(0^-)}{s}$$

$$\Rightarrow \frac{1}{s} = \frac{s}{s+1} I_{L2} - \frac{i_{L1}(0^-)}{s(s+1)} + I_{L2}$$

$$\therefore I_{L2} = \left[\frac{1}{s} + \frac{i_{L1}(0^-)}{s(s+1)} \right] / \left(\frac{2s+1}{s+1} \right)$$

$$V_{out}(s) = I_{L2}(s) \cdot s = \left(1 + \frac{i_{L1}(0^-)}{s+1} \right) / \left(\frac{2s+1}{s+1} \right)$$

$$= \frac{s+1+i_{L1}(0^-)}{s+1} \cdot \frac{s+1}{2s+1} = \frac{1}{2} \frac{s+1+i_{L1}(0^-)}{s+\frac{1}{2}} \rightarrow$$

$$= \frac{1}{2} \left(1 + \frac{\frac{1}{2} + i_{L1}(0^-)}{s + \frac{1}{2}} \right)$$

$$\therefore V_{out}(t) = \frac{1}{2} \delta(t) + \frac{1}{2} \left(\frac{1}{2} + i_{L1}(0^-) \right) e^{-\frac{1}{2}t}$$

B) For the exponential part to be 0,

$$i_{L1}(0^-) = -\frac{1}{2}$$

$$\therefore i_{L2}(0^-) = -i_{L1}(0^-) = \frac{1}{2}$$

30