

May 8, 2008

MID-TERM EXAMINATION

Do all work in this examination packet. There are three questions. Each counts 10 points. Good luck!

1. The switch has been in position **a** for a long time. At $t = 0$, the switch moves instantaneously to position **b**.


a.) (1 point) At $t = 0^+$, what is the initial value of v_a ?

b.) (2 points) What is the initial value of dv_a/dt ?


c.) (2 points) For $t > 0$, find the roots of the system's characteristic equation.

d.) (1 point) For $t > 0$, the sub-system is (check one box):
 undamped; underdamped;
 critically damped; overdamped.

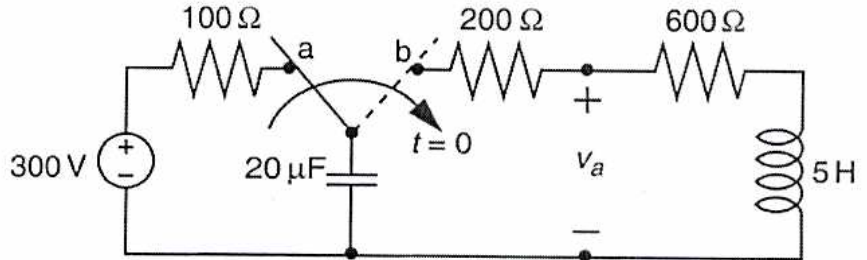e.) (4 points) Obtain the numerical expression for $v_a(t)$ for $t \geq 0$.



a) For $t > 0$:

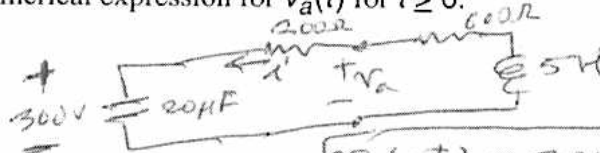

Since $i(0^-) = i(0^+) = 0$: $v_a(0^+) = 300V$

b) $v_a = 200i + (5 \times 10^{-4}) \int i(x) dx + 300$

$\Rightarrow \frac{dv_a(0^+)}{dt} = 200 \frac{di(0^+)}{dt} + (5 \times 10^{-4}) i(0^+) = 200 \frac{di(0^+)}{dt}$

and also: $-L \frac{di(0^+)}{dt} = 300 \Rightarrow \frac{di(0^+)}{dt} = -0.2 \times 300 = -60 A/s$

$\therefore \frac{dv_a(0^+)}{dt} = -12,000 V/s$

c) $L \frac{di}{dt} + Ri + \frac{1}{C} \int i(x) dx + 300 = 0$

$\Rightarrow L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0 \Rightarrow 5s^2 + 800s + 5 \times 10^4 = 0$

$s = \frac{-800 \pm \sqrt{64 \times 10^4 - 4 \times 25 \times 10^4}}{10}$


$= -80 \pm \sqrt{64 - 100} j = -80 \pm j10\sqrt{36}$
 $= -80 \pm j60$

1.) (cont'd.)

Answer to c : $-80 \pm j60$



d) underdamped

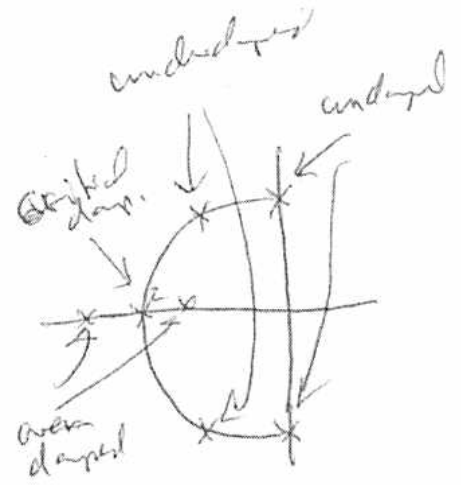

e) From answers to c) & d):

$$v_a = B_1 e^{-80t} \cos 60t + B_2 e^{-80t} \sin 60t$$


$$\begin{cases} v_a(0) = B_1 = \underline{300V.} \\ \frac{dv_a}{dt}(0) = -80B_1 + 60B_2 = -12,000 \end{cases}$$

$$\Rightarrow B_2 = \underline{200V.}$$


$$\Rightarrow v_a(t) = 300e^{-80t} \cos 60t + 200e^{-80t} \sin 60t$$

for $t \geq 0$


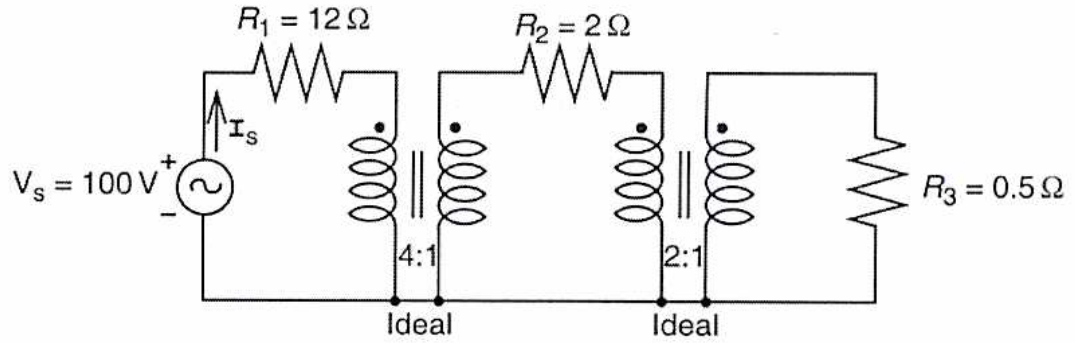
2A. (5 points) Determine the current supplied by the source V_s .



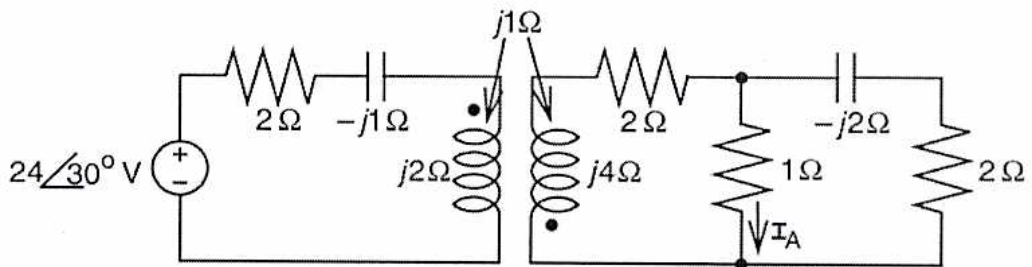2B. (5 points) Determine I_A in the circuit below.




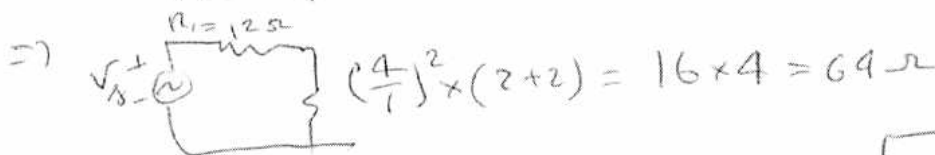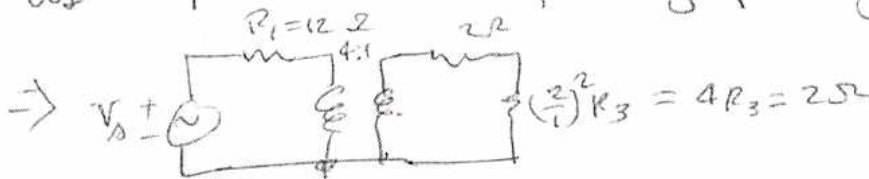2A: Use impedance transformation property of ideal transformer:



$$\Rightarrow I_s = V_s / (12 + 64) = 100 / 76 = \boxed{1.32 \text{ A}}$$

2B: The right end of the circuit is:

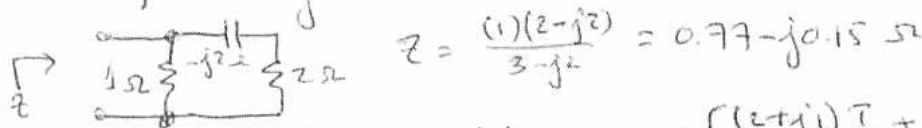

Mesh eqns. for the circuit are now:


$$\begin{cases} (2+j1)I_1 + (j1)I_2 = 24\angle 30^\circ \\ (j1)I_1 + (2+j4+0.77-j0.15)I_2 = 0 \end{cases}$$

$$\begin{bmatrix} (2+j1) & j1 \\ j1 & 2.77+j3.85 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{pmatrix} 24\angle 30^\circ \\ 0 \end{pmatrix} \begin{cases} \Delta = (2+j1)(2.77+j3.85) + 1 = 2.69 + j10.47 \\ I_2 = \frac{(j1)(24\angle 30^\circ)}{\Delta} = 2.22 \angle -135.57^\circ \end{cases}$$

using current division: $I_A = I_2 \frac{2-j2}{(3-j2)} = 1.74 \angle -146.88^\circ$


3A. (six points).

- a.) (1 point) Find the average power dissipated in the line for this source/line/load circuit.
- b.) (2 points) Find the capacitive reactance that, when connected in parallel with the load, will make the load look purely resistive.
- c.) (1 point) What is the equivalent impedance of the load in (b)?
- d.) (1 point) Find the average power dissipated in the line when the capacitive reactance is connected across the load.
- e.) (1 point) Express the power loss in (d) as a percentage of the power loss found in (a).

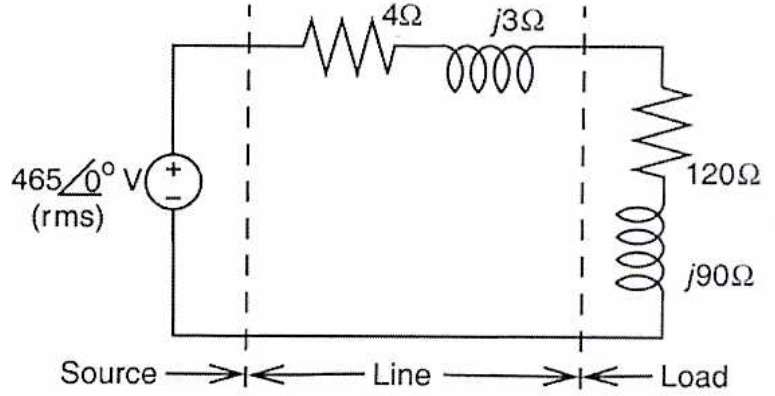

3B. (four points)

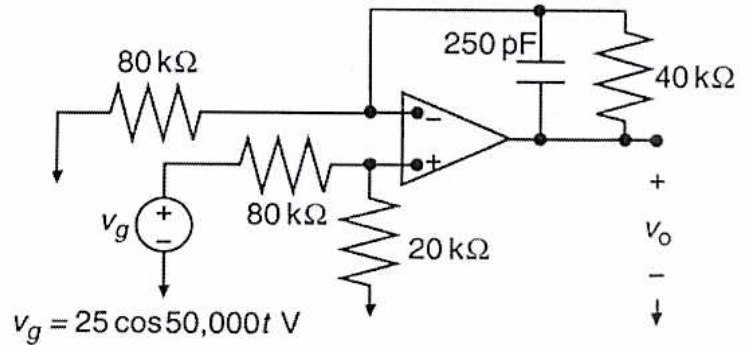The op amp in this circuit is ideal.
Find the steady-state expression for $v_o(t)$.



$$3A. (a) I = \frac{465 \angle 0^\circ}{124 + j93} = 2.4 - j1.8 = 3 \angle -36.87^\circ \text{ A (rms)} \Rightarrow P = (3)^2(4) = \boxed{36 \text{ W}}$$

$$(b) Y_L = \frac{1}{120 + j90} = 5.33 - j4 \text{ mS}; \therefore X_C = \frac{1}{-4 \times 10^{-3}} = \boxed{-250 \Omega}$$

$$(c) Z_L = \frac{1}{5.33 \times 10^{-3}} = \boxed{187.5 \Omega} \quad (d) I = \frac{465 \angle 0^\circ}{191.5 + j3} = 2.43 \angle 0.9^\circ \text{ A} \Rightarrow P = (2.43)^2(4) = \boxed{23.58 \text{ W}}$$

$$(e) \% = \frac{23.58}{36}(100) = \boxed{65.5\%}$$
 Thus, the power loss after the capacitor is added is 65.5% of the power loss before cap. added.

$$3B. V_g = 25 \angle 0^\circ \text{ V} \Rightarrow V_p = \frac{20}{100} V_g = 5 \angle 0^\circ \text{ V} \quad \& \quad V_n = V_p = 5 \angle 0^\circ \text{ V}.$$

$$\frac{5}{80,000} + \frac{5 - V_o}{Z_p} = 0$$

$$Z_p = -j80,000 \parallel 40,000 = 32,000 - j16,000 \Omega$$

$$V_o = \frac{5 Z_p}{80,000} + 5 = 7 - j1 = 7.07 \angle -8.13^\circ \text{ V}$$

$$\Rightarrow \boxed{v_o(t) = 7.07 \cos(50,000t - 8.13^\circ) \text{ V}}$$