

Problem 1: Consider the level shifter circuit shown in Fig. 1 below. It was designed to generate $V_{L,dc} = 1.2V$ across a load resistor, $R_L = 1.2 k\Omega$ by shifting down a constant 2V input by one forward diode drop, $V_{D,ON} = 0.8V$. Assume $T = 300K$.

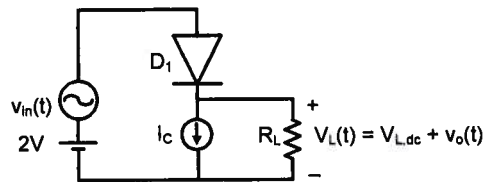


Figure 1

- (a) Calculate the level shifter output, $v_o(t)$, if $v_{in}(t) = 10\sin(10t)$ mV. Assume $I_C = 9mA$.
 (b) What should be the minimum value of I_C such that $|v_o(t)/v_{in}(t)| \geq 0.99$?
 (8 + 12 = 20 points)


Solution:

$$a.) I_C = 9 mA$$

$$I_{R_L} = 1.2V / 1.2k = 1 mA \Rightarrow I_D = 10 mA$$

$$r_d = \frac{26mV}{10 mA} = 2.6 \text{ ohms}$$

Small signal model:

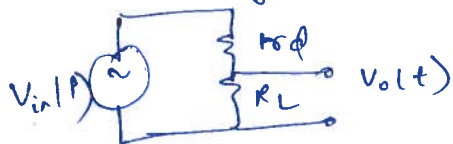

$$v_o(t) = \left(\frac{R_L}{r_d + R_L} \right) (10 mV \sin(10t)) = 9.98 \sin(10t)$$

$$b.) \left| \frac{v_o(t)}{v_{in}(t)} \right| > 0.99 \Rightarrow \frac{R_L}{r_d + R_L} > 0.99$$

$$\Rightarrow r_d < 12.1 \text{ ohms}$$

$$\Rightarrow I_D > 2.14 mA$$

$$\Rightarrow I_C + I_L > 2.14 mA$$

$$\Rightarrow I_C > 2.14 mA - 1 mA > 1.14 mA$$

Problem 2: Consider the circuit shown in Figure 2. Assume that the diodes are identical with $V_{D,ON} = 0.8V$, that $V_{ab}(t) = 5\cos(2\pi \times 10^6 t)$ for all $t \geq 0$, and that all capacitors have zero initial charge.


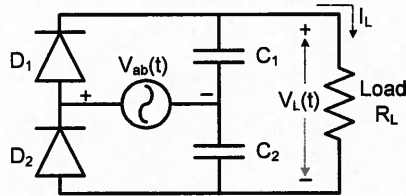


Figure 2


- (a) (3 points) What do you think is the purpose of this circuit? Limit your answer to one sentence.
- (b) (7 points) Sketch the output voltage waveform, $V_L(t)$, for the first two cycles of $V_{ab}(t)$ after $t = 0$. Assume that $C_1 = C_2 = C$ and that the time constant $R_L C$ is much greater than the period of $V_{ab}(t)$.
- (c) (5 points) What is the minimum diode breakdown voltage magnitude to ensure proper operation?
- (d) (10 points) Calculate the ripple in $V_L(t)$ in the steady state, given that $C_1 = C_2 = 100nF$ and $R_L = 100k\Omega$.
- (e) (Bonus question: 10 points) Due to inevitable errors in the printed circuit board assembly process, C_2 ended up being only half of C_1 i.e. $C_1 = 100nF$, but $C_2 = 50nF$. Calculate the new steady state peak-to-peak value of $V_L(t)$.
- Note:** The bonus question will be graded only if you have made non-trivial attempts at all other parts of the Problem #2.

Solution:

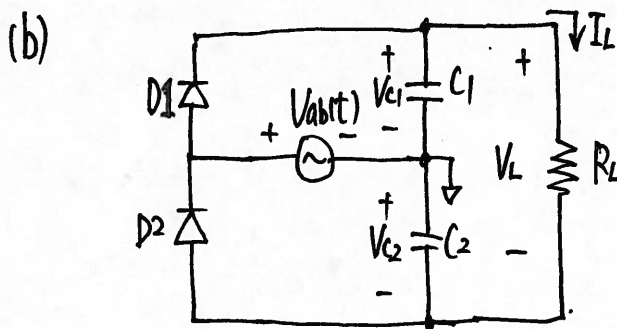(a) This circuit serves as a voltage doubler.



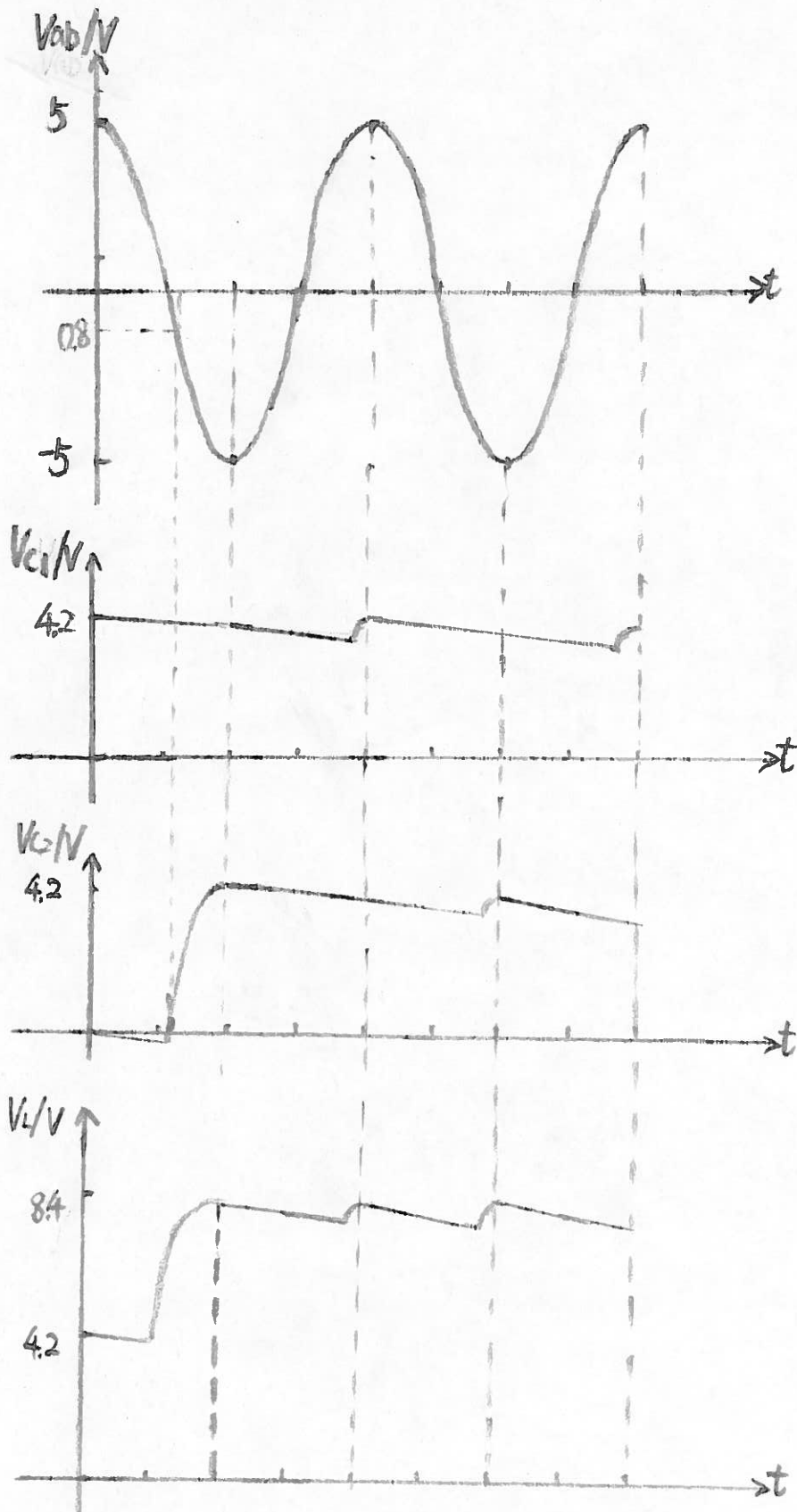A clear way to sketch $V_L(t)$ is to investigate $V_{C1}(t)$ and $V_{C2}(t)$, then add them together since $V_L(t) = V_{C1}(t) + V_{C2}(t)$.



(c) Choose '-' side of $V_{ab}(t)$ as shown in previous figure for convenience. For D1, ~~the~~ $V_{D1,n} \approx 4.2V$ since $V_{c1} \approx 4.2V$ as the ripple of $V_{c1}(t)$ is quite small (will be shown in (d)).

The negative peak voltage of V_{D1} is $-5V$.

Therefore the minimum break voltage for $D1$ should be $9.2V$.

Similarly the minimum break voltage for $D2$ should also be $9.2V$.

(d) From the plots in (b), we know the ripple ~~in~~ V_L is almost the ripple of V_{C1} (V_{C2}).


Since V_L is almost $8.4V$, $I_L = \frac{V_L}{R_L} = \frac{8.4V}{100k\Omega} = 0.084mA$.

The period of V_{ab} is $T = 1\mu s$.

Thus the ripple of V_{C1} (V_{C2}) is

$$\frac{I_L \cdot T}{C_1 \text{ or } C_2} = \frac{0.084 \times 10^{-3} A \times 1 \times 10^{-6} s}{100 \times 10^{-9} F} = 0.84 mV$$

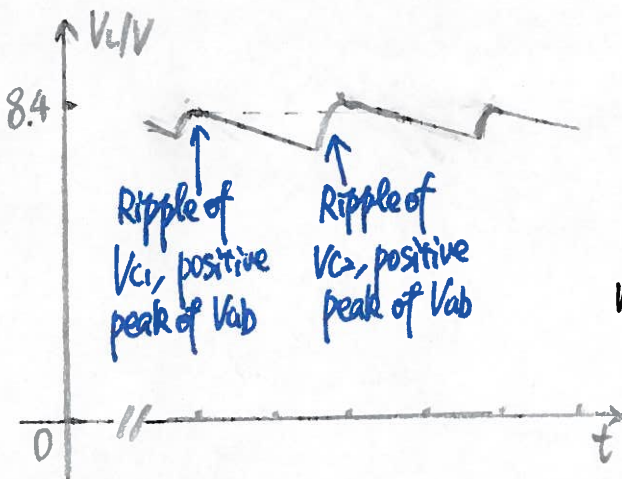(e) With the insight gained from (d), when C_2 decreases to $50nF$, we would expect V_{C2} to show ~~the~~ twice the ripple than V_{C1} . Therefore ~~the~~ ~~shape~~ $V_L(t)$, the superposition of V_{C1} and V_{C2} , is as below (in steady state).



~~We see actually two ripples, the smaller one due to V_{C1}~~

We see two bumps in one period of V_{ab} : the smaller one at the positive peak of V_{ab} for recharging C_1 ; the larger one at the negative peak of V_{ab} for recharging C_2 .

Therefore the ripple of V_L is the ripple of V_{C2} , which is

$$\frac{I_L \cdot T}{C_2} = \frac{0.084 \times 10^{-3} A \times 1 \times 10^{-6} s}{50 \times 10^{-9} F} = 1.68 mV$$

Problem 3: Consider the diode-capacitor circuit shown in Fig. 3. What is the steady state voltage, $V_C(t)$, on the capacitor if the following input is applied to it, assuming $V_{D,ON} = 0$:

$$v_{in}(t) = (1 + m(t))\sin(1000t),$$

where $m(t)$ is a zero mean, square wave of amplitude 0.2, and a period of 1 second?

(5 points)


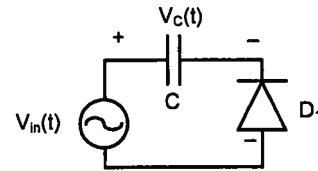
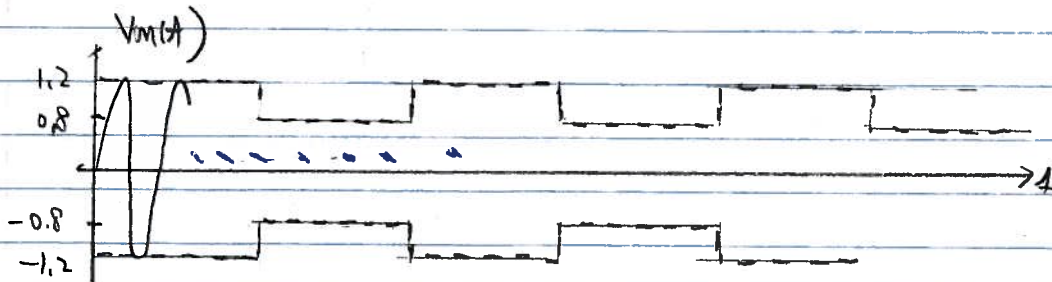
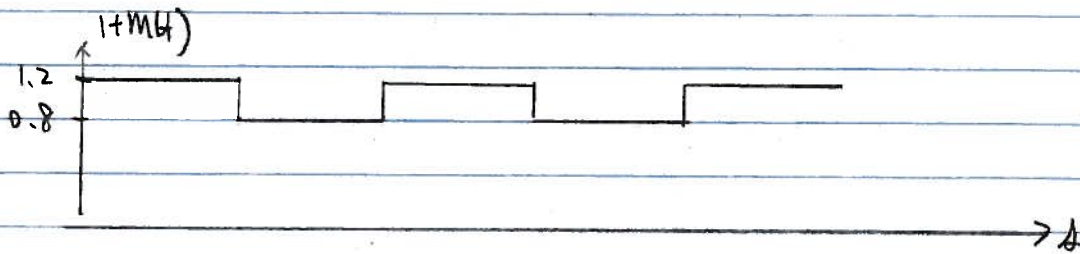


Figure 3

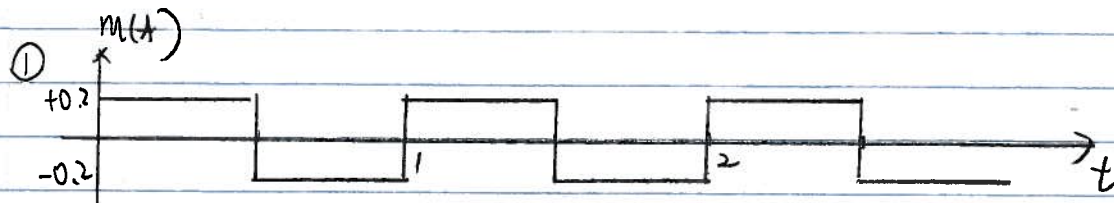

② The most negative value of $V_C(t)$ is $-1.2V$

The steady state $V_C(t)$ is $-1.2V$ ✘