



University of California, Los Angeles
Henry Samueli School of Engineering and Applied Science
Department of Electrical and Computer Engineering

D. Marković

Thu, April 28

EE115C: SPRING 2022—MIDTERM

NAME	<i>Solution</i> Last First
SID	

Please write answers in the boxes provided.

Answers elsewhere will not be graded.

You have 110 minutes.

The test is planned so that you roughly spend 2 minutes per point + 10 minutes to check your answers.

Budget your time properly.

If you get stuck, move on...

Good luck!

Problem 1 ____/10

Problem 2 ____/10


Problem 3 ____/15

Problem 4 ____/15

Total (50)	
-------------------	--

 Problem 1: MOS Transistor – Regions of Operation (10 pts)

Determine the range of V_x for different regions of operation, as indicated in the table below. If a region of operation is not possible, mark the case with DNE (does not exist).



Parameters:

$$|V_{TP}| = 0.2 \text{ V}$$

$$|V_{DSATP}^*| = 0.2 \text{ V}$$

$$V_x \text{ range: } -1 \text{ V} \leq V_x \leq 1 \text{ V}$$

Solution:

V_x is **source** when $V_x > 0.1\text{V}$

V_x is **drain** when $V_x < 0.1\text{V}$


Source: PMOS is cutoff until $V_x > 0.7\text{V}$ (enters “saturation”)
 $V_x > 0.1\text{V}$ @ $V_x = 0.9\text{V}$, PMOS enters V-Sat

Drain: PMOS is cutoff
 $V_x < 0.1\text{V}$

In both of the above scenarios, linear regime DNE when PMOS is on

Cutoff	Linear	“Saturation”	V-Sat
$-1\text{V} \leq V_x \leq 0.7\text{V}$	DNE	$0.7\text{V} \leq V_x \leq 0.9\text{V}$	$0.9\text{V} \leq V_x \leq 1\text{V}$

Problem 2: VTC (10 pts)

 

(a) Calculate V_{OL} and V_{OH} from the VTC. (2 pts)

$$V_{OL} = f(V_{OH}), V_{OH} = f(V_{OL})$$

$$\rightarrow V_{OL} = 0.2V$$

$$\rightarrow V_{OH} = 0.8V$$

$$V_{OL} = 0.2V$$

$$V_{OH} = 0.8V$$

(b) Calculate V_{IL} and V_{IH} from the VTC. (2 pts)

Intersect points with gain = -1

$$\rightarrow V_{IL} = 0.2V$$

$$\rightarrow V_{IH} = 0.6V$$

$$V_{IL} = 0.2V$$

$$V_{IH} = 0.6V$$

(c) Calculate noise margins, NM_L and NM_H . (2 pts)

$$NM_L = V_{IL} - V_{OL} = 0V$$

$$NM_H = V_{OH} - V_{IH} = 0.2V$$

$$NM_L = 0V$$

$$NM_H = 0.2V$$

(d) Estimate the gain in the mid-region of the VTC. (2 pts)

From the VTC geometry

$$\text{gain} = -1.5$$


$$\text{gain} = -1.5$$

(e) Calculate $E_{0 \rightarrow 1}$ if the circuit drives $C_L = 5fF$ at the output. Assume $V_{DD} = 1V$. (2 pts)

$$E_{0 \rightarrow 1} = C_L \cdot V_{DD} \cdot (V_{OH} - V_{OL}) = 3fJ$$

$$E_{0 \rightarrow 1} = 3fJ$$


PROBLEM 3: Elmore Delay (15 pts)

 

In the circuit shown above, a 2-input NAND gate drives an interconnect, which is modeled by the RC network connected to the NAND gate as shown. Calculate τ_{HL} from A to Y when B = 1 and A = 0 \rightarrow 1. Also calculate τ_{HL} from B to Y when A = 1 and B = 0 \rightarrow 1. Are the two time constants different? Briefly (in one sentence) explain why. NMOS transistors have shared diffusion.

Assume: $R_w = 3 \text{ k}\Omega$, $C_w = 5 \text{ fF}$, $R_{on,N} = 2.5 \text{ k}\Omega$ (each NMOS), $R_{on,P} = 3 \text{ k}\Omega$ (each PMOS), also assume $C_{diffusion} = 1.2 \text{ fF}$, $C_{gate} = 2 \text{ fF}$ for all transistors.

 Draw equivalent RC network for A: 0 \rightarrow 1 (3pts)




Elmore delay calculation: (3 pts)

$$\tau_{HL}(A: 0 \rightarrow 1) = 5k \cdot 3.6f + 5k \cdot 10f + 8k \cdot 5f + 11k \cdot 10f = 218ps$$

$\tau_{HL}(A: 0 \rightarrow 1) = 218ps$

 Draw equivalent RC network for B: 0 → 1 (3 pts)



Elmore delay calculation: (3 pts)


$$\tau_{HL}(B: 0 \rightarrow 1) = \tau_{HL}(B: 0 \rightarrow 1) + 2.5k \cdot 1.2f = 218ps + 3ps = 221ps$$

$$\tau_{HL}(B: 0 \rightarrow 1) = 221ps$$

Explain the difference in the two time constants: (3 pts)

The time constant for B:0→1 is larger (by 3ps) since the intermediate node capacitance needs to be discharged.

 Problem 4: Sizing and Dynamic Power (15 pts)




For this question assume a unit inverter of size $W_p = 3\mu m, W_n = 2\mu m, R_N = R_P = R_0$ for the unit inverter, and $C'_{gate} = 2 \frac{fF}{\mu m}, C'_{diffusion} = 1.5 \frac{fF}{\mu m}$ for individual transistors (per μm of transistor width). Assume $V_{DD} = 1V$ and clock frequency of 1GHz.

- (a) Write down the expression for the **logic function F** in terms of A, B, C and D. (2 pts)

$$F = \overline{A \cdot B \cdot C + D}$$

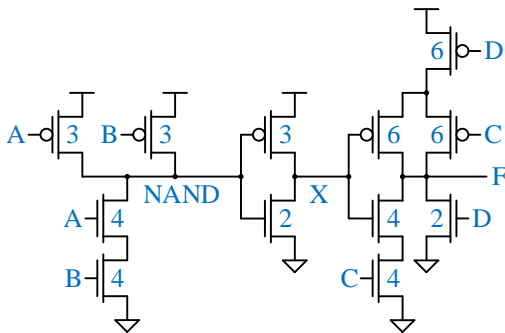- (b) Draw **transistor-level schematic of the whole circuit**. Choose appropriate width for the transistors such that the worst-case pull-up and pull-down strength matches that of a unit inverter. **Annotate the transistor width (in μm) on the schematic.** (3 pts)



(c) Calculate the switching probability $\alpha_{0 \rightarrow 1}$ at X and F if all inputs have a probability of logic “1” equal to 0.5, i.e. $p(A=1) = p(B=1) = p(C=1) = p(D=1) = 0.5$. (4 pts)

$$p(X = 1) = p(A = 1) \cdot p(B = 1) = \frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$$

$$\alpha_{X:0 \rightarrow 1} = p(X = 0) \cdot p(X = 1) = \frac{3}{4} \cdot \frac{1}{4} = \frac{3}{16}$$

$$p(F = 1) = p(D = 0) \cdot (1 - p(C = 1) \cdot p(X = 1)) = \frac{1}{2} \cdot \left(1 - \frac{1}{2} \cdot \frac{1}{4}\right) = \frac{7}{16}$$

$$\alpha_{F:0 \rightarrow 1} = p(F = 0) \cdot p(F = 1) = \frac{9}{16} \cdot \frac{7}{16} = \frac{63}{256}$$

Node	X	F
$\alpha_{0 \rightarrow 1}$	3/16 (0.1875)	63/256 (0.246)

(d) Calculate the total average switching power $P_{sw,tot}$ (neglect short-circuit) dissipated by the circuit. Ignore inter-node (diffusion) capacitance inside the stacks. Consider $C_{diffusion}$ and C_{gate} at the output of the NAND (inside the AND gate), nodes X and F . Tabulate node capacitance at each of the nodes in the table provided below. (6 pts)

$$C_{NAND} = 5 \cdot C'_{gate} + 10 \cdot C'_{diffusion} = 25fF$$

$$C_X = 10 \cdot C'_{gate} + 5 \cdot C'_{diffusion} = 27.5fF$$

$$C_F = 18 \cdot C'_{diffusion} = 27fF$$

Node	C_{node} [fF]
NAND	25
X	27.5
F	27

From (c): $\alpha_{NAND:0 \rightarrow 1} = \alpha_{X:0 \rightarrow 1} = \frac{3}{16}$, $\alpha_{F:0 \rightarrow 1} = \frac{63}{256}$

$$P_{sw,NAND} = \alpha_{NAND:0 \rightarrow 1} \cdot f_{clk} \cdot C_{NAND} \cdot V_{DD}^2 = 4.69\mu W$$

$$P_{sw,X} = \alpha_{X:0 \rightarrow 1} \cdot f_{clk} \cdot C_X \cdot V_{DD}^2 = 5.16\mu W$$

$$P_{sw,F} = \alpha_{F:0 \rightarrow 1} \cdot f_{clk} \cdot C_F \cdot V_{DD}^2 = 6.64\mu W$$

$$P_{sw,tot} = P_{sw,NAND} + P_{sw,X} + P_{sw,F}$$

$$P_{sw,tot} = 16.49 \mu W$$