EEM16 Midterm

MELODY SZE WEI CHEN

TOTAL POINTS

64 / 80

QUESTION 1 Problem 120 pts

1.1 (a-c) **9 / 12**

✓ - 1 pts Question1 (a): 4 pts. Missing, or having 1 extra prime implicants ✓ - 2 pts Question1 (c): 4 pts. Missing or having extra

terms

 This "1X" is also a prime implicant, since it is also **1** the largest circle can be drawn to cover this 1.

1.2 (d-f) **4 / 8**

✓ - 2 pts Question1 (e): 2 pts. ✓ - 1 pts Question1 (f): 3 pts. Incorrect hazard condition ✓ - 1 pts Question1 (f): 3 pts. Incorrect term to remove the risk.

QUESTION 2

2 Problem 2 **17 / 20**

✓ - 3 pts (c) not using the fewest NOR (7 gates)

QUESTION 3

3 Problem 3 **20 / 20**

✓ - 0 pts Correct

QUESTION 4

Problem 4 20 pts

4.1 (a) **8 / 8**

✓ - 0 pts Correct

4.2 (b) **3 / 5**

✓ - 5 pts incorrect

+ 3 Point adjustment

 \bullet

partial... shouldn't split into 2 groups of 8.

4.3 (c) **3 / 7**

✓ - 4 pts incorrect separation into 2 one-hot

Ill gradescope

Prof. C.K. Yang

Midterm Exam

Name (Last, First): Melody Chen 705120273 Student Id #:

Do not start working until instructed to do so.

- 1. You must answer in the **space provided** for answers after every question. We will ignore answers written anywhere else in the booklet. All pages in this booklet must be accounted for otherwise it will not be graded.
- 2. You are permitted 1 page of notes 8.5x11 (front and back).
- 3. You may not use any electronic device.

Following table to be filled by course staff only

Question #1

Consider the following Karnaugh Map for the Boolean function, Y. A blank truth table is provided for your convenience.

Prof. C.K. Yang

(d) Express as a minimal sum of product, $\neg Y$.

(f) If the logic is implemented using its minimal sum-of-product expression, is there a risk of a static hazard? Circle one: Yes **No**

 $\label{eq:2.1} \begin{array}{ccccc} \eta & g & & \mathbb{R}^3 & & \mathbb{R}_{\left[\frac{1}{2},\frac{1}{2}\right]} & & \mathbb{R}_{\left[\frac{1}{2},\frac{1}{2}\right]} \end{array}$

Under what input conditions?

What product term(s) would you add to remove the risk? <u>Hue GNUS</u> WHM don't could

UCLA | ECEM16/CSM51A | Spring 2019 Question #2

P

Prof. C.K. Yang

(a) Rewrite the following Boolean equation as a sum-of-products or product-of-sum. Hint: apply DeMorgan's theorem.

Answer:
$$
W = \sqrt{(CV(a \land \neg b))} \lor (d \land \neg e)
$$

\nAnswer: $W = (CV(a \land \neg b)) \land (d \land \neg e) = ((V(\overline{a} \lor b)) \land (\overline{a} \lor e)$.

$$
w = (CVaVb)NGVe
$$

(b) Rewrite the following Boolean equation as a sum-of-products or product-of-sum.

Answer:
$$
\frac{x}{x} = \frac{((\sqrt{a}) \cdot \sqrt{(\sqrt{b})})(\sqrt{d} \cdot \sqrt{e})}{(\sqrt{(\sqrt{a})})(\sqrt{(\sqrt{b})})(\
$$

UCLA | ECEM16/CSM51A | Spring 2019 Prof. C.K. Yang Question #3 The following 12-bit word can be used to represent different numbers depending on the encoding 12b'1011_1101_0110 = 300

(a) If the world is 2's comptement, what is the corresponding integer? - 066. (b) If we convert the word into base-4, what's the represented number? $413030 = 2$
1- $\frac{189}{189}$ (c) If we take answer in (b), write the 3's complement of the base-4 number. (d) If the word is unsigned fixed point 6.6, what is the corresponding number? $0/10(10.11-110)$ What is the absolute accuracy of this representation? $\frac{18}{18} \times 10^{-3}$ $\frac{(01)}{(11)}$ $\frac{(101)}{(101)}$ $\frac{(0110)}{(0110)}$ (e) What is this word in Hexadecimal? **BD** (f) If the word is 6E5 floating point number (IEEE format S+EEEEE+MMMMMM), R What is the corresponding real number? $\frac{1.3475}{1.3475}$ $\frac{1}{5.9}$ 0 11 11 0 10 10 (g) In base-20 system and using 3 "vigits" (base-20 digits) in 20's complement: $E = \sqrt{2\pi}$ How would one represent a base-10 integer -1616? $5.19.4$ Vhat is the most positive value in base-10 integer that can be represented? 1.010110 × 2 E-bias $20\sqrt{\frac{616716}{80}}$

UCLA | ECEM16/CSM51A | Spring 2019 Question #4

Prof. C.K. Yang

(a) Two 4-bit binary inputs, $b1[3:0]$ and $b2[3:0]$, are needs to be decoded into a single 2-hot output vector, twoh[15:0]. This 2-hot vector has up to two positions of 1's and the remainder are 0's. If b1 is the same as b2, then only a single 1 is asserted. Design this logic. You may use 2:4 Decoders as building blocks and any number of AND, OR, or INV gates. Try to minimize the amount you use. You may describe connections to avoid an overly complex drawing of every signal and line.

ore indice for $201000 + 1$ 515.0 16 decode into one not, $b1[3.2]$ $1bh(F)$ twonfis] $61[1:0]$ Imf_{41} $-woV142$. 151 161 $\{$ $16h(x)$ $\frac{1}{2}$ ζ $\vert \vert$ 01 Skepeat this for ba[3:0] $2bhLf$ ζ $\overline{4}$ 266 $25h$ ら $bə[3:3]^{+}$ $\overline{\mathbf{C}}$ $h_{2}[1:0]+$ $\mathbf 0$ want to output one 6 of 8

 \mathcal{C}

 $\left\{ \right.$

Prof. C.K. Yang

(b) Next, you are tasked to code the twoh[15:0] signals into a vector that indicates a range, similar to a thermometer code. The 16-bit input, twoh[15:0], produces 16-bit outputs, rangeh[15:0], whereby the positions in between the 2 asserted signals of the twoh[15:0] are all $1's.$ For instance, with b1[3:0]=4'b0110 and b2[3:0]=4'b0010, rangeh[15:0]=16b'0000_0000_0011_1110. You may use any building block we have covered in lecture as well as any number of AND, OR, or INV gates. Again you can describe connections to avoid drawing every signal and line.

\n $\begin{array}{r}\n 2.5\overline{0} \\ 1.0\n \end{array}$ \n	\n $\begin{array}{r}\n 2.5\overline{0} \\ 3.0\n \end{array}$ \n										
\n $\begin{array}{r}\n 2.5\overline{0} \\ 3.0\n \end{array}$ \n											
\n $\begin{array}{r}\n 2.5\overline{0} \\ 3.0\n \end{array}$ \n	\n $\begin{array}{r}\n 2.5\overline{0} \\ 3.0\n \end{array}$ \n	\n<									

Prof. C.K. Yang

(c) Finally, encode inverse the function of (a) by accepting the twoh[15:0] signal as input and output 2 binary values bo1[3:0] and bo2[3:0] to indicate the binary position of the two hot bits. You may use any building block we have covered in lecture as well as any number of AND, OR, or INV gates. Again you can describe connections to avoid drawing every signal and line.

 $b02[3.0]$. t_{w} oh [15:8] $8 - 4$ $T_{w0}h[7=0]$ ily
avator b_0 2[3 $5\sqrt{1}$ O twon[7:0]