

check 2 & 3

Problem 1 (10 points)

Reduce the following expression using Boolean algebra postulates and theorems. Show intermediate steps and mention the rules used at each step.

$$f(w, x, y, z) = \overline{\overline{xy}} + z + z + xy + wz$$

$$\begin{aligned} & \overline{\overline{xy}} + z + z + xy + wz \\ & (x+y)\overline{\overline{z}} + z + xy + wz \\ & x\overline{\overline{z}} + y\overline{\overline{z}} + z + xy + wz \\ & z + wz + xy + x\overline{\overline{z}} + y\overline{\overline{z}} \\ & z + xy + x\overline{\overline{z}} + y\overline{\overline{z}} \\ & z + xy\overline{\overline{z}} + xy\overline{\overline{z}} + x\overline{\overline{z}} + y\overline{\overline{z}} \\ & z(1+xy) + \overline{\overline{z}}(xy+x+y) \\ & z(1) + \overline{\overline{z}}(x+y) \\ & z + \overline{\overline{z}}(x+y) \\ & (\overline{\overline{z}})(z + \overline{\overline{z}}) \\ & (\overline{\overline{z}}z + \overline{\overline{z}}\overline{\overline{z}}) \\ & (0 + \overline{\overline{z}}\overline{\overline{z}}) \\ & (\overline{\overline{z}}\overline{\overline{z}}) \\ & z + x + y \\ & \boxed{x + y + z} \end{aligned}$$


DeMorgan's
distributive
commutative
absorption
combining (reverse)

distributive
absorption ($1+a=a$)
double complement
(identity)

DeMorgan's
distributive
identity ($aa'=0$)
identity ($0+a=a$)

DeMorgan's
commutative

to check

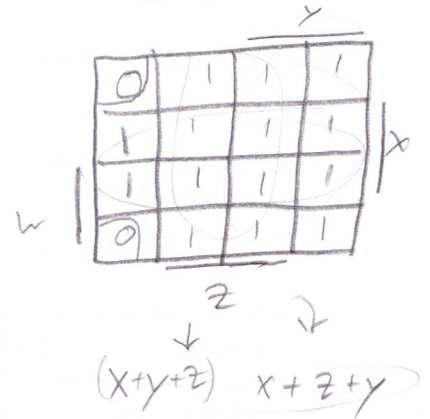

✓ 10

A faint handwritten table with two columns and approximately 6 rows. The text is illegible due to fading. The table appears to be a data table or a list of items.

Faint handwritten text, possibly a list or notes, covering the lower half of the page. The text is mostly illegible.


15

Problem 2 (15 points)


Consider the following function

$$f(a, b, c, d) = \Sigma m(1, 3, 4, 9, 11, 13).$$

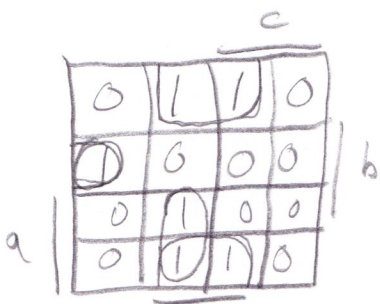- (a) (8 points) Use K-maps to minimize **both** the sum of products and products of sums form. Write the simplified Boolean expressions.
- (b) (7 points) Implement the function using minimal number of gates. You can use either NOR gates or NAND gates with maximum number of four inputs. Assume that inputs are available in both uncomplemented and complemented form.



SOP

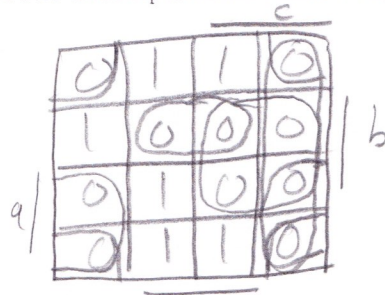

POS

$(c' + d)$ is not essential & not needed

$$b'd + ac'd + a'bc'd'$$


Sum of products

3 ands, 1 or
↓
4 nands

$$(b+d)(a'+d)(b'+c')(a+b'+d')$$

product of sums

4 or's, 1 and
↓
5 nands

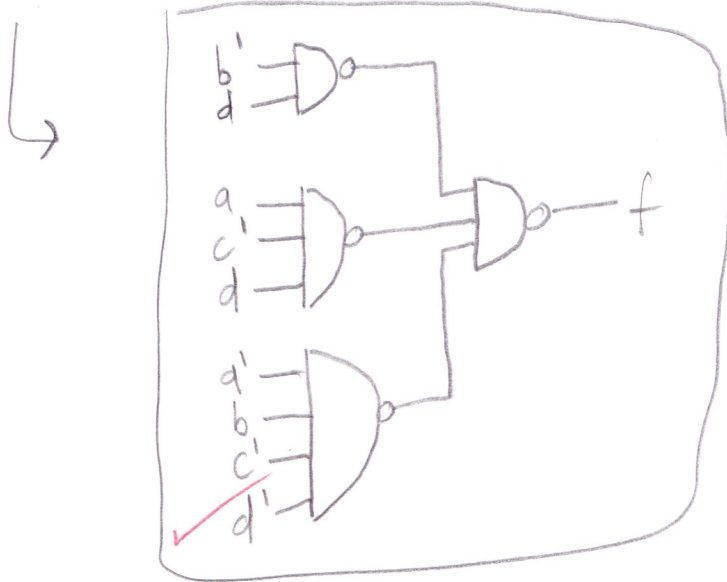

$$\overline{b'd + ac'd + a'bc'd'}$$

$$(\overline{b'd})(\overline{ac'd})(\overline{a'bc'd'}) \rightarrow \text{nand-nand}$$

[Faint, illegible handwritten text, likely bleed-through from the reverse side of the page.]


Problem 3 (20 points)

Consider the following function

$$f(a, b, c, d) = \overline{(ab + d)}(\overline{b + d})$$

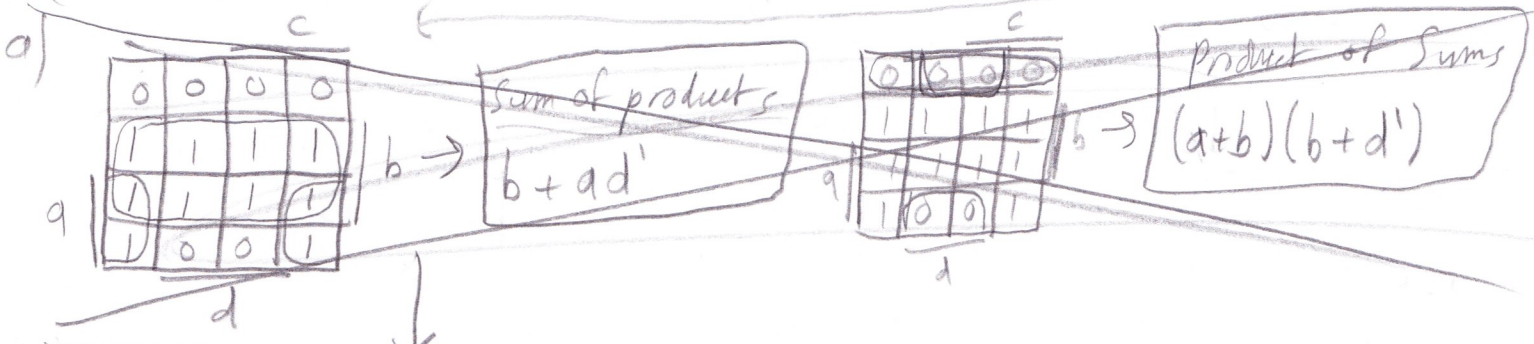- (a) (6 points) Find minimal sum-of-products and products-of-sums expressions for the switching expression f .
- (b) (8 points) Determine the prime implicants and the essential prime implicants for this expression.
- (c) (6 points) Does this function have a unique minimal sum-of-products? If not, list any other minimal sum-of-products expressions. Does this function have a unique minimal product-of-sums? If not, list any other minimal product-of-sums expressions.

$$\overline{(ab + d)}(\overline{b + d}) = \overline{(ab + d)} + (\overline{b + d}) = (a + \overline{b}) \cdot \overline{d} + (\overline{bd}) = a\overline{d} + \overline{b}\overline{d} + \overline{bd}$$



b) Prime implicants: b, ad'
 Essential prime implicants: b, ad'

← both are prime & contain minterms not included in any other implicant

c) This function has a unique minimal sum-of-products & product-of-sums.

↑
 Due to all the prime implicants & implicates being essential.

correct a & b are on other page

a) $\begin{array}{c} \text{c} \\ \begin{array}{|c|c|c|c|} \hline 1 & 0 & 0 & 1 \\ \hline 0 & 1 & 1 & 0 \\ \hline 1 & 1 & 1 & 1 \\ \hline 1 & 0 & 0 & 1 \\ \hline \end{array} \\ \text{d} \end{array} \Big| \begin{array}{c} \text{b} \\ \text{a} \end{array} \rightarrow \boxed{\begin{array}{l} \text{sum of products} \\ bd + \bar{b}\bar{d} + a\bar{d} \end{array}} \checkmark$


a) $\begin{array}{c} \text{d} \text{ c} \\ \begin{array}{|c|c|c|c|} \hline 1 & 0 & 0 & 1 \\ \hline 0 & 1 & 1 & 0 \\ \hline 1 & 1 & 1 & 1 \\ \hline 1 & 0 & 0 & 1 \\ \hline \end{array} \\ \text{d} \end{array} \Big| \begin{array}{c} \text{b} \\ \text{a} \end{array} \rightarrow \boxed{\begin{array}{l} \text{product of sums} \\ (b+d') \cdot (a+b'+d) \end{array}} \checkmark$

b) prime implicants: $bd, \bar{b}\bar{d}, a\bar{d}, ab$ \leftarrow all are prime & essential
 EP I: $bd, \bar{b}\bar{d}, a\bar{d}$ \times

c) see first page

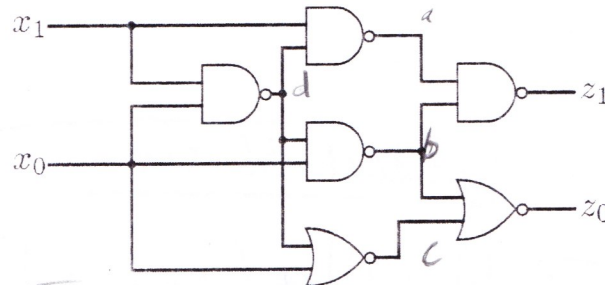Problem 4 (10 points)

10 Analyze the NAND-NOR network shown in the figure below. Obtain switching expressions for the outputs.



$$z_1 = \overline{ab} = \overline{(x_1 d)(x_0 d)} = x_1 d + x_0 d = d(x_1 + x_0) = \overline{x_0 x_1} (x_1 + x_0)$$

$$= (\overline{x_0} + \overline{x_1})(x_0 + x_1)$$

$$= (\overline{x_0} + \overline{x_1})x_0 + (\overline{x_0} + \overline{x_1})x_1$$

$$= \overline{x_0}x_0 + \overline{x_1}x_0 + \overline{x_0}x_1 + \overline{x_1}x_1$$

$$= 0 + x_0\overline{x_1} + \overline{x_0}x_1 + 0$$

$$= x_0\overline{x_1} + \overline{x_0}x_1$$

$$= x_0 \oplus x_1 = z_1$$

$$z_0 = \overline{b+c}$$

$$a = \overline{x_1 d} = \overline{x_1 (x_0 x_1)} = \overline{x_1} + (x_0 x_1)$$

$$b = \overline{x_0 d} = \overline{x_0 (x_0 x_1)} = \overline{x_0} + (x_0 x_1)$$

$$c = \overline{x_0 + d} = \overline{x_0 + (x_0 x_1)} = \overline{x_0} (x_0 x_1)$$

$$d = \overline{x_0 x_1}$$

$$\rightarrow z_0 = \overline{x_0 d + x_0 + d} = \overline{(x_0 d)(x_0 + d)} = x_0 x_0 d + x_0 d d = x_0 d + x_0 d = x_0 d$$

$$x_0 (\overline{x_0 x_1}) = x_0 (\overline{x_0} + \overline{x_1}) = x_0 \overline{x_0} + x_0 \overline{x_1} = 0 + x_0 \overline{x_1}$$

$$= x_0 \overline{x_1}$$


$$z_1 = x_0 \overline{x_1} + \overline{x_0} x_1 = x_0 \oplus x_1$$

$$z_0 = x_0 \overline{x_1}$$

[Faint handwritten notes and diagrams, possibly related to a circuit or system analysis, are visible but illegible due to low contrast.]

Problem 5 (15 points)

Consider the two circuits

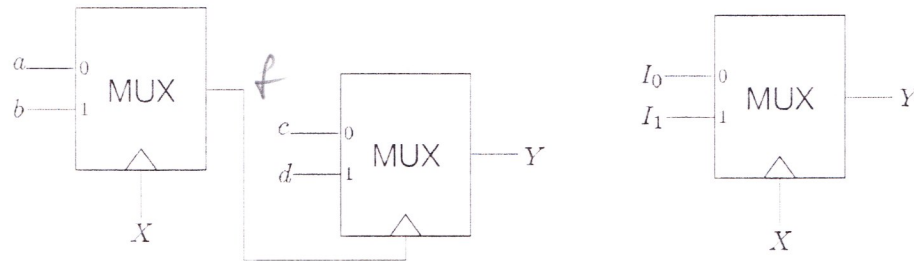(a) (8 points) Find I_0, I_1 , so that both circuits are equivalent.(b) (7 points) Write the Boolean expression of Y in terms of X, a, b, c , and d .a) left side

$$Y = c\bar{f} + df$$

$$f = a\bar{X} + bX$$

$$Y = c(a\bar{X} + bX) + d(a\bar{X} + bX)$$

$$= ca\bar{X} + cbX + da\bar{X} + dbX$$

$$= (ca + da)\bar{X} + (cb + db)X$$

$$I_0\bar{X} + I_1X = (ca + da)\bar{X} + (cb + db)X$$

$$b) \quad Y = ca\bar{X} + cbX + da\bar{X} + dbX$$

(from part A)

right side

$$Y = I_0\bar{X} + I_1X$$

$$\begin{aligned} I_0 &= ca + da = a(c+d) \\ I_1 &= cd + db = d(c+b) \end{aligned}$$

a) 4

b) 3

[Faint handwritten notes, possibly including a diagram or equations, are visible in this area.]

15 Problem 6 (15 points)

Design a combinational network that has a three-bit input x representing the digits 0 to 7, and a three-bit output y representing the same set of integers. The function of the system is


$$y = (3x + 1) \pmod{8}$$

Use a binary decoder, a binary encoder, and ~~(one or more)~~ OR gates.

| X | Y |
|---|---|
| 0 | 1 |
| 1 | 4 |
| 2 | 7 |
| 3 | 2 |
| 4 | 5 |
| 5 | 0 |
| 6 | 3 |
| 7 | 6 |

$(0+1) \pmod{8} = 1$
 $(3+1) \pmod{8} = 4$
 etc.
 $(6+1) \pmod{8} \rightarrow 7$
 $(9+1) \pmod{8} \rightarrow 10 \pmod{8} = 2$
 $(12+1) \pmod{8} \rightarrow 13 \pmod{8} = 5$
 $(15+1) \pmod{8} \rightarrow 16 \pmod{8} = 0$
 $(18+1) \pmod{8} \rightarrow 19 \pmod{8} = 3$
 $(21+1) \pmod{8} \rightarrow 22 \pmod{8} = 6$

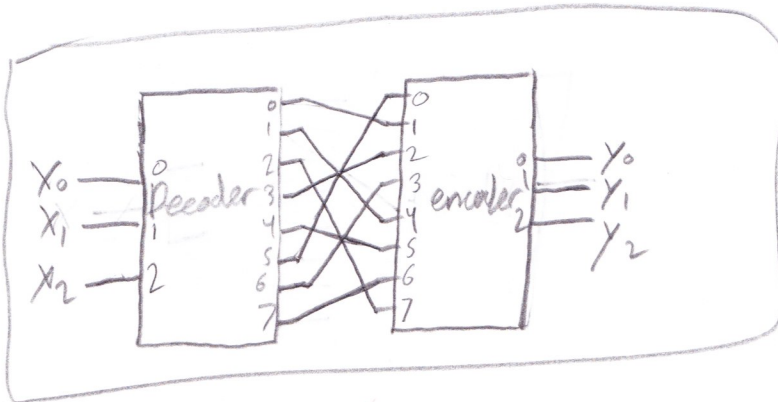Simply remap to this using the decoder & encoder



[Faint, illegible handwritten text covering the majority of the page]

Problem 7 (15 points)

Compute $z = a + 2b - c$ in 2's complement for $a = -7$, $b = 12$, and $c = -97$. Perform calculations on bit-vectors representing a , b , and c and show every step of your work. How many bits should z have to represent the correct result? Check your work by showing, for each step, the corresponding values in decimal number system.

$$z = a + 2b - c$$

$$z = -7 + 2(12) - (-97)$$

$$z = -7 + 24 + 97$$

$$z = 24 + 90$$

$$z = 114$$

$a = -7 = \text{neg}(0000\ 0111) = 1111\ 1000 + 1 = 1111\ 1001 = -7$
 $b = 12 = 0000\ 1100 = b$
 $c = -97 = \text{neg}(0110\ 0001) = 1001\ 1110 + 1 = 1001\ 1111 = -97$
 $12 = 64 + 32 + 16 + 8 + 4 + 2 + 1$

in 2's complement, will need **8 bits**
 8 bits \rightarrow 127 to -128 \rightarrow enough to represent 114

$$z = a + 2b - c$$

$$z = a + b(\text{bit shifted left by 1}) + (-c)$$

$$= 1111\ 1001$$

$$+ 0001\ 1000$$

$$= -7$$

$$+ 24$$

$$= 17$$

$1001\ 1111$ $\xrightarrow{\text{invert bits \& add 1}}$ $0110\ 0000 + 1$
 $0110\ 0001$
 $= 97$

$$z = 17 + (-c)$$

$$z = 17 + (-(-97))$$

$$z = 17 + 97$$

$$z = 114$$

correct

$$0111\ 0010 = 64 + 32 + 16 + 2 = 80 + 34 = 114$$

8 bits

15

