

Question 1: Number System Conversion

Find the value of x in the following equations. Show your work for credit.

a) $15670_8 = x_{16}$

$001 \mid 101 \quad 110 \quad 111 \quad 000$ $0001 \quad 1011 \quad 1011 \quad 1000$ $x_{16} = 1BB8$

b) $277_{10} = x_8$

$\begin{array}{r} 34 \\ 8 \overline{) 277} \\ -24 \\ \hline 37 \\ -32 \\ \hline 5 \end{array} \quad \begin{array}{r} 4 \\ 8 \overline{) 34} \\ -32 \\ \hline 2 \\ \end{array} \quad \begin{array}{r} 0 \\ 8 \overline{) 4} \\ -0 \\ \hline 4 \end{array}$ $x_8 = 425$

Question 2: Universal Set

Show that the set {XNOR, OR} is a universal. You can use the constant 0.

XNOR	0	1
0	1	0
1	0	1

$$z = x_1 x_0 + x_1' x_0'$$

$$x_0 = 0 \quad z = x_1 0 + x_1' \cdot 1 = x_1'$$

known universal set { NOT, OR }

To implement NOT

$$\text{XNOR}(x, 0) = x'$$

$$\circ \overline{x} \overline{\overline{x}} - x'$$

$$\text{OR} = \text{OR}$$

thus { XNOR, OR } is an universal set because it can implement a known universal set { NOT, OR }.

Question 3: Boolean Algebra

a) Find the minimal representation of the following Boolean function. Show your work for credit.

$$f = a' + a(a'b + b'c)'$$

$$\begin{aligned}
 f &= a' + a(a'b')(b'c') \\
 &= a' + a(a+b')(b+c') \\
 &= a' + (a+ab')(b+c') \\
 &= a' + ab + ac' + ab'c' \\
 &= a' + a(b+c' + b'c') \\
 &= a' + a(b+c+c') \\
 &= a' + a(b+c)
 \end{aligned}$$

$$f = a' + b + c'$$



b) Find all the minterms for the following switching expression. Show your work for credit.

$$F(a, b, c, d) = ((bd + b')' + ac)'$$

$$\begin{aligned}
 F(a, b, c, d) &= ((bd + b')' + ac)' \\
 &= ((bd)'(b')' + ac)' \\
 &= ((b' + d')(b) + ac)' \\
 &= (bd' + ac)' \\
 &= (bd')'(ac)' \\
 &= (b' + d)(a' + c') \\
 &= a'b' + b'c' + a'd + c'd \\
 &= a'b'(c + c') + (a + a')b'c'
 \end{aligned}$$

$a'b'$	$a'b'c$	$a'b'c'd$	3
	$a'b'c'$	$a'b'c'd'$	2
	$a'b'c'$	$a'b'c'd$	1
		$a'b'c'd'$	0
$b'c'$	$ab'c'$	$ab'c'd$	9
	$a'b'c'$	$ab'c'd'$	8
	$a'b'c'$	$a'b'c'd$	1
		$a'b'c'd'$	0
$a'd$	$a'bd$	$a'bcd$	7
	$a'b'd$	$a'bcd$	5
		$a'b'cd$	3
		$a'b'c'd$	1
$c'd$	$ac'd$	$abc'd$	13
	$a'c'd$	$ab'c'd$	9
		$a'b'c'd$	5
		$a'b'c'd$	1

$$= a'b'c + a'b'c' + ab'c' + \cancel{ab'c'd'} + a'bd' + a'b'd' + ac'd + a'c'd$$

$$= a'b'cd + a'b'cd' + a'b'c'd + a'b'c'd' + ab'c'd + ab'c'd' + a'b'cd' +$$

$$a'b'c'd' + ab'c'd' + ab'c'd' + ab'c'd + ab'c'd + a'b'c'd + a'bc'd +$$


$$a'bc'd.$$

$\sum m(0,1,2,3,5,7,8,9,13)$

Question 4: Multiplexers

Implement the $f(a, b, c, d) = \text{one-set}(0, 1, 3, 4, 5, 7, 8, 9, 11, 12, 13, 15)$ using the smallest number of multiplexers. Note that no other gates are available, but use can use the constants 0 and 1. For credit show your work.

<u>a, b, c, d</u>	<u>f</u>
0 0 0 0	1
1 0 0 1	1
2 0 0 1 0	0
3 0 0 1 1	1
4 0 1 0 0	1
5 0 1 0 1	1
6 0 1 1 0	0
7 0 1 1 1	1
8 1 0 0 0	1
9 1 0 0 1	1
10 1 0 1 0	0
11 1 0 1 1	1
12 1 1 0 0	1
13 1 1 0 1	1
14 1 1 1 0	0
15 1 1 1 1	1

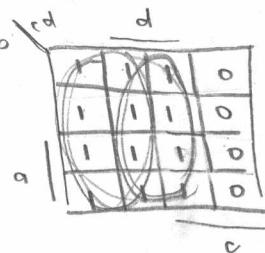


$$z = c' + d$$

$$z = c' + d$$

$$= (1)d + (c')d'$$

$$z = (1)d + (0c + 1c')d'$$

15

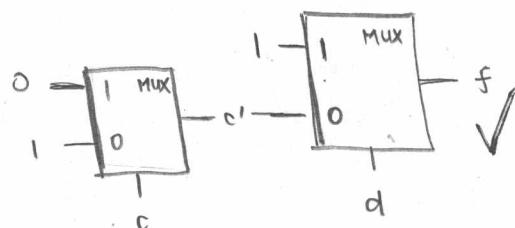

$$z = x_1 s + x_0 s'$$

$$z = 0c + 1c' = c'$$

25

Question 5: NOR-NOR network

Give a minimal NOR-NOR network that implements functionality $x(x_1, x_0) \bmod y(y_1, y_0) = r(r_1, r_0)$. For example if $x=11$ and $y=10$, the $r=01$. That is 3 modulo 2 is 1. Division by 0 will never be requested.


a) Provide the truth table.

$x_1 x_0$	$y_1 y_0$	$r_1 r_0$
0 0	0 0	--
0 0	0 1	0 0
0 0	1 0	0 0
0 0	1 1	0 0
0 1	0 0	--
0 1	0 1	0 0
0 1	1 0	0 1
0 1	1 1	0 1
1 0	0 0	--
1 0	0 1	0 0
1 0	1 0	0 0
1 0	1 1	1 0
1 1	0 0	--
1 1	0 1	0 0
1 1	1 0	0 1
1 1	1 1	0 0

$x \bmod y = r$

✓

b) Provide the k-maps.

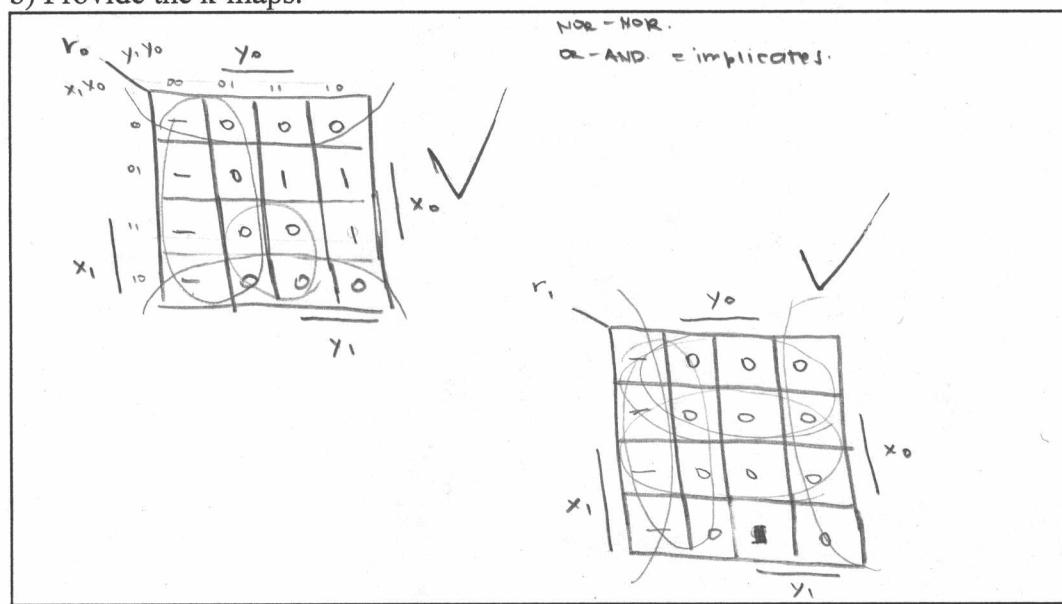



c) Provide the switching expressions.

$$r_0 = (x_0)(y_1) \underline{(x_1' + y_0')}$$

$$r_1 = \underline{(x_1)(x_0')(y_1)(y_0)}$$

✓


d) Provide the NOR-NOR network. Assume you have the negation of the input bits available.

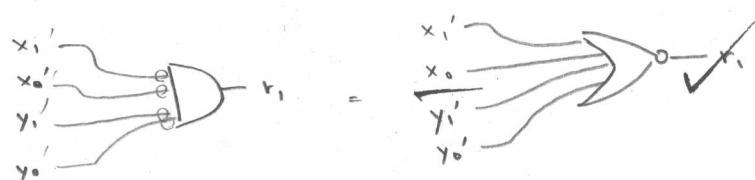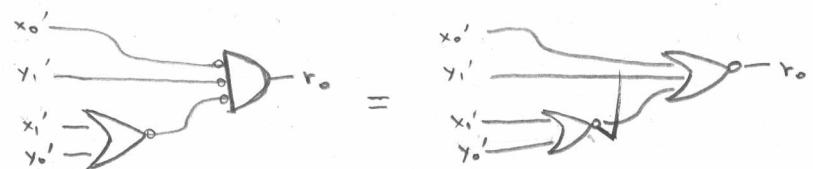

Question 6: State Diagram

Design a Mealy state diagram for a digital lock with the following functionality. Assume that there are two push-buttons, A and B, that are available to enter the combination, and you are guaranteed that the buttons can not be activated simultaneously.

- a. The combination is A-A-B-A-B-A. If this sequence is correctly entered, an output signal is asserted that causes the lock to open.
 - b. For any state, three B pulses in a row should reset to the initial state.

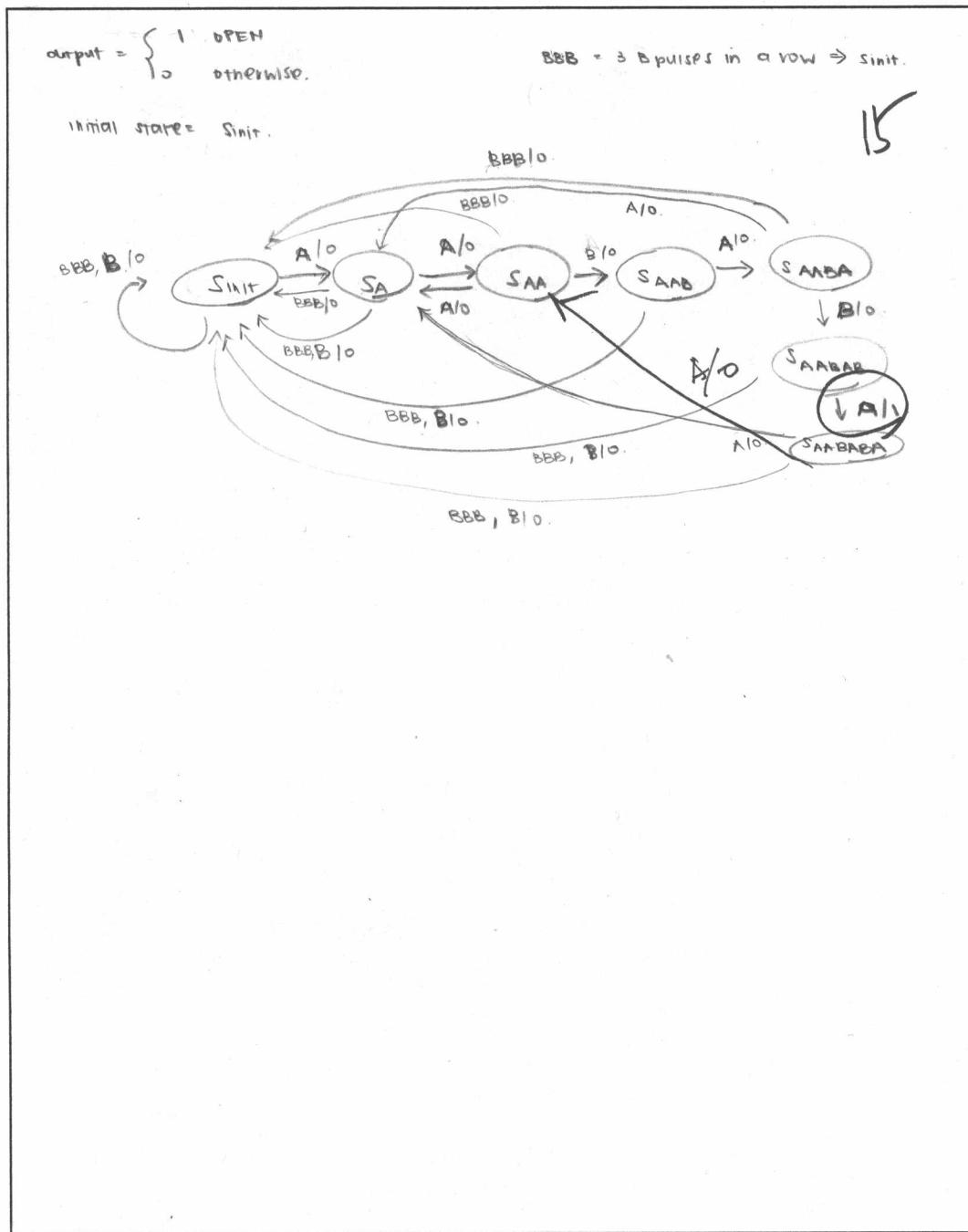

Question 7: State Table Minimization

Reduce the state table shown below and show the equivalent minimal state table. Show all the steps for credit.

Present State	State Inputs	
	x=a	x=b
A	B, 0	C, 0
B	D, 0	E, 0
C	F, 0	G, 0
D	D, 0	G, 0
E	F, 0	G, 0
F	D, 0	E, 1
G	F, 0	G, 0

Group 1: A, B, C, D, E, G.

Group 2: F

	A	B	C	D	E	G	F
x=a	1	1	2	1	2	2	
x=b	1	1	1	1	1	1	

Group 1 : ABD.

Group 2 : CEG

Group 3 : F.

	A	B	D	C	E	G	F
x=a	1	1	1	3	3	3	
x=b	2	2	2	2	2	2	

STOP.

MINIMIZED GROUPS:

Group 1 : ABD

Group 2 : C, E, G

Group 3 : F.

Minimized Table.

PS	Input	
	x=a	x=b
1	1, 0	2, 0
2	3, 0	2, 0
3	1, 0	2, 1
	NS, Output	

