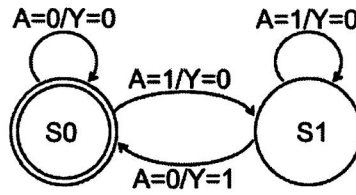


This page is left intentionally blank and can be used for scratch work.

Consider the following sequential machine with input A, output Y, and two states S1 and S0.



- (a) If you encode these 2 states with a single state variable, Q, where Q=1 corresponds to S1 and Q=0 corresponds to S0. Write **down Boolean equations** for next state (Q_{next}), and output Y as function of the inputs (Q and A). Show your work (i.e. with a truth table).

A	Q	Y	Q_{next}
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	1

$\left. \begin{array}{l} \text{Y=1 when A=0 and Q=1.} \\ \text{Q}_{next} = 1 \text{ when A=1.} \end{array} \right\}$

$Q_{next} = \underline{A}$

$Y = \underline{\neg A \wedge Q}$

(b) Explain in one sentence why this is a Mealy Finite State Machine.

The output Y depends not only on the current state Q but also directly on the input A , and Y is labeled on the state diagram's transitions (arrows).

(c) Explain in one or two sentences what this circuit does (functionality) in a brief high level description (for instance, when and under what conditions is the output asserted 1'b1 in relation to the input)

The output Y is asserted when the input A changes from 1 to 0.

(d) You are to change this from a Mealy to a Moore FSM maintaining the functionality but not the timing of the output. Draw the new state diagram.

