

ECE3 Fall 2020

Name Wang | Kevin
Family (Last) Name Given (First) Name

Final Exam

UID 805503382

**DO NOT OPEN UNTIL
INSTRUCTED TO DO SO.**

- We will copy some graded exam papers for archival purposes!
- Put your name in the blank on EVERY page.
- Show your setup.
- Circle your answers.
- Add notes to help the graders determine your intentions.

Problem	Value	Score	Problem	Value	Score
1	5		7	7	
2	4		8	7	
3	5		9	7	
4	5		10	18	
5	5		11	10	
6	7		12	20	
			TOTAL	100	

1


If you double the current through an ideal battery, is the potential difference across the battery doubled?

- a. Yes, because Ohm's Law says that $V = IR$
- ~~b. Yes, because as you increase the resistance, you increase the potential difference~~
- c. No, because as you double the current, you halve the potential difference
- d. No, because the potential difference is a property of the battery
- ~~e. No, because the potential difference is a property of everything in the circuit~~

2

In the world of EE3, is this a legal circuit?

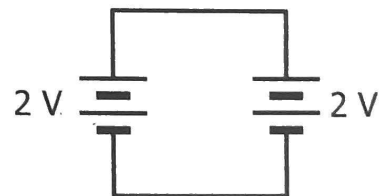
- a. Yes, because the batteries are exchanging power.
- b. Yes, because the batteries are in series.
- c. No, because the batteries oppose each other.
- d. No, because the currents cancel each other out.



3

Is the 2 A current source providing or absorbing power?

The current source is providing power

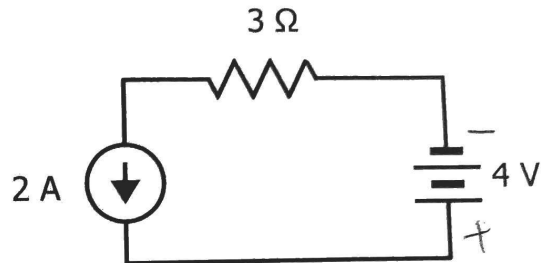

4


It is usually good for a battery to have a low output impedance because:

- a. The voltage output is usually lower, and so requires less power to operate.
- b. The load has less effect on the battery's output voltage.
- c. Ideal battery voltages are affected by the load.
- d. High output impedance means that the battery can drive only low-resistance loads.

5

Ideal voltmeters have infinite input impedance.

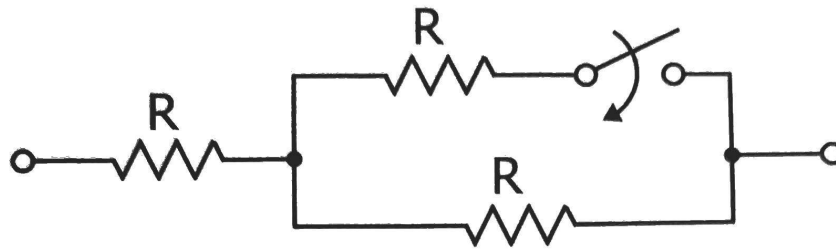- a. True, because low input impedance means that the voltmeter draws less power.
- b. True, because high input impedance adds no load to the circuit.
- c. False, because infinite input impedance voltmeters are unaffected by the circuit.
- d. False, because infinite input impedance is a sign of a non-functioning circuit.



6

How does the resistance between the endpoints change when the switch is closed?

- a. It increases
- b. It decreases
- c. It does not change

Parallel


7

In this circuit, $R_1 < R_2$. Which resistor dissipates the most power?

a. Neither; they dissipate the same power.

b. R_1

c. R_2

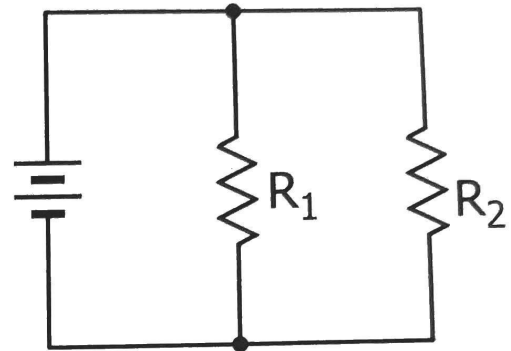

$$\frac{V^2}{R}$$



R_1

is smaller
so


it dissipates the most power

For the question on this page, assume that the lamp brightness increases with increasing current. Also, assume that all lamps are equal, and all batteries are equal. Select the ONE BEST answer.

8

If you increase the resistance of C, what happens to the brightness of lamps A and B?

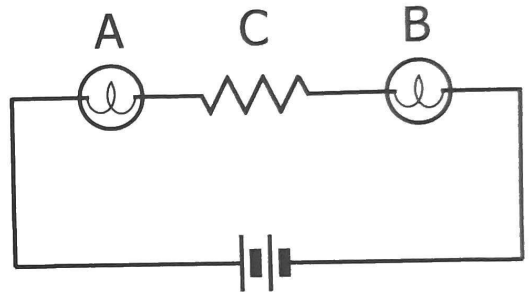- a. A stays the same, B decreases
- b. A decreases, B stays the same
- c. A and B increase
- d. A and B decrease
- e. A and B stay the same




↑ total resistance, ↓ current

For the question on this page, assume that the lamp brightness increases with increasing current. Also, assume that all lamps are equal, and all batteries are equal. Select the ONE BEST answer.

9

Rank the currents at points 1, 2, 3, 4, 5, and 6 from highest to lowest.

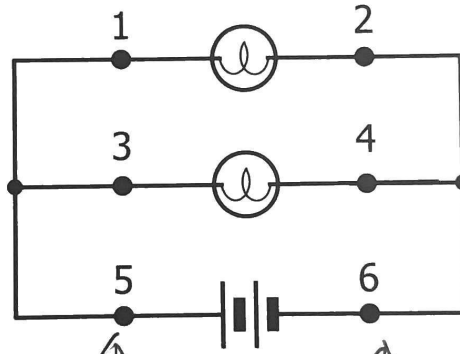- a. 5,1,3,2,4,6
- b. 5,3,1,4,2,6
- c. 5 = 6, 3 = 4, 1 = 2
- d. 5 = 6, 1 = 2 = 3 = 4
- e. 1 = 2 = 3 = 4 = 5 = 6




largest smallest

$$10 \angle 40^\circ \rightarrow 7.66$$

10

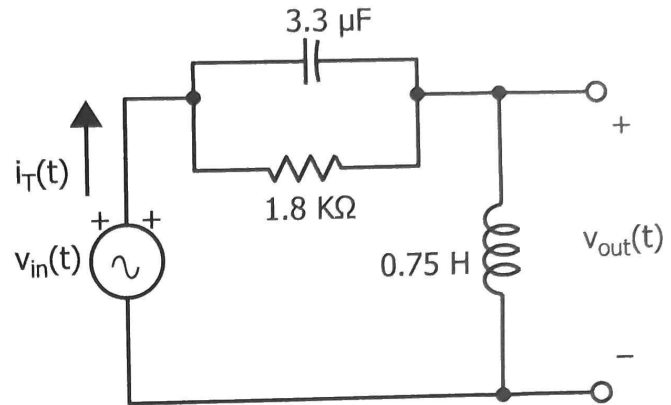If $v_{in}(t) = 10 \cos(1000t + 40^\circ)$,
compute $i_T(t)$.



$$\frac{1}{z_{||}} = \frac{1}{R} + \frac{1}{X_C j} = \frac{1}{R} + \omega C j$$

$$= \frac{1}{1.8 \text{ k}\Omega} + 1000 (3.3) \mu\text{F}$$

$$\frac{1}{z} = 5.55 \text{E-}4 + 0.0033 j$$

$$z_{\text{parallel}} = \frac{1}{5.55 \text{E-}4 + 0.0033 j}$$

$$z_{\text{tot}} = z_{\text{parallel}} + \omega L j$$

$$= \frac{1}{5.55 \text{E-}4 + 0.0033 j} + 750 j$$

$$z_{\text{tot}} = 49.56 + 294.69 j + 750 j = 49.56 + 455.305 j$$


$$i_T(t) = \frac{v_{in}(t)}{z_{\text{tot}}} = \frac{7.66}{49.56 + 455.305 j} = \boxed{0.018 - 0.0106 j}$$

Final Exam

UID _____

11

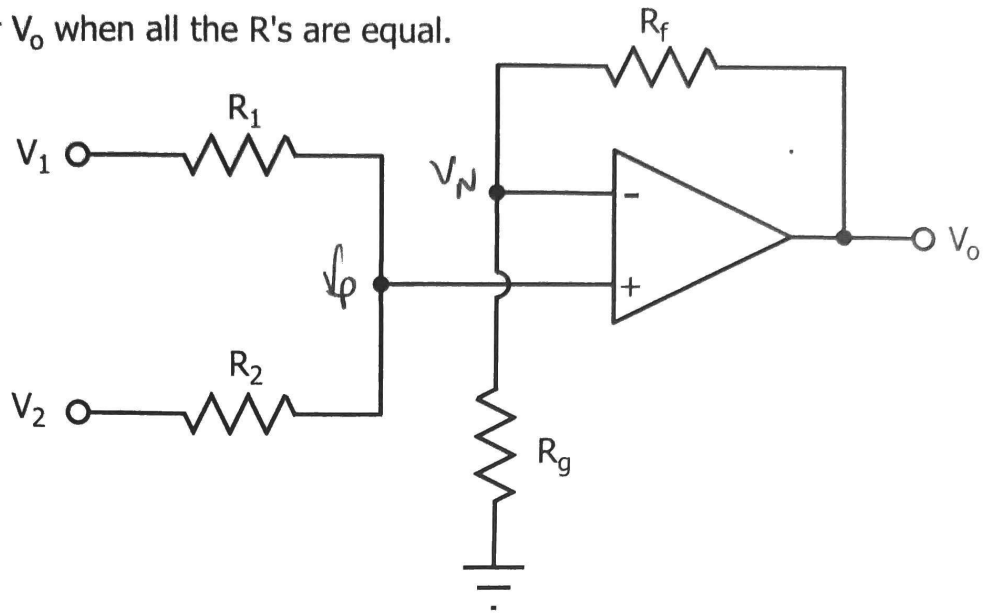Find an expression for V_o when all the R's are equal.



$$\frac{V_N - V_o}{R_f} + \frac{V_N}{R_g} = 0 \Rightarrow \frac{V_N - V_o}{R} + \frac{V_N}{R} = 0$$

$$\frac{V_p - V_1}{R_1} + \frac{V_p - V_2}{R_2} = 0 \quad \frac{V_p - V_1}{R} + \frac{V_p - V_2}{R} = 0$$

$$V_N = V_p = V$$

$$\frac{V - V_o}{R} + \frac{V}{R} = 0$$

$$\frac{V - V_1}{R} + \frac{V - V_2}{R} = 0$$


$$\frac{V - V_o}{R} + \frac{V}{R} = \frac{V - V_1}{R} + \frac{V - V_2}{R}$$

$$V - V_o + V = V - V_1 + V - V_2$$

$$-V_o = -V_1 - V_2$$

$$\boxed{V_o = V_1 + V_2}$$

12

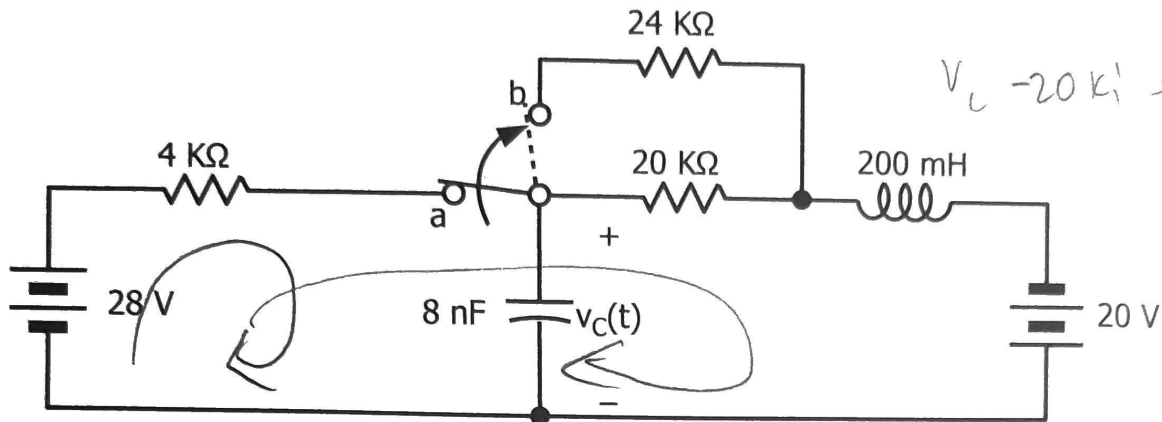

The switch has been in position a for a long time. All transients have died out. At $t = 0$, the switch moves instantaneously to position b.

- a. At $t=0^+$ (the first instant that the switch is in position b), what is the current through the inductor?

$$28 - 4k i - 20k i + 20 = 0$$

$$i = .002 \text{ A}$$

before flip

$$i(0^-) = i(0^+) = .002 \text{ A}$$

- b. At $t=0^-$ (the last instant that the switch is in position a), what is the direction of the current through the $4k\Omega$ resistor? Circle one:

- Left to Right
- Right to Left

- c. At $t=0^+$ (the first instant that the switch is in position b), what is the voltage across the capacitor? Note the assumed polarity of the capacitor voltage!

$$v_C(0^-) = v_C(0^+) = 20 \text{ V}$$

$$28 - 4k(.002) - v_C = 0$$

$$v_C = 20$$