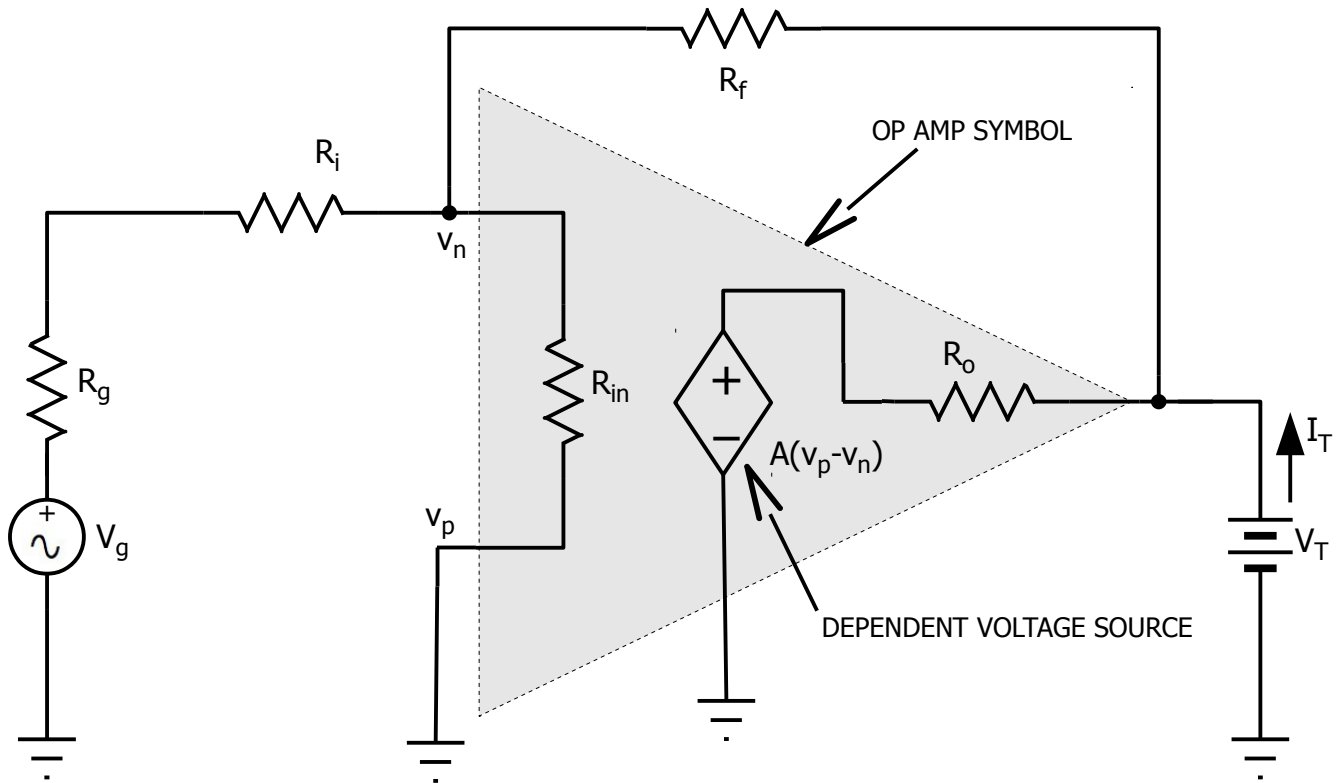


# EE3 Fall 2020 Final Exam Practice Problems

1



How does one compute the output impedance of an inverting op amp circuit (as opposed to the op amp itself)? One method is to use a slightly-more-realistic equivalent circuit (inside the dashed line of the op amp symbol), and then determine its Thévenin resistance. One can do this by applying a “test” voltage  $V_T$  to the output after de-activating the independent sources, and then computing the resulting  $I_T$ . The ratio of  $V_T$  to  $I_T$  is the Thévenin resistance and the output impedance<sup>‡</sup>. Assume that  $R_g=0$ ,  $R_i=10\text{ K}\Omega$ ,  $R_f=10\text{ K}\Omega$ ,  $R_o=10\ \Omega$ ,  $R_{in}=1\text{ M}\Omega$ , and  $A = 1e5$ , and compute the output impedance of the op amp circuit. **You will see that the output resistance of the whole circuit is dramatically lower than that of  $R_o$  (the op amp itself).**

Dependent voltage source:  $V_{ds} = A(v_p - v_n) = -Av_n$

①  $-I_T + \frac{V_T - (-Av_n)}{R_o} + \frac{V_T - v_n}{R_f} = 0$

Let  $R_s = R_i + R_g$

Then  $v_n = V_T \left( \frac{R_s \parallel R_{in}}{R_s \parallel R_{in} + R_f} \right) = V_T \left( \frac{R_s \cdot R_{in}}{R_s \cdot R_{in} + R_f(R_s + R_{in})} \right)$

Let  $K = \left( \frac{R_s \cdot R_{in}}{R_s \cdot R_{in} + R_f(R_s + R_{in})} \right)$

Then  $v_n = V_T K$

Plug into ①:

$-I_T + \frac{V_T + AV_T K}{R_o} + \frac{V_T(1-K)}{R_f} = 0$

$V_T \left( \frac{1}{R_o} + \frac{AK}{R_o} + \frac{1-K}{R_f} \right) = I_T$

$R_{out} = R_{th} = \frac{V_T}{I_T} = \frac{1}{\frac{1}{R_o} + \frac{AK}{R_o} + \frac{1-K}{R_f}} = 0.201e-3\ \Omega \ll R_o = 10\ \Omega$


<sup>‡</sup> See Nilsson, 8/e, TK454 .N54 2008 (at SEL), Example 4.11

# EE3 Fall 2020

## Final Exam Practice Problems

2. Let  $R_4 = R_2$ , and  $R_3 = R_1$ . Find  $V_o = f(V_s, R's)$ . HINT: write 2 KCL equations at the input.

$$V_o = \frac{R_2}{R_1}(V_2 - V_1)$$

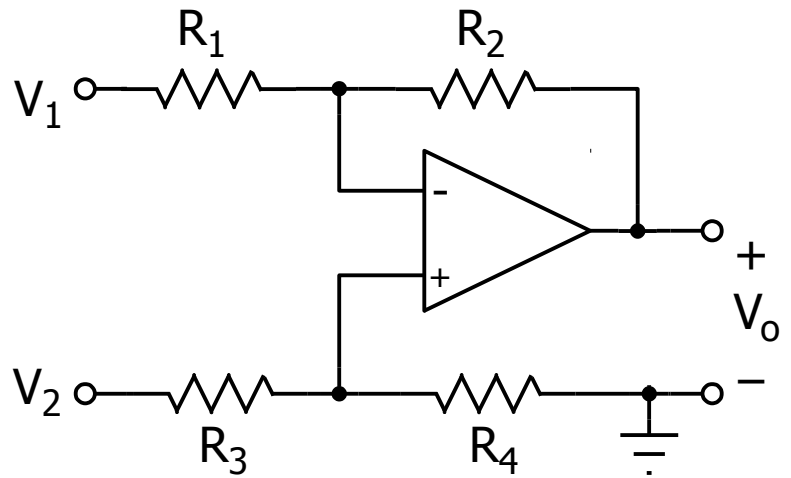

Write 2 KCL equations:

$$\frac{v_n - V_1}{R_1} + \frac{v_n - V_o}{R_2} = 0$$

$$\frac{v_p - V_2}{R_3} + \frac{v_p}{R_4} = 0$$

But  $R_3 = R_1$  and  $R_4 = R_2$ , so

$$\frac{v_n - V_1}{R_1} + \frac{v_n - V_o}{R_2} = 0$$

$$\frac{v_p - V_2}{R_1} + \frac{v_p}{R_2} = 0$$

$v_n$ ,  $v_p$ , and  $V_o$  are unknown, so we need a third equation.

$$v_p = v_n = v$$

$$\frac{v - V_1}{R_1} + \frac{v - V_o}{R_2} = 0 = \frac{v - V_2}{R_1} + \frac{v}{R_2}$$


$$\frac{-V_1}{R_1} - \frac{V_o}{R_2} = -\frac{V_2}{R_2}$$

$$V_o = \frac{R_2}{R_1}(V_2 - V_1)$$

So this is a *differential amplifier* that provides a controllable gain on the difference between two input voltages.

# EE3 Fall 2020

## Final Exam Practice Problems

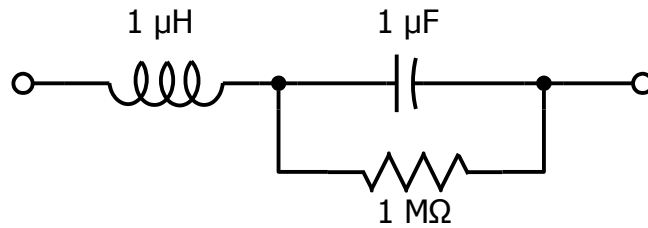


3. This is a more-realistic model of a 1 μF capacitor. The capacitor leads have inductance (1 μH), and the dielectric between the capacitor plates is less than perfect (1 MΩ). Find the frequency where the capacitor stops being a capacitor and starts being an inductor (AKA the series resonant frequency).

At the resonant frequency  $\omega_0$ ,  $X_L = X_C$

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1e6 \text{ rad/s}$$

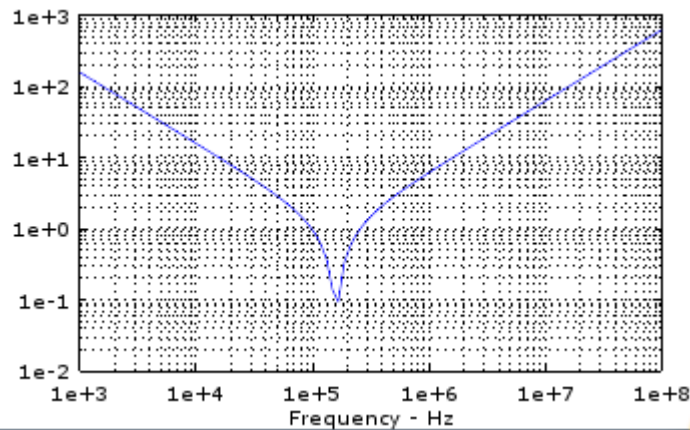
$$f_0 = \frac{\omega_0}{2\pi} = 159 \text{ KHz}$$



# EE3 Fall 2020

## Final Exam Practice Problems

4. This is a second-order circuit. There is an initial voltage on the capacitor (assuming clockwise current)  $v_C(0^-) = +12$  V, and an initial current in the inductor  $i_L(0^-) = 30$  mA clockwise. In order to solve the differential equation for  $i(t)$ , the initial voltages  $v_C(0^+)$  and  $v_R(0^+)$ , and  $di(t)/dt|_{t=0^+}$  must be found. Using what you know about inductors, capacitors, and KCL/KVL, find these values.

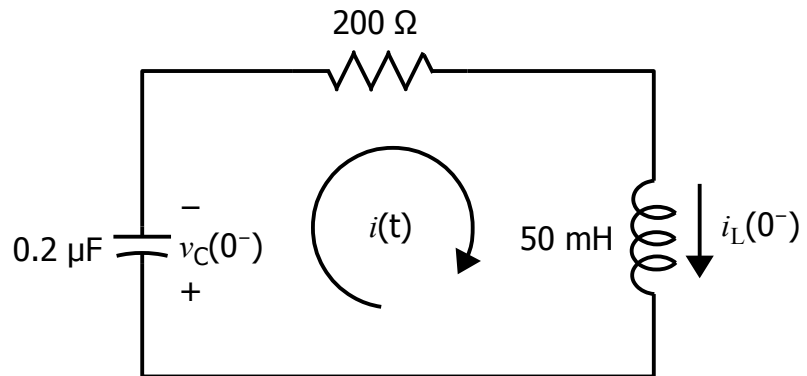

$$i(0^+) = i_L(0^-) = 30 \text{ mA}$$

$$v_C(0^+) = v_C(0^-) = 12 \text{ V}$$

$$v_R(0^+) = i(0^+)R = 0.030 \cdot 200 = 6 \text{ V, + to left}$$

$$\text{KVL@}t=0^+ : +12 + 6 + v_L(0^+) = 0$$

$$v_L(0^+) = -18 \text{ V, + at bottom}$$


Because  $v_L(0^+) = L \left[ \frac{di(t)}{dt} \right]_{t=0^+}$ , it follows that

$$\frac{di(t)}{dt} \Big|_{t=0^+} = \left( \frac{1}{0.05} \right) \cdot (-18) = -360 \text{ A/s}$$

EE3 Fall 2020  
Final Exam Practice Problems

5. Find the power dissipated by the 5 Ω resistor.

9.47 W

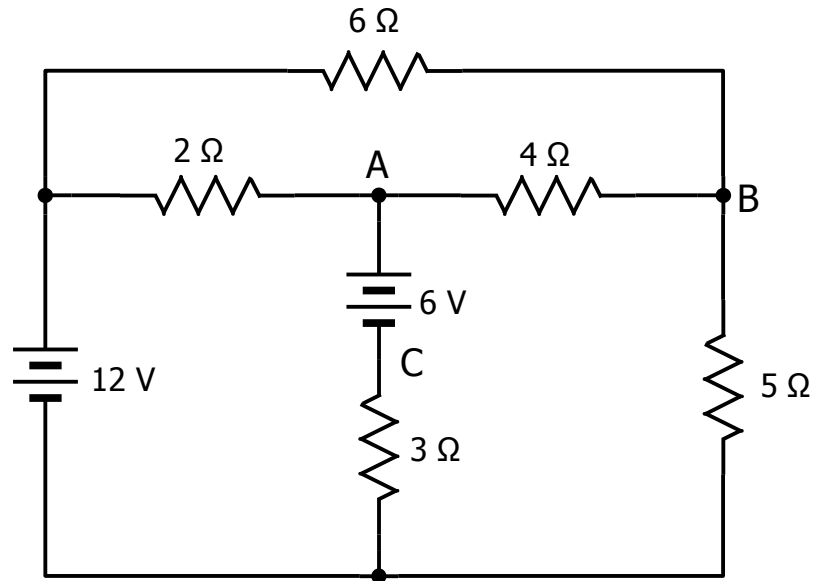

$$\frac{V_A - 12}{2} + \frac{V_C}{3} + \frac{V_A - V_B}{4} = 0$$

$$\frac{V_B - V_A}{4} + \frac{V_B}{5} + \frac{V_B - 12}{6} = 0$$

$$V_C = V_A - 6$$

$$0.75V_A - 0.25V_B + 0.333V_C = 6$$

$$-0.25V_A + 0.617V_B = 2$$

$$V_A - V_C = 6$$

$$V_A = 8.97 \text{ V}$$

$$V_B = 6.88 \text{ V}$$


$$V_C = 2.97 \text{ V}$$

$$P_5 = \frac{(V_B)^2}{5} = \frac{6.88^2}{5} = 9.47 \text{ W}$$

# EE3 Fall 2020

## Final Exam Practice Problems

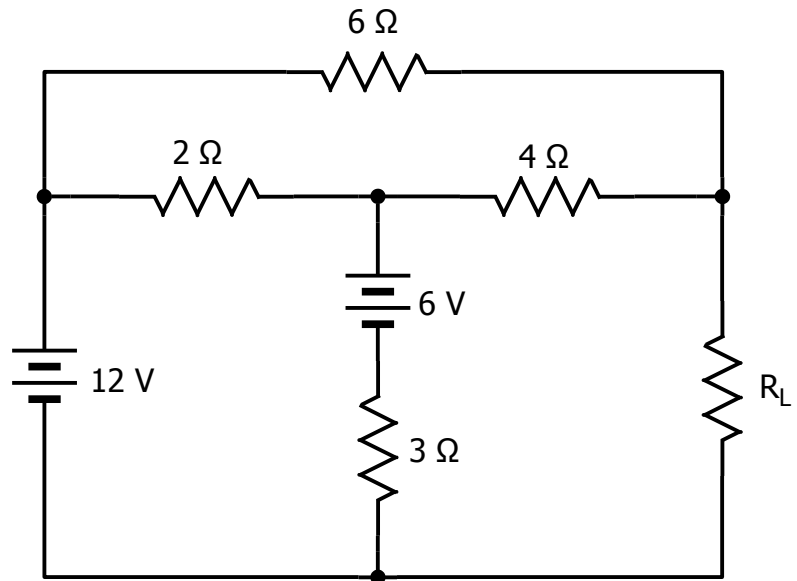6. Find the value of  $R_L$  for maximum power transfer to  $R_L$ .



Find the Thévenin Equivalent Resistance.

Open Circuit Voltage

$$V_1 = 12$$

$$\frac{V_2 - 12}{2} + \frac{V_2 - 6}{3} + \frac{V_2 - V_{OC}}{4} = 0$$

$$\frac{V_{OC} - V_2}{4} + \frac{V_{OC} - 12}{6} = 0$$

$$6V_2 - 72 + 4V_2 - 24 + 3V_2 - 3V_{OC} = 0$$

$$-3V_2 + 3V_{OC} + 2V_{OC} - 24 = 0$$

$$13V_2 - 3V_{OC} = 96$$

$$-3V_2 + 5V_{OC} = 24$$

$$V_2 = 9.8571 \text{ V}$$

$$V_{OC} = 10.7143 \text{ V}$$

Short Circuit Current

$$\frac{V_1 - 12}{2} + \frac{V_1 - 6}{3} + \frac{V_1}{4} = 0$$

$$V_1 = 7.3846 \text{ V}$$

$$I_4 = \frac{V_1}{4} = 1.8462 \text{ A}$$

$$I_6 = \frac{12}{6} = 2 \text{ A}$$

$$I_{SC} = I_4 + I_6 = 3.8462 \text{ A}$$

$$R_{\max\_pwr} = R_{th} = \frac{V_{OC}}{I_{SC}} = 2.79 \text{ } \Omega$$

2.79  $\Omega$