

Write your name here:

SURAJ VATHSA

Write your UCLA ID here

205092512

## Final, Physics 1B, Winter 2020

- Time for exam: 90 minutes (including time to upload the exam to gradescope)  
    **Start time 11:30am** (Pacific) and **end time 1:00 pm** (Pacific)
- Please upload all your answers as **single pdf to gradescope**. You can write on the printed out exam, use separate sheets of paper or ipad.
- Please write your name and UID on the top of each sheet you submit.
- Gradescope allows late submissions. This is to accommodate CAE students who have extra time. If you do not have this accommodation please submit by 1pm.
- Open book, you can use the textbook and all the material posted on the class website. Googling answers is not allowed and not helpful
- Calculators allowed, computer algebra systems (Mathematica, Maple) are not.
- Consulting other students for help or collaborating during the exam is not allowed.
- You can ask questions on questionsly, clarifications will be emailed to students
- The exam has 4 questions and 12 pages.
- Useful quantities


$$\begin{aligned}\epsilon_0 &= 8.85 \times 10^{-12} C^2 m^{-2} N^{-1} \\ m_{electron} &= 9.11 \times 10^{-31} kg \\ m_{proton} &= 1.67 \times 10^{-27} kg \\ q_e &= -1.602 \times 10^{-19} C\end{aligned}$$

Good luck !!

Write your name and UID here:

**Problem 1: [15pts] Concept questions**

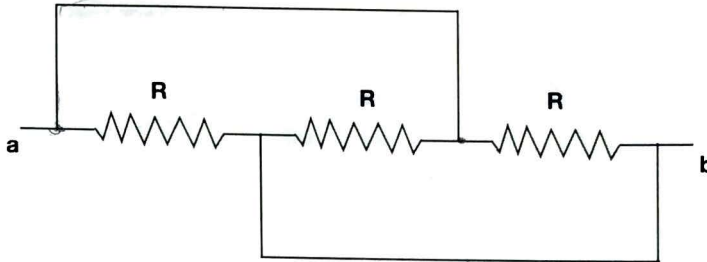a) [5pts] You have three resistors all with the same resistance  $R$ , which are connected by ideal wires (with zero resistance), what is the equivalent resistance of the combination ?



(1)  $3R$

(2)  $\frac{1}{3}R$


(3)  $\frac{2}{3}R$

(4)  $\frac{3}{2}R$

(5)  $R$

Write your name and UID here:

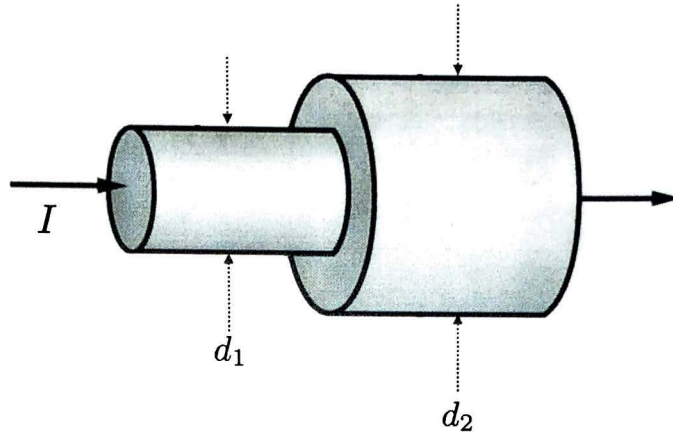b) [5pts] Two wires are made out of the same material, the left wire has diameter  $d_1 = 3\text{mm}$  and the right one has diameter  $d_2 = 6\text{mm}$ , there is a current of  $I = 2$  Ampere entering the left wire. What is the relation of the drift velocity  $v_d^{\text{right}}$  of the electrons of the right wire to the drift velocity  $v_d^{\text{left}}$  the electrons of the left wire ?



- (1)  $v_d^{\text{right}} = 2v_d^{\text{left}}$
- (2)  $v_d^{\text{right}} = v_d^{\text{left}}$
- (3)  $v_d^{\text{right}} = 4v_d^{\text{left}}$
- (4)  $v_d^{\text{right}} = \frac{1}{4}v_d^{\text{left}}$
- (5)  $v_d^{\text{right}} = \frac{1}{2}v_d^{\text{left}}$
- (6)  $v_d^{\text{right}} = \frac{1}{\sqrt{2}}v_d^{\text{left}}$

Write your name and UID here:

c) [5pts] A loudspeaker broadcasts a sine wave with frequency  $f_s$  and a microphone measures the frequency. Consider two situations: a) The loudspeaker is on a cart moving towards the microphone with speed  $v = 30\text{m/s}$  and the microphone is at rest. b) The microphone on a cart moving towards the loudspeaker with speed  $v = 30\text{m/s}$  and the loudspeaker is at rest. What is true about the frequency the microphone records in the two cases a) and b) (Denoted as  $f_a$  and  $f_b$ ) ? Assume speed of sound in air is  $343\text{ m/s}$ .

(1)  $f_s = f_a = f_b$

(2)  $f_a > f_b > f_s$

(3)  $f_b > f_a > f_s$


(4)  $f_a = f_b > f_s$

(5)  $f_a < f_b < f_s$


(6)  $f_b < f_a < f_s$

Write your name and UID here:

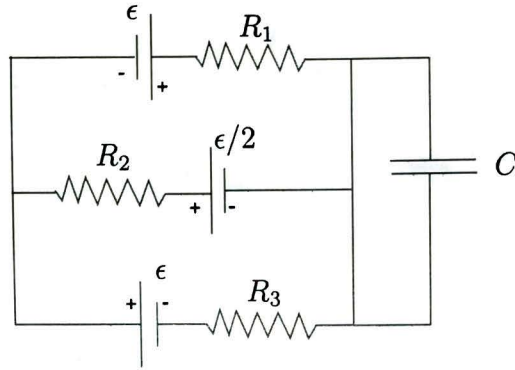**Problem 2:** [30pts] Consider the following circuit, with three ideal batteries with the emf which are multiples of  $\epsilon > 0$  (see figure) and three resistors with resistances  $R_1, R_2, R_3$ . As well as a capacitor of capacitance  $C$ .



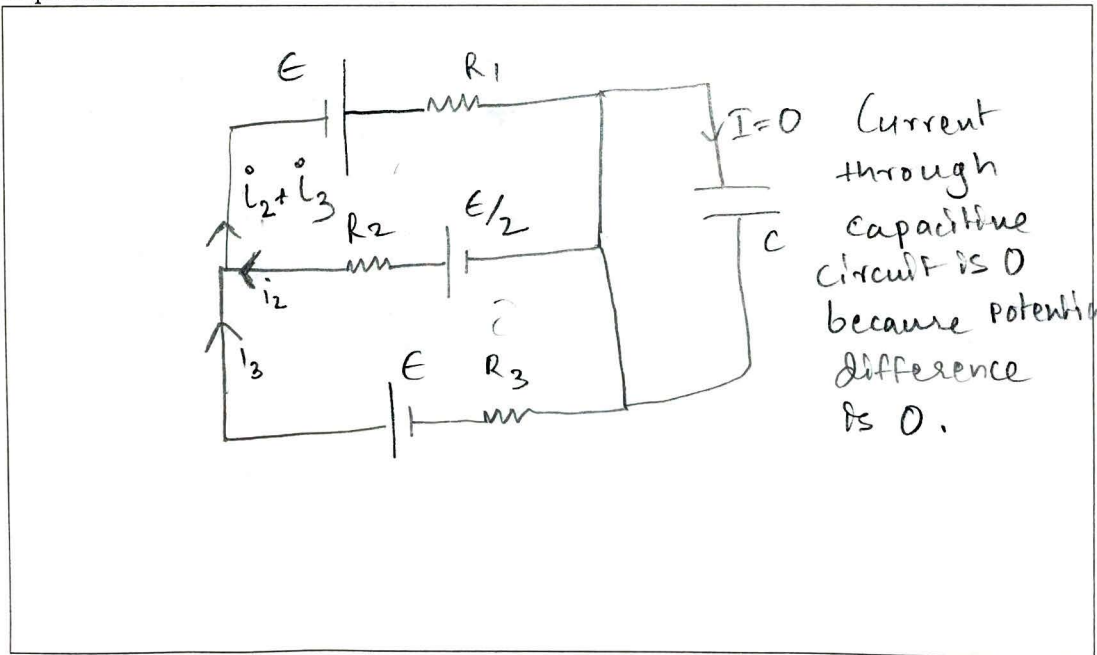a) [10pts] Label all the currents and their directions in the circuit. Redraw the circuit if you answer on a separate sheet. Use the Kirchoff junction rule to eliminate as many currents as possible.



Write your name and UID here:

b) [10pts] Use the Kirchoff loop rule to obtain equations to solve for the remaining currents.

$$\begin{aligned} \epsilon - (i_2 + i_3)R_1 + \epsilon/2 + i_2 R_2 &= 0 \\ \epsilon/2 - i_2 R_2 + i_2 R_1 + i_3 R_1 &= \frac{3\epsilon}{2} \\ i_3 &= \frac{1}{R_1} \left( \frac{3\epsilon}{2} - i_2 R_2 - i_2 R_1 \right) \\ \epsilon/2 - i_2 R_2 - \epsilon + i_3 R_3 &= 0 \\ \frac{1}{R_1} \left( \frac{3\epsilon}{2} - i_2 R_2 - i_2 R_1 \right) R_3 - i_2 R_2 &= \epsilon/2 \\ \Rightarrow \frac{3\epsilon R_3}{2R_1} - \frac{i_2 R_2 R_3}{R_1} - i_2 R_3 - i_2 R_2 &= \epsilon/2 \\ i_2 &= \frac{1}{R_2 R_3 + R_3 + R_2} \left( \frac{3\epsilon R_3}{2R_1} - \frac{\epsilon}{2} \right) \end{aligned}$$

if  $i_3$  at back


c) [10pts] By choosing the resistances you can make the current through **one** resistor vanishes, which one is it? Find the relation of the resistances for which this current vanishes. What is the power the battery next to this resistor puts into the circuit (or the circuit puts into the battery)?

$$\begin{aligned} \text{Assume } i_2 &= 0 \\ \frac{3\epsilon R_3}{2R_1} &= \frac{\epsilon}{2} \\ \Rightarrow 3R_3 &= R_1 \quad \therefore \text{Current through } R_2 = 0 \\ P &= 0 \text{ as current through branch} = 0 \end{aligned}$$

Write your name and UID here:

**Problem 3: [30pts] Capacitors**

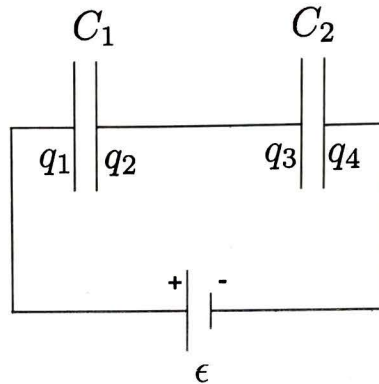a) [10pts] Consider two fully charged plate capacitors with capacitance  $C_1, C_2$  connected to an ideal battery of emf  $\epsilon > 0$ . Express the charges  $q_1, q_2, q_3, q_4$  on the four plates in terms of  $\epsilon$  and  $C_1, C_2$ . Explain in your own words why  $q_2 + q_3 = 0$ .



$$q_1 = +1 \times \left| \frac{E \times C_1 C_2}{C_1 + C_2} \right| \quad q_2 = -1 \times \left| \frac{E \times C_1 C_2}{C_1 + C_2} \right|$$

$$q_4 = -1 \times \left| \frac{E \times C_1 C_2}{C_1 + C_2} \right| \quad q_3 = +1 \times \left| \frac{E \times C_1 C_2}{C_1 + C_2} \right|$$

As  $E$  is connected to the circuit, electrons leave left side of  $C_1$  and electrons accumulate on right side of  $C_2$  to create equal and opposite charges. This polarizes the inner plates to create opposite charges - i.e. electrons leave left side of  $C_2$  and enter right side of  $C_1$  to maintain constant electric field between plates in  $C_1$  &  $C_2$ .

$\therefore q_2 + q_3 = 0$

Write your name and UID here:

b) [10pts] You disconnect the fully charged capacitors from the battery and after that insert a dielectric with  $K > 1$  in the capacitor  $C_2$ , completely filling the space between the plates. Does the value of  $q_1, q_2, q_3, q_4$  change? Calculate the energy stored in the capacitors after the dielectric is inserted in terms of  $C_1, C_2, \epsilon$  and  $K$ .

Since battery is disconnected, the charges have no source/sink.  $\therefore$  The charges remain the same but the capacitance and potential difference of the capacitors change.

$$U_{\text{initial}} = \frac{1}{2} \frac{Q^2}{C_1 + C_2} = \frac{1}{2} \cdot \frac{C_1^2 C_2^2 \cdot V^2}{(C_1 + C_2)^2} = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} V^2$$

$$= \frac{E^2 \cdot C_1^2 C_2^2}{(C_1 + C_2)^2} \cdot \frac{1}{2} \frac{1}{\epsilon_0} \frac{1}{d^2}$$

$$= E^2 C_1 C_2$$

$\therefore U$  after  $\frac{1}{2} \frac{Q^2}{C_1 + C_2}$  decreases


$$U_{C_2} = \frac{E^2 C_1^2 C_2^2}{(C_1 + C_2)^2} \cdot \frac{1}{2K} = \frac{E^2 C_1^2 C_2}{2K(C_1 + C_2)^2}$$

$$\therefore U_{\text{total}} = U_{C_1} + U_{C_2} = \frac{E^2 C_1 C_2^2}{2(C_1 + C_2)^2} + \frac{E^2 C_1^2 C_2}{2K(C_1 + C_2)^2}$$



Write your name and UID here:

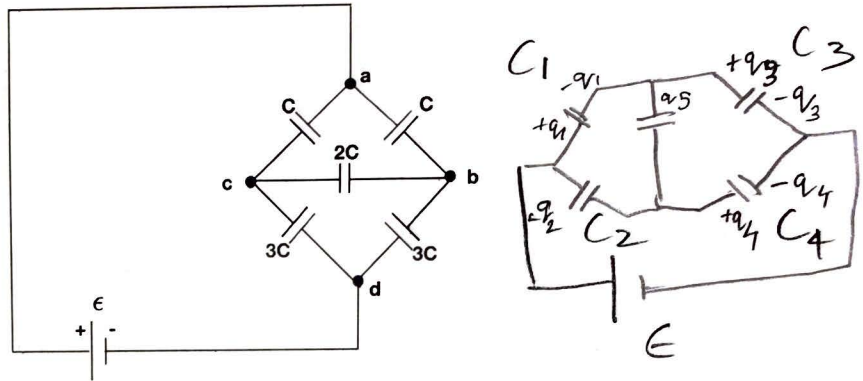c) [10pts] Consider the following arrangement of fully charged capacitors with capacitances which are multiples of  $C$  and connected to an ideal battery with emf  $\epsilon$ . Calculate the voltage differences  $V_c - V_b$  and  $V_d - V_b$  in term of  $\epsilon$  and  $C$ .



In the above circuit we have a wheatstone bridge configuration

$$\frac{C_1}{C_2} = \frac{C_3}{C_4} \Rightarrow \frac{C_1}{C_3} = \frac{C_2}{C_4} = \frac{1}{3}$$

$$\therefore V_c - V_b = 0$$


$$C_{\text{effective}} = 2 \times \frac{1}{\frac{1}{3C} + \frac{3}{3C}} = \frac{3C}{2}$$

$$Q_{\text{total}} = C_{\text{effective}} \times \epsilon = \frac{3C\epsilon}{2}$$

$\therefore$  Charge gets split up equally because effective capacitance is equal on both branches.

$$\therefore Q_4 = \frac{3C\epsilon}{4} \Rightarrow V_4 = \frac{Q_4}{C_4}$$
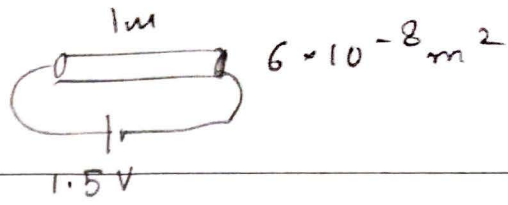
$$10 \quad V_d - V_b = \frac{\epsilon}{4}$$



Write your name and UID here:

**Problem 4: [20pts]** A copper wire of length  $l = 1\text{m}$  and cross sectional area  $6.00 \times 10^{-8}\text{m}^2$  is connected to an ideal battery with emf  $\epsilon = 1.50\text{V}$ . The resistivity of copper is  $\rho = 1.68 \times 10^{-8}\Omega\text{m}$ .

a) [10pts] How many electrons flow through a given cross section of the wire in a second?

$$R = \frac{\rho l}{A} \Rightarrow I = \frac{V}{R} = \frac{VA}{\frac{\rho l}{A}} = \frac{VA}{\rho l}$$

$$= \frac{1.50\text{V} \times 6 \times 10^{-8}\text{m}^2}{1.68 \times 10^{-8}\Omega\text{m} \times 1\text{m}}$$

$$= 5.357\text{A}$$

$$I = \frac{Q}{t} = \frac{n e}{t} \Rightarrow n = \frac{I t}{e} = \frac{5.357 \times 1}{1.6 \times 10^{-19}}$$

$$= 3.35 \times 10^{19} \text{ electrons per sec.}$$

b) [10pts] You slowly stretch the wire so that it is 2 meter long (the density stays constant) and connect it to the same battery. (Carefully think what this does to the geometry of the wire) How many electrons flow through a given cross section of the stretched wire in a second? [If you could not do a) assume  $n_e = 7 \times 10^{18}$ .]

length = 2m

$A = \frac{A}{2}$

$$\Rightarrow I = \frac{VA}{4 \cdot \rho l} = \frac{1}{4} \times 3.35 \times 10^{19}$$

$$\text{electrons } n_e = 8.37 \times 10^{18} \text{ electrons per sec.}$$

Write your name and UID here:

-additional space for calculation-

$$\star i_3 = \frac{1}{R_1} \left( \frac{3E}{2} - \left( \frac{1}{\frac{R_2 R_3}{R_1} + R_3 + R_2} \left( \frac{3E R_3}{2 R_1} - \frac{E_2}{2} \right) \right) (R_2 + R_1) \right)$$

$$i_1 = i_2 + i_3$$

26  
answer