

Physics Final 1B

3/19/20

Winter 2020 Gutperle

LOS 114 897

Jacob Nahben

1a. Parallel $\left(\frac{1}{R} + \frac{1}{R} + \frac{1}{R}\right)^{-1} = \frac{R}{3}$

$\textcircled{2} \quad \frac{1}{3} R$

1b. $\vec{J} = \frac{I}{A} = nq\vec{v}_d$

$\frac{2}{9\pi} = nq\vec{v}_d \text{ left}$

$\frac{2}{36\pi} = nq\vec{v}_d \text{ right}$

$\frac{2}{9\pi v_L} = \frac{2}{36\pi v_R}$

$4v_R = v_L$

$v_R = \frac{1}{4} v_L \quad \textcircled{4}$

1c.

$f_a = \frac{v}{v - v_s} f_s$


$f_b = \frac{v + v_L}{v} f_s$

$f_a = \frac{343}{313} f_s = 1.095 f_s$

$f_b = \frac{373}{343} f_s = 1.087 f_s$

$f_a > f_b > f_s \quad \textcircled{2}$

2.
a)

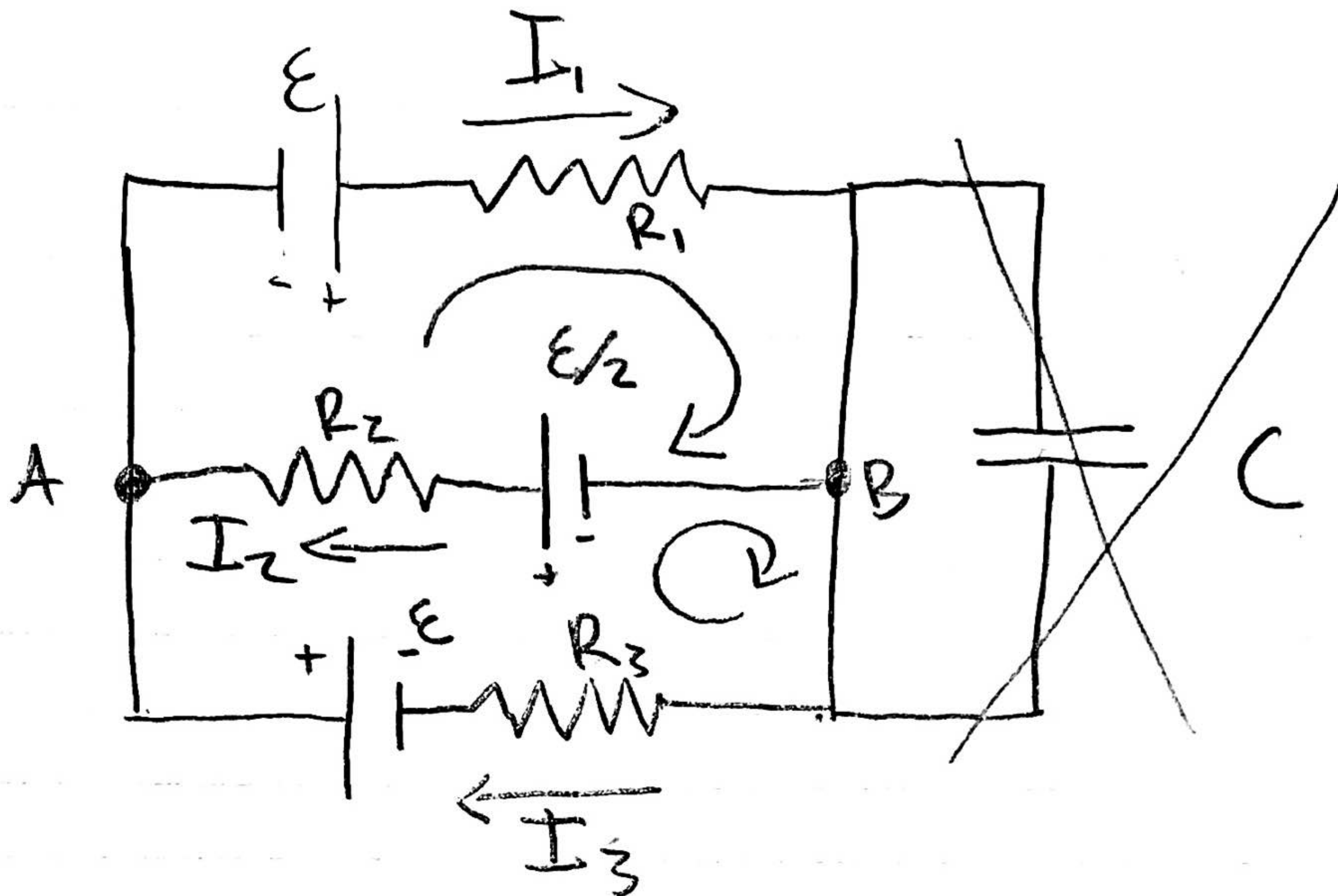

Capacitors
are treated
as open
switches

Ⓐ $I_2 + I_3 - I_1 = 0$
 Ⓑ $I_1 - I_2 - I_3 = 0$

$$I_1 = I_2 + I_3$$

Ⓑ Top Loop: $I_1 R_1 - \frac{\epsilon}{2} + I_2 R_2 - \epsilon = 0$
 $(I_2 + I_3) R_1 + I_2 R_2 - \frac{3\epsilon}{2} = 0$

Bottom Loop: $-I_2 R_2 + \frac{\epsilon}{2} + I_3 R_3 - \epsilon = 0$

$$I_2 R_1 + I_3 R_1 + I_2 R_2 - \frac{3\epsilon}{2} = 0$$

$$-I_2 R_2 + I_3 R_3 = \frac{\epsilon}{2} \quad \text{plug in}$$

$$\Rightarrow I_2 R_1 + I_3 R_1 + I_2 R_2 - 3(-I_2 R_2 + I_3 R_3) = 0$$

$$\Rightarrow I_2 R_1 + I_3 R_1 + I_2 R_2 + 3I_2 R_2 - 3I_3 R_3 = 0$$

$$\Rightarrow I_2 (R_1 + 4R_2) + I_3 (R_1 - 3R_3) = 0$$

$$I_2 = \frac{-I_3 (R_1 - 3R_3)}{R_1 + 4R_2}$$

2c) Current through R_2 can vanish



Current from left must equal current from right

So $I_1 = I_3$ this is the case when $R_1 = R_3$ because both sections of the circuit have a battery \mathcal{E} & one resistor

$$I_1 = I_2 + I_3 \Rightarrow I_1 = I_2 + I_1 \quad I_2 = 0 \quad \checkmark$$

3a) Capacitors in series $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} \quad Q = CV$$

$$q_1 = q_3 = \mathcal{E} \left(\frac{C_1 C_2}{C_1 + C_2} \right) \quad q_2 = q_4 = - \mathcal{E} \left(\frac{C_1 C_2}{C_1 + C_2} \right)$$

$q_2 + q_3 = 0$ because for capacitors in series the charge is the same for both capacitors. In this case, q_2 is the negative side of C_1 and q_3 is the positive side of C_2 . Since $q_2 \neq q_3$ have same magnitude, but opposite signs, their sum is zero

3b. yes the charge changes

$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \quad \text{now} \Rightarrow \quad V = Q' \left(\frac{1}{C_1} + \frac{1}{KC_2} \right)$$

$$Q \left(\frac{C_2 + C_1}{C_1 C_2} \right) = Q' \left(\frac{KC_2 + C_1}{KC_2 C_1} \right)$$

$$Q' = Q \left(\frac{C_2 + C_1}{C_1 C_2} \right) \left(\frac{KC_2 C_1}{KC_2 + C_1} \right)$$

$$Q' = Q \left(\frac{C_2 + C_1}{KC_2 + C_1} \right)$$

new charge

Energy: $U = \frac{Q^2}{2C} = \frac{CV^2}{2} = \frac{QV}{2}$

$$C_{eq} = \frac{KC_2 + C_1}{KC_2 C_1} \quad V = \mathcal{E}$$

$$U = \frac{1}{2} \left(\frac{KC_2 + C_1}{KC_2 C_1} \right) \mathcal{E}^2$$

3c) Charge splits in half at a then for each side $\frac{2}{5}Q$ of charge go to the $2C$ & $\frac{3}{5}Q$ of charge go through each of the $3C$ capacitors

Because of symmetry, charge is zero through $2C$, so voltage $V_{cb} = 0$

$$\mathcal{E} = \frac{Q}{2C} + \frac{Q}{6C} = \frac{3Q + Q}{6C} = \frac{4Q}{6C} = \frac{2Q}{3C} = \mathcal{E} \quad Q = \frac{3C\mathcal{E}}{2}$$

$$V_{db} = \frac{Q}{6C} = \frac{1}{2} \cdot \frac{3C\mathcal{E}}{2} = \frac{3C\mathcal{E}}{4}$$

$$V_{db} = \frac{\mathcal{E}}{4}$$

$$4a) \quad J = \frac{I}{A} = nqvd \quad J = \sigma E \quad \rho = \frac{1}{\sigma} \quad R = \frac{\rho l}{A}$$

$$V = IR \quad \frac{E}{R} = I \quad R = \frac{(1.68 \times 10^{-8})(1)}{6 \times 10^{-8}} = 0.28 \Omega$$

$$\frac{1.5 \text{ V}}{0.28 \Omega} = \frac{5.357 \text{ A}}{(6 \times 10^{-8} \text{ m}^2)(1.602 \times 10^{-19})} = 5.57 \times 10^{26} \text{ electron m/s}$$

$$4b) \quad R' = 4R \quad \frac{I'}{A'} = \frac{I}{A} = J' = J$$

$$A' = \frac{1}{4} A$$

Same number of electrons
 7×10^{18}