

**Problem 1. (28 points)**

A converging lens with focal length  $f$  is placed a distance  $f$  to the left of a diverging lens whose focal length has the same magnitude. An object is placed a distance  $(3/2)f$  to the left of the converging lens.

- (8 points)** If the diverging lens weren't there, where would the image of the object form? Would it be upright or inverted? Would it be real or virtual? What would be its lateral magnification? Draw a ray diagram for this system.
- (10 points)** Now consider the full scenario including the diverging lens. Determine the location of the final image for this double lens system, and draw a ray diagram showing what happens to all three principal rays emanating from the tip of the object. Make sure to clearly indicate where the rays or their extensions converge to form the final image. That is the total lateral magnification for this system? Is the final image real or virtual? Is it upright or inverted?
- (10 points)** Since we like lenses so much, suppose that we now insert a third converging lens with focal length  $f$  at a distance  $f$  to the right of the diverging lens. Where will the final image form now? Will it be real or virtual? Will it be upright or inverted? Draw a ray diagram that shows what happens to all three principal rays in this triple lens system.

(a) we know:

$$\frac{1}{s} + \frac{1}{s'} = \frac{1}{f}$$

$$\Rightarrow \frac{1}{\frac{3}{2}f} + \frac{1}{s'} = \frac{1}{f}$$


$$\Rightarrow \frac{1}{s'} = \frac{1}{f} - \frac{2}{3f} = \frac{1}{3f} \therefore s' = 3f \quad \downarrow 2$$

$8/2$


Therefore image is formed  $3f$  to the right of the lens and will be real.

$$m = \frac{-s'}{s} = \frac{-3f}{\frac{3}{2}f} = -3f \times \frac{2}{3f} = -2 \quad \downarrow 2$$

So it's magnified by 2 and inverted. H

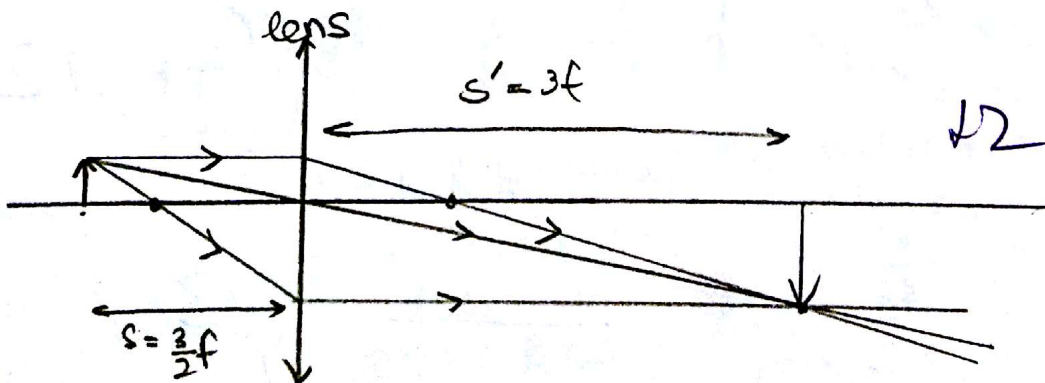

(b)

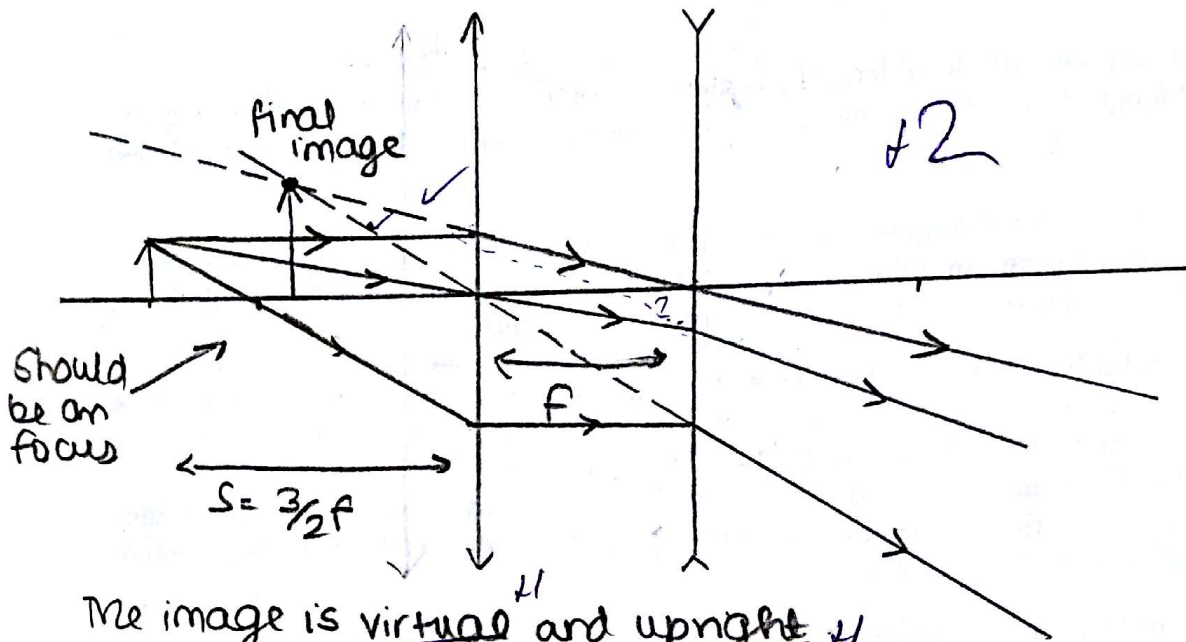

The image is virtual and upright +1  
 Since image of first lens is  $s' = 3f$ .

For the second lens:

$$\frac{1}{s} + \frac{1}{s'} = \frac{1}{f} \Rightarrow \frac{-1}{2f} + \frac{1}{s'} = \frac{-1}{f}$$

$$\Rightarrow \frac{1}{s'} = -\frac{1}{f} + \frac{1}{2f} = \frac{-1}{2f}$$

$$\therefore s' = -2f \quad +2$$

9/10

It is  $2f$  to the left of the second lens.

$$m = -\frac{s'}{s} = \frac{+2f}{-2f} = -1 \quad m_p = -2$$

$$\therefore \text{total } m = (-1)(-2) = \underline{2} \quad +1$$

10/10

(c) Adding a third lens: the object is now the final image

$$\therefore s = 3f \quad +1$$


$$\frac{1}{s'} + \frac{1}{s} = \frac{1}{f} \Rightarrow \frac{1}{s'} = \frac{1}{f} - \frac{1}{3f} = \frac{2}{3f} \therefore s' = \underline{\underline{\frac{3}{2}f}} \quad +2$$

Image will be formed  $\frac{3}{2}f$  to the right of lens 3.

$$m = -\frac{s'}{s} = \frac{-3/2f}{3f} = -\frac{1}{2}$$

therefore it is inverted and real +3


$$\text{total } m = -\frac{1}{2} \times 2 = \underline{-1}$$

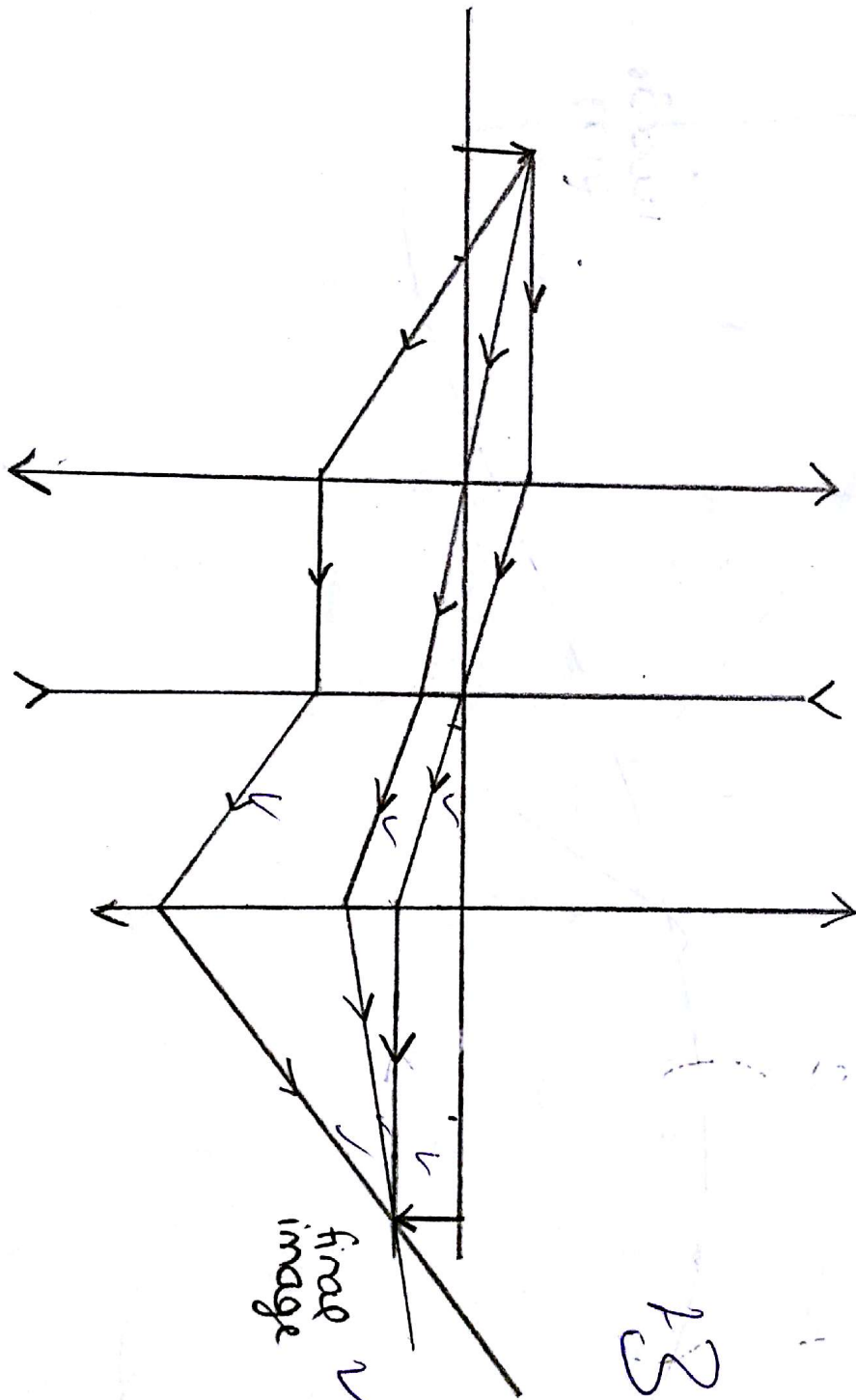



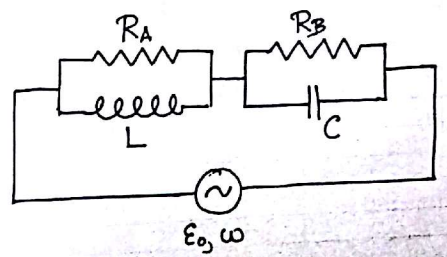**Problem 2. (34 points)**

Consider the AC circuit depicted below. Make sure all boxed, mathematical answers are written only in terms of the quantities labeled on the diagram.



- (6 points) What is the phase difference between the voltage in the inductor and the voltage in resistor  $A$ ? What is the phase difference between the current in the inductor and the current in resistor  $A$ ? Draw a phasor diagram containing the voltage and current phasors for these circuit elements.
- (6 points) What is the phase difference between the voltage in the capacitor and the voltage in resistor  $B$ ? What is the phase difference between the current in the capacitor and the current in resistor  $B$ ? Draw a phasor diagram containing the voltage and current phasors for these circuit elements.
- (6 points) Let  $I_A, I_L, I_B, I_C$  be amplitudes of the current in resistor  $A$ , the inductor, resistor  $B$ , and the capacitor respectively. Using physical intuition (no math) about how inductors and capacitors behave at low and high frequencies, what would you expect for the ratios  $I_L/I_A$  and  $I_C/I_B$  in the low and high frequency limits respectively?
- (4 points) Compute the ratios  $I_L/I_A$  and  $I_C/I_B$ . Do your mathematical results agree with your physical intuition?
- (2 points) Let  $i_A, i_L, i_B, i_C$  denote the time-dependent currents in resistor  $A$ , the inductor, resistor  $B$ , and the capacitor respectively. What is the relationship between these currents according to the junction rule?
- (8 points) What is the ratio  $I_A/I_B$ ?
- (2 points) What is the ratio  $V_A/V_B$ ?

(a) we know:  $\mathcal{E} = \mathcal{E}_0 \cos(\omega t)$

we know  $\Rightarrow V_{R_A} = V_L = \mathcal{E}_1$  [loop rule]

$\therefore$  phase difference in voltage is zero

Since:  $V_{R_A} = i_R R_A$   
 $i_R = \frac{V_{R_A}}{R_A} = \frac{\mathcal{E}_0}{R_A} \cos(\omega t)$


also:

$$V_L = L \frac{di_L}{dt}$$

$$\therefore \frac{di_L}{dt} = \frac{V_L}{L} \quad \therefore i_L = \int \frac{V_L}{L} dt = \frac{\epsilon_0}{\omega L} \sin(\omega t)$$

$$\therefore i_L = \frac{\epsilon_0}{\omega L} \cos(\omega t - \pi/2)$$

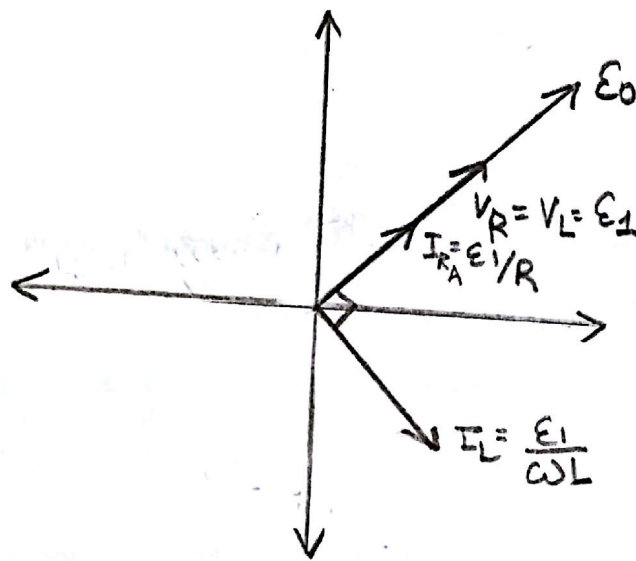$\therefore \phi$  diff in currents is  $\boxed{-\pi/2}$  where current in inductor lags



$E_1$  is some quantity of  $E_0(t)$

+

(b) again through loop rule:

$$V_{R_B} = V_C = E_2$$

[zero phase difference in voltages]

however:


$$V_{R_B} = i R_B \quad \therefore i R_B = \frac{\epsilon_0 \cos(\omega t)}{R_B}$$

also:

$$V_C = \frac{q}{C} \quad \therefore q = V_C C$$

$$\therefore \frac{dq}{dt} = i = \frac{d(V_C C)}{dt} = -\epsilon_0 \omega C \sin(\omega t) = \epsilon_0 \omega C \cos(\omega t + \pi/2)$$

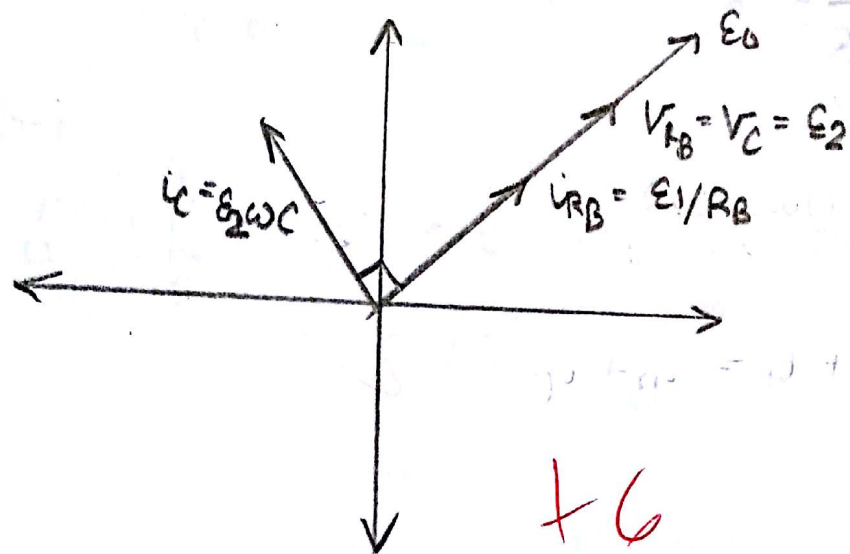$\therefore \phi$  diff of current is  $\pi/2$  where the capacitor leads



(c) we know that inductors are low-pass filters and therefore allow a higher current flow for small values of  $\omega$

$$\therefore \frac{I_L}{I_A} \rightarrow \infty \text{ as } \omega \rightarrow 0$$

$$\frac{I_L}{I_A} \rightarrow 0 \text{ as } \omega \rightarrow \infty$$

+5 +6

similarly capacitors are high pass filters:

$$\frac{I_C}{I_B} \rightarrow 0 \text{ as } \omega \rightarrow 0$$

$$\frac{I_C}{I_B} \rightarrow \infty \text{ as } \omega \rightarrow \infty$$

(d) for inductor:

$$I_L = \frac{E_1}{\omega L}$$

$$I_A = \frac{E_1}{R_A}$$

$$\therefore \frac{I_L}{I_A} = \frac{R_A}{\omega L} \quad \checkmark \text{ This agrees as } \frac{I_L}{I_A} \rightarrow \infty, \text{ for } \omega \rightarrow 0 \text{ and vice versa.}$$

for capacitor:

$$I_C = E_2 \omega C$$

$$I_B = \frac{E_2}{R_B}$$



$$\therefore \frac{I_C}{I_B} = R_B \omega C$$

[ This agrees as the ratio tends to  $\infty$  as  $\omega \rightarrow \infty$  and zero as  $\omega \rightarrow 0$  ]

121

e) According to the junction rule:


[ between the two elements ]

$$i_A + i_L = i_B + i_C \quad \times 2$$

f) since:

$$i_A = i_B + i_C - i_L$$

$\Rightarrow$

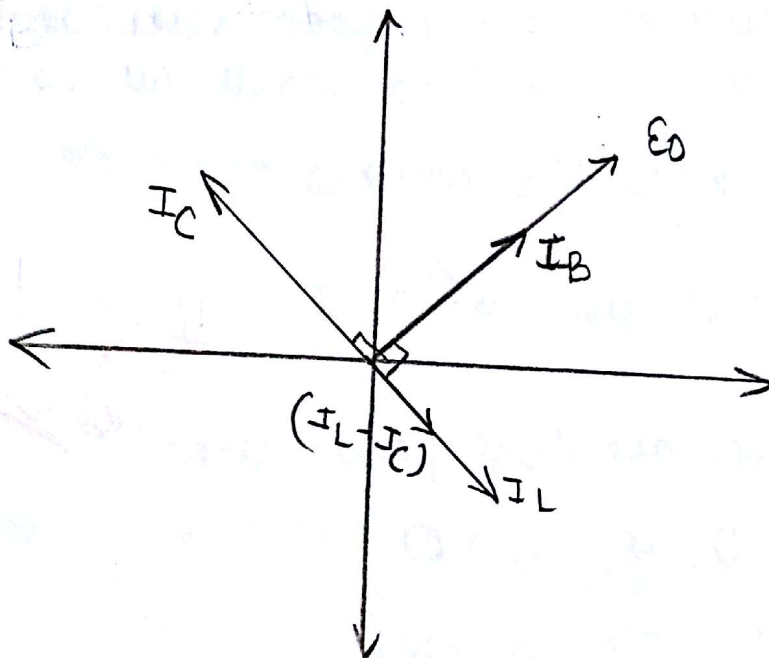

$I_A$  is the vector sum

$$\therefore I_A^2 = I_B^2 + (I_L - I_C)^2 \quad \therefore I_A = \sqrt{I_B^2 + (I_L - I_C)^2}$$

Similarly, we get that:

$$I_B = I_A + I_L - I_C$$

Using phasors:

$$I_B^2 = I_A^2 + (I_L - I_C)^2 \quad \therefore I_B = \sqrt{I_A^2 + (I_L - I_C)^2}$$

$$\frac{I_A}{I_B} = \frac{\sqrt{I_B^2 + (I_L - I_C)^2}}{\sqrt{I_A^2 + (I_L - I_C)^2}} = \frac{\sqrt{\left(\frac{E_0}{R_B}\right)^2 + \left(\frac{E_1}{\omega L} - E_2 \omega C\right)^2}}{\sqrt{\left(\frac{E_0}{R_A}\right)^2 + \left(\frac{E_0}{\omega L} - E_2 \omega C\right)^2}}$$

where  $E_1, E_2 = E_0 \cos(\omega t) + 2$

(Q) since  $V = IR$

$$\frac{V_A}{V_B} = \frac{I_A R_A}{I_B R_B} = \frac{R_A}{R_B} \text{ (answer to part (Q))}$$

+ 2



Problem	Score
1	27 / 28
2	28 / 34
<b>Total</b>	<b>55 / 62</b>