

**You must show your work to receive credit.** An answer written down with no work will receive no credit.

**On this entire exam, you may use without proof any expression for impedance and/or phase angle derived in class or the book.**

## Problem 1

– points

Consider an electromagnetic wave in vacuum whose magnetic field is measured to be

$$\vec{B} = B_0 \cos((\alpha x - \beta t)^2) \hat{z},$$

where  $\alpha$  and  $\beta$  are constants such that  $\beta/\alpha = c$ .

(a)

Find the electric field of this EM wave.

One of Maxwell's differential equations is

$$\nabla \times \vec{B} = \frac{1}{c^2} \frac{\partial \vec{E}}{\partial t}.$$

We can compute:

$$\begin{aligned} \nabla \times \vec{B} &= \begin{vmatrix} \hat{x} & \hat{y} & \hat{z} \\ \partial_x & \partial_y & \partial_z \\ 0 & 0 & B_0 \cos((\alpha x - \beta t)^2) \end{vmatrix} \\ &= 2B_0\alpha(\alpha x - \beta t) \sin((\alpha x - \beta t)^2) \hat{y}. \end{aligned}$$

One can check that the following electric field satisfies the above equation:

$$\begin{aligned} \vec{E} &= B_0 c^2 \frac{\alpha}{\beta} \cos((\alpha x - \beta t)^2) \hat{y} \\ &= B_0 c \cos((\alpha x - \beta t)^2) \hat{y} \end{aligned}$$

(a)

(b)

Find the intensity of this EM wave, in terms of  $B_0$ ,  $c$ ,  $\alpha$ ,  $\beta$ ,  $\mu_0$ ,  $x$ , and/or  $\epsilon_0$ . You need not evaluate any integrals you find.

**This problem doesn't really make sense if we define the intensity (as we did in class) as the time-average of the intensity over one period, since there is no well-defined period.** The clarification on CW was "Instead of computing the intensity in part (b), compute the average power per unit area over some time  $t_0$  carried by the wave."

The Poynting vector is

$$\vec{S} = \frac{1}{\mu_0} \vec{E} \times \vec{B} = \frac{B_0^2 c}{\mu_0} \cos^2((\alpha x - \beta t)^2) \hat{x}.$$


We can then take a time-average of this quantity at time  $t$ , over some time period  $t_0$ :

$$I_{t_0}(t) = \frac{B_0^2 c}{\mu_0} \left| \frac{1}{t_0} \int_t^{t+t_0} \cos^2((\alpha x - \beta t)^2) dt \right|.$$
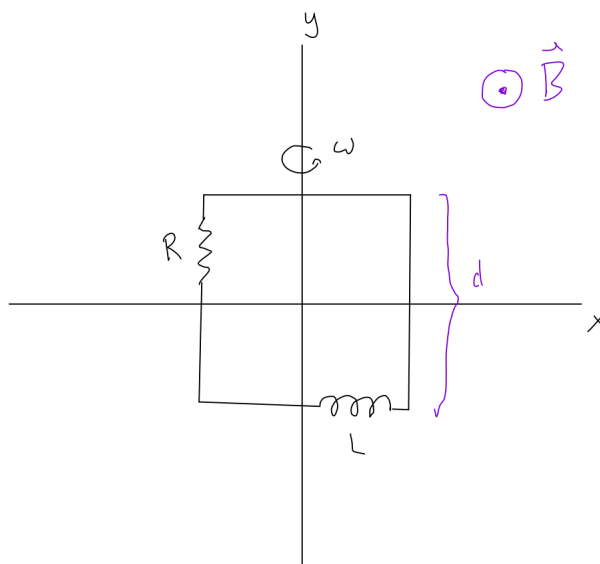
## Problem 2

– points

Consider a square loop of wire of side length  $d$  centered at the origin. Attached in series in the wire are a resistor  $R$  and an inductor  $L$ . Initially the square lies in the  $xy$  plane; the loop begins to rotate with constant speed around the  $y$  axis with angular frequency  $\omega$ . There is a constant, uniform magnetic field  $\vec{B} = B\hat{z}$  everywhere.



(a)

Calculate the magnitude (not amplitude!) of the emf in the loop of wire as a function of time.

The magnetic flux through the loop is

$$|\Phi_B(t)| = |Bd^2 \cos \omega t|.$$

By Faraday's law, we have

$$|\mathcal{E}| = \left| \frac{d\Phi_B}{dt} \right| = |\omega B d^2 \sin \omega t|.$$

(a)

(b)

Calculate the amplitude of the current induced in the loop.

The loop is driven with a sinusoidal driving emf

$$|v(t)| = |\omega B d^2 \sin \omega t|.$$

The impedance of this circuit is

$$Z(\omega) = \sqrt{R^2 + (\omega L)^2}.$$

Thus the amplitude of the current is

$$I = V/Z(\omega) = \frac{\omega B d^2}{\sqrt{R^2 + (\omega L)^2}}$$

(b)

## Problem 3

– points

Consider an LRC series circuit driven by a source supplying the emf

$$v(t) = \alpha \int_0^{\infty} e^{-\omega/\omega_0} \cos(\omega t) d\omega,$$

where  $\omega_0$  and  $\alpha$  are constants. Find the current that flows in the circuit, in terms of  $t$ ,  $\alpha$ ,  $\omega_0$ ,  $L$ ,  $R$ , and/or  $C$ . **Explain your reasoning.** You need not evaluate any integrals you encounter.

This is simply a *continuous* sum of periodic driving emfs weighted by the exponential function. Each “piece” of the current response will additionally be weighted by the impedance:

$$i(t) = \alpha \int_0^{\infty} \frac{e^{-\omega/\omega_0}}{Z(\omega)} \cos(\omega t - \phi(\omega)) d\omega,$$

where

$$Z(\omega) = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

$$\phi(\omega) = \tan^{-1} \left( \frac{\omega L - 1/\omega C}{R} \right).$$

Note: in a lecture I had incorrectly written the current for multiple oscillating sources *without* the phase factor  $\phi(\omega)$ . Grading should be lenient with regards to this factor.

## Problem 4

– points

Consider an LRC series circuit driven by a source of emf with angular frequency  $\omega = 1/\sqrt{LC}$ . You measure the amplitude of the charge on the capacitor to be  $Q_0$ . Calculate the amplitude of the source emf, as a function of  $L$ ,  $R$ ,  $C$ , and/or  $Q$ .

$$i = \frac{dq}{dt} = Q\omega \cos(\omega t).$$

Then

$$\begin{aligned} V = IZ &= Q\omega Z(\omega) \\ &= Q\omega \sqrt{R^2 + (\omega L - 1/\omega C)^2} \\ &= \frac{QR}{\sqrt{LC}}. \end{aligned}$$